

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. November 8, 2022

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hour and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		7
2c		8
2d (218 only)		10 (218A only)
3a		5
3b		5
3c		7.5
3d		7.5
4		15
5a		10
5b (218 only)		15 (218A only)
6		10
total		100 (145), 125 (218A)


Name: Solution

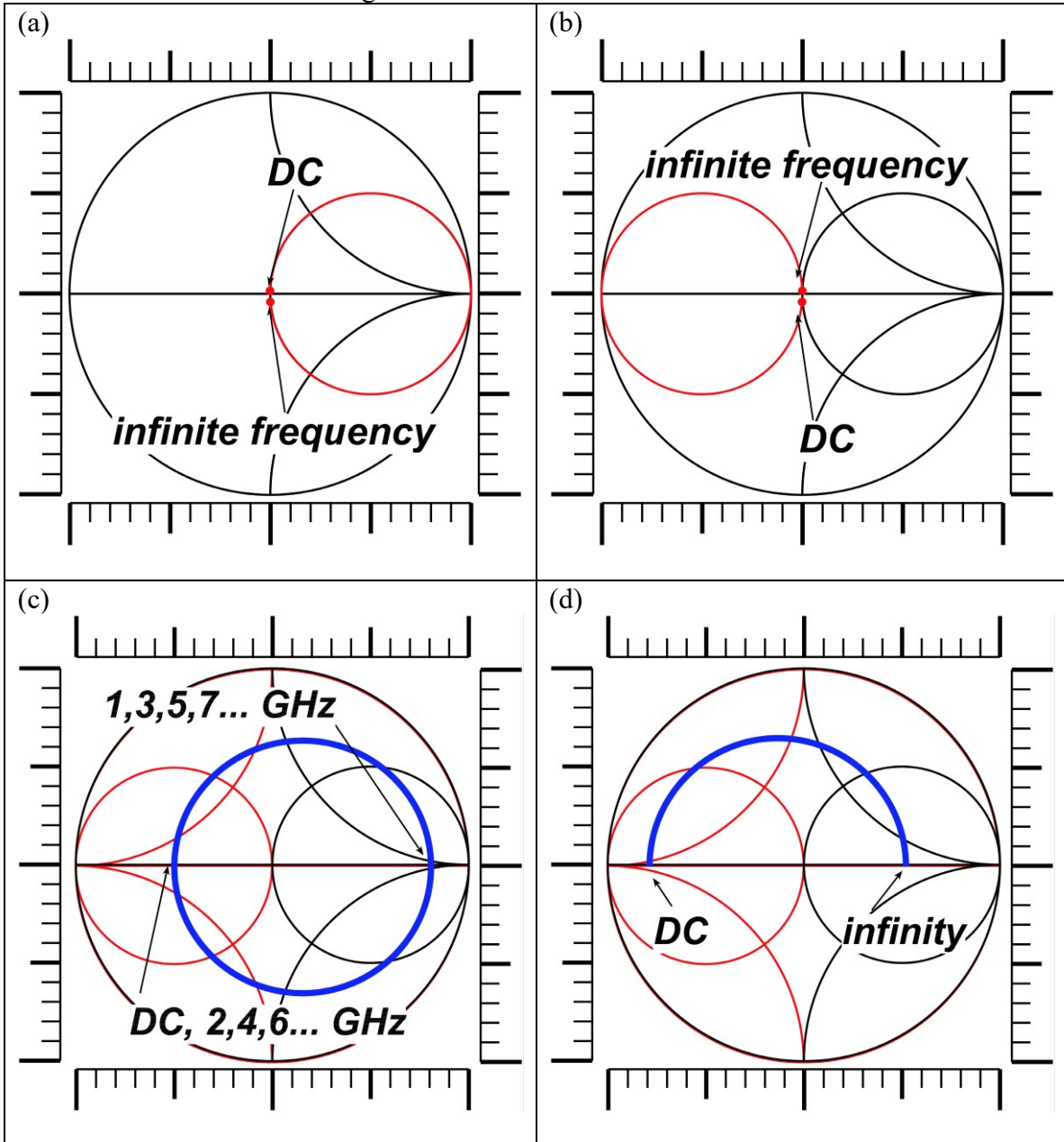Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



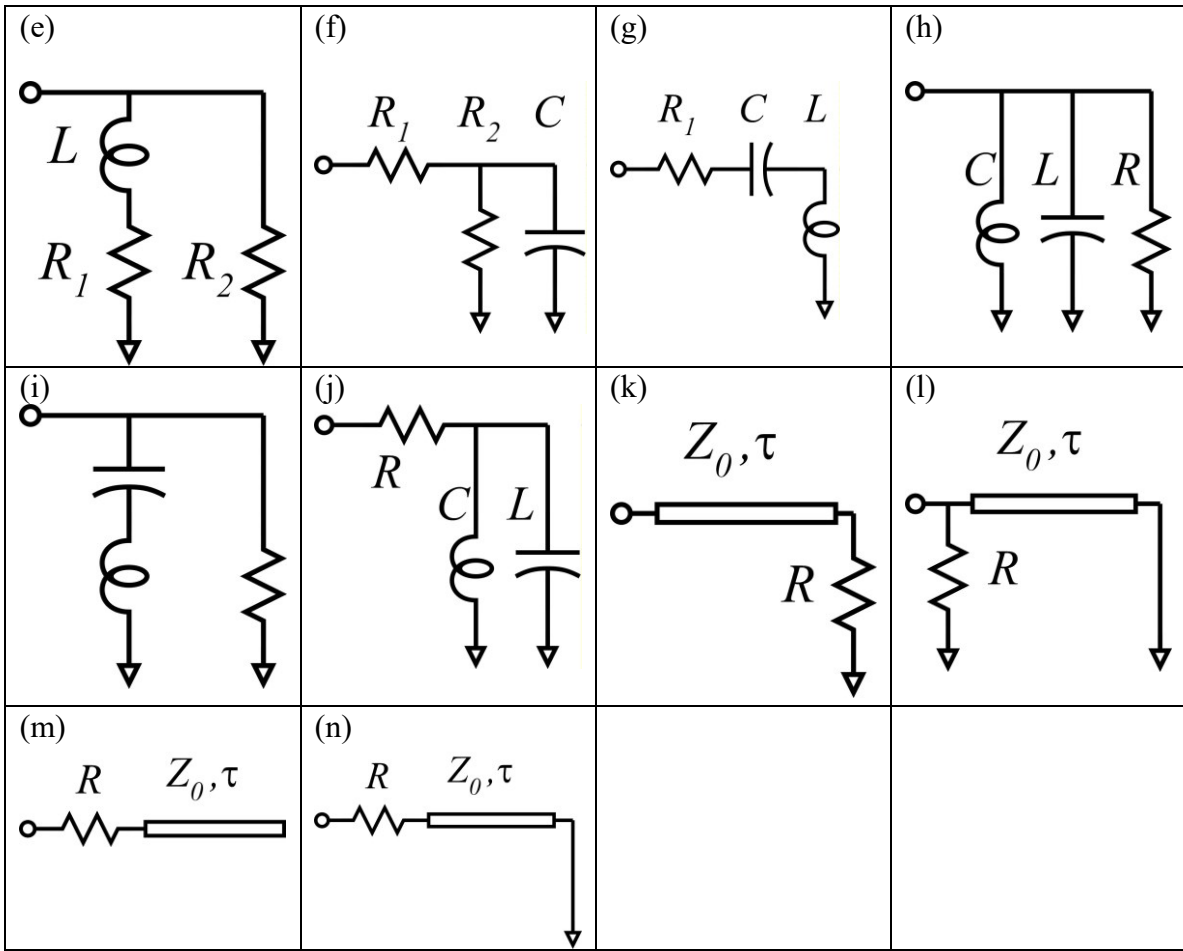



First match each Smith Chart with each circuit. *Then determine as many component values as is possible* (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

Smith chart (a). Circuit= $\frac{j}{R + 50\Omega}$.
 Component values: $R = 50\Omega$, _____, _____,



Smith chart (b). Circuit= $\frac{i}{R + 50\Omega}$.
 Component values: $R = 50\Omega$, _____, _____,

Smith chart (c). Circuit= $\frac{K}{R + 50\Omega}$.
 Component values: $R = 450\Omega$, $\tau = 25\mu\text{s}$, $Z_{line} = 50\Omega \cdot \sqrt{3}$,

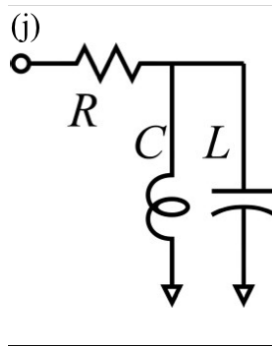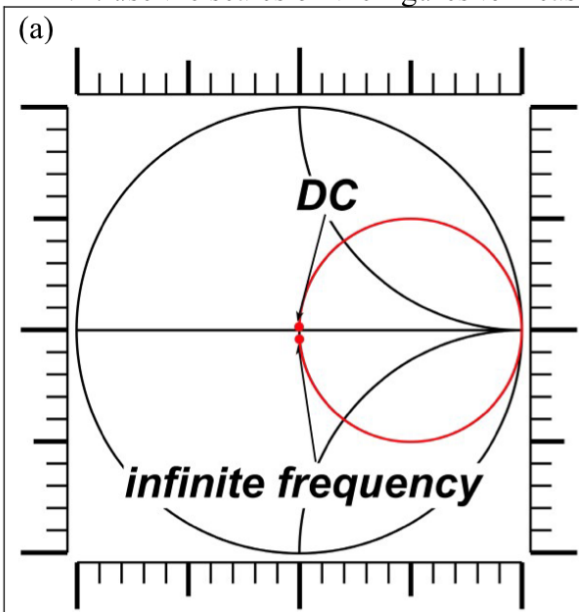Smith chart (d). Circuit= $\frac{d}{R_1 + 225\Omega + R_2 + 450\Omega}$.
 Component values: $R_1 = 225\Omega$, $R_2 = 450\Omega$,




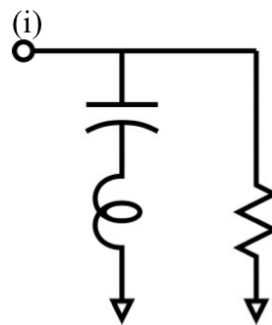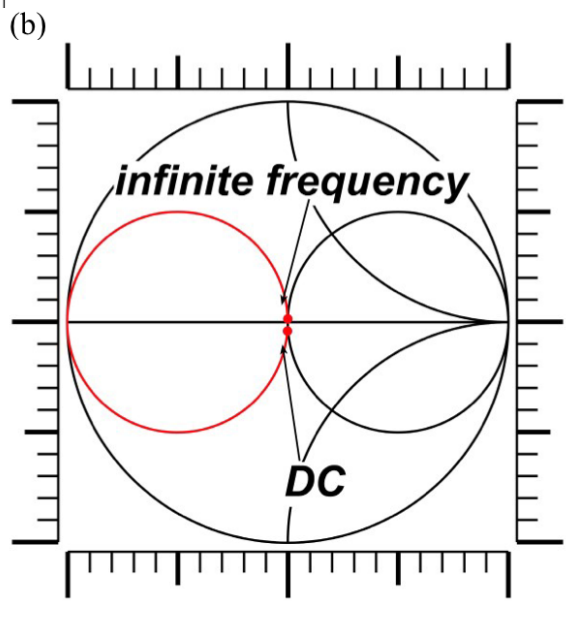a) 5pts for correctly recognizing the circuit.
 2.5pts for resistor value.



b) 5pts for correctly recognizing the circuit.
 2.5pts for resistor value.

1/2 pt.

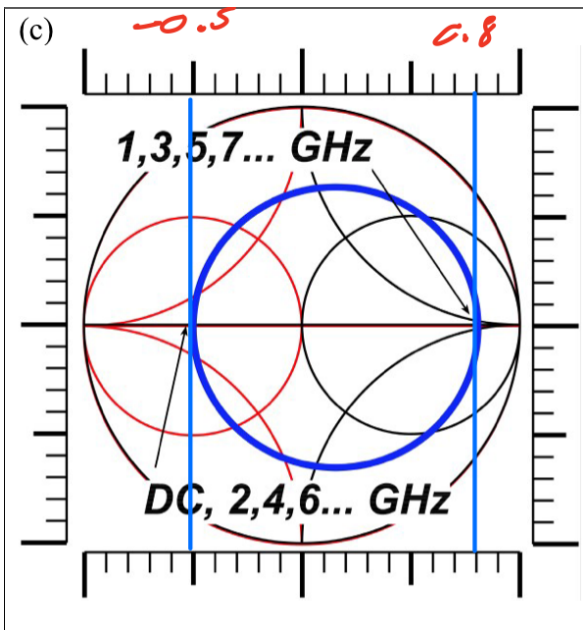


$$\Gamma = -0.5 \rightarrow$$

$$\zeta = \frac{1 + \Gamma}{1 - \Gamma} = \frac{0.5}{1.5} = \frac{1}{3}$$

$$\Gamma = 0.8$$
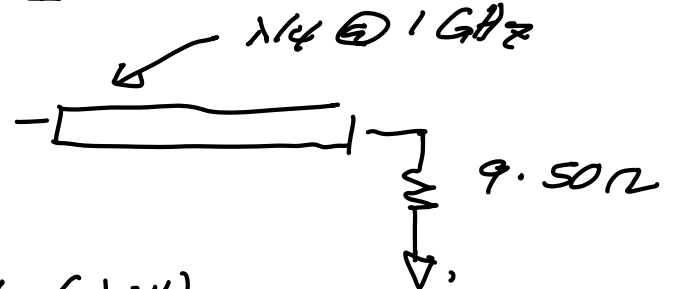
$$\zeta = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1.8}{0.2} = 9$$




$$Z_L @ 1 \text{ GHz } (\lambda/4) = \frac{50 \Omega}{3}$$

$$\textcircled{2} \rightarrow Z_{0, \text{line}} = \sqrt{Z_L Z_0} = \sqrt{\frac{50 \Omega}{3} \cdot 9.50 \Omega}$$

$$= 50 \Omega \cdot \sqrt{3}$$
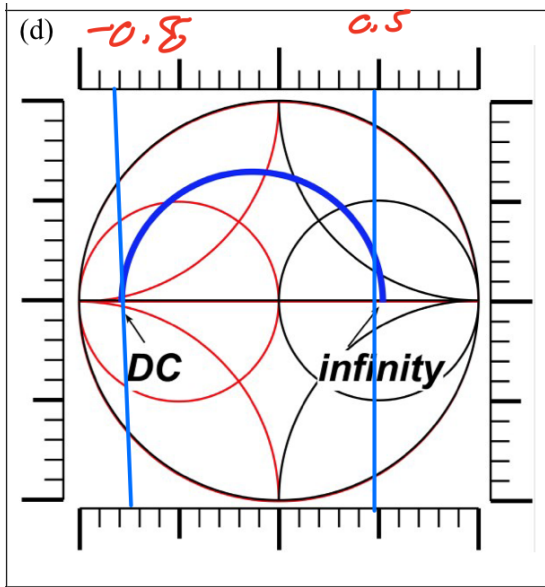
$$\textcircled{1} \left[\begin{array}{l} \text{line is } \lambda/4 @ 1 \text{ GHz} \\ \text{line is } 1 @ 4 \text{ GHz} \rightarrow \tau = 250 \text{ ps} \end{array} \right.$$




$$\Gamma = 0,5$$

$$\rightarrow \xi = \frac{1+\Gamma}{1-\Gamma} = \frac{1,5}{0,5} = 3$$

$$\rightarrow 150 \Omega$$

$$\Gamma = -0,8$$
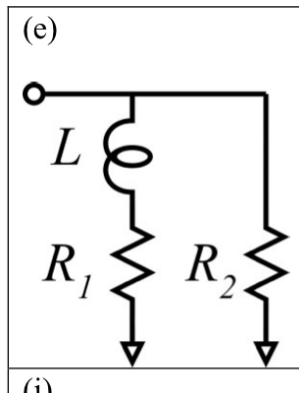
$$\xi = \frac{1+\Gamma}{1-\Gamma} = \frac{1,8}{0,2} = 9 \rightarrow 450 \Omega$$



1.5

$$\rightarrow R_2 = 450 \Omega$$

$$R_1 \parallel R_2 = 150 \Omega$$


$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_1} + \frac{1}{450 \Omega} = \frac{1}{150 \Omega}$$

$$\frac{1}{R_1} = \frac{1}{150 \Omega} - \frac{1}{450 \Omega} \rightarrow R_1 = 225 \Omega$$





Problem 2, 25 points (ece145A), 35 points (ece218A)
 2-port parameters and Transistor models

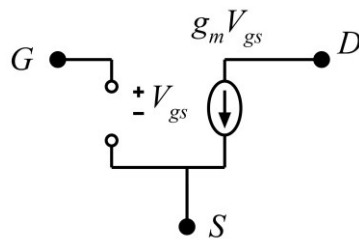Part a, 10 points

At the right is the equivalent circuit for a FET. The transconductance g_m is 1 mS.



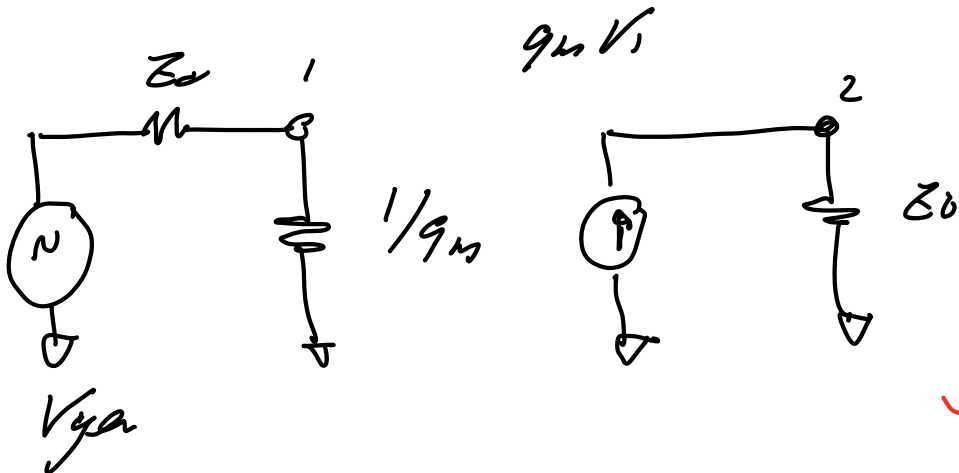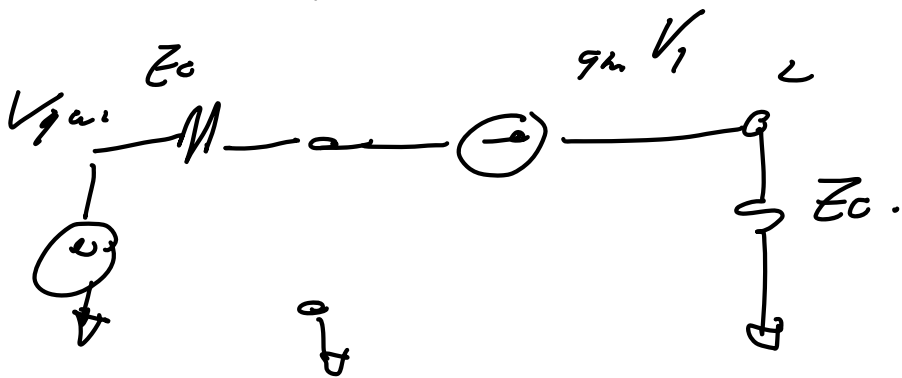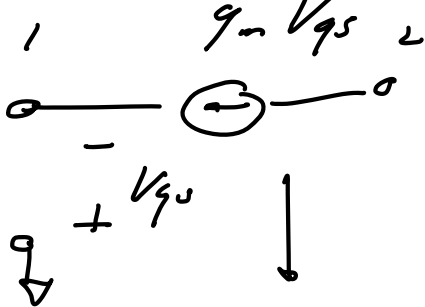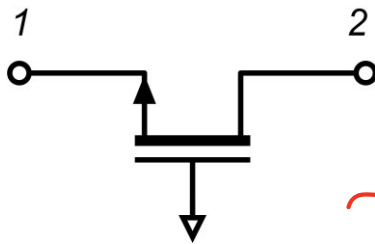Now, given this model, for the network at the right, give the numerical values of S_{21} and S_{11} . The reference Z_0 is 50 Ohms.



4

$$Z_{in} = 1/g_m = 1000 \Omega \quad 50$$

$$S_{11} = \frac{1000 \Omega - 1}{1000 \Omega + 1} = \frac{20 - 1}{20 + 1} = 19/21 = S_{11}$$

$$\left. \begin{aligned} V_1 &= V_{gen} \cdot \frac{1/g_m}{1/g_m + Z_0} \\ V_2 &= g_m Z_0 \cdot V_1 \end{aligned} \right\} \frac{V_2}{V_{gen}} = \frac{Z_0}{1/g_m + Z_0}$$


$$S_{21} = \frac{2V_2}{V_1} \Big|_{Z_1 = Z_2 = Z_0} = \frac{2Z_0}{1/g_m + Z_0}$$

$$= \frac{100 \Omega}{1000 \Omega + 500 \Omega}$$

$$S_{21} = \frac{100}{1050}$$

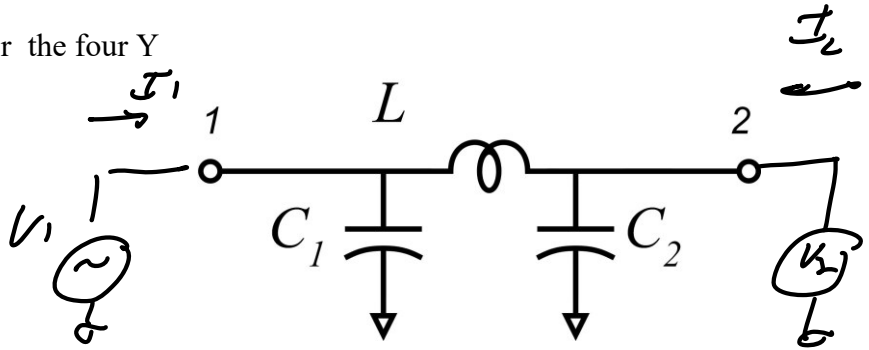Part b, 7 points

Derive algebraic expressions for the four Y parameters for this network




$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} j\omega C_1 + \frac{1}{j\omega L} & -1/j\omega L \\ -1/j\omega L & j\omega C_2 + \frac{1}{j\omega L} \end{bmatrix}}_{Y_{ij}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

1.75 pts each

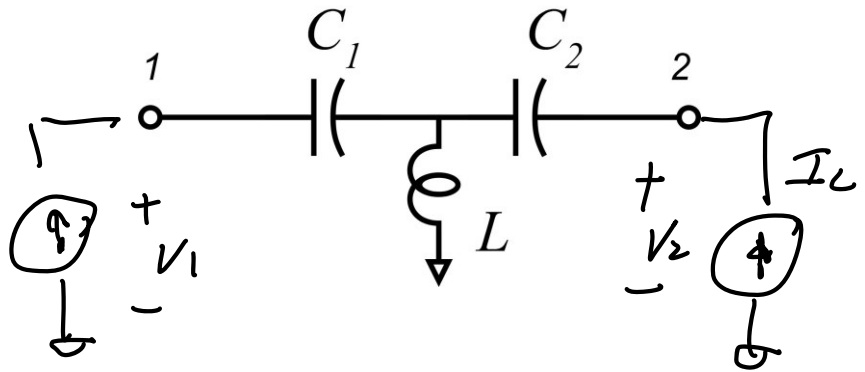Part c, 8 points

Derive algebraic expressions for the four Z parameters for this network



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{j\omega C_1} + j\omega L & j\omega L \\ j\omega L & \frac{1}{j\omega C_2} + j\omega L \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


Z_{ij}

2 pts
each

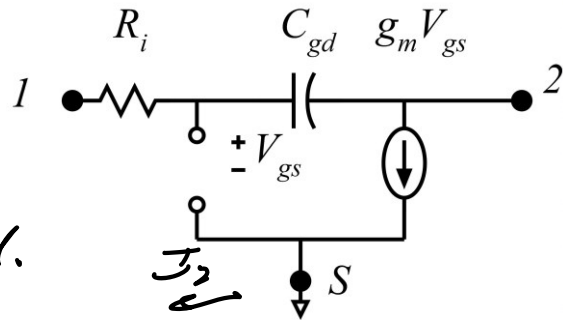Part d, ECE218A students only 10 points

Compute the Y parameters for network, to second order in $j\omega C_{gd}R_i$. The Taylor series expansion

$(1+\varepsilon)^{-1} = 1 - \varepsilon + \varepsilon^2 + O(\varepsilon^3)$ may be useful



2

$$V_x = \frac{V_1 \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} + \frac{V_2 R}{R + \frac{1}{j\omega C}}$$

$$= \frac{V_1}{1 + j\omega RC} + \frac{V_2 j\omega RC}{1 + j\omega RC}$$

$$= \frac{V_1}{1 + \alpha} + \frac{V_2 \alpha}{1 + \alpha} \quad \text{where } \alpha = j\omega RC$$

2

$$\approx V_1 (1 - \alpha + \alpha^2) + V_2 \alpha (1 - \alpha + \alpha^2)$$

$$\approx V_1 (1 - \alpha + \alpha^2) + V_2 (\alpha - \alpha^2)$$

2

$$I_1 = (V_1 - V_x) G \quad \text{where } G = 1/R_i$$

$$RI_1 = V_1 - V_1 (1 - \alpha + \alpha^2) - V_2 (\alpha - \alpha^2)$$

$$= V_1 (\alpha - \alpha^2) - V_2 (\alpha - \alpha^2)$$

$$I_1 = V_1 \cdot \frac{1}{R} (j\omega RC + \omega^2 R^2 C^2)$$

$$- V_2 \frac{1}{R} (j\omega RC + \omega^2 R^2 C^2)$$

$$= V_1 [j\omega C + \omega^2 RC^2]$$

$$+ V_2 [-j\omega C - \omega^2 RC^2]$$

$\leftarrow Y_{11}$

$\leftarrow Y_{12}$

$$I_2 = g_m V_x + (V_2 - V_x) j\omega C$$

$$= j\omega C V_2 + (g_m - j\omega C) V_x$$

$$I_2 - j\omega C V_2 = (g_m - j\omega C) V_x$$

$$(V_1 (1 - \alpha + \alpha^2) + V_2 (\alpha - \alpha^2))$$

$$I_2 = V_1 g_m (1 - j\omega C / g_m) \cdot (1 - j\omega RC + \omega^2 R^2 C^2) + V_2 [j\omega C + (g_m - j\omega C) (j\omega RC + \omega^2 R^2 C^2)]$$

$$= V_1 g_m (1 - j\omega C / g_m) \cdot (1 - j\omega RC + \omega^2 R^2 C^2)$$

$$+ V_2 [j\omega C + j\omega RC g_m + \omega^2 R^2 C^2 g_m + \omega^2 C^2 R^2]$$

$\leftarrow Y_{21}$

$\uparrow Y_{22}$

\leftarrow note I have

dropped $j\omega C (\omega^2 R^2 C^2)$

term, as this is 3rd order


Problem 3, 25 points (ECE145A), 25 points (ECE 218A)

Available source power relationships, lumped/distributed relationships.

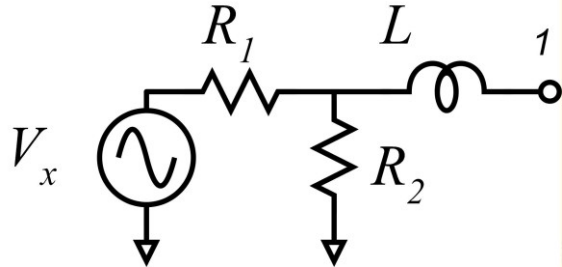
Part a, 5 points

V_s is 2V RMS at 10GHz. R_1 and R_2 are both 50 Ohms, L is 0.795 nH.

At 10GHz, what is the available signal power? Draw the circuit diagram of a load network, with element values specified, that would, when connected to the source, absorb this amount of power from the generator.




Thouvenin equivalent:

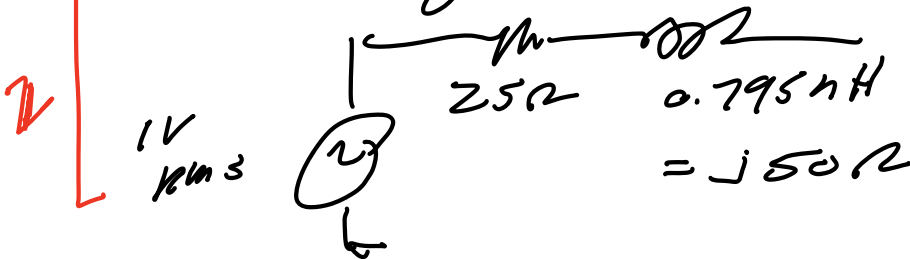

$$P_{avg} = \frac{(1V)^2}{4(25\Omega)} = \frac{(1V)^2}{100\Omega} = 10 \text{ mW}$$

Optimum load
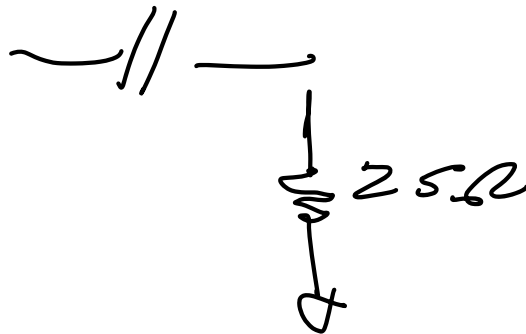
$$-j50\Omega = \frac{1}{j\omega C} \rightarrow C = 0.32 \text{ pF}$$



Part b, 5 points

A coaxial cable has 50 Ohms characteristic impedance, is 10 meters long, and the insulating dielectric has a dielectric constant of 2.0.

a) What is the total capacitance of the cable ?

b) What is the total inductance of the cable ?

$$v = \frac{3 \cdot 10^8 \text{ m/s}}{\sqrt{2}}$$


1 [
$$\tau = \frac{10 \text{ m}}{3 \cdot 10^8 \text{ m/s}} \cdot \sqrt{2} = 47.1 \text{ ns}$$

2 [
$$L = Z_0 \cdot \tau = 2.36 \text{ } \mu\text{H}$$

2 [
$$C = \tau / Z_0 = 943 \text{ pF}$$

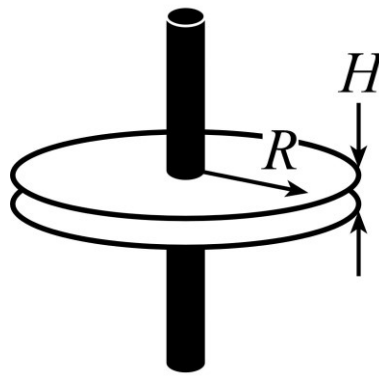Part c, 7.5 points

A capacitor has round plates of radius $R=1$ cm, and separation $H = 0.1$ mm. Between the plates is an insulator whose dielectric constant is 100.



- What is the capacitor's impedance at 1 kHz?
- At what frequencies is the impedance infinity Ohms?
- At what frequencies is the impedance zero Ohms?

Area $= A = \pi R^2$ $\sqrt{100}$ 1 cm

2.
$$C = \frac{\epsilon_r \epsilon_0 \cdot A}{d} = \frac{\epsilon_r \epsilon_0}{d} \cdot \pi R^2 = 2.78 \text{ nF}$$

$d = 0.1 \text{ mm}$

B) Speed of light delay, center-edge =

0.5
$$\tau = \frac{1 \text{ cm}}{3 \cdot 10^8 \text{ m/s}} \cdot \sqrt{100} = \frac{1}{3} \text{ ns} = \frac{1}{3} \text{ GHz}$$

$z \rightarrow 0$ when $l = 0\lambda, \lambda/2, 2\lambda/2, 3\lambda/2, \dots = n(\lambda/2)$

2.5
$$DC, \frac{1}{2} \cdot 3 \text{ GHz}, \frac{2}{2} \cdot 3 \text{ GHz}, \frac{3}{2} \cdot 3 \text{ GHz} \dots$$

C) $z \rightarrow \infty$ when $\lambda/4, 3\lambda/4, \dots$

2.5
$$\rightarrow \frac{3}{4} \text{ GHz}, 3 \cdot \frac{3}{4} \text{ GHz}, 5 \cdot \frac{3}{4} \text{ GHz} \dots$$

$$v = c = 3 \cdot 10^8 \text{ m/s}$$

$$Z_0 = 377 \Omega \cdot \frac{1 \text{ mm}}{1 \text{ mm} + 5 \text{ mm}} = \frac{377}{6} \Omega$$

$$L = 10 \text{ cm}$$

$$\tau = \frac{10 \text{ cm}}{3 \cdot 10^8 \text{ m/s}} = \frac{10^{-2} \text{ m}}{3 \cdot 10^8 \text{ m/s}} = \frac{1}{3} \cdot 10^{-10} \text{ sec}$$

Part d, 7.5 points


Using the approximate formula for transmission-line characteristic impedance,

$$Z_0 \approx \sqrt{\frac{H}{W}} \cdot \frac{H}{H+W}, \text{ if } H=1 \text{ mm, } W=5 \text{ mm, and } L=10 \text{ cm, we have two metal plates that are short-circuited at a distance } L \text{ from the drive point.}$$

a) what is the approximate inductance between the two ends of the wire?

b) At what frequencies is the impedance infinity Ohms?

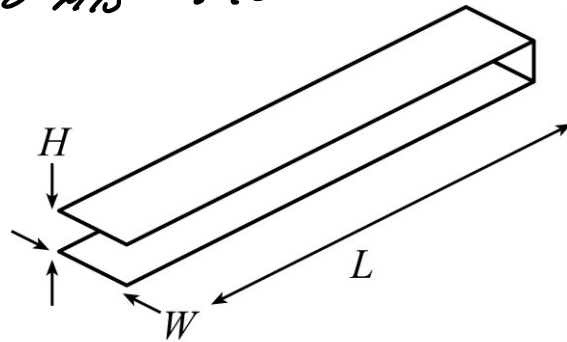c) At what frequencies is the impedance zero Ohms?



$$a) \quad L = Z_0 \cdot \tau = \frac{377 \Omega}{6} \cdot \frac{1}{3} \cdot 10^{-10} \text{ sec} = \frac{377}{18} \cdot 10^{-10} \text{ H} = \frac{377}{180} \text{ nH} = 2.09 \text{ nH}$$

$$1/\tau = \frac{10^{10}}{3} \text{ Hz} = \frac{10}{3} \text{ GHz}$$

$$c) \quad Z \rightarrow 0 \text{ when } L = 0 \cdot \frac{\lambda}{2}, 2 \cdot \frac{\lambda}{2}, 3 \cdot \frac{\lambda}{2}, \dots, n \cdot \frac{\lambda}{2}$$

$$f = \text{dc}, \frac{5}{3} \text{ GHz}, 2 \cdot \frac{5}{3} \text{ GHz}, 3 \cdot \frac{5}{3} \text{ GHz}, \dots$$

$$d) \quad Z \rightarrow \infty \text{ when } L = 1 \cdot \frac{\lambda}{4}, 3 \cdot \frac{\lambda}{4}, 5 \cdot \frac{\lambda}{4}, \dots$$


$$f = \frac{5}{6} \text{ GHz}, 3 \cdot \frac{5}{6} \text{ GHz}, 5 \cdot \frac{5}{6} \text{ GHz}, \dots$$

Problem 4, 15 points


Impedance-matching exercise.

At 10GHz signal frequency, an antenna has an input impedance of $100+j0$ Ohms. Design a matching network, using a series inductor and a shunt capacitor, which matches this impedance to 25 Ohms. Use a Smith chart with 50 Ohms impedance normalization

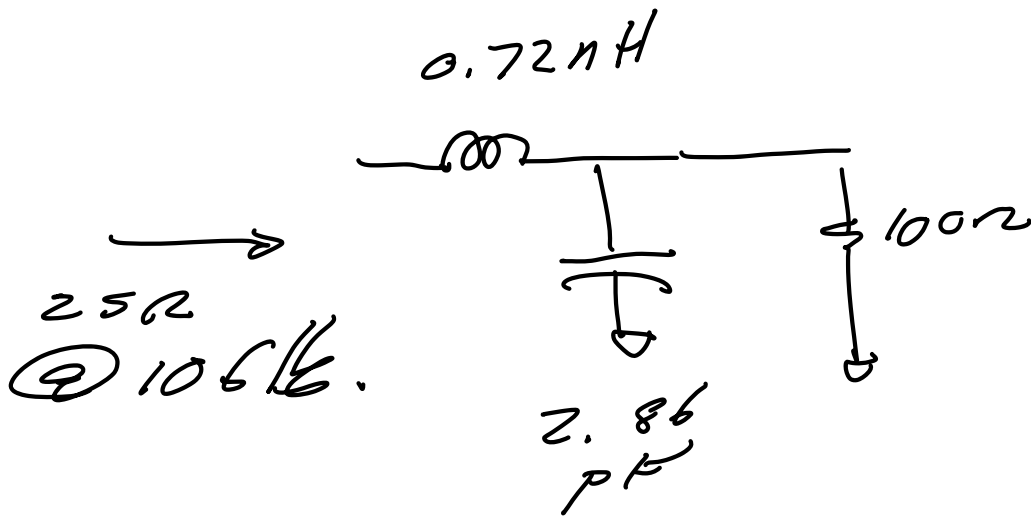Give all element values. Either use a separate impedance-admittance chart , or use the attached one below..



50 Ω chart

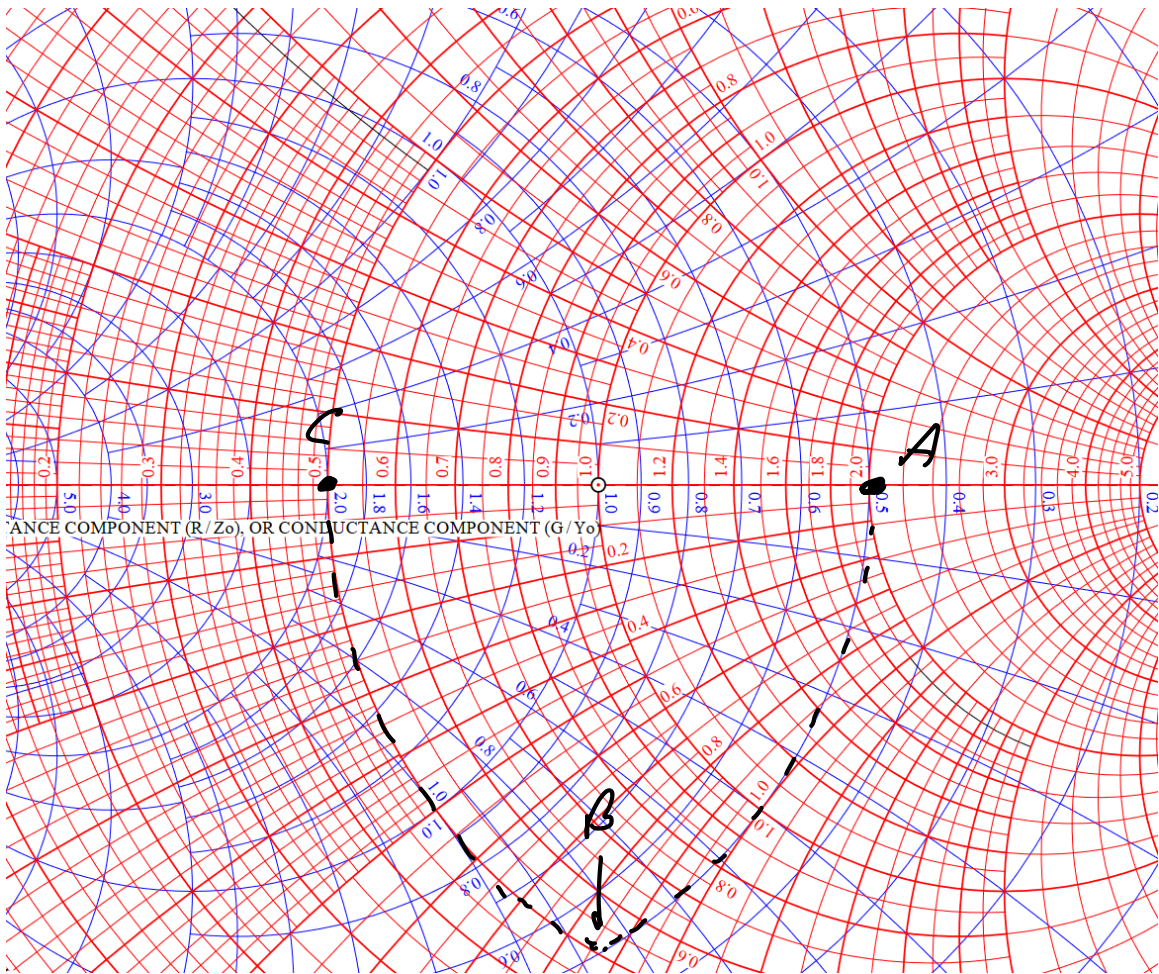

2 [A) $\underline{z} = 2 + j0$; $y = 1/2 + j0$

2 [b) $y = 1/2 + j0.9$

4 $\Delta y = j0.9$
 $\Delta Y = \frac{j0.9}{50\Omega} = j\omega C$
 $C = \frac{0.9}{50\Omega \cdot 2\pi \cdot 10^6 \frac{1}{s}} = 2.86 \text{ pF}$

2 [c) $\underline{z} = 0.5 - j0.9$


2 [c) $\underline{z} = 0.5 + j0$ $\Delta \underline{z} = j0.9$
 $\Delta \underline{z} = j0.9 \cdot 50\Omega = j\omega L \rightarrow L = \frac{0.9 \cdot 50\Omega}{2\pi(10^6 \frac{1}{s})} = 0.72 \text{ nH}$

Problem 5, 10 points (ece145A), 25 points (218A)


Signal flow graphs

Part a, 10 points

Find b_{out}/a_{gen} for this network.

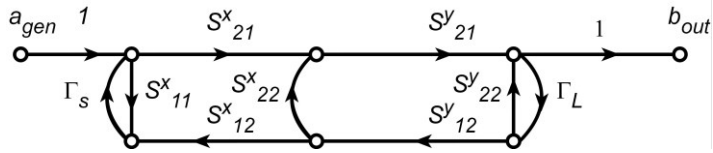

Loops

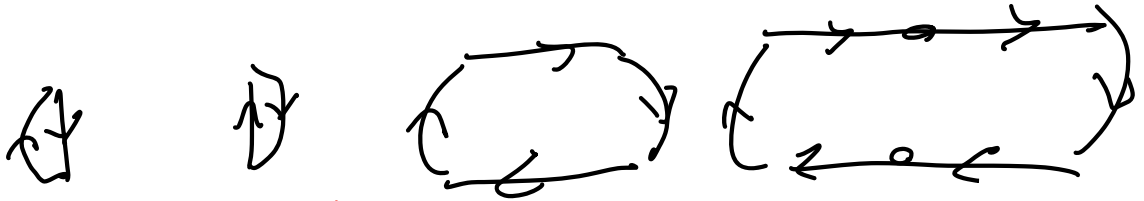

$$T = \frac{S_{21}^x S_{21}^y}{D} \quad \text{where}$$

$$D = 1 - \Gamma_s S_{11}^x - \Gamma_L S_{22}^y - \Gamma_s S_{21}^x S_{21}^y \Gamma_L S_{12}^y S_{12}^x \quad \text{1st order}$$





$$- S_{22}^x S_{21}^y \Gamma_L S_{12}^y \quad \text{1st order}$$

$$+ \Gamma_s S_{11}^x S_{22}^y \Gamma_L + \Gamma_s S_{11}^x S_{22}^x S_{21}^y \Gamma_L S_{12}^y \quad \text{2nd order}$$

$$T_{\sigma} = \frac{S_{21}^X S_{21}^Y}{D} \quad \text{where } D = \dots$$

① ↗

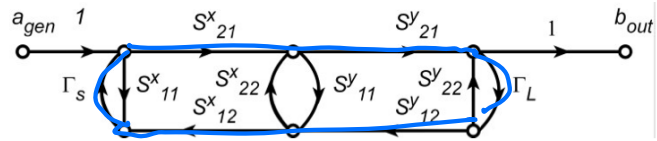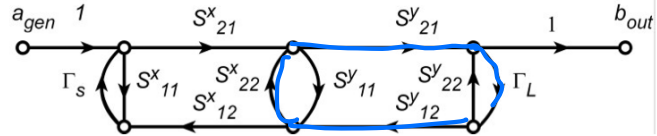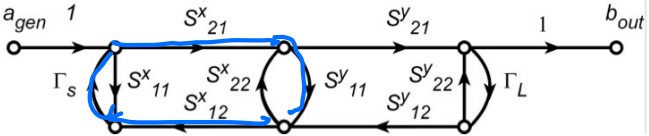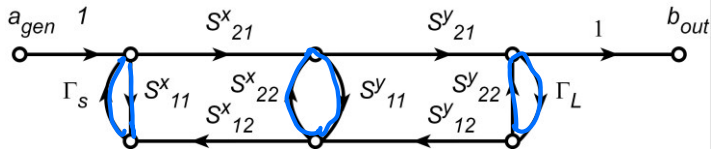Part b, (218A only) 15 points
Find b_{out}/a_{gen} for this network.



$$D = 1$$

$$\left. \begin{aligned} & -\Gamma_s S_{11}^X - S_{22}^X S_{11}^Y - S_{22}^Y \Gamma_L \\ & -\Gamma_s S_{21}^X S_{11}^Y S_{12}^X - S_{22}^X S_{21}^Y \Gamma_L S_{12}^Y \\ & - S_{21}^X S_{21}^Y \Gamma_L S_{12}^Y S_{12}^X \Gamma_s \end{aligned} \right\} \begin{array}{l} \text{1st order} \\ \text{1 pt ead.} \end{array}$$

$$\left. \begin{aligned} & + \Gamma_s S_{11}^X S_{22}^X S_{11}^Y + \Gamma_s S_{11}^X S_{21}^Y \Gamma_L + S_{22}^Y \Gamma_L S_{21}^X S_{11}^Y \\ & + \Gamma_s S_{11}^X S_{22}^X S_{21}^Y \Gamma_L S_{12}^Y + S_{22}^Y \Gamma_L \Gamma_s S_{21}^X S_{11}^Y S_{12}^X \end{aligned} \right\} \begin{array}{l} \text{2nd} \\ \text{2 pts} \end{array}$$

$$- \Gamma_s S_{11}^X S_{22}^X S_{11}^Y S_{21}^Y \Gamma_L \left. \begin{array}{l} \text{3rd} \\ \text{3 pts} \end{array} \right\}$$

1 pt each

$$2 \left[\begin{array}{l} T_s = 1/2 \\ \Gamma_s = 0 \\ \Gamma_L = -1 \end{array} \right.$$

Problem 6, 10 points


Transmission lines in the time domain.

V_{gen} is a 1V step-function occurring at $t=0$ seconds. Z_{line} is 50 Ohms. The line is 2 meters long and has a dielectric constant of 4.0.

R_2 is zero Ohms

R_1 is 50 Ohms.

Plot $V_{in}(t)$ on the graph below.

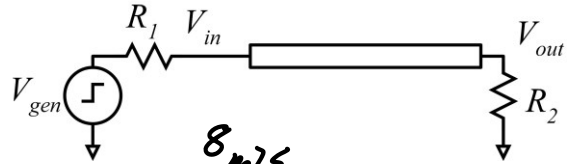

$$2 \left[\begin{array}{l} v = \frac{3 \cdot 10^8 \text{ m/s}}{2} \\ \tau = \frac{2 \text{ m}}{1.5 \cdot 10^8 \text{ m/s}} = \frac{2}{1.5} \cdot 10^{-8} \text{ s} = \frac{4}{3} \cdot 10^{-8} \text{ s} = 13.3 \text{ ns} \end{array} \right.$$

