
Flip-Flops and Sequential Circuit Design

ECE 152A – Winter 2012

Reading Assignment

- Brown and Vranesic
 - 7 Flip-Flops, Registers, Counters and a Simple Processor
 - 7.5 T Flip-Flop
 - 7.5.1 Configurable Flip-Flops
 - 7.6 JK Flip-Flop
 - 7.7 Summary of Terminology
 - 7.8 Registers
 - 7.8.1 Shift Register
 - 7.8.2 Parallel-Access Shift Register

Reading Assignment

- Brown and Vranesic (cont)
 - 7 Flip-Flops, Registers, Counters and a Simple Processor (cont)
 - 7.9 Counters
 - 7.9.1 Asynchronous Counters
 - 7.9.2 Synchronous Counters
 - 7.9.3 Counters with Parallel Load
 - 7.10 Reset Synchronization

Reading Assignment

- Brown and Vranesic (cont)
 - 7 Flip-Flops, Registers, Counters and a Simple Processor (cont)
 - 7.11 Other Types of Counters
 - 7.11.1 BCD Counter
 - 7.11.2 Ring Counter
 - 7.11.3 Johnson Counter
 - 7.11.4 Remarks on Counter Design

Reading Assignment

- Brown and Vranesic (cont)

- 8 Synchronous Sequential Circuits

- 8.1 Basic Design Steps

- 8.1.1 State Diagram

- 8.1.2 State Table

- 8.1.3 State Assignment

- 8.1.4 Choice of Flip-Flops and Derivation of Next-State and Output Expressions

- 8.1.5 Timing Diagram

- 8.1.6 Summary of Design Steps

Reading Assignment

- Brown and Vranesic (cont)
 - 8 Synchronous Sequential Circuits (cont)
 - 8.2 State-Assignment Problem
 - One-Hot Encoding
 - 8.7 Design of a Counter Using the Sequential Circuit Approach
 - 8.7.1 State Diagram and State Table for Modulo-8 Counter
 - 8.7.2 State Assignment
 - 8.7.3 Implementation Using D-Type Flip-Flops
 - 8.7.4 Implementation Using JK-Type Flip-Flops
 - 8.7.5 Example – A Different Counter

Reading Assignment

■ Roth

□ 11 Latches and Flip-Flops


- 11.5 S-R Flip-Flop
- 11.6 J-K Flip-Flop
- 11.7 T Flip-Flop
- 11.8 Flip-Flops with Additional Inputs
- 11.9 Summary

□ 12 Registers and Counters

 - 12.5 Counter Design Using S-R and J-K Flip-Flops
- 12.6 Derivation of Flip-Flop Input Equations – Summary

The JK Flip-Flop

- Allows $J = K = 1$ condition
 - Implemented with a gated SR latch and feedback of Q and Q^*
 - Q toggles ($Q^+ = Q'$) on $J = K = 1$




The JK Flip-Flop (cont)

- Characteristic table and equation
 - Karnaugh map of characteristic table
 - Characteristic equation
 - $Q^+ = JQ' + K'Q$

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(b) Characteristic table

 


$$Q(t+1) = JQ' + K'Q$$

 (c) Characteristic equation

The JK Flip-Flop (cont)

- Implementation using a D flip-flop
 - Characteristic Function at D input




The JK Flip-Flop

- State table

PS (Q)	NS (Q ⁺)			
	JK = 00	01	10	11
0	0	0	1	1
1	1	0	1	0



The JK Flip-Flop

- State diagram

 


The JK Flip-Flop

  - With clock circuitry and timing
 - Positive edge triggered JK flip-flop




The Master Slave JK Flip-Flop

 - Master Slave JK Flip-Flop
 - Rising edge triggered
 - note CLK inverted to master



The Master Slave JK Flip-Flop

 - Master Slave JK Flip-Flop
 - Falling edge triggered
 - note CLK (CP) inverted to slave




The Master Slave JK Flip-Flop

- Master active on $CLK = 1$
- Slave active on $CLK = 0$
 - Latch data in master on $CLK = 1$
 - Transfer data to slave (output) on $CLK = 0$
- Timing Diagram Initial Conditions
 - $CLK = 0, J = 1, K = 0, Y = 0, Q = 0$

The Master Slave JK Flip-Flop

- Timing Diagram

 


The JK Flip-Flop (cont)

- What happens if $J = K = 1$ for an indefinite period of time (i.e., much greater than clock period)?
 - Output oscillates at $\frac{1}{2}$ the frequency of the clock
 - Divide by two counter

The T (Toggle or Trigger) Flip-Flop

- Connect J and K inputs together
 - Combined input “T”

Characteristic Table

 

Characteristic Equation

Timing Diagram


The T Flip-Flop

- State Table

PS (Q)	NS (Q ⁺)	
	T = 0	T = 1
0	0	1
1	1	0

The T Flip-Flop


- State Diagram

 

The T Flip-Flop (from JK/D)

$$Q^+ = JQ' + K'Q$$

$$Q^+ = T'Q + TQ' = T \text{ XOR } Q$$

 


Counter Design with T Flip-Flops

- 3 bit binary counter design example
 - “State” refers to Q’s of flip-flops
 - 3 bits, 8 states
 - Decimal 0 through 7
- No inputs
 - Transition on every clock edge
 - i.e., state changes on every clock edge
 - Assume clocked, synchronous flip-flops

Counter Design with T Flip-Flops

- State Diagram

 


Counter Design with T Flip-Flops

- State table

PS			NS		
A	B	C	A ⁺	B ⁺	C ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Counter Design with T Flip-Flops



Next State Maps

 

$$A^+ = AB' + AC' + A'BC = D_A$$

$$B^+ = B'C + BC' = D_B$$

$$C^+ = C' = D_C$$

  

Counter Design with T Flip-Flops

- Using D flip-flops, inputs are derived directly from next state maps
 - $D = Q^+$
- Using T flip flops
 - Excitation table (used for design)
 - $T = Q \text{ XOR } Q^+$
 - Need to find inputs to T flip-flops
 - Mapping state changes
 - $Q \rightarrow Q^+$ requires $T = ?$

Counter Design with T Flip-Flops

- T Flip-Flop Excitation Table
 - $T = Q \text{ XOR } Q^+$

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0

Counter Design with T Flip-Flops

■ State Variable A

□ $T_A = A^+ \text{ (XOR) } A$

		BC			
		00	01	11	10
A					
A=0	{			$A^+ = 1$	
A=1	{	$A^+ = 1$	$A^+ = 1$		$A^+ = 1$

$$A^+ = AB' + AC' + A'BC = D_A$$

		BC			
		00	01	11	10
A					
0				$T=1$	
1				$T=1$	

$$T_A = BC$$

Counter Design with T Flip-Flops

- State Variable B
 - $T_B = B^+ \text{ (XOR) } B$

BC		B=0		B=1	
		00	01	11	10
A	0		$B^+ = 1$		$B^+ = 1$
	1		$B^+ = 1$		$B^+ = 1$

$$B^+ = B'C + BC' = D_B$$

BC		00	01	11	10
		A		$T=1$	$T=1$
	0		$T=1$	$T=1$	
	1		$T=1$	$T=1$	

$$T_B = C$$

Counter Design with T Flip-Flops

- State Variable C

- $T_C = C^+ \text{ (XOR) } C$

BC		C=0		C=1		C=0	
		00	01	11	10	10	00
A	0	C ⁺ = 1					C ⁺ = 1
	1	C ⁺ = 1					C ⁺ = 1

$$C^+ = C' = D_C$$

BC		00	01	11	10
		A	0	T=1	T=1
1	T=1		T=1	T=1	T=1


$$T_C = 1$$

Counter Design with T Flip-Flops

- Implement design using T Flip-Flops with asynchronous preset and clear
 - Asynchronous preset (PRN) and clear (CLR_N) override clock and other inputs
 - Preset : $Q \rightarrow 1$, Clear : $Q \rightarrow 0$
 - Used to initialize system (all flip-flops) to known state
 - Bubbles indicate “low true” or “active low”
 - $TA = BC$, $TB = C$, $TC = 1$


Counter Design with T Flip-Flops

■ Schematic

 


Counter Design with T Flip-Flops

 - Timing Diagram
 - ❑ QA toggles when $B = C = 1$
 - ❑ QB toggles when $C = 1$
 - ❑ QC toggles on every clock edge



Counter Design with JK Flip-Flops

- State Diagram

 

Counter Design with JK Flip-Flops

■ State Table

PS			NS		
A	B	C	A ⁺	B ⁺	C ⁺
0	0	0	1	0	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	0	1	0

Counter Design with JK Flip-Flops

Next State Maps

		BC			
		00	01	11	10
A	0	1	X		
	1	1	X		X

$$A^+ = B' = D_A$$

$$B^+ = A + BC' = D_B$$

$$C^+ = AB' + BC' = D_C$$

		BC			
		00	01	11	10
A	0		X		1
	1	1	X	1	X


		BC			
		00	01	11	10
A	0		X		1
	1	1	X		X

Counter Design with JK Flip-Flops

- JK Flip-Flop Excitation Table

- Recall JK state diagram
- Create excitation table from state diagram

- $Q^+ = JQ' + K'Q$

 

Counter Design with JK Flip-Flops

- State Variable A

- $A^+ = B'$

		BC			
		00	01	11	10
A	A=0	$A^+=1$	$A^+=X$		
	A=1	$A^+=1$	$A^+=X$		$A^+=X$

		BC			
		00	01	11	10
A	0	1	X	0	0
	1	X	X	X	X

$$J_A = B'$$

		BC			
		00	01	11	10
A	0	X	X	X	X
	1	0	X	1	X

$$K_A = B$$

Counter Design with JK Flip-Flops

- State Variable B

- $B^+ = A + BC'$

		BC			
		00	01	11	10
A	0	0	X	X	X
	1	1	X	X	X

		B=0		B=1	
		00	01	11	10
A	0		$B^+=X$		$B^+=1$
	1	$B^+=1$	$B^+=X$	$B^+=1$	$B^+=X$

$J_B = A$

		BC			
		00	01	11	10
A	0	X	X	1	0
	1	X	X	0	X

$K_B = A'C$

Counter Design with JK Flip-Flops

- State Variable C

- $C^+ = AB' + BC'$

BC	C=0		C=1	
	00	01	11	10
A				
0		$C^+=X$		$C^+=1$
1	$C^+=1$	$C^+=X$		$C^+=X$

A	BC			
	00	01	11	10
0	0	X	X	1
1	1	X	X	X

$$J_C = A + B$$

A	BC			
	00	01	11	10
0	X	X	1	X
1	X	X	1	X

$$K_C = 1$$