

# Mealy and Moore Machines

ECE 152A – Winter 2012

# Reading Assignment

- Brown and Vranesic
  - 8 Synchronous Sequential Circuits
    - 8.3 Mealy State Model

# Reading Assignment

- Roth

- 13 Analysis of Clocked Sequential Circuits

- 13.1 A Sequential Parity Checker
    - 13.2 Analysis by Signal Tracing and Timing Charts
    - 13.3 State Tables and Graphs
    - 13.4 General Models for Sequential Circuits

# Finite State Machines

- Thus far, sequential circuit (counter and register) outputs limited to state variables
- In general, sequential circuits (or Finite State Machines, FSM's) have outputs in addition to the state variables
  - For example, vending machine controllers generate output signals to dispense product, provide change, illuminate displays, etc.

# Finite State Machines

- Two types (or models) of sequential circuits (or finite state machines)
  - Mealy machine
    - Output is function of present state and present input
  - Moore machine
    - Output is function of present state only
- Analysis first, then proceed to the design of general finite state machines

# Analysis by Signal Tracing and Timing Diagrams

## ■ Timing Analysis


- ❑ Determine flip-flop input equations
- ❑ Determine output equations
  - Mealy or Moore model
- ❑ Generate timing diagram illustrating circuit's response to a particular input sequence
  - Outputs as well as to state

# Moore Network Example

- Implemented with falling edge triggered (by way of external inverter) JK flip-flops
- Schematic (following slide)
  - $J_A = x \quad K_A = xB'$
  - $J_B = x \quad K_B = x \text{ XOR } A' = xA + x'A'$
  - $z = B$  (function of present state only)

# Moore Network Example

## ■ Schematic

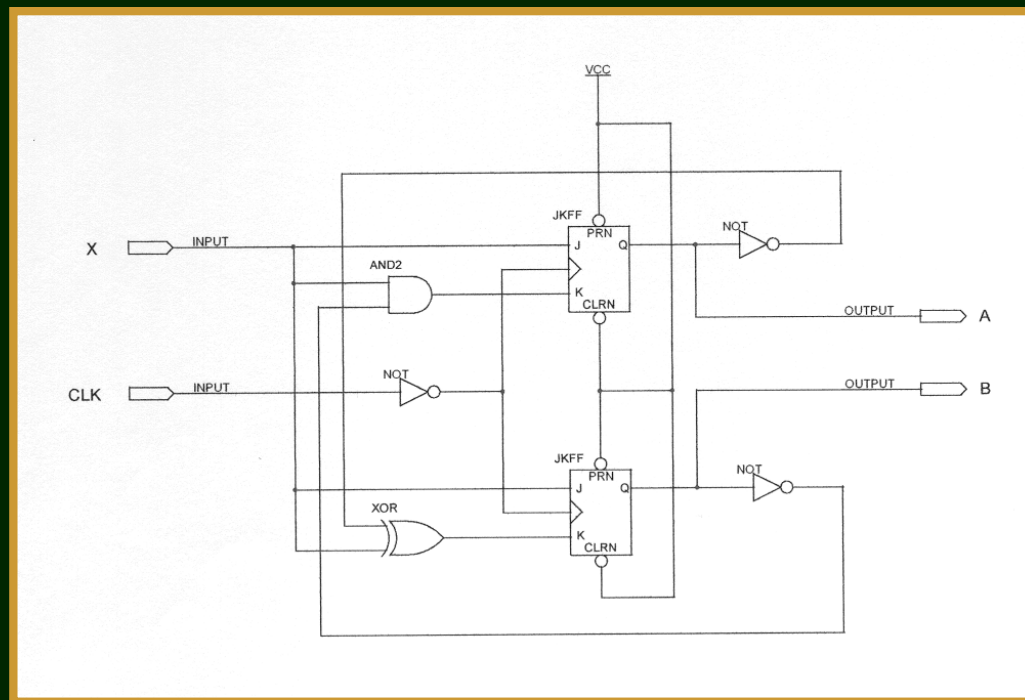




# Moore Network Example

- Timing Diagram and Analysis
  - Initial conditions:
    - $A = B = z = 0$
  - Input sequence:
    - $x = 10101$
  - All state and output transitions occur after the falling clock edge
    - Assumes  $x$  changes on rising edge
      - Best case assumption for satisfying setup and hold time

# Moore Network Example
 
## ■ Timing Diagram (Functional Simulation)

$$\begin{aligned} J_A &= x & K_A &= xB' \\ J_B &= x & K_B &= x \text{ XOR } A' = xA + x'A' \\ z &= B \end{aligned}$$



# Mealy Network Example

- Implemented with falling edge triggered (by way of external inverter) JK flip-flops
- Schematic (following slide)
  - $J_A = xB$        $K_A = x$
  - $J_B = x$        $K_B = xA$
  - $z = xB' + xA + x'A'B$ 
    - function of present state and present input

## ■ Schematic



# Mealy Network Example

## ■ Timing Diagram and Analysis

### □ Initial conditions:

- $A = B = 0$
- $z = 1$

### □ Input sequence:

- $x = 10101$

### □ Analysis again assumes $x$ changes on rising edge of clock

### □ All state transitions occur after the falling clock edge (as with Moore machine)

# Mealy Network Example

- Timing Diagram and Analysis (cont)
  - Output transitions occur in response to both input and state transitions
    - “glitches” may be generated by transitions in inputs
    - Moore machines don’t glitch because outputs are associated with present state only
  - Assumes gate delays to output(s) much shorter than clock period
    - All outputs stable before occurrence of active clock edge


# Mealy Network Example

- Timing Diagram (Timing Simulation)

$$\begin{aligned} J_A &= xB \\ J_B &= x \end{aligned}$$

$$K_A = x$$
$$K_B = xA$$

$$z = xB' + xA + x'A'B$$

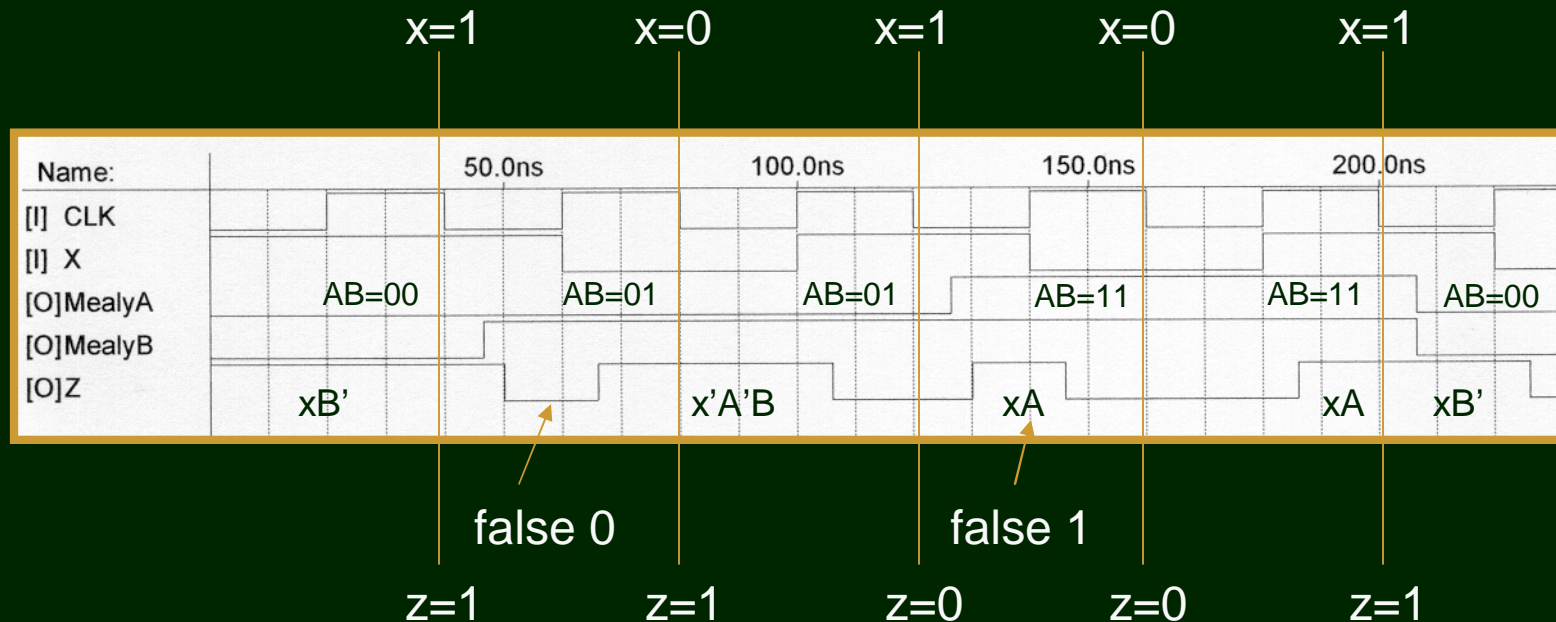

# Mealy Machines and Glitches

- In synchronous network, glitches don't matter
  - All data transfers occur around common, falling (or rising) clock edge
    - Register transfer operations
    - Outputs sampled only on active clock edge
  - Output is stable before and after active clock edge
    - Setup and hold times satisfied



# FSM Outputs & Timing - Summary

- For Moore machine, output is valid after state transition
  - Output associated with stable present state
- For Mealy machine, output is valid on occurrence of active clock edge
  - Output associated with transition from present state to next state
  - Output in Mealy machine occurs one clock period before output in equivalent Moore machine

# Derivation of State Tables and Diagrams

- Timing diagram illustrates the sequential circuit's response to a particular input sequence
  - May not include all states and all transitions
- In general, analysis needs to produce state diagram and state table
- Reverse of design process
  - Begin with implementation, derive state diagram

# Derivation of State Tables and Diagrams

- Returning to Moore machine example
  - Flip-Flop inputs and circuit output functions
    - $J_A = x$                        $K_A = xB'$
    - $J_B = x$                        $K_B = x \text{ XOR } A' = xA + x'A'$
    - $z = B$  (function of present state only)
- Begin with characteristic equation for JK Flip-Flop
  - $Q^+ = JQ' + K'Q$

# Derivation of State Tables and Diagrams

- Using characteristic function, generate next state equations and maps for each flip flop

- $Q^+ = JQ' + K'Q \rightarrow A^+ = J_A Q' + K_A' Q$


- $A^+ = xA' + (xB')' \quad A = xA' + x'A + AB$

- $Q^+ = JQ' + K'Q \rightarrow B^+ = J_B Q' + K_B' Q$


- $B^+ = xB' + (x \text{ xor } A')'B = xB' + xA'B + x'AB$

# Derivation of State Tables and Diagrams

## ■ Next State Maps

 

$$A^+ = xA' + x'A + AB$$

 

$$B^+ = xB' + xA'B + x'AB$$


# Derivation of State Tables and Diagrams

## ■ State Table

PS AB	NS		z (=B)
	X=0 AB	X=1 AB	
00	00	11	0
01	00	11	1
10	10	01	0
11	11	10	1

# Derivation of State Tables and Diagrams

## ■ State Diagram

 

PS AB	NS		z (=B)
	X=0 AB	X=1 AB	
00	00	11	0
01	00	11	1
10	10	01	0
11	11	10	1

# Derivation of State Tables and Diagrams

- Mealy machine example
  - Flip-Flop inputs and circuit output functions
    - $J_A = xB$        $K_A = x$
    - $J_B = x$        $K_B = xA$
    - $z = xB' + xA + x'A'B$
- Once again, begin with characteristic Equation for JK Flip-Flop
  - $Q^+ = JQ' + K'Q$



# Derivation of State Tables and Diagrams

- Generate next state equations and maps for each flip flop

- $Q^+ = JQ' + K'Q \rightarrow A^+ = J_A Q' + K_A' Q$

- $A^+ = xBA' + x'A$

- $Q^+ = JQ' + K'Q \rightarrow B^+ = J_B Q' + K_B' Q$

- $B^+ = xB' + (xA)'B = xB' + x'B + A'B$

# Derivation of State Tables and Diagrams

## ■ Next state and output maps

x	AB			
	00	01	11	10
0			1	1
1		1		

$$A^+ = xBA' + x'A$$

$$B^+ = xB' + x'B + A'B$$

$$z = xB' + xA + x'A'B$$

x	AB			
	00	01	11	10
0		1	1	
1	1	1		1

x	AB			
	00	01	11	10
0		1		
1	1		1	1


# Derivation of State Tables and Diagrams

## ■ State Table

PS AB	NS	
	x=0 AB,z	x=1 AB,z
00	00,0	01,1
01	01,1	11,0
10	10,0	01,1
11	11,0	00,1

# Derivation of State Tables and Diagrams

## ■ State Diagram

 

PS AB	NS	
	x=0 AB,z	x=1 AB,z
00	00,0	01,1
01	01,1	11,0
10	10,0	01,1
11	11,0	00,1