

# Sequential Circuit Design with Verilog

ECE 152A – Winter 2012

## Reading Assignment

- Brown and Vranesic
  - 6 Combinational – Circuit Building Blocks
    - 6.6 Verilog for Combinational Circuits
      - 6.6.1 The Conditional Operator
      - 6.6.2 The If-Else Statement
      - 6.6.3 The Case Statement

## Reading Assignment

- **Brown and Vranesic (cont)**

- 7 Flip-Flops, Registers, Counters, and a Simple Processor

- 7.12 Using Storage Elements with CAD Tools

- 7.12.2 Using Verilog Constructs for Storage Elements

- 7.12.3 Blocking and Non-Blocking Assignments

- 7.12.4 Non-Blocking Assignments for Combinational Circuits

- 7.12.5 Flip-Flops with Clear Capability

- 7.13 Using Registers and Counters with CAD Tools

- 7.13.3 Using Verilog Constructs for Registers and Counters

## The Gated D Latch

- **Transparent on high phase of clock**

```
module D_latch(D, Clk, Q);
  input D, Clk;
  output Q;
  reg Q;

  always @(D or Clk)
    if (Clk)
      Q = D;
endmodule
```

## The Gated D Latch

- The “if” construct
  - When D or CLK change value:
    - if CLK = 1, set Q = D
  - Since there is no else, assignment occurs only when CLK = 1
    - Q follows D when CLK = 1
    - Q remains latched on CLK = 0
  - “Always” construct triggered by change in value of D or CLK
    - Either change can cause the output to change

## The Gated D Latch

- The “always” construct
  - Responds to changes in the signals on the sensitivity list
    - always @ (D or Clk)
  - Example above is “level sensitive”
    - When D or Clk changes value
  - Make edge triggered by using Verilog keywords posedge and negedge
    - i.e., always @ (posedge Clk)

## The Edge Triggered D Flip-Flop

- Positive edge triggered

```
module flipflop(D, Clock, Q);  
    input D, Clock;  
    output Q;  
    reg Q;  
  
    always @(posedge Clock)  
        Q = D; // Q+ = D, characteristic function  
  
endmodule
```

## The Edge Triggered D Flip-Flop

- D is not included on sensitivity list since it cannot cause output (Q) to change
  - No transparent phase with edge triggered flip-flops
- Characteristic function used in assignment statement
  - Defining next state (Q<sup>+</sup>) of the flip-flop

## The Edge Triggered JK Flip-Flop

- Assign characteristic function to Q on rising clock edge ( $Q^+ = JQ' + K'Q$ )

```
module JKflipflop(J,K, Clock, Q);
  input J,K, Clock;
  output Q;
  reg Q;

  always @(posedge Clock)
    Q = J && ~Q || ~K && Q; // Q+ = JQ' + K'Q

endmodule
```


February 15, 2012

ECE 152A - Digital Design Principles

9

## The Edge Triggered JK Flip-Flop

- Functional Simulation

 

February 15, 2012

ECE 152A - Digital Design Principles

10

## The Edge Triggered T Flip-Flop

- Assign characteristic function to Q on rising clock edge ( $Q^+ = T \text{ XOR } Q$ )


```
module Tflipflop(T, Clock, Q);
  input T, Clock;
  output Q;
  reg Q;

  always @(posedge Clock)
    Q = T ^ Q; // Q = T XOR Q

endmodule
```

## The Edge Triggered T Flip-Flop

- Functional Simulation

 

## Blocking and Non-Blocking Assignments

- **Q = D**
  - Equal sign (=) signifies a blocking assignment
- **Statements are evaluated in the order in which they are written**
  - If a variable is given a value by a blocking assignment, the new value is used in evaluating all subsequent statements in the block

## Blocking and Non-Blocking Assignments

### ■ Blocking Assignment Statement Example

```
module example1(D, Clock, Q1, Q2);
  input D, Clock;
  output Q1, Q2;
  reg Q1, Q2;

  always @(posedge Clock)
  begin
    Q1 = D;
    Q2 = Q1;
  end


endmodule
```

## Blocking and Non-Blocking Assignments

- Example synthesizes two positive edge triggered D flip-flops
  - Both flip-flops triggered by same clock edge
- Both assignments in always block are blocking
  - Q1 gets the value D
  - Q2 then gets the new value of Q1
    - $Q1^+$ , which is now D
 
## Blocking and Non-Blocking Assignments

- The synthesized circuit with blocking assignment statements






## Blocking and Non-Blocking Assignments

- Non-Blocking Statements (`<=>`)
  - Non-blocking assignment statements in an always block are evaluated using the values of the variables when the block is entered

```
always @(posedge Clock)
begin
    Q1 <= D; // substitute
    Q2 <= Q1; // non-blocking assignments
end
```

## Blocking and Non-Blocking Assignments

 - Q2 gets the value of Q1 when the always block is entered
  - The synthesized circuit with non-blocking assignment statements
    - Flip-flops connected in cascade



## Blocking and Non-Blocking Assignments

### ■ Blocking Assignment Statement Example

```
module example3(x1, x2, x3, Clock, f, g);
  input x1, x2, x3, Clock;
  output f, g;
  reg f, g;

  always @(posedge Clock)
  begin
    f = x1 & x2;
    g = f | x3;
  end


endmodule
```

## Blocking and Non-Blocking Assignments

- Both f and g are implemented as the outputs of D flip-flops
  - Synthesized as flip-flops because the sensitivity list of the always block specifies posedge Clock
- “g” gets the new value (Q<sup>+</sup>) of “f” OR’d with x<sub>3</sub>
 
## Blocking and Non-Blocking Assignments

- The synthesized circuit
  - Blocking assignment statements



February 15, 2012

ECE 152A - Digital Design Principles

21

## Blocking and Non-Blocking Assignments

- If assignment statements changed to non-blocking

```
always @(posedge Clock)
begin
  f <= x1 & x2;
  g <= f | x3;
end
```

- “g” gets the previous value of “f” (the value when the always block is entered, i.e., Q)


February 15, 2012

ECE 152A - Digital Design Principles

22
 
## Blocking and Non-Blocking Assignments

- The synthesized circuit
  - Non-blocking assignment statements



## Blocking and Non-Blocking Assignments

- General Rule
  - The results of non-blocking assignments are visible only after all of the statements in the always block have been evaluated
  - When there are multiple assignments to the same variable inside an always block, the result of the last assignment is maintained

# Flip-Flops with Clear

## ■ Asynchronous Clear

```
module flipflop(D, Clock, Resetn, Q);
  input D, Clock, Resetn;
  output Q;
  reg Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      Q <= D;

endmodule
```

# Flip-Flops with Clear

## ■ Synchronous Clear

```
module flipflop(D, Clock, Resetn, Q);
  input D, Clock, Resetn;
  output Q;
  reg Q;

  always @(posedge Clock)
    if (!Resetn) // check value of reset on clock edge
      Q <= 0;
    else
      Q <= D;

endmodule
```

## 4-Bit Binary Counter

### ■ Counter includes reset and enable

```
module upcount(Resetn, Clock, E, Q);
    input Resetn, Clock, E;
    output [3:0] Q;
    reg [3:0] Q;

    always @(negedge Resetn or posedge Clock)
        if (!Resetn)
            Q <= 0; // asynchronous reset overrides enable
        else if (E)
            Q <= Q + 1; // synthesizes adder circuit

endmodule
```


February 15, 2012

ECE 152A - Digital Design Principles

27

## 4-Bit Binary Counter

### ■ Functional Simulation

 


February 15, 2012

ECE 152A - Digital Design Principles

28
 
## Finite State Machine (FSM) Design

- Recall state diagram for JK flip-flop counter from previous lecture



February 15, 2012

ECE 152A - Digital Design Principles

29

## Finite State Machine (FSM) Design

- The State Table

PS			NS		
A	B	C	A <sup>+</sup>	B <sup>+</sup>	C <sup>+</sup>
0	0	0	1	0	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	0	1	0

February 15, 2012

ECE 152A - Digital Design Principles

30

## Finite State Machine (FSM) Design

- Can't use addition operator because sequence is not binary count
  - See previous example
- Use parameter statement to define states

```
parameter [2:0] A = 3'b000, B = 3'b100, C = 3'b111,  
                D = 3'b010, E = 3'b011;
```

## Finite State Machine (FSM) Design

- Use case statement to implement state transitions

```
always @ (posedge clock)  
case(count)  
  A: count <= B;  
  B: count <= C;  
  C: count <= D;  
  D: count <= E;  
  E: count <= A;  
  default: count <= A;  
endcase
```



# Finite State Machine (FSM) Design

## ■ The complete module

```
module jk_counter(count, clock);  
  
    input clock;  
    output [2:0] count;  
  
    reg [2:0] count;  
    parameter [2:0] A = 3'b000, B = 3'b100, C = 3'b111,  
                  D = 3'b010, E = 3'b011;  
  
    always @ (posedge clock)  
    case(count)  
        A: count <= B;  
        B: count <= C;  
        C: count <= D;  
        D: count <= E;  
        E: count <= A;  
        default: count <= A;  
    endcase  
  
endmodule
```

# Finite State Machine (FSM) Design

## ■ Functional Simulation

