

ECE 137 A Mid-Term Exam

Thursday, February 8, 2019

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted

There are 3 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.),
AFTER STATING and approximately Justifying them.

Name: _____

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		10	2f		15
1b		5	3a		8
1c		5	3b		8
1d		10	3c		4
1e		15			
2a		10			
2b		5			
2c		5			
2d		10			
2e		5			
TOTAL					100

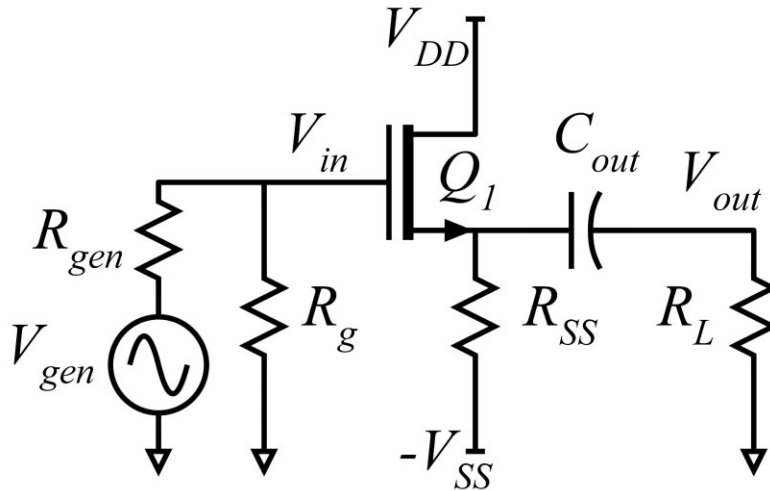Problem 1, 30 points

You will be working on the circuit below:



The transistor has

$$K_{\mu} = \mu c_{gs} W_g / 2L_g = 0.55 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$$

$$K_v = c_{gs} v_{inj} W_g = 0.69 \text{mA/V} \cdot (W_g / 1\mu\text{m})$$

$$\Delta V = v_{inj} L_g / \mu = 0.625 \text{V}, V_{th} = 0.3 \text{V}, 1/\lambda = 20 \text{V}$$

The supplies are +2V and -2 V

You are to bias the transistor at 10mA drain current, and with -0.5 V DC source voltage.

$$R_g = 1 \text{ M}\Omega, R_{gen} = 30 \text{ k}\Omega, R_L = 500 \Omega$$

C_{out} is very large (AC short-circuit at the signal frequency)

Part a, 10 points


DC bias.

Find the following:

FET gate width W_g _____ R_{ss} _____

Part b, 5 points

DC bias

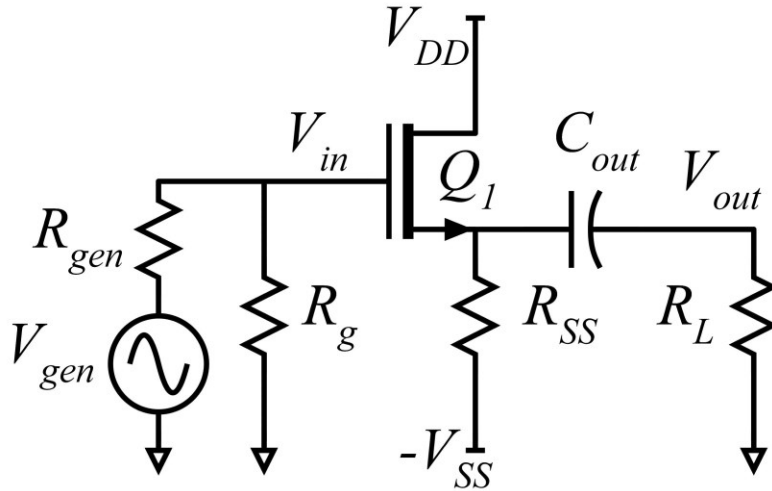

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**, give **all resistor values**, and give the **FET width**.

Part c, 5 points

Find the FET small signal parameters

$g_m =$ _____ $R_{ds} =$ _____

Part d, 10 points.


Find the small signal voltage gain V_{out}/V_{in} and the amplifier small-signal input resistance.

$V_{out}/V_{in} =$ _____

$R_{in, \text{ amplifier}} =$ _____

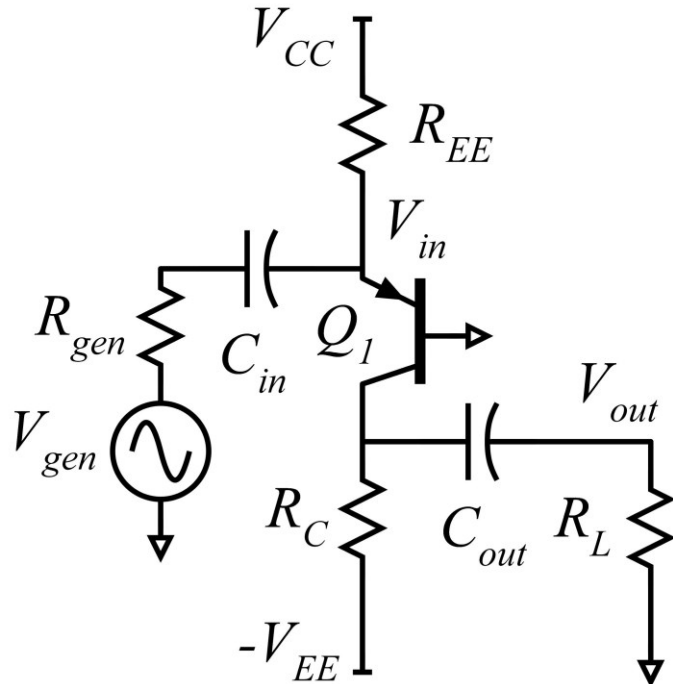Problem 2, 50 points

You will be working on the circuit below:



Q1: $\beta = 100$, $V_A = \text{infinity V}$, $V_{ce,sat} = 0.5\text{V}$

The supplies are +10V and -10 V.

You will bias the transistor with 1mA collector current.

The DC collector bias voltage is -5V.

R_L is 1 k Ω , R_{gen} is 100 Ω ,

C_{out} and C_{in} are very large (AC short-circuit at the signal frequency)

Part a, 10 points


DC bias.

Find the following:

$$R_{EE} = \underline{\hspace{2cm}} \quad R_C = \underline{\hspace{2cm}}$$

Part b, 5 points

DC bias

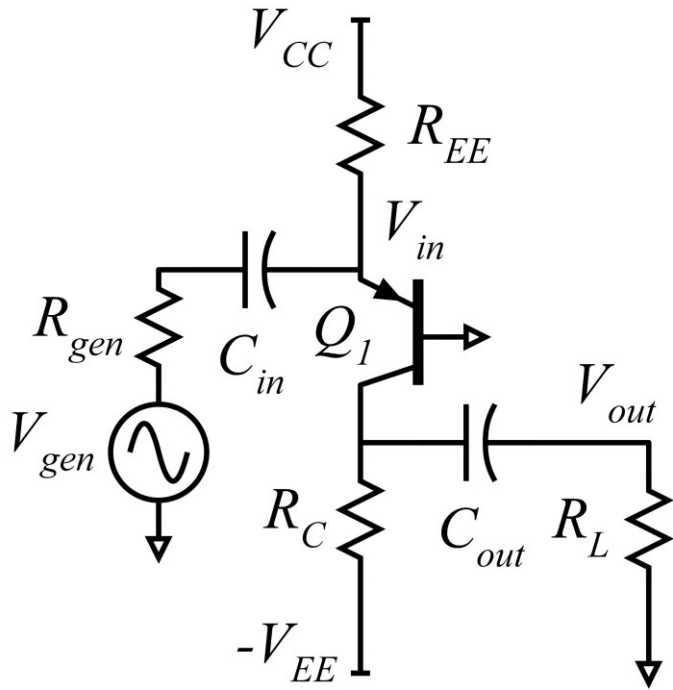

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**, and give **all resistor values**,

Part c, 5 points

Find the small signal parameters of Q1.

$g_m =$ _____ $R_{ce} =$ _____ $R_{be} =$ _____

Part d, 10 points.

Find the small signal voltage gain (V_{out}/V_{in}) of Q1 and the amplifier small-signal input resistance.

$V_{out}/V_{in} =$ _____

$R_{in,amp} =$ _____

Part e, 5 points

Find (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$(V_{in}/V_{gen}) =$ _____

$(V_{out}/V_{gen}) =$ _____


Part f, 15 points

Now you must find the maximum signal swings. Find the output voltage due to saturation and cutoff in Q2. ***Give the sign (+ or -) in your answers below.***

Cutoff of Q1; Maximum ΔV_{out} resulting = _____

Saturation of Q1; Maximum ΔV_{out} resulting = _____

Problem 3, 20 points
nodal analysis

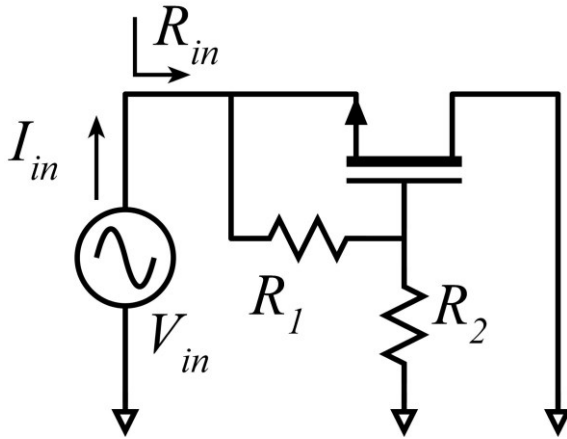

You will be working on the circuit to the left.

Ignore DC bias analysis. You don't need it.

The transistor has transconductance g_m .

The drain-source resistance R_{ds} of the transistor is infinity (so you don't need to draw it!)

Part a, 8 points

Draw the small-signal equivalent circuit

Part b, 8 points

Find, by nodal analysis, a small-signal expression for $R_{in} = V_{in}/I_{in}$.

$R_{in} =$ _____

Part c, 4 points

$g_m = 1 \text{ mS}$, $R_1 = 10 \text{ k}\Omega$, $R_2 = 500 \text{ }\Omega$.
Give a numerical value for R_{in} .

$R_{in} =$ _____