

ECE 137 A Mid-Term Exam

Tuesday February 9, 2021

Closed book: Class crib sheet and 1 page personal notes permitted.

There are 2 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.) , ***AFTER STATING and approximately Justifying them.***

Name: SOLUTION

Part	Points Received	Points Possible
1a		9
1b		5
1c		6
1d		15
1e		15
1f		6
1g		14
2a		12
2b		13
2c		5
TOTAL		100

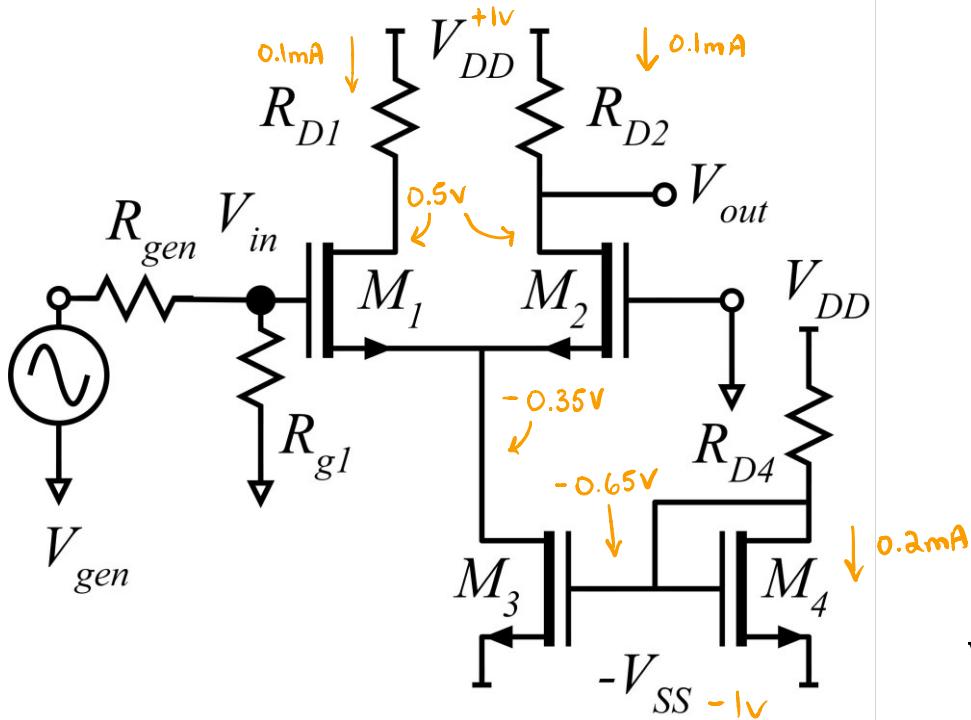Problem 1, 70 points

You will be working on the circuit below:



$$V_{gs1} = V_{gs2} = 0.35V$$

$$V_{gs3} = V_{gs4} = 0.35V$$

The transistors all have: $K_\mu = \mu c_{gs} W_g / 2L_g = 10\text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$

$$K_v = c_{gs} v_{inj} W_g = 2\text{mA/V} \cdot (W_g / 1\mu\text{m})$$

$$\Delta V = v_{inj} L_g / \mu = 0.1\text{V}, V_{th} = 0.3\text{V}, 1/\lambda = 10\text{V}$$

The supplies are +1V and -1V

$R_{gen} = 100 \text{ kOhms}$, $R_{g1} = 1 \text{ MOhms}$,

Part a, 9 points

DC bias.

The sources of M1 and M2 are to be biased at -0.35 Volts

The drains of M1 and M2 are to be biased at +0.5 volts.

The gates of M3 and M4 are to be biased at -0.65 Volts.

M1 and M2 are to be biased at 0.1 mA drain current

M4 is to be biased at 0.2 mA drain current.

Find the following:

$$RD1 = \underline{5K\Omega} \quad RD2 = \underline{5K\Omega} \quad RD4 = \underline{8.25K\Omega}$$

$$Wg1 = \underline{3.69\mu m} \quad Wg2 = \underline{3.69\mu m} \quad Wg3 = \underline{7.51\mu m} \quad Wg4 = \underline{7.73\mu m}$$

3 [

$$R_{D_1} = (V_{DD} - V_{D_1}) / I_{D_1} = (1V - 0.5V) / 0.1mA = \underline{5K\Omega}$$
$$R_{D_2} = (V_{DD} - V_{D_2}) / I_{D_2} = \underline{5K\Omega}$$
$$R_{D_4} = (V_{DD} - V_{G_{14}}) / I_{D_4} = (1V + 0.65V) / 0.2mA = \underline{8.25K\Omega}$$

$$V_{GS1} = V_{GS2} = V_{GS3} = V_{GS4} = 0.35V$$

1 [$V_{GS} - V_{th} = 0.35V - 0.3V = 50mV < \Delta V = 100mV \Rightarrow$ All FETs are mobility-saturated]

$$W_g = 1\mu m \times I_D / [K\mu(V_{GS} - V_{th})^2(1 + \lambda V_{DS})]$$


2 [$W_{g1} = W_{g2} = 1\mu m \times (0.1mA) / [10mA/V^2(0.35V - 0.3V)^2(1 + 1/10V^{-1} \cdot 0.85V)] = \underline{3.69\mu m}$]

1.5 [$W_{g3} = 1\mu m \times (0.2mA) / [10mA/V^2(0.35V - 0.3V)^2(1 + 1/10V^{-1} \cdot 0.65V)] = \underline{7.51\mu m}$]

1.5 [$W_{g4} = 1\mu m \times (0.2mA) / [10mA/V^2(0.35V - 0.3V)^2(1 + 1/10V^{-1} \cdot 0.35)] = \underline{7.73\mu m}$]

Part b, 5 points

DC bias

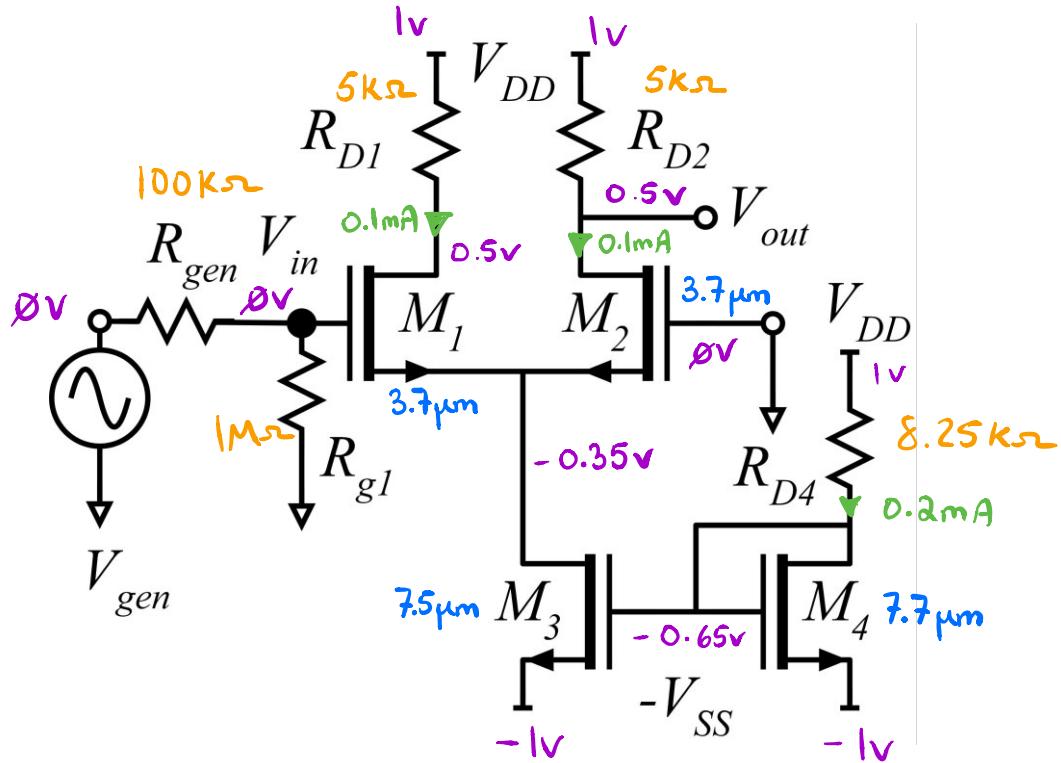

On the circuit diagram above (or on a hand-redrawing of the figure), label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**. **Also label all resistor values, and the width of all MOSFETs.**

+2 Voltages

+1 Resistors

+1 Currents

+1 widths

Part c, 6 points

Find the small signal parameters of all FETs

Transistor	M1	M2	M3	M4
gm	<u>4mS</u>	<u>4mS</u>	<u>8mS</u>	<u>8mS</u>
R _{DS}	<u>108.5 kΩ</u>	<u>108.5 kΩ</u>	<u>53.25 kΩ</u>	<u>51.75 kΩ</u>

3

$$g_{m1} = g_{m2} = \frac{2 I_{D1}}{V_{gs1} - V_{th}} = \frac{2 \times 0.1mA}{(0.35V - 0.3V)} = \underline{4mS}$$

$$g_{m3} = g_{m4} = \frac{2 I_{D3}}{V_{gs3} - V_{th}} = \frac{2 \times 0.2mA}{(0.35V - 0.3V)} = \underline{8mS}$$

| [

$$R_{DS_1} = R_{DS_2} = [1/\lambda + V_{DS_1}] / I_{D1} = [10V + 850mV] / 0.1mA = \underline{108.5 kΩ}$$

| [

$$R_{DS_3} = [10V + 650mV] / 0.2mA = \underline{53.25 kΩ}$$

| [


$$R_{DS_4} = [10V + 350mV] / 0.2mA = \underline{51.75 kΩ}$$

Part d, 15 points.

Find the small signal voltage gain (V_{d2}/V_{s2}) of M2 and M2's small-signal input resistance.

$$V_{d2}/V_{s2} = \underline{19.16 \text{ V/V}}$$

$$R_{in,M2} = \underline{260.9 \Omega}$$

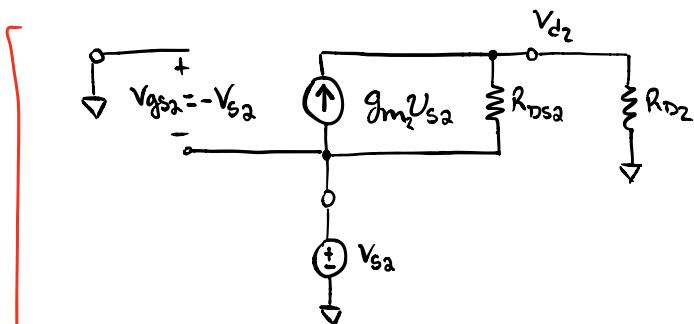

10

$$(V_{s2} - V_{d2})/R_{dss2} + g_{m2}V_{s2} = V_{d2}/R_{D2} \quad (\text{Nodal})$$

$$(V_{s2} - V_{d2})R_{D2} + g_{m2}V_{s2}R_{dss2}R_{D2} = V_{d2}R_{dss2}$$

$$V_{s2}(1 + g_{m2}R_{dss2})R_{D2} = V_{d2}(R_{D2} + R_{dss2})$$

$$\frac{V_{d2}}{V_{s2}} = \frac{(1 + g_{m2}R_{dss2})R_{D2}}{R_{D2} + R_{dss2}} = \frac{(1 + 4ms \times 108.5k\Omega)(5k\Omega)}{108.5k\Omega + 5k\Omega} = \underline{19.16 \text{ V/V}}$$

5

$$R_{in,M2} = R_{D2} \times \frac{V_{s2}}{V_{d2}} = (5k\Omega)(19.16) = \underline{260.9 \Omega}$$

$$\text{or } R_{in,M2} = \frac{R_{dss2} + R_{D2}}{g_{m2}R_{dss2}}$$

Part e, 15 points

Find the small signal voltage gain (V_{s1}/V_{g1}) of M1 and the *** amplifier *** input resistance.

$$V_{s1}/V_{g1} = \underline{0.51 \text{ V/V}}$$

$$R_{in, \text{amplifier}} = \underline{1 \text{ M}\Omega}$$

3 [$R_{in, \text{amp}} = R_{g1} \parallel R_{in, M_1} = 1 \text{ M}\Omega \parallel \infty = \underline{1 \text{ M}\Omega}$

12

$$V_{s1} = g_m V_{gs1} (R_s' \parallel R_{ds1}) + g_m V_{gs2} (R_s \parallel R_{ds2}) + g_m V_{gs3} (R_s \parallel R_{ds3})$$

$$= g_m (V_{g1} - V_{s1}) (R_s' \parallel R_{ds1})$$

$$= g_m (R_s' \parallel R_{ds1}) V_{g1} - g_m (R_s' \parallel R_{ds1}) V_{s1}$$

$$\frac{V_{s1}}{V_{g1}} = \frac{g_m (R_s' \parallel R_{ds1})}{g_m (R_s' \parallel R_{ds1}) + 1} = \frac{(R_s' \parallel R_{ds1})}{(R_s' \parallel R_{ds1}) + 1/g_m1}$$

$$= \frac{R_{in,M2} \parallel R_{ds3} \parallel R_{ds1}}{R_{in,M2} \parallel R_{ds3} \parallel R_{ds1} + 1/g_m1} \approx \frac{R_{in,M2}}{R_{in,M2} + 1/g_m1} = \frac{261\Omega}{261\Omega + 1/4ms}$$

$$= \underline{0.51 \text{ V/V}}$$

Part f, 6 points

Find (V_{out}/V_{in}) , (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$$(V_{out}/V_{in}) = \underline{9.77 \text{ v/v}}$$

$$(V_{in}/V_{gen}) = \underline{0.91 \text{ v/v}}$$

$$(V_{out}/V_{gen}) = \underline{8.9 \text{ v/v}}$$

$$2 [V_{out}/V_{in} = (V_{s1}/V_{g1})(V_{d2}/V_{s2}) = (19.16)(0.51) = \underline{9.77 \text{ v/v}}$$

$$2 [V_{in}/V_{gen} = \frac{R_{in,Amp}}{R_{in,Amp} + R_{gen}} = \frac{R_{g1}}{R_{g1} + R_{gen}} = \frac{1M\Omega}{1M\Omega + 100k\Omega} = \underline{0.91 \text{ v/v}}$$

$$2 [V_{out}/V_{gen} = V_{out}/V_{in} \times V_{in}/V_{gen} = (9.77)(0.91) = \underline{8.9 \text{ v/v}}$$

Part g, 14 points

Now you must find the maximum signal swings.

Give the sign (+ or -) in your answers below.

Cutoff of M1; Maximum ΔV_{out} resulting = -0.5 V

Knee voltage of M1; Maximum ΔV_{out} resulting = +15.3 V

Cutoff of M2; Maximum ΔV_{out} resulting = +0.5 V

Knee of M2; Maximum ΔV_{out} resulting = -0.8 V

3 [M_1 Cutoff $\rightarrow I_{D_1} = 0, I_{D_2} = 0.2 \text{ mA}$

$$V_{out} = V_{DD} - I_{D_2} R_{D2} = 1V - (0.2\text{mA})(5\text{k}\Omega) = 0.8V$$
$$\Delta V_{out} = -0.5V$$

3 [M_2 Cutoff $\rightarrow I_{D_2} = 0 \text{ mA}, V_{out} = V_{DD} = 1V$

$$\Delta V_{out} = +0.5V$$

4 [Knee Voltage, M_1 : $V_{GS_1} - V_{th} = 0.35V - 0.3V = 50\text{mV}$

$$V_{DS_1} = 0.5V - (-0.35V) = 0.85V$$
$$V_{S_1} \text{ goes up } 0.8V$$
$$\Delta V_{out} = \frac{V_{D2}}{V_{S2}} \times 0.8V = (19.16)(0.8V)$$
$$= +15.3V$$

Obviously you'll Saturate


4

$$\text{Knee Voltage, } M_2 : V_{gs2} - V_{th} = 50 \text{ mV}$$

$$V_{DG_1, \min} = -V_{th} = -0.3 \text{ V}$$

$$\Delta V_{out} = -0.3 \text{ V} - 0.5 \text{ V} = -\underline{0.8 \text{ V}}$$

Problem 2, 30 points
nodal analysis

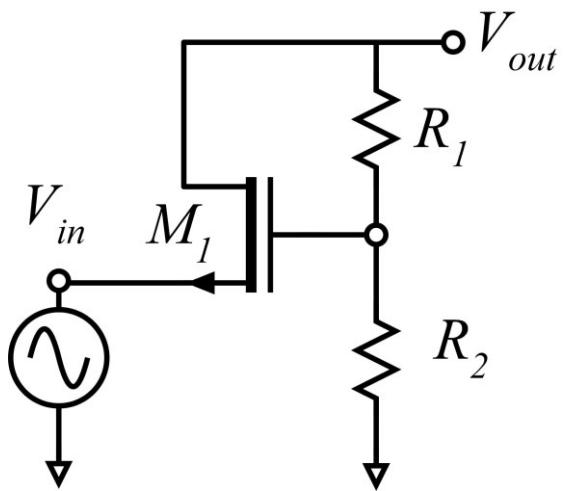



You will be working on the circuit to the left.

Ignore DC bias analysis. You don't need it.

The transistor has transconductance g_{m1} .
 The drain-source resistance R_{ds} is infinity
 (so you don't need to draw it!)

Part a, 12 points

Draw the small-signal equivalent circuit

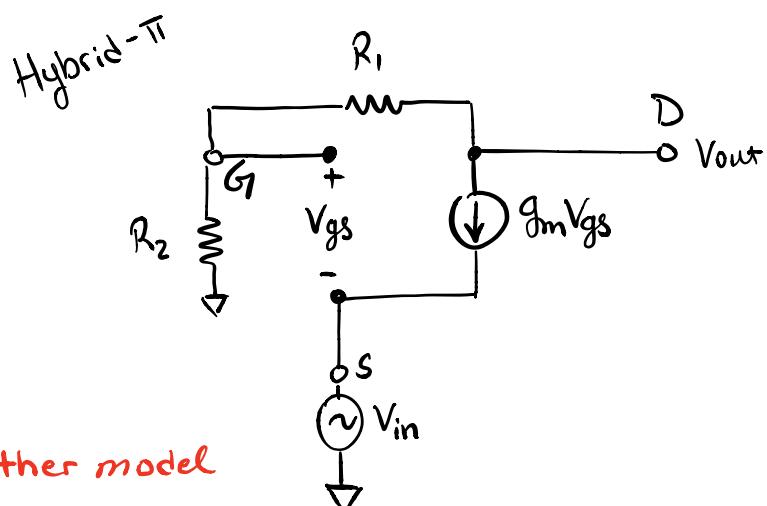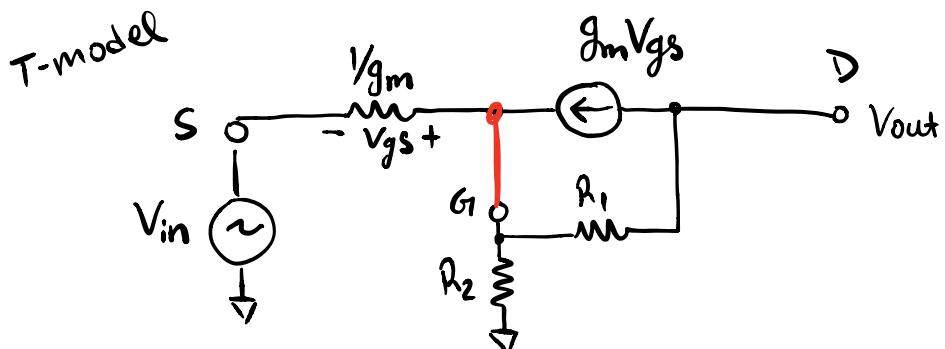

+12 either model

Part b, 13 points

Find, by nodal analysis, a small-signal expression for V_{out}/V_{in} .

$$V_{out}/V_{in} = \frac{g_m(R_1 + R_2)}{(1 + g_m R_2)}$$

$$V_{gs} = V_g - V_{in} = \frac{R_2}{R_1 + R_2} V_{out} - V_{in}$$

$$V_{out} = -g_m V_{gs}(R_1 + R_2) \Rightarrow V_{gs} = \frac{-1}{g_m(R_1 + R_2)} V_{out}$$

$$\left[\frac{1}{g_m(R_1 + R_2)} + \frac{R_2}{R_1 + R_2} \right] V_{out} = \frac{1 + g_m R_2}{g_m(R_1 + R_2)} V_{out} = V_{in}$$

$$V_{out}/V_{in} = \frac{g_m(R_1 + R_2)}{1 + g_m R_2}$$

Part c, 5 points

$gm = 1 \text{ mS}$, $R_1 = 90\text{k}\Omega$, $R_2 = 10\text{k}\Omega$
Give a numerical value for V_{out}/V_{in} .

$$V_{out}/V_{in} = \underline{\underline{9.09 \text{ V/V}}}$$

$$\begin{aligned} V_{out}/V_{in} &= \frac{gm(R_1 + R_2)}{1 + gmR_2} \\ &= \frac{(1\text{mS})(100\text{k}\Omega)}{1 + (1\text{mS})(10\text{k}\Omega)} = \underline{\underline{9.09 \text{ V/V}}} \end{aligned}$$