

Final Exam, ECE 137A

Thursday March 23, 2023, Noon - 3 p.m.

Name: _____

Closed Book Exam:

Class Crib-Sheet and 2 pages (4 surfaces) of student notes permitted

Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

Show your work:


Full credit will not be given for correct answers if supporting work is missing.

Good luck

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		5	2c		5
1b		5	2d		15
1c		5	2e		10
1d		10	3a		5
1e		10	3b		10
2a		10	3c		5
2b		5			
total		100			

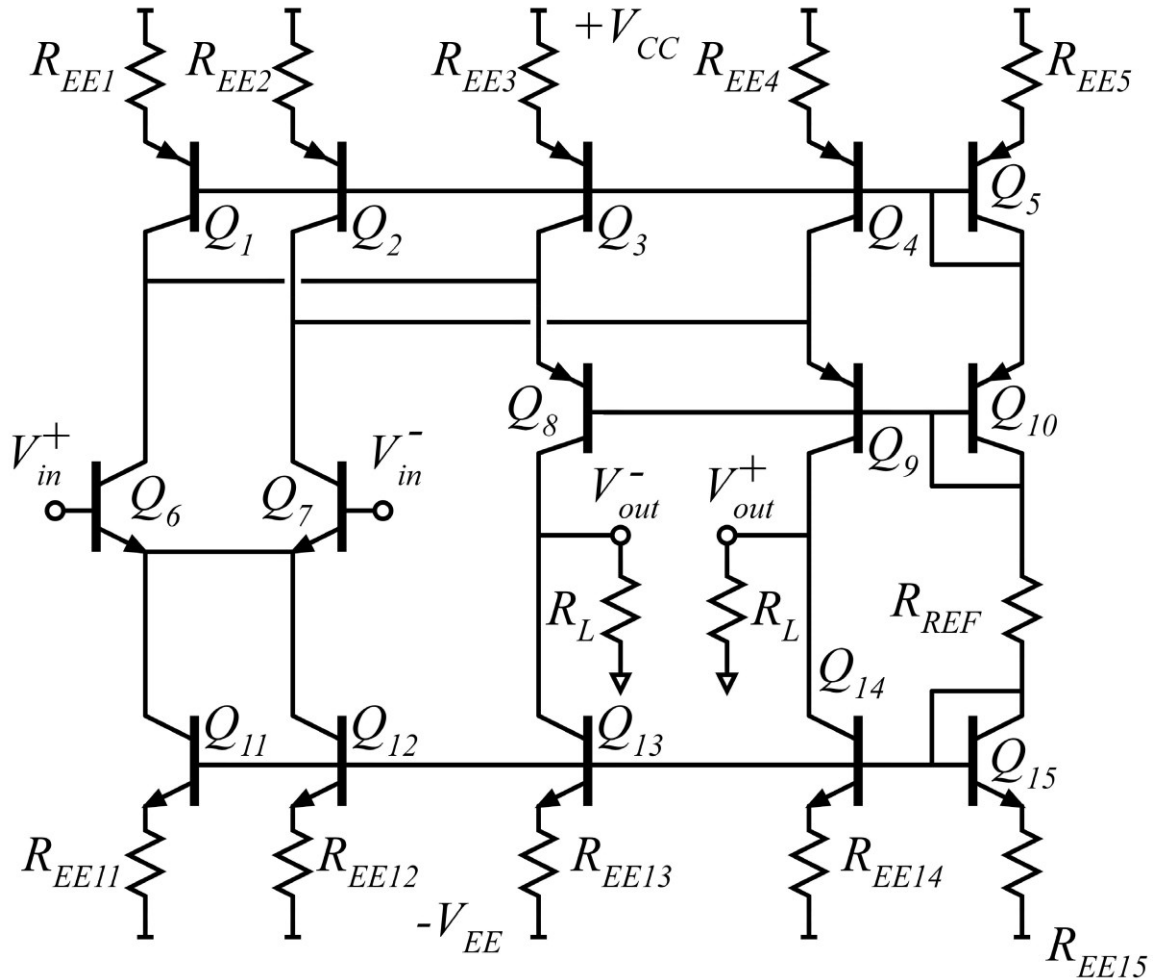Problem 1, 35 points

This is an NOT an Op-Amp: Analyze under the assumption that the differential and common mode input voltages are at zero volts.



All the transistors have the same (matched) I_S , have $\beta = \infty$, and $V_A = \infty$ Volts .

$V_{CE(sat)} = 0.5V$. V_{be} is approximately 0.7 V, but use the exact relationship

$V_{be} = (kT/q) \ln(I_E / I_S)$ when appropriate. The supplies are +3 Volts and -3 Volts. All transistors have the same I_S , and all are biased at 1 mA collector current.

The DC voltage drops across REE5 and REE15 are both 300 mV. $R_L = 1$ kOhm.

Part a, 5 points

DC bias


Find the value of the following resistors:

$R_{ee5} =$ _____ $R_{ee15} =$ _____ $R_{REF} =$ _____

$R_{ee11} =$ _____ $R_{ee12} =$ _____

Part b, 5 points

DC bias

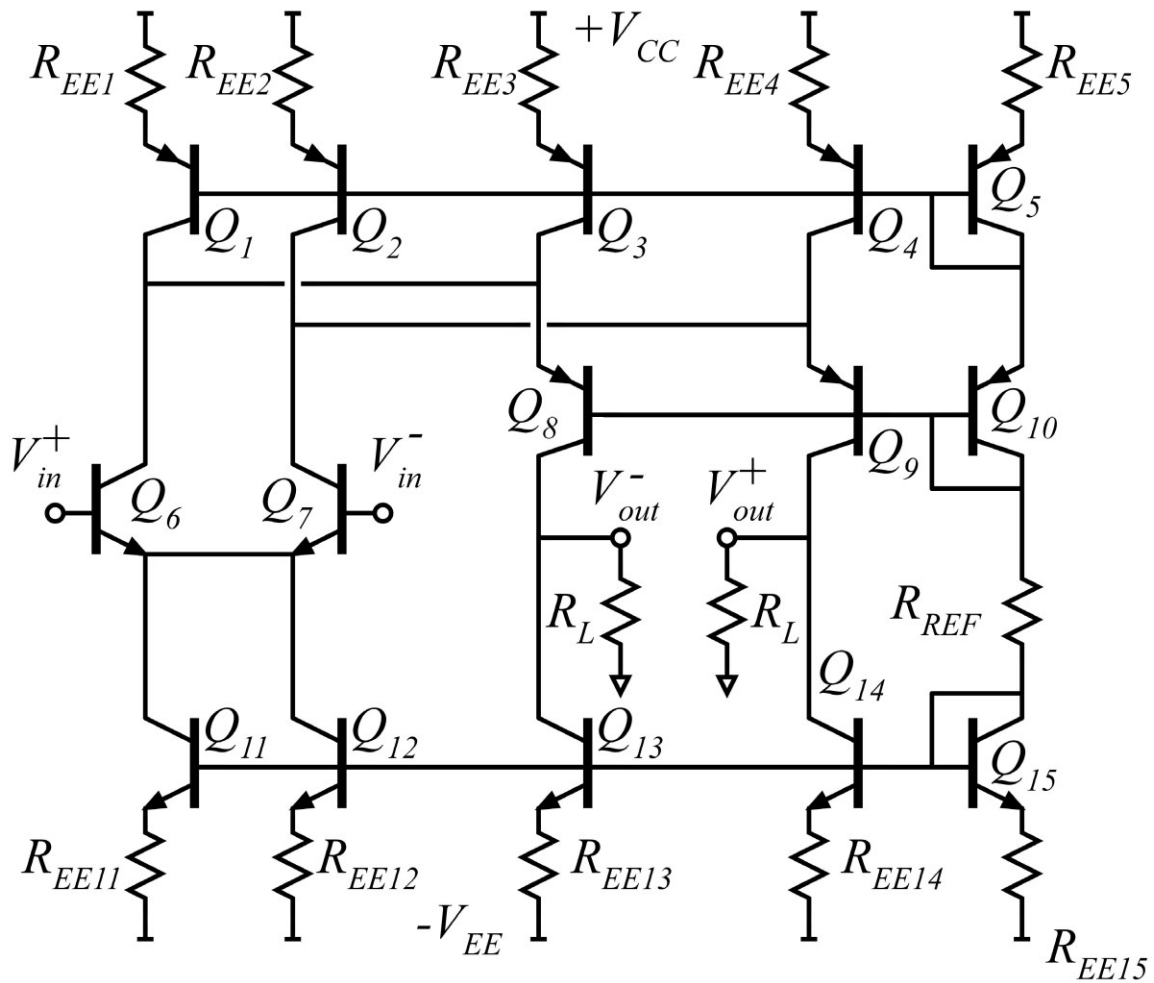

On the circuit diagram above, label the DC voltages at **ALL** nodes.

Part c, 5 points

find the following for all transistors

$g_m =$ _____ $R_{be} =$ _____ $R_{ce} =$ _____

Part d, 10 points.

Find the following

Overall voltage gain $(V_{out}^+ - V_{out}^-) / (V_{in}^+ - V_{in}^-) =$ _____

Differential input impedance $R_{in, Diff} =$ _____


Part e, 10 points

Maximum output voltage swings ***at V_{out}^+ (not V_{out}^-)*** (*show all your work*).

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q6		Do not calculate
Transistor Q7		Do not calculate
Transistor Q9		
Transistor Q14	Do not calculate	

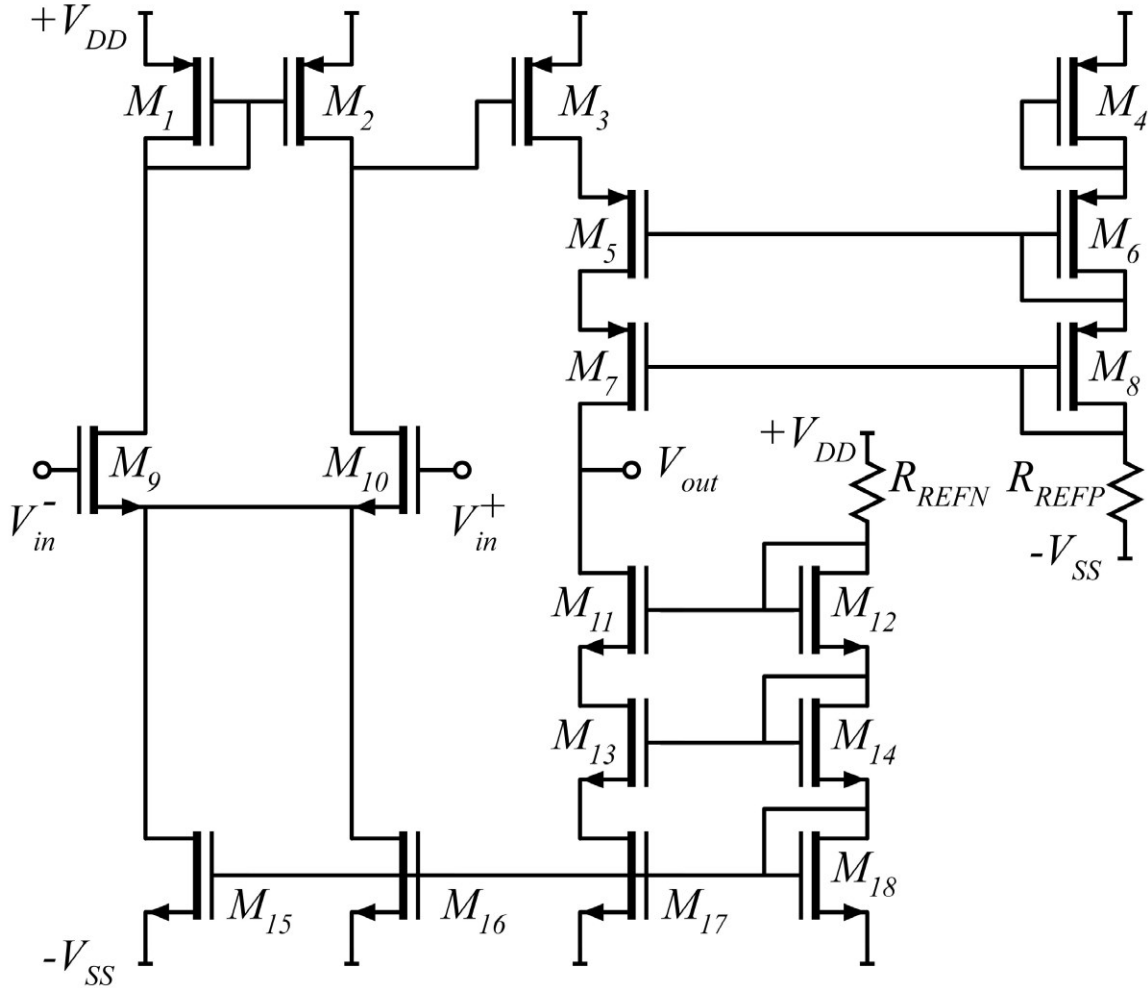Problem 2, 45 points

This is an Op-Amp---analyze the bias under the assumption that DC output voltage V_{out} is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.



The NMOSFETs have $K_{\mu} = 10 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$ $K_v = 2.0 \text{mA/V} \cdot (W_g / 1\mu\text{m})$, $\Delta V = 0.10 \text{V}$, $V_{th} = 0.2 \text{V}$, $1/\lambda = 5 \text{V}$. The PMOS have identical parameters, except, of course, V_{th} is negative. $V_{DD} = +0.75 \text{V}$, $-V_{SS} = -0.75 \text{V}$ All transistors have $|V_{gs}| = 0.25 \text{V}$ and are biased at $I_D = 50 \mu\text{A}$.

Part a, 10 points

DC bias.

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.

(Hint, this should give $V_{i-} = 0V$)

Find the following:


Gate widths of M9 and M10 = _____

Gate width of M15 and M16 = _____

Gate width of **all other MOSFETS** = _____

value of R_{REFN} = _____ value of R_{REFP} = _____

DC bias

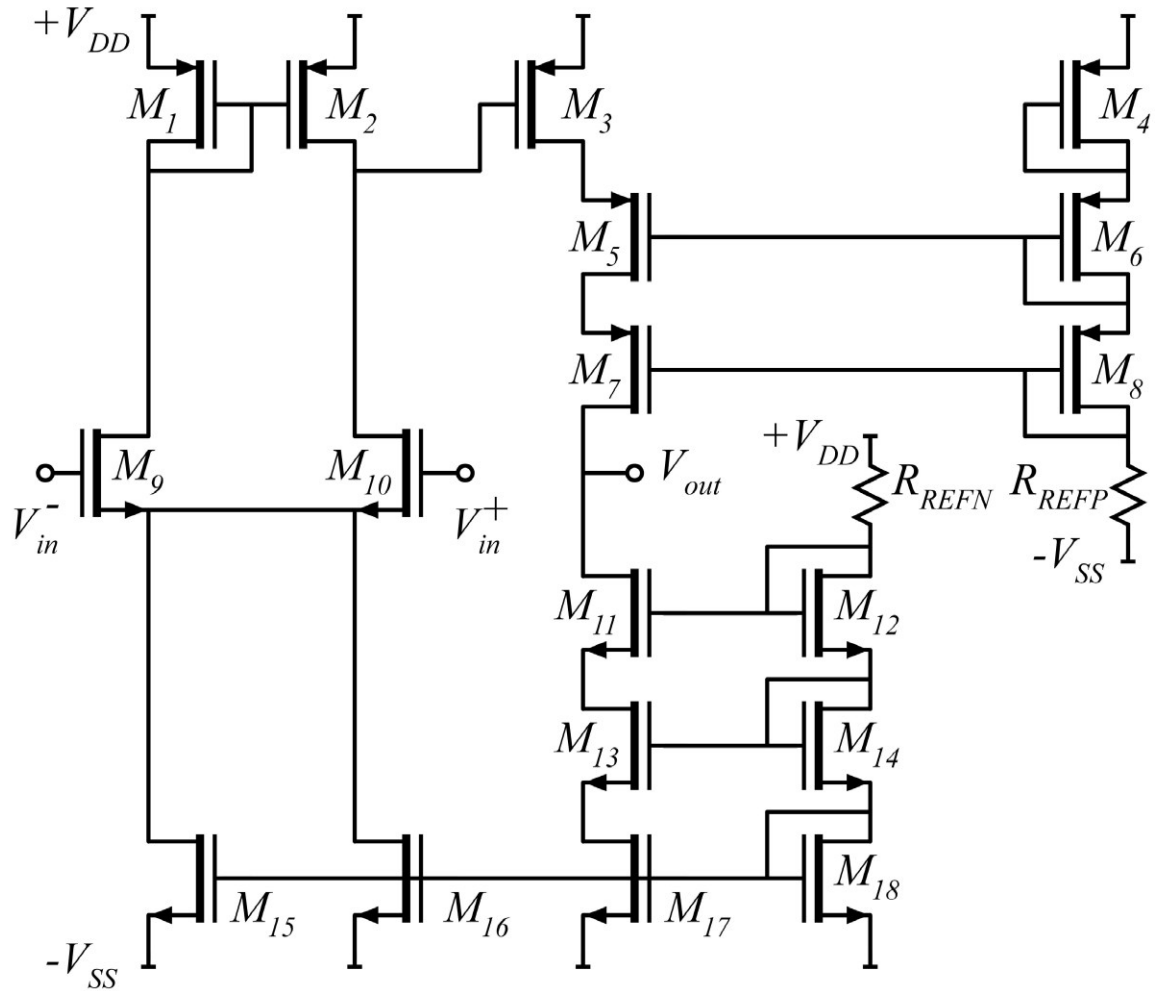

On the circuit diagram above, label the DC voltages at **ALL nodes**.

Part c, 5 points.

Find the following

	Voltage Gain	Input impedance
Transistor combination M1,2,9, 10,15, 16		

Part d, 15 points.

Find the following

	Voltage Gain	Input impedance
Transistor combination M3,5,7,11,13,17		
Overall op-amp $V_{out} / (V_{in}^+ - V_{in}^-)$		

Note


1) You can analyze M3, M5, and M7 as separate stages, or as a combined stage using Norton/Thevenin methods. Don't ask for hints as to how to do this.

Part e, 10 points

Maximum output voltage swings ***at V_{out}^+ (not V_{out}^-)*** (*show all your work*).

	magnitude and sign of maximum output signal swing due to <i>knee voltage</i> (saturation)
Transistor M7	
Transistor M11	
Transistor M2	

Problem 3, 20 points

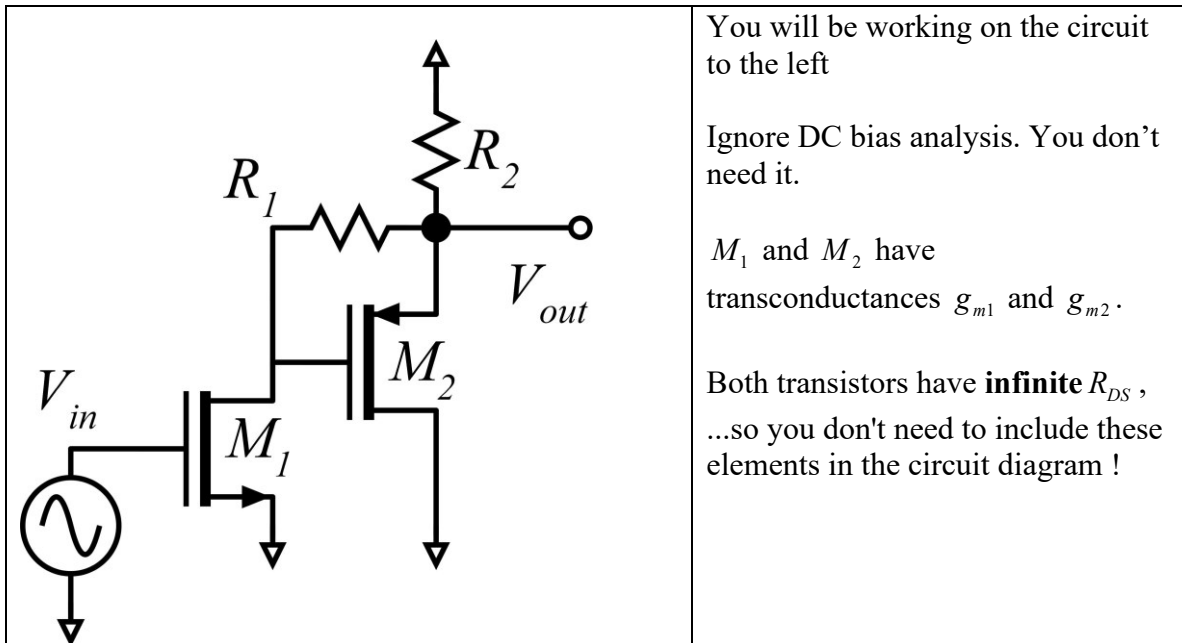

Part a, 5 points

Draw a small-signal equivalent circuit of the circuit.

Part b, 10 points

Derive an algebraic expression for V_{out} / V_{in} in terms of g_{m1} , g_{m2} , R_1 , and R_2

$$V_{out} / V_{in} =$$

Part c, 5 points

Set $g_{m1}=1 \text{ mS}$, $g_{m2}=2 \text{ mS}$, $R_1=1 \text{ k}\Omega$, and $R_2=2 \text{ k}\Omega$.

Find the numerical value of V_{out} / V_{in}

$$V_{out} / V_{in} =$$

