

ECE 137 A Mid-Term Exam

Wednesday, February 5, 2025

Do not open exam until instructed to.

Closed book: Class crib sheet and 1 page (both sides) personal notes permitted

There are 3 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.),
AFTER STATING and approximately Justifying them.

Name: Solution

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		10	2e		3
1b		5	3a		8
1c		5	3b		8
1d		10	3c		4
1e		2			
1f		15			
2a		10			
2b		5			
2c		5			
2d		10			
TOTAL					100

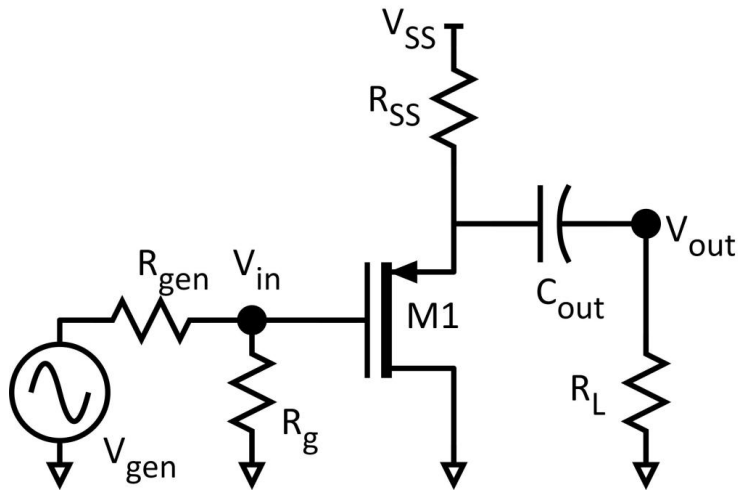Problem 1, 47 points

You will be working on the circuit below:



The transistor has

$$M1: K_{\mu} = \mu c_{gs} W_g / 2L_g = 10 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$$

$$K_v = c_{gs} v_{inj} W_g = 2 \text{mA/V} \cdot (W_g / 1\mu\text{m})$$

$$\Delta V = v_{inj} L_g / \mu = 0.1 \text{V}, |V_{th}| = 0.25 \text{V}, 1/\lambda = 5 \text{V}$$

The supply is +2.0V.

You are to bias the transistor at 1mA drain current,
and with +0.35 V DC source voltage.

$$R_{gen} = 100 \text{ k}\Omega, R_g = 1 \text{ M}\Omega, R_L = 5 \text{ k}\Omega$$

C_{out} is very large (AC short-circuit at the signal frequency)

Part a, 10 points

DC bias.

Find the following:

FET gate width $W_g = 9.35 \mu m$ $R_{ss} = 1.65 k\Omega$

$$2 \quad \left[V_{gs} - V_{th} = 0.1 V \right]$$


$$2 \quad \left[I_D = K_{\mu} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds}) = 1 mA \right. \\ \left. 1 mA = K_{\mu} (0.1 V)^2 (1 + 0.35 V / 5 V) \right]$$

$$3 \quad \left[K_{\mu} = \frac{1 mA}{10^{-2} V^2} \cdot \frac{1}{1 + 0.35/5} = 93.5 mA/V^2 \right. \\ \left. W_g = 1 \mu m \cdot \frac{93.5 mA/V^2}{10 mA/V^2} = 9.35 \mu m \right]$$

$$3 \quad \left[R_{ss} = \frac{2 V - 0.35 V}{1 mA} = \frac{1.65 V}{1 mA} = 1.65 k\Omega \right]$$

Part b, 5 points

DC bias

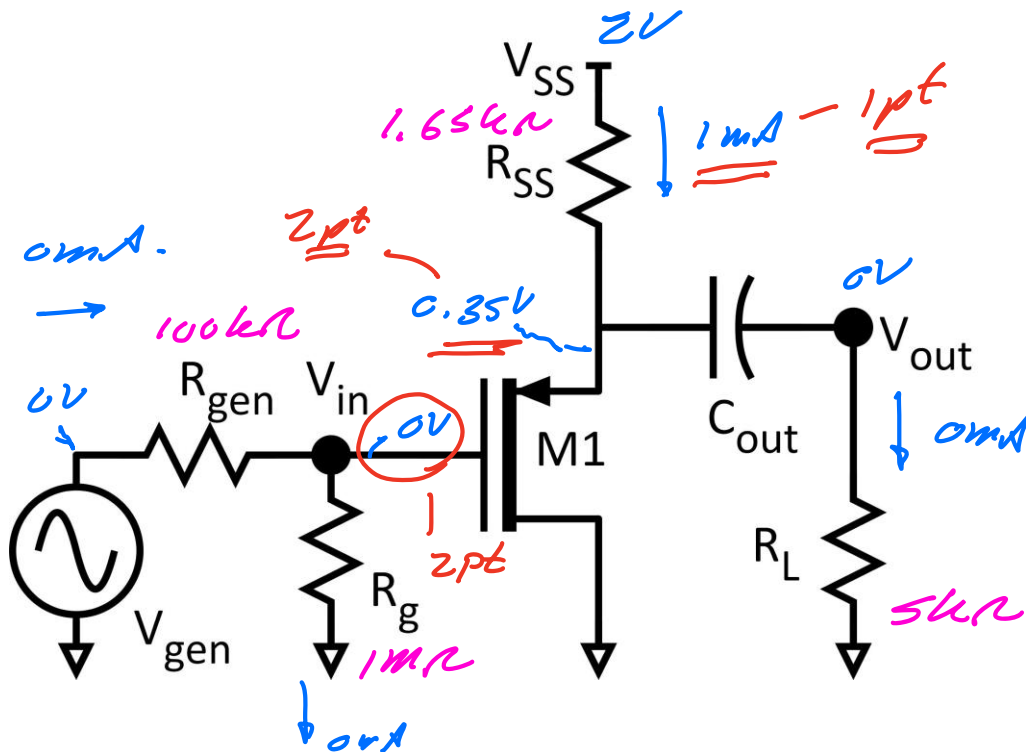

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**, give **all resistor values**, and give the **FET width**.


This is mostly for the TAs to use
in understanding what values, correct or incorrect, have been used to solve the problem

Part c, 5 points

Find the FET small signal parameters

$g_m = \underline{20\text{ mS}}$ $R_{ds} = \underline{5\text{ k}\Omega}$

DC bias

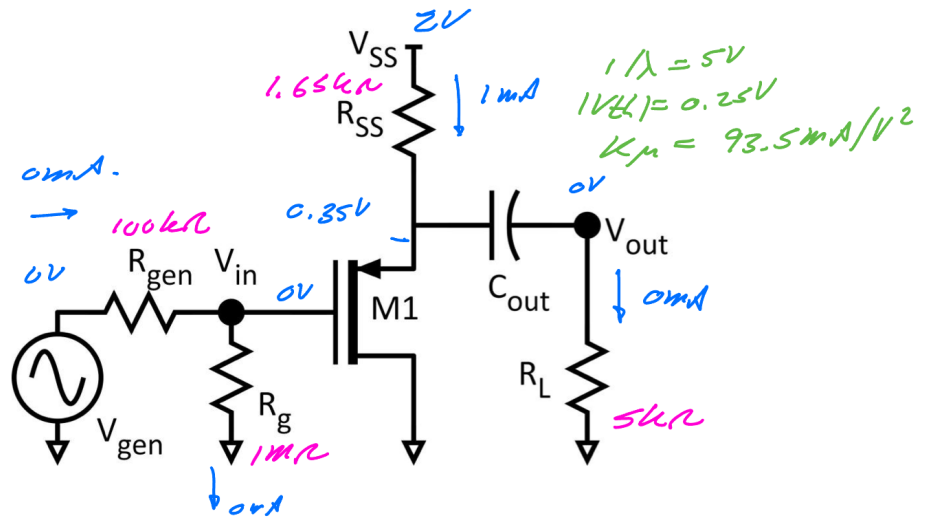

3 mobility limited:

$$g_m = 2 I_D (V_{GS} - V_{th}) = 2(1\text{ mA}) / 100\text{ mV} = \underline{20\text{ mS}}$$

2

$$R_{DS} \approx 1/I_D = 5\text{ V} / 1\text{ mA} = 5\text{ k}\Omega$$


Part d, 10 points.

Find the small signal voltage gain V_{out}/V_{in} and the amplifier small-signal input resistance.

$V_{out}/V_{in} = \underline{0.95^2}$

$R_{in, \text{ amplifier}} = \underline{1 \text{ M}\Omega}$

DC bias

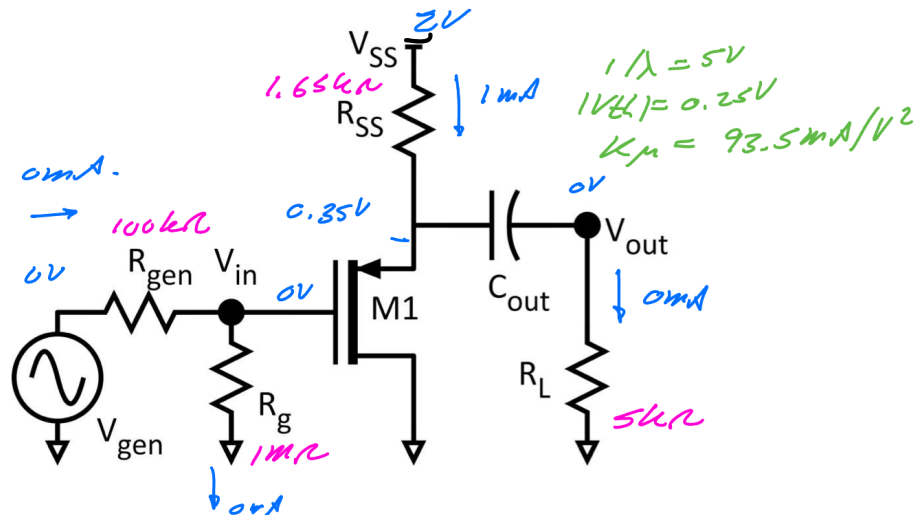

$$3 \left[R_{Leq} = R_L \parallel R_{SS} \parallel R_{DS} \right. \\ \left. = 1.65 \text{ k}\Omega \parallel 5 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 994 \Omega \right]$$

$$2 \left[1/g_m = 1/20 \text{ mS} = 50 \Omega \right]$$

$$3 \left[V_o/V_{in} = R_{Leq} / (R_{Leq} + 1/g_m) \right. \\ \left. = 994 \Omega / (994 \Omega + 50 \Omega) = 0.95^2 \right]$$

$$2 \left[R_{in} = R_g = 1 \text{ M}\Omega \right]$$


Find (V_{in}/V_{gen}) and (V_{out}/V_{gen})

Find (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$$(V_{in}/V_{gen}) = \underline{0.909}$$

(Vout/Vgen) = 0.866

DC bias

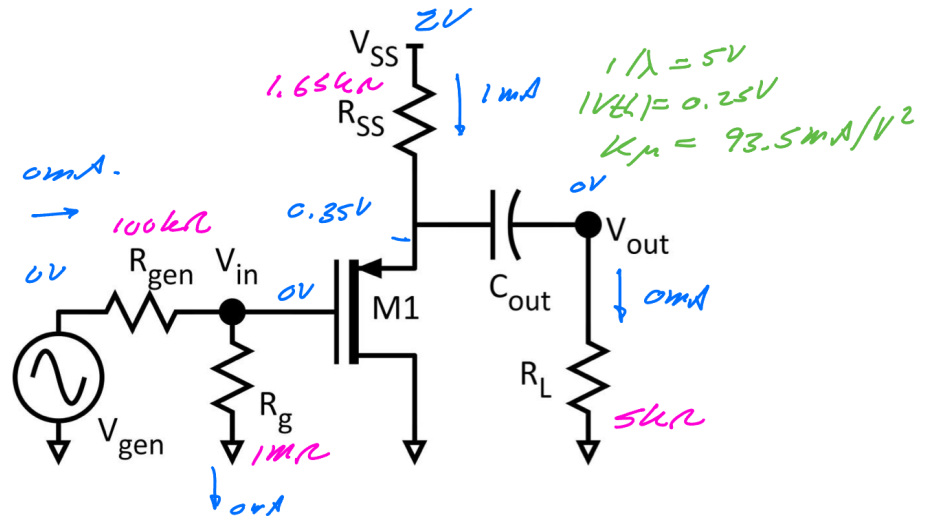

$$V_{in}/V_{gen} = R_{in} / [R_{in} + R_{gen}] = 0.909$$


$$V_{out}/V_{gen} = V_o/V_{in} \cdot V_{in}/V_{gen}$$

$$= 0.952 \cdot 0.909 = 0.866$$

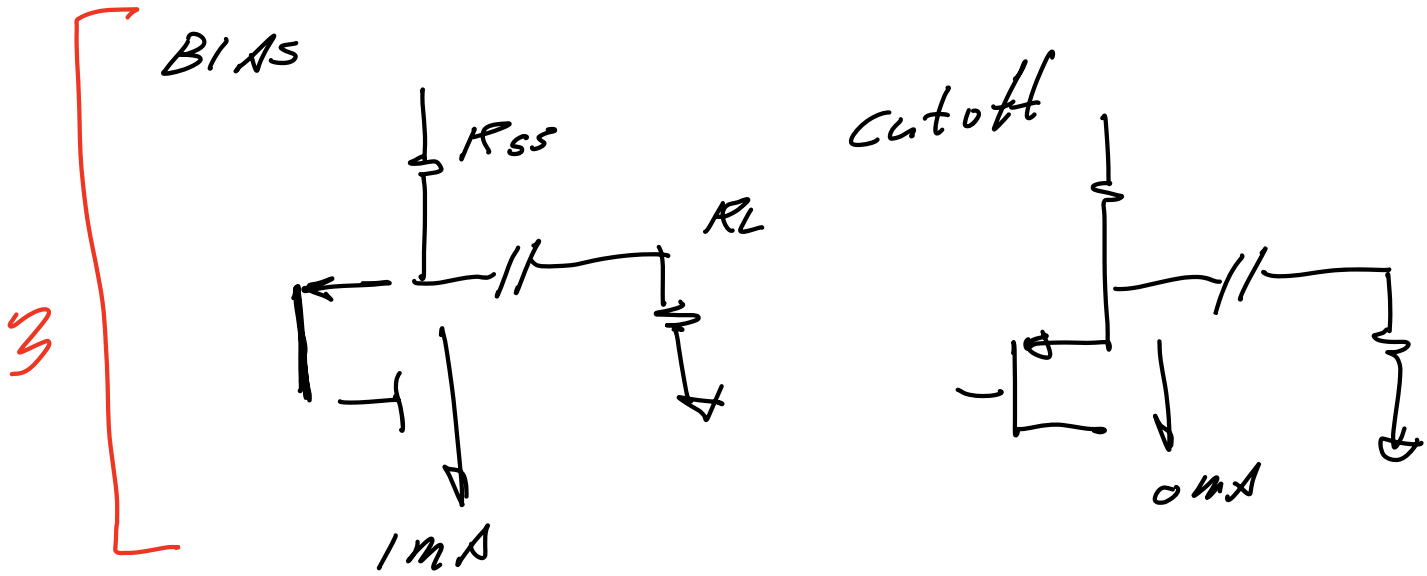Part f, 15 points

Now you must find the maximum signal swings. Find the output voltage due to the knee voltage and cutoff in M1. **Give the sign (+ or -) in your answers below.**

Cutoff of M1; Maximum ΔV_{out} resulting = 1.24V $\uparrow$
 Knee voltage of M1; Maximum ΔV_{out} resulting = -0.24V $\downarrow$




2

$$\Delta I_D = 1 \text{ mA decrease}$$

2

$$\begin{aligned} \Delta V_{source} &= \Delta V_{out} = 1 \text{ mA} \cdot (R_{ss} || R_L) \\ &= 1 \text{ mA} (1.24 \text{ k}\Omega) \\ &= 1.24 \text{ V } \uparrow \end{aligned}$$

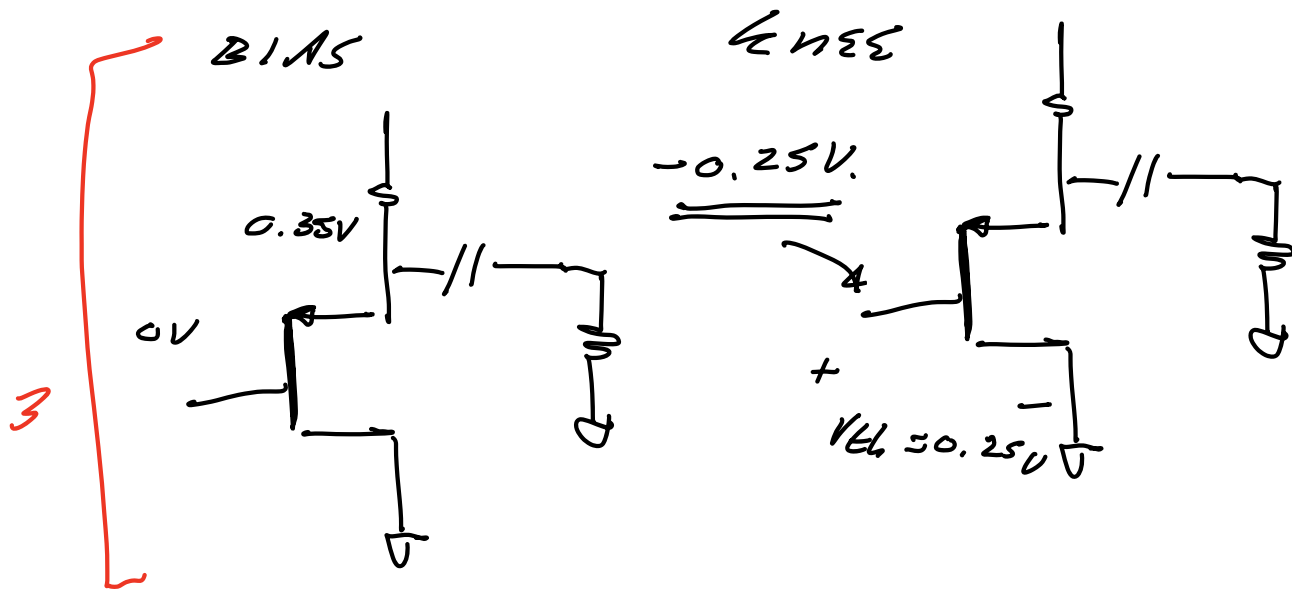

2

so $\Delta V_{i2} = -0.25V$


3

$\rightarrow \Delta V_{out} = -0.25V \cdot (V_o/V_{i2})$
 $= -0.25V (0.952) = -0.24V$

-1 pt if the
gain is skipped.

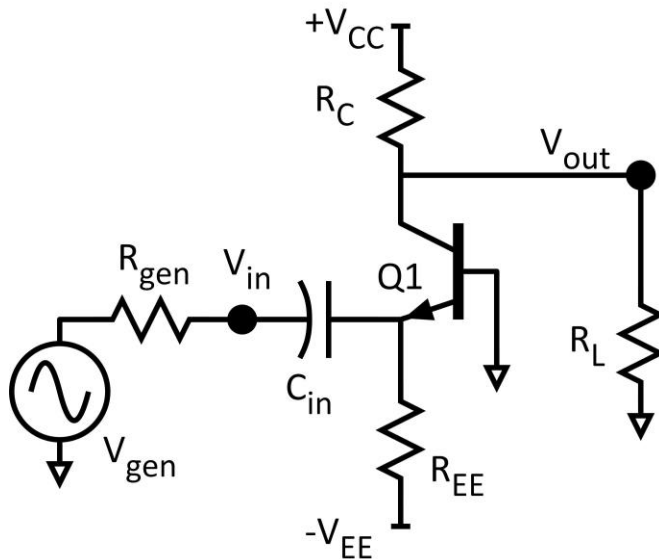Problem 2, 33 points

You will be working on the circuit below:



Q1: $\beta = 10^8$, $V_A = \text{infinity}$ Volts, $V_{ce,sat} = 0.5\text{V}$

The supplies are $+2.5\text{V}$ and -2.5V .

You will bias the transistor with 5mA collector current.

You will bias the transistor with $V_{out} = 0$ Volts.

R_L is $1\text{ k}\Omega$, R_{gen} is $50\ \Omega$.

C_{in} is very large (AC short-circuit at the signal frequency)

Part a, 10 points

DC bias.

Find the following:

$R_{EE} = \underline{360\Omega}$


DC voltage at the emitter of Q1: $V_{DC_emitter} = \underline{-0.7V}$

Hint: there is no DC blocking capacitor in series with V_{out} .

4
$$R_{EE} = \frac{2.5V - 0.7V}{5mA}$$

3
$$= \frac{1.8V}{5mA} = \frac{3.6V}{10mA}$$

$$= 360\Omega$$

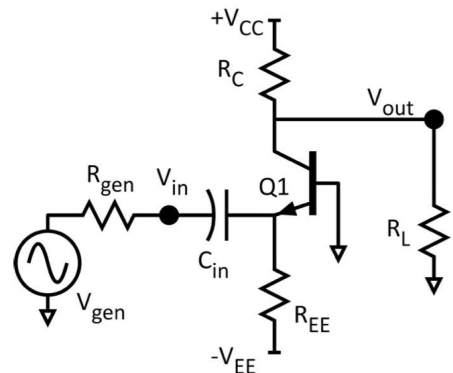

Q1: $\beta = 10^3$, $V_A = \text{infinity}$ Volts, $V_{CE,sat} = 0.5V$

The supplies are $+2.5V$ and $-2.5V$.

You will bias the transistor with $5mA$ collector current.


You will bias the transistor with $V_{out} = 0$ Volts.

R_L is $1k\Omega$, R_{gen} is 50Ω .

C_{in} is very large (AC short-circuit at the signal frequency)

Part b, 5 points

DC bias

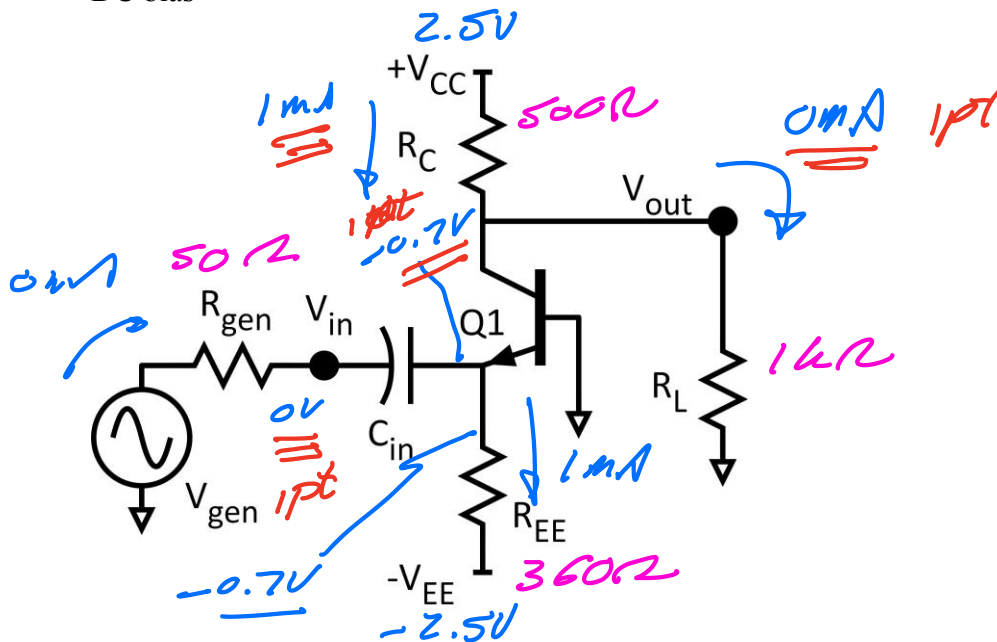

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**, and give **all resistor values**,

$$R_C = \frac{2.5V}{5mA} = \frac{5V}{10mA} = 500\Omega \quad] \quad 1pt$$

This is mostly for the TAs
to use

in understanding what values,

correct or incorrect,
have been used to solve the problem

Part c, 5 points


Find the small signal parameters of Q1.

$g_m = 190 \text{ mS}$

$R_{ce} = \infty \Omega$

$R_{be} = \infty, \text{ large, or } 5 \cdot 10^8 \Omega - \text{all ok.}$

DC bias

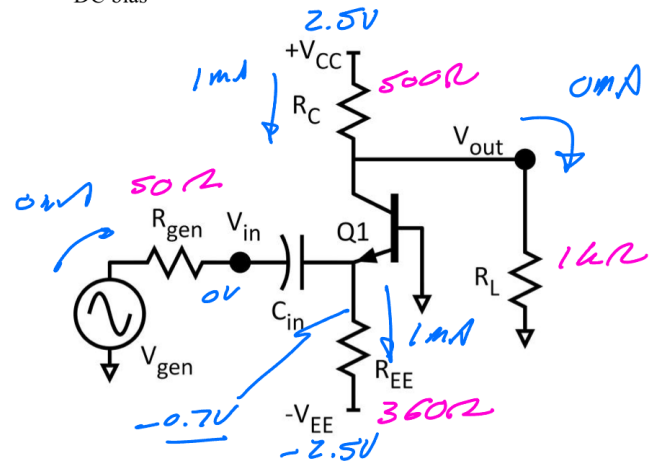

$$3 \left[g_m = \frac{5 \text{ mA}}{26 \text{ mV}} = \frac{10 \text{ mA}}{52 \text{ mV}} = \frac{1}{5.2 \Omega} = 192 \text{ mS} \right]$$

$$1 \left[R_{ce} = \infty \Omega \text{ because } V_A \rightarrow \infty \text{ V} \right]$$


$$1 \left[R_{be} = \beta / g_m = 10^8 \cdot 5.2 \Omega \rightarrow \text{large.} \right]$$

Part d, 10 points.

Find the small signal voltage gain (V_{out}/V_{in}) of Q1 and the amplifier small-signal input resistance.

$V_{out}/V_{in} = \underline{64}$

$R_{in,amp} = \underline{5.1 \Omega}$

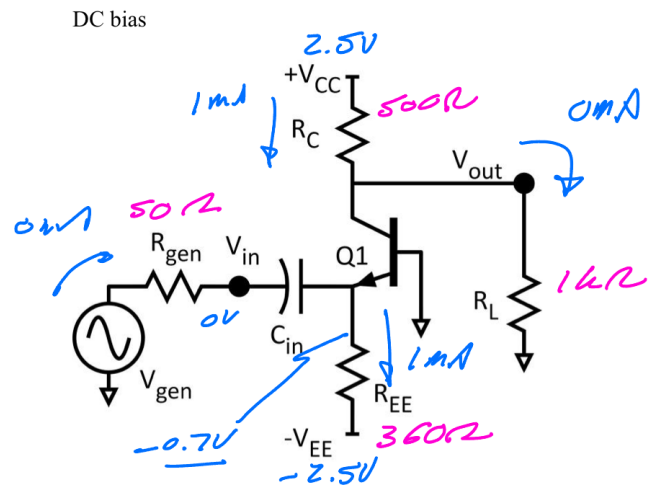

3
$$R_{L_{eq}} = 1k\Omega // 500\Omega // R_{EE}$$

$$= 333.3\Omega$$

2
$$R_{i_T} = 1/g_m = 5.2\Omega$$

3
$$V_{out}/V_{in} = R_{L_{eq}}/R_{i_T} = 333.3\Omega/5.2\Omega = 64.10$$


2
$$R_{i_{amp}} = R_{i_T} // R_{EE} = 5.2\Omega // 360\Omega = 5.12\Omega$$

Part e, 3 points

Find (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$(V_{in}/V_{gen}) = \underline{0.0929}$


$(V_{out}/V_{gen}) = \underline{5.95}$

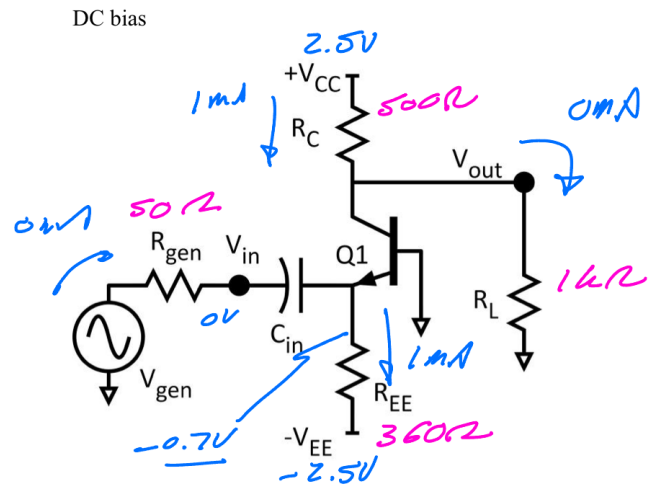

$$V_{in}/V_{gen} = \frac{R_{in}}{R_{in} + R_{gen}} = \frac{5.12k}{5.12k + 50} = 0.0929$$

$$V_o/V_{gen} = V_o/V_i \cdot V_{in}/V_{gen} = 64.1 \cdot 0.0929 = 5.95$$

Problem 3, 20 points
nodal analysis

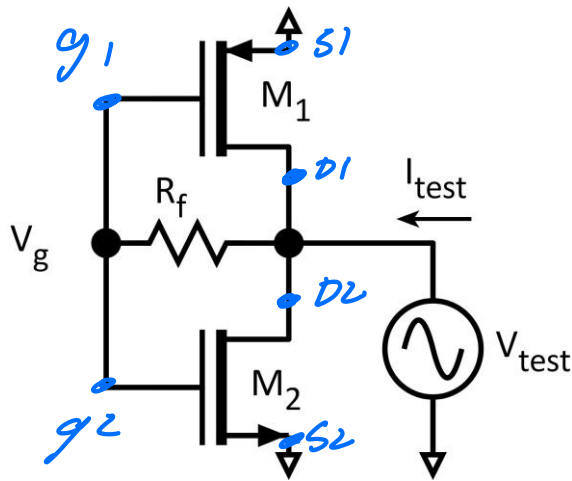

You will be working on the circuit to the left.

Ignore DC bias analysis. You don't need it.


The transistors M1 and M2 have transconductance

$$g_{m1} = g_{m2} = g_m$$

The drain-source resistances are $R_{DS1} = R_{DS2} = R_{DS} = \infty \Omega$ (infinite resistance is an open-circuit, so you don't need to draw them!)

Part a, 8 points

Draw the small-signal equivalent circuit

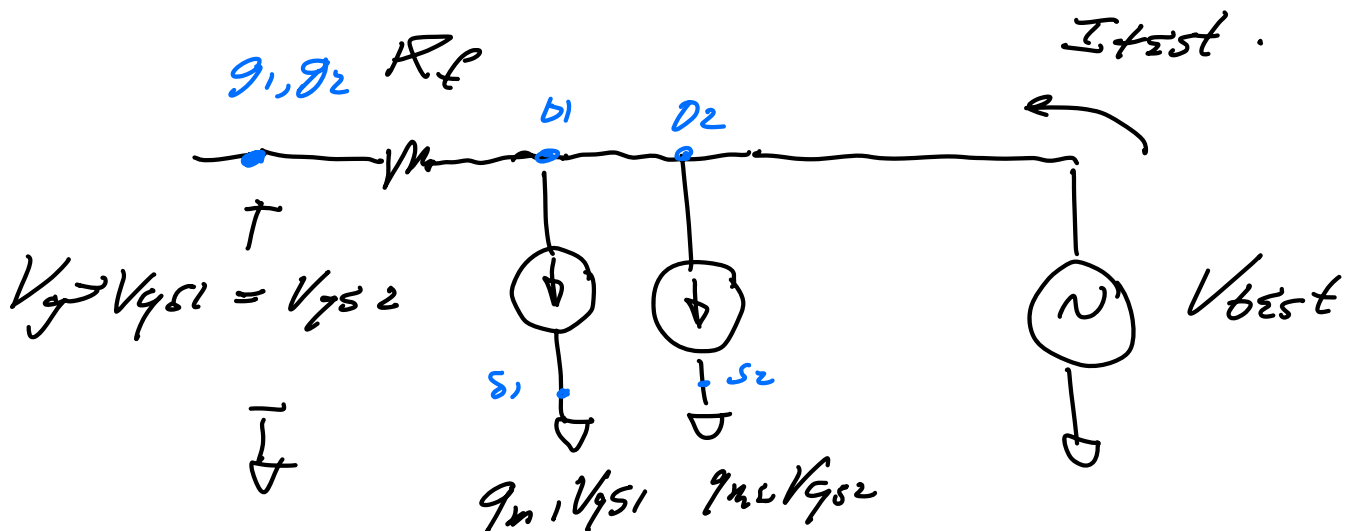


location of V_{gs} must be identified
otherwise, -4 pts

Part b, 8 points

Find, by nodal analysis, a small-signal expression for $G_{out} = 1/R_{out} = I_{test}/V_{test}$

$$G_{out} = 2g_m$$

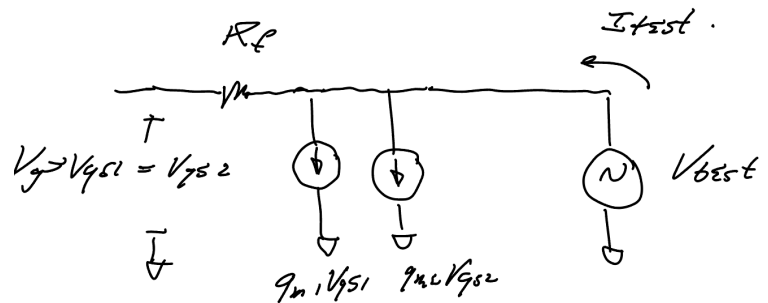

$V_g = V_{test}$ because current in R_f is zero.

$$\Rightarrow I_{test} = (g_{m1} + g_{m2}) \cdot V_{test}$$

$$= 2g_m V_{test}$$

$$G_{out} = 2g_m$$

Part c, 4 points

$g_m = 1 \text{ mS}$, $R_F = 1 \text{ k}\Omega$,

Give a numerical value for G_{out}

$$G_{out} = \underline{2 \text{ mS}}$$

$$4) \left[G_{out} = 2 g_m = 2 \text{ mS} \right]$$