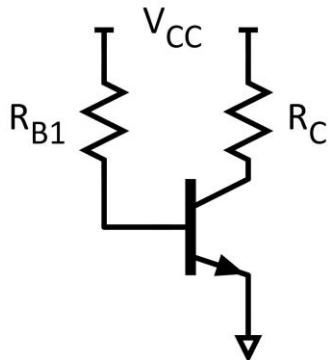


ECE137A Problem set #1

Problem 1. bipolar transistor biasing. Assume a $V_{be(on)}$ of 0.9 volts.



a)


$\beta = 50$

$V_{cc} = 5$ volts

We want 1 mA collector current,
and $V_{ce} = 2.5$ Volts

Find R_c and R_b

(this biasing circuit *not* recommended)

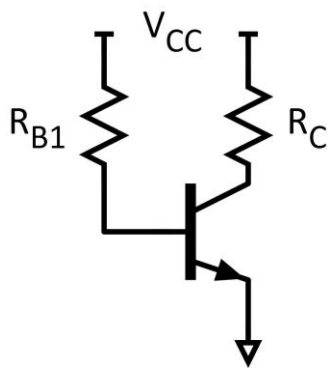


b) Bias stability of the circuit of problem 1(a).

First, keeping the same values for R_b and R_c you found above, compute the collector current and the collector voltage if β is increased to 200.

Second, keeping the same values for R_b and R_c you found above, compute collector current and the collector voltage if β is returned back to its original value but V_{cc} is increased 10%.

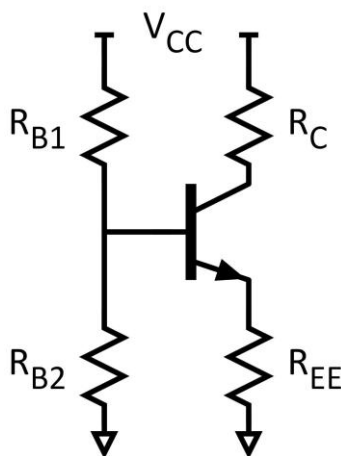Caution: You *must* consider the possibility of saturation.



c)

$\beta = 50$

$V_{cc} = 5$ volts


collector current = 1 mA

Collector voltage $V_c = 3$ Volts

Emitter voltage $V_e = 1$ volts

current in $R_{b2} = 10$ microamps

Find R_{b1} , R_{b2} , R_{ee} , R_c

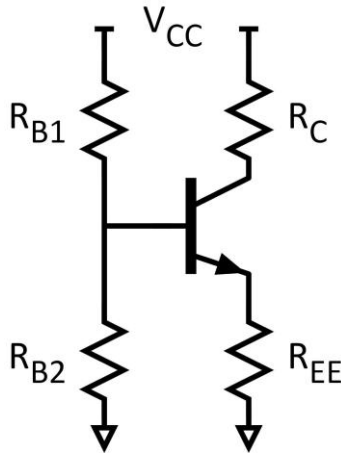


d) Bias stability of the circuit of problem 1(c).

First, keeping the same values for R_{B1} , R_{B2} , R_{EE} and R_C you found above, compute the collector current and the collector voltage if β is increased by a factor of two.

Second, keeping the same values for R_{B1} , R_{B2} , R_{EE} and R_C you found above, compute the collector current and the collector voltage if β is returned back to its original value but V_{CC} is increased 10%.

Caution: You *must* consider the possibility of saturation.

Problem 2 MOS Biasing:

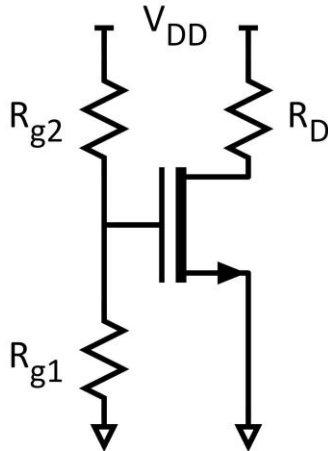

a)

The MOSFET has a 0.3V threshold,

$$K_{\mu} = \mu c_{gs} W_g / 2L_g = 10 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m}),$$

$$K_v = c_{gs} v_{inj} W_g = 2.0 \text{mA/V} \cdot (W_g / 1\mu\text{m})$$

$$\Delta V = v_{inj} L_g / \mu = 100 \text{mV}, \text{ and}$$

$$W_g = 1 \mu\text{m}. R_{g1} \text{ is } 100 \text{ k}\Omega. V_{DD} \text{ is } 0.8 \text{ Volts.}$$

$\lambda = 0$. We would like to bias the MOSFET at 0.1 mA drain current and 0.5 volts between drain and source.

Please find the required values of R_{g2} and R_D .

b) Bias stability of the circuit of problem 2(a).

First, keeping the same values for R_{g1} , R_{g2} , and R_D you found above, compute the drain current and the drain voltage if K_{μ} and K_v are both increased 10%.

Second, using the original value of K_{μ} and K_v , and keeping the same values for R_{g1} , R_{g2} , and R_D you found in 2(a), compute the drain current and the drain voltage if the power supply voltage is increased 10%.

