
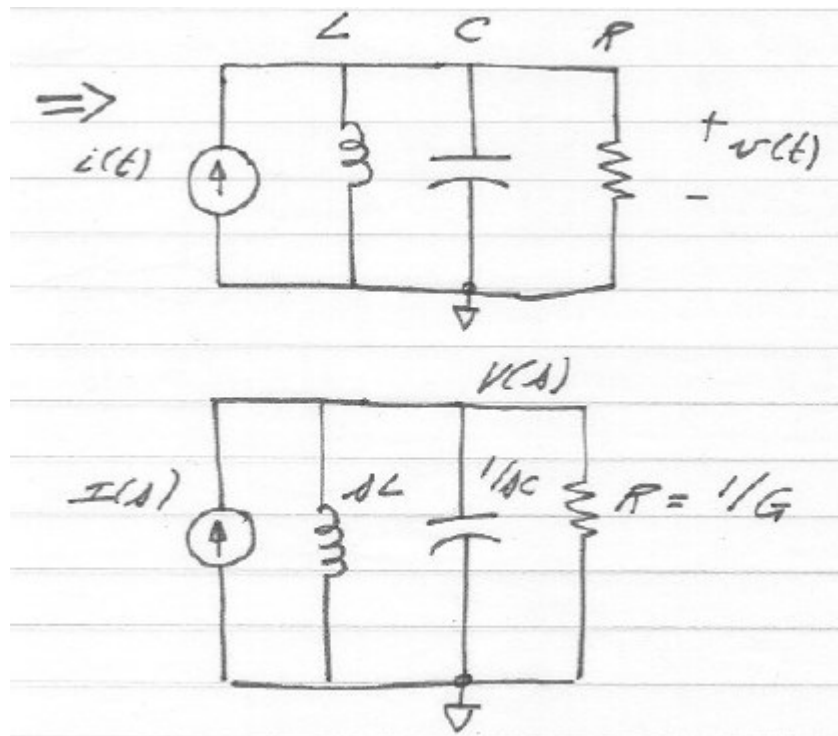


# ECE137A, Notes Set 16: Second-Order Circuits

***Mark Rodwell,  
Doluca Family Chair, ECE Department  
University of California, Santa Barbara  
rodwell@ece.ucsb.edu***

# Parallel RLC Resonance

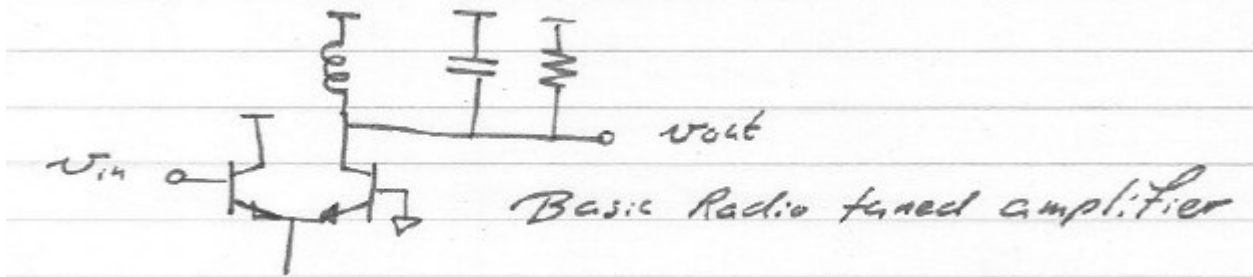

# Parallel RLC Resonance: Analysis

$$V[AC + 1/sL + G] = I$$

$$V/I = \frac{1}{AC + 1/sL + G} = \frac{sL}{1 + sLR + s^2LC}$$

put in standard ("canonical") form

$$\frac{V(s)}{I(s)} = Z(s) = R \frac{(2\zeta/\omega_n)s}{s^2/\omega_n^2 + (2\zeta/\omega_n)s + 1}$$

$\omega_n$  = the natural resonant frequency

$\alpha = \zeta\omega_n$  = the exponential damping coefficient

$\zeta$  = the damping factor

Equating terms for this specific problem only


$$\omega_n = 1/\sqrt{LC}, \quad \alpha = 1/2RC$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$
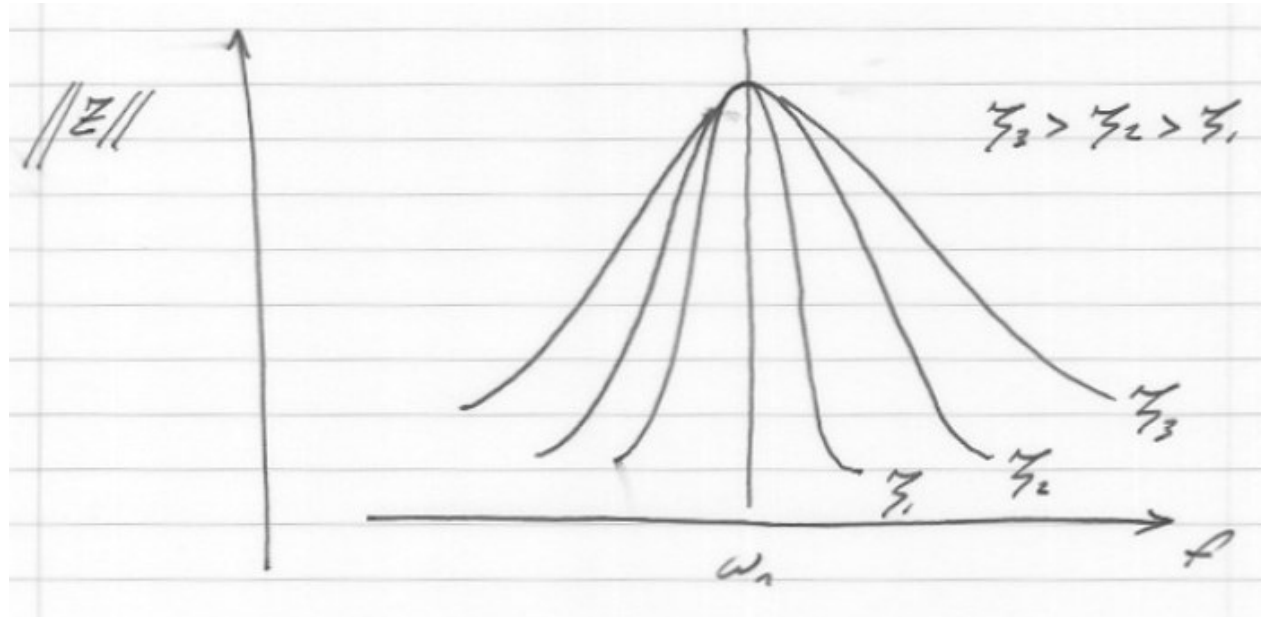
# Parallel RLC Resonance: Frequency Response

response to signal  $v_0 e^{j\omega t} \rightarrow A = \frac{1}{j\omega + 0}$

$$\frac{V(j\omega)}{I(j\omega)} = Z(j\omega) = R \frac{j\omega(2\zeta/\omega_n)}{1 + j\omega(2\zeta/\omega_n) - \omega^2/\omega_n^2}$$




The larger  $\zeta$  is, the wider the resonant peak in frequency.
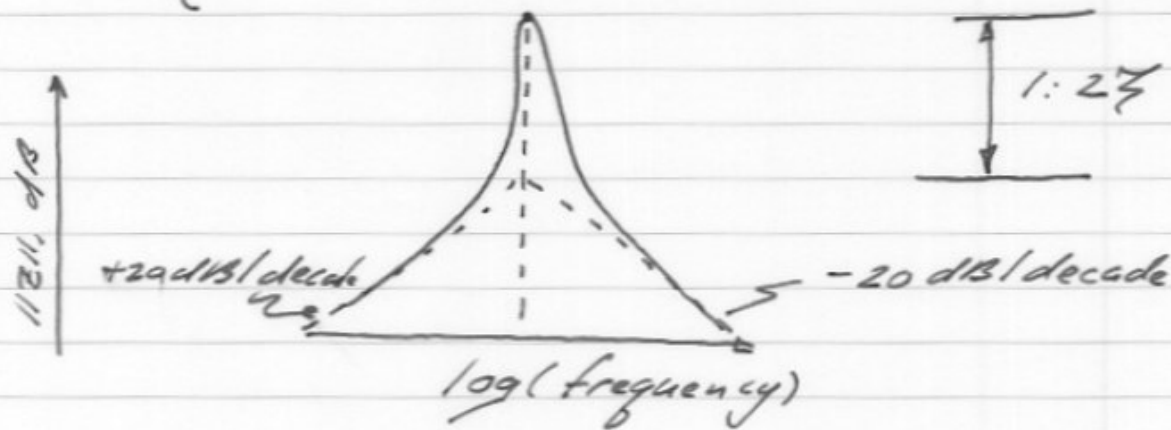
# Bode Plot of Resonance

$$Z(j\omega) = R \frac{j\omega(2\zeta/\omega_n)}{1 + j\omega(2\zeta/\omega_n) - \omega^2/\omega_n^2}$$

$$= \begin{cases} R \cdot (j\omega/\omega_n) 2\zeta & \text{for } \omega \ll \omega_n \\ R \cdot 1 & \text{for } \omega = \omega_n \\ R \cdot (\omega_n/j\omega) 2\zeta & \text{for } \omega \gg \omega_n \end{cases}$$



- Consider what will happen to the curve as we vary  $\zeta$

- Note asymptotes of  $\pm 20 \text{ dB/decade}$  and the  $2\zeta:1$  resonant peak.

# Poles, Zeros

$$V(s)/I(s) = Z(s) = R \frac{s(2\zeta/\omega_n)}{s^2/\omega_n^2 + s(2\zeta/\omega_n) + 1}$$

re-arrange into 2 useful forms:

$$Z(s) = R \frac{s(2\zeta\omega_n)}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

$\zeta\omega_n = \alpha$ 
 $\omega_d^2 = (1 - \zeta^2)\omega_n^2$


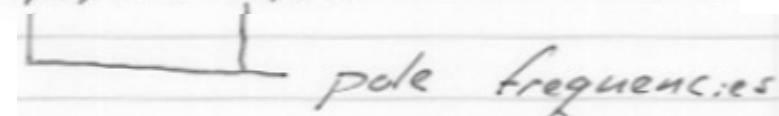
this form for inverse Laplace transform

# Poles, Zeros

$$V(s)/I(s) = Z(s) = R \frac{s(2\zeta/\omega_n)}{s^2/\omega_n^2 + s(2\zeta/\omega_n) + 1}$$



$$Z(s) = R \frac{s(2\zeta\omega_n)}{(s + \zeta\omega_n - j\omega_d)(s + \zeta\omega_n + j\omega_d)}$$

$$= R \frac{s(2\zeta\omega_n)}{(s - s_{p1})(s - s_{p2})}$$

$$s_{p1,2} = -\zeta\omega_n \pm j\omega_d$$

# Root Constellation

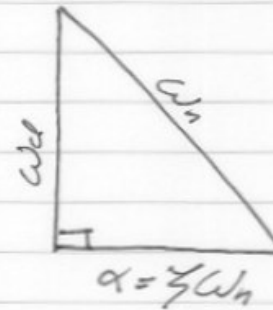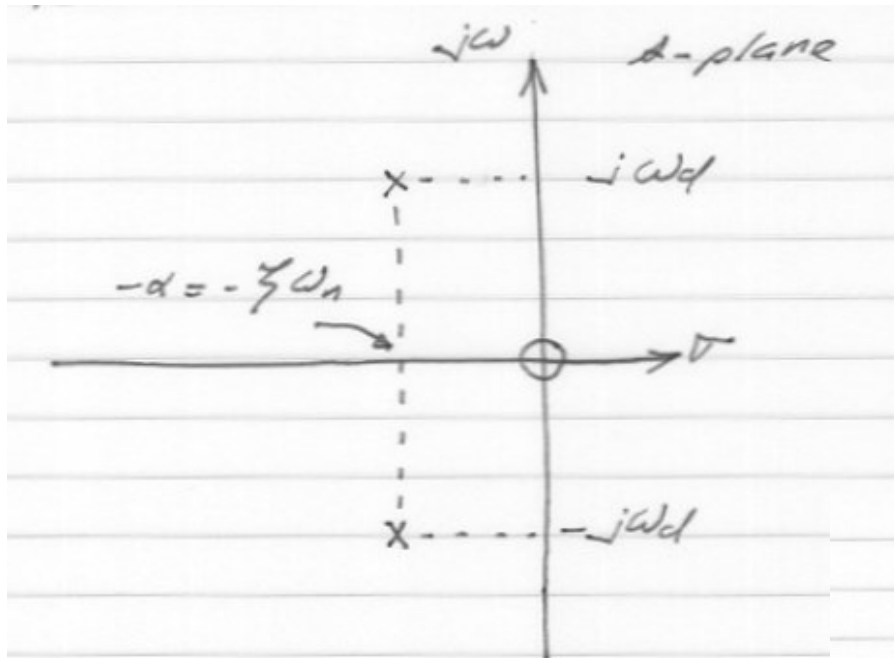

Very  
important

$$\omega_d^2 + (\zeta\omega_n)^2 = \omega_n^2$$



$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$




# Root Constellation: For Underdamped System

$$s_{p1,2} = -\zeta\omega_n \pm j\omega_d$$

$$\text{where } \omega_d = \omega_n \cdot \sqrt{1 - \zeta^2}$$
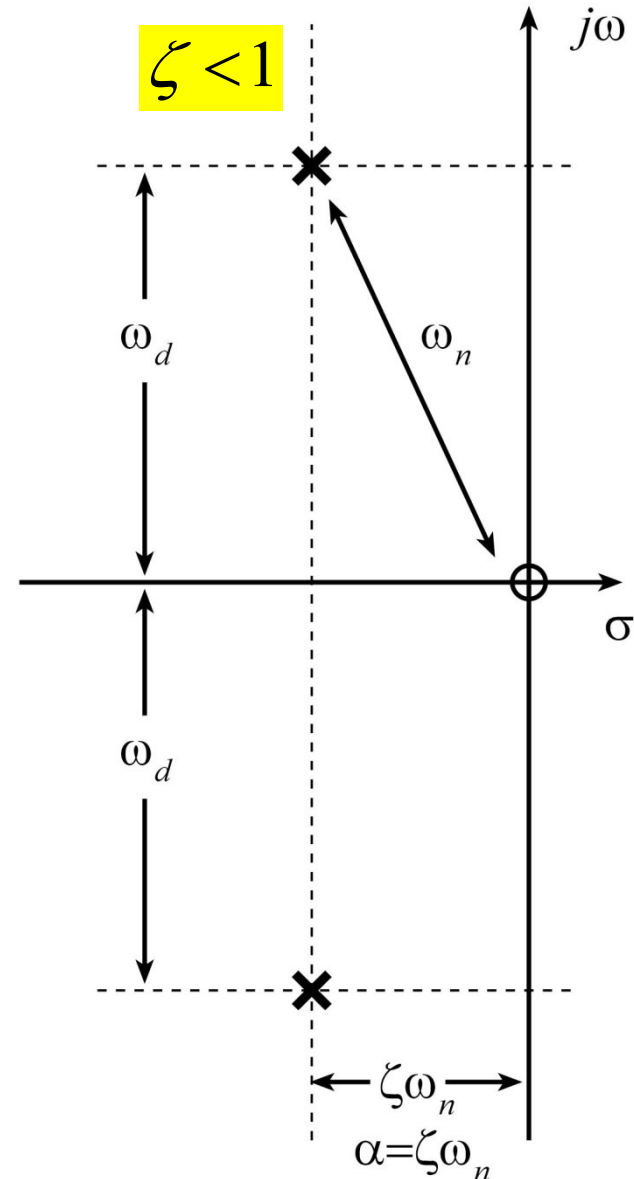
$$H(s) = \frac{s(2\zeta / \omega_n)}{1 + s(2\zeta / \omega_n) + s^2 / \omega_n^2}$$



# Root Constellation: For Overdamped System

$$s_{p1,2} = -\zeta\omega_n \pm j\omega_d$$

but if  $\zeta > 1$ ,

then  $\omega_d = \omega_n \cdot \sqrt{1 - \zeta^2}$  is complex.


If  $\zeta > 1$ , then use

$$j\omega_d = j\omega_n \cdot \sqrt{1 - \zeta^2} = \omega_n \cdot \sqrt{\zeta^2 - 1}$$

So

$$\begin{aligned} s_{p1,2} &= -\zeta\omega_n \pm j\omega_d \\ &= -\zeta\omega_n \pm \omega_n \cdot \sqrt{\zeta^2 - 1} \end{aligned}$$

$$\zeta > 1$$

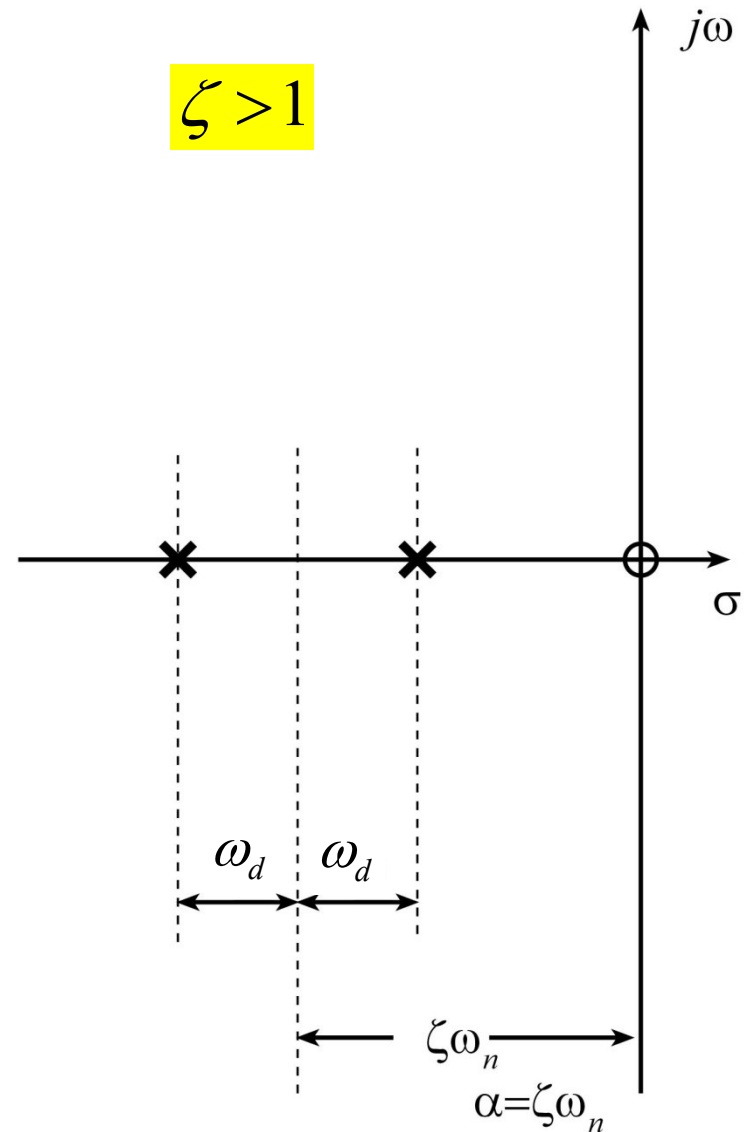


# Root Constellation: For Overdamped System

$$s_{p1,2} = -\zeta\omega_n \pm j\omega_d$$

$$= -\zeta\omega_n \pm \omega_n \cdot \sqrt{\zeta^2 - 1}$$

$$\zeta > 1$$

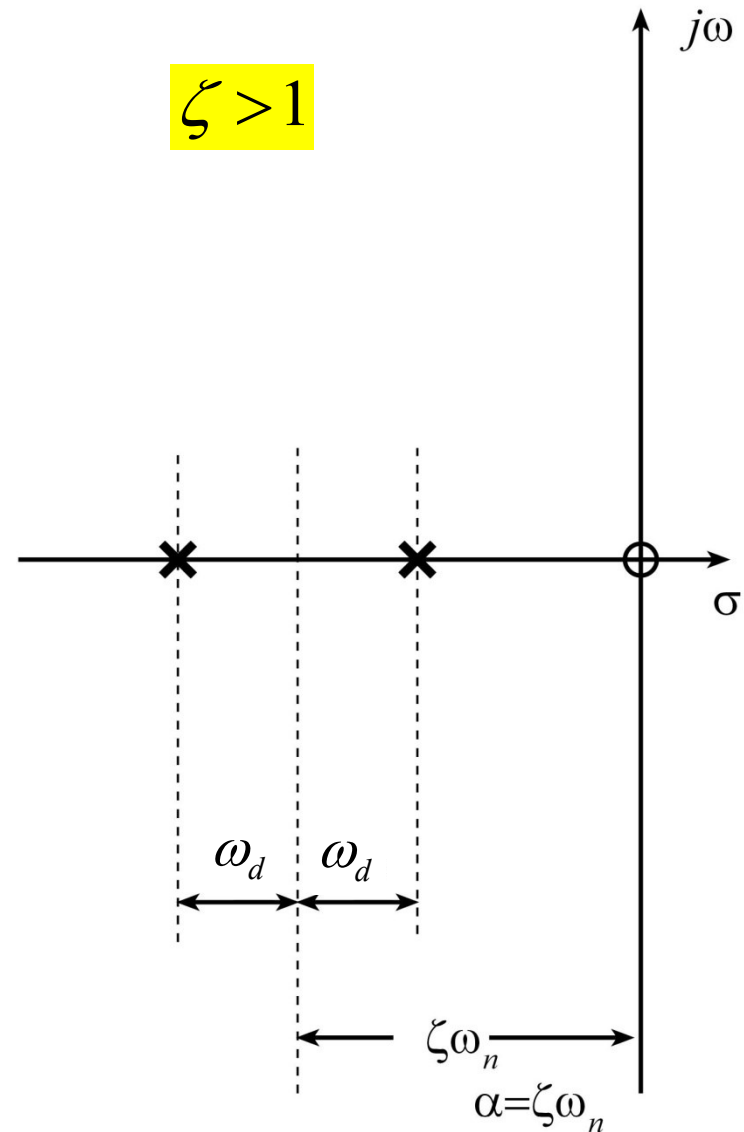


$$H(s) = \frac{s(2\zeta / \omega_n)}{1 + s(2\zeta / \omega_n) + s^2 / \omega_n^2}$$
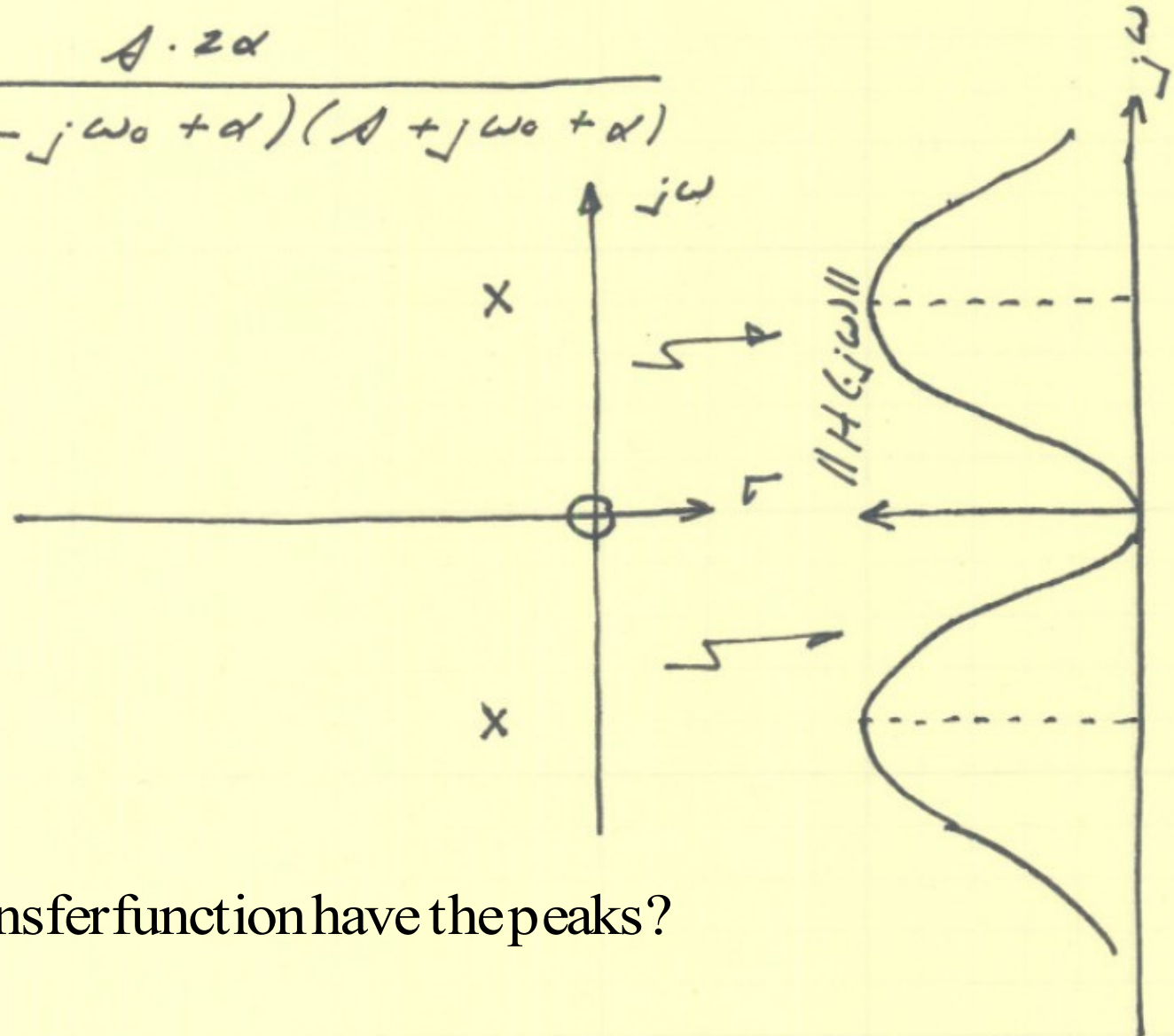
# Root Constellation and Frequency Response: Complex Poles

$$H(j\omega) =$$

$$\frac{A \cdot 2\alpha}{(s - j\omega_0 + \alpha)(s + j\omega_0 + \alpha)}$$




Why does the transfer function have the peaks?
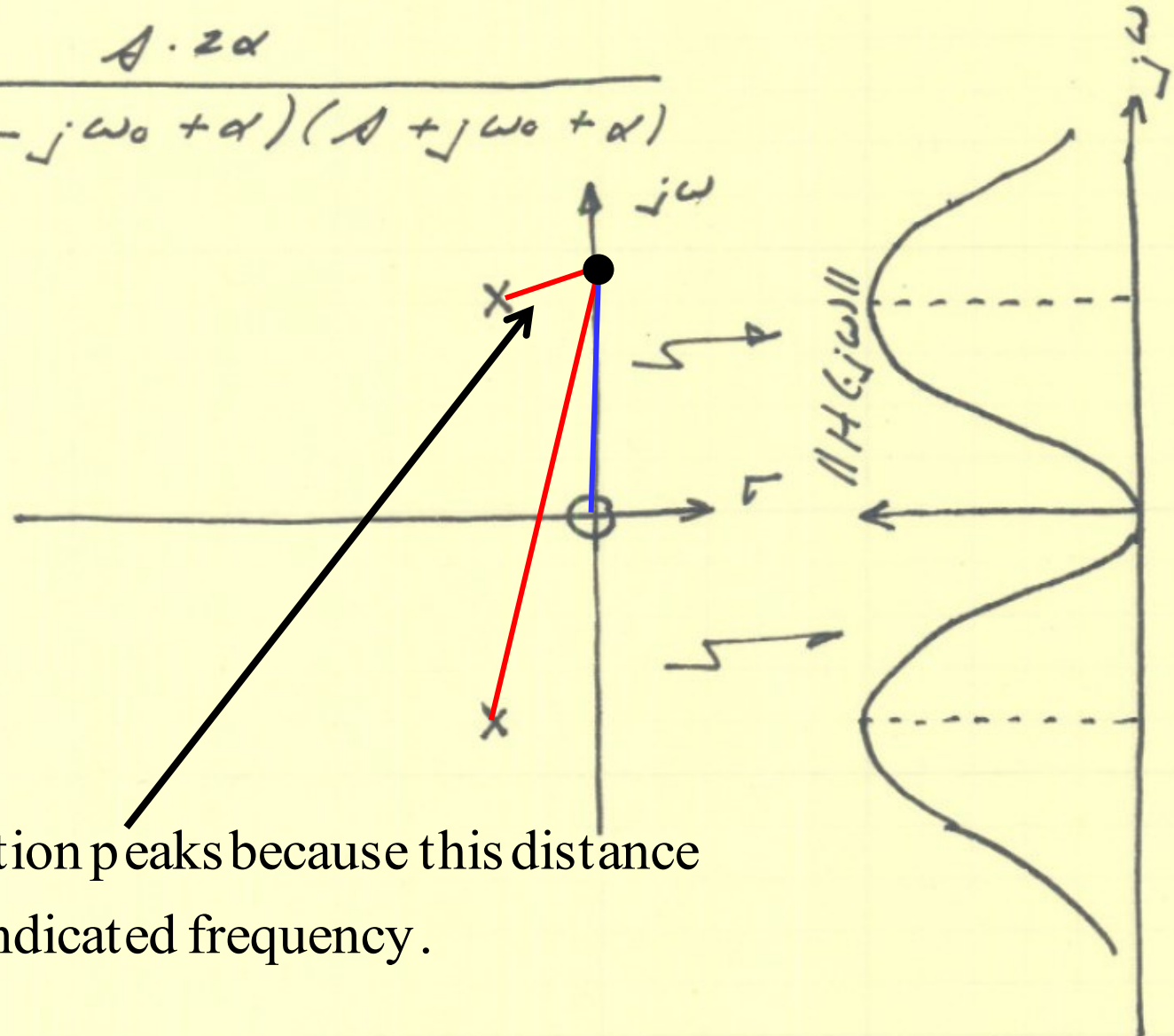
# Root Constellation and Frequency Response: Complex Poles

$$H(j\omega) =$$


$$\frac{A \cdot 2\alpha}{(s - j\omega_0 + \alpha)(s + j\omega_0 + \alpha)}$$



The transfer function peaks because this distance gets small at the indicated frequency.
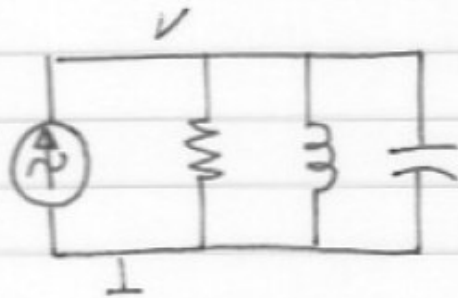
# Quality factor of an Energy Storage Element

$$Q = \frac{2\pi \cdot \text{Maximum energy stored}}{\text{energy dissipated in one cycle}}$$



$$I = I_0 \cos \omega_n t, \quad \omega_n = 1/\sqrt{LC}$$

$$V = \underbrace{R I_0}_{V_0} \cos \omega_n t \quad \text{because } \omega = \omega_n$$

Energy in Capacitor

$$E_C = \frac{1}{2} C V^2 = \frac{1}{2} C V_0^2 \cos^2(\omega_n t)$$

Energy in inductor

$$I_L = (1/L) \int V(t) dt = (V_0/L)(\omega_n)^{-1} \sin(\omega_n t)$$

$$E_L = \frac{1}{2} L I_L^2 = (V_0^2 L \omega_n^{-2}) \sin^2(\omega_n t) = \frac{1}{2} C V_0^2 \sin^2(\omega_n t)$$

# Quality factor of an Energy Storage Element

Total Energy stored:  $E_T = E_C + E_L = \frac{1}{2} C V_0^2$  !

Energy Dissipated in 1 cycle


$$E = P \cdot T = (V_0^2 / 2R) \left( \frac{1}{f} \right) = (V_0^2 / 2R) \left( \frac{2\pi}{\omega_n} \right)$$

Q factor.

$$Q = \frac{2\pi \left( \frac{1}{2} C V_0^2 \right)}{2\pi \left( \frac{1}{2} V_0^2 / R \omega_n \right)} = \underline{C R \omega_n} = R \sqrt{\frac{C}{L}} = \frac{1}{2\zeta}$$

$$Q = \omega_n / 2\alpha = 1/2\zeta$$

# -3 dB (Half-Power) Bandwidth

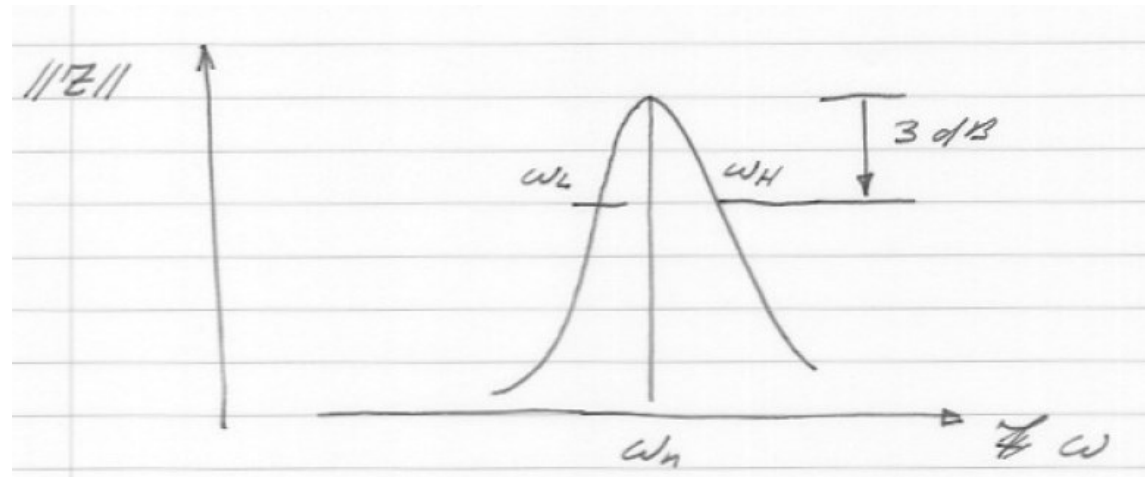

After some math:


$$\omega_L = \omega_n \left[ \sqrt{1 + \zeta^2} - \zeta \right]$$

$$\omega_H = \omega_n \left[ \sqrt{1 + \zeta^2} + \zeta \right]$$

$$\text{3 dB bandwidth} = \omega_H - \omega_L = 2\zeta \omega_n = \omega_n / Q$$



# Series RLC Circuit

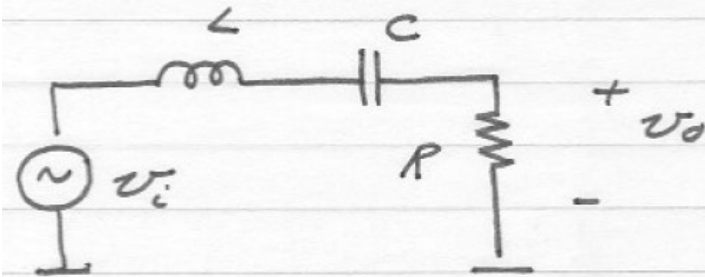

$$\frac{v_o}{v_i} = \frac{R}{R + j\omega L + 1/j\omega C} = \frac{A RC}{1 + A RC + A^2 LC}$$


$$= \frac{A \cdot 2\zeta/\omega_n}{1 + A \cdot 2\zeta/\omega_n + A^2/\omega_n^2}$$

Canonical Form.

$$\omega_n = 1/\sqrt{LC}$$

$$2\zeta/\omega_n = 2\zeta[\sqrt{LC}] = RC \Rightarrow \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

# Another Resonant Circuit

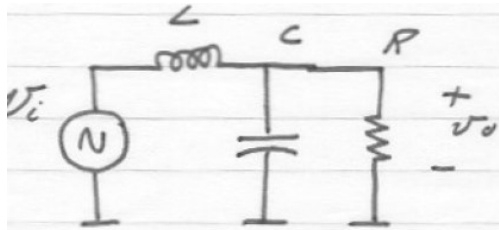

$$v_o/R + v_o/\Delta C + v_o/\Delta L - v_i/\Delta L = 0$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{1/\Delta L}{1/R + \Delta C + 1/\Delta L}$$

$$= \frac{1}{1 + \Delta(L/R) + \Delta^2 LC}$$

$$= \frac{1}{1 + (2\zeta/\omega_n)\Delta + \Delta^2/\omega_n^2}$$


$$\omega_n = 1/\sqrt{LC}$$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$
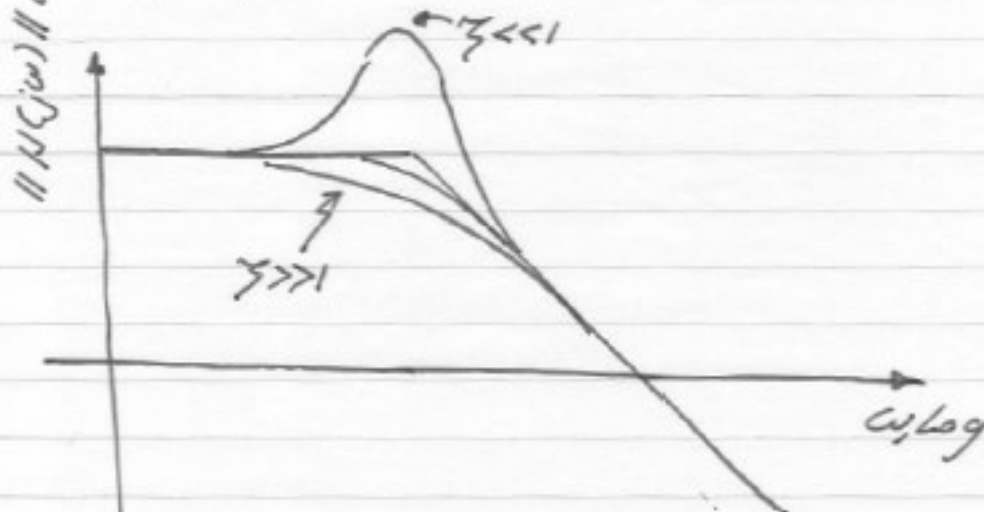
# Another Resonant Circuit

$$H(j\omega) = \frac{1}{1 + (2\zeta/\omega_n) \cdot j\omega - \omega^2/\omega_n^2}$$


$$= \begin{cases} 1 & \text{for } \omega \ll \omega_n \\ 1/2\zeta & \text{for } \omega = \omega_n \\ -(\omega_n/\omega)^2 & \text{for } \omega \gg \omega_n \end{cases}$$



The case  $\zeta \geq 1/\sqrt{2}$  gives no peaking



Peaking gets stronger for small  $\zeta$ .

# Low-Pass, 2nd-Order Filters

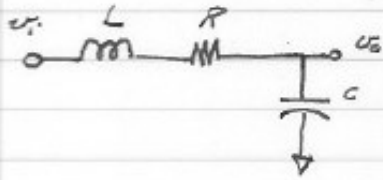


$$\frac{v_o}{v_i} = \frac{1/sC}{1/sC + R + sL} = \frac{1}{1 + sRC + s^2LC}$$
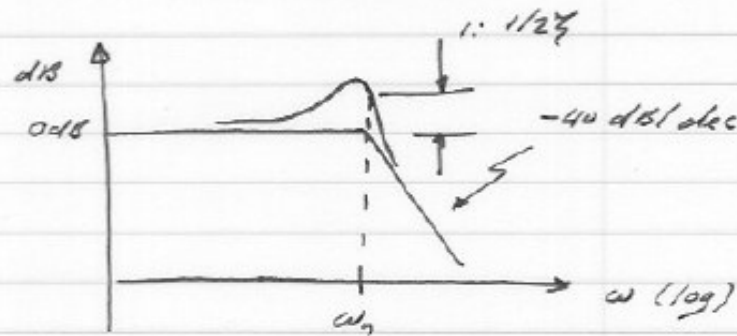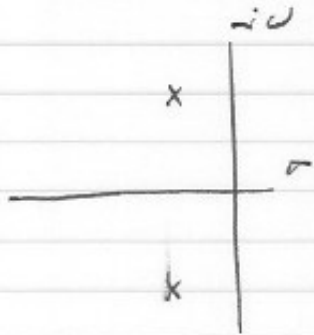
$$= \frac{1}{1 + s(2\zeta/\omega_n) + s^2/\omega_n^2}$$



$$\frac{v_o}{v_i} = \begin{cases} 1 & \omega \ll \omega_n & \text{Low Pass form} \\ 1/2\zeta & \omega = \omega_n & \text{no zero, 2 complex poles} \\ \omega_n^2/\omega^2 & \omega \gg \omega_n \end{cases}$$


# Band-Pass 2nd-Order Filters

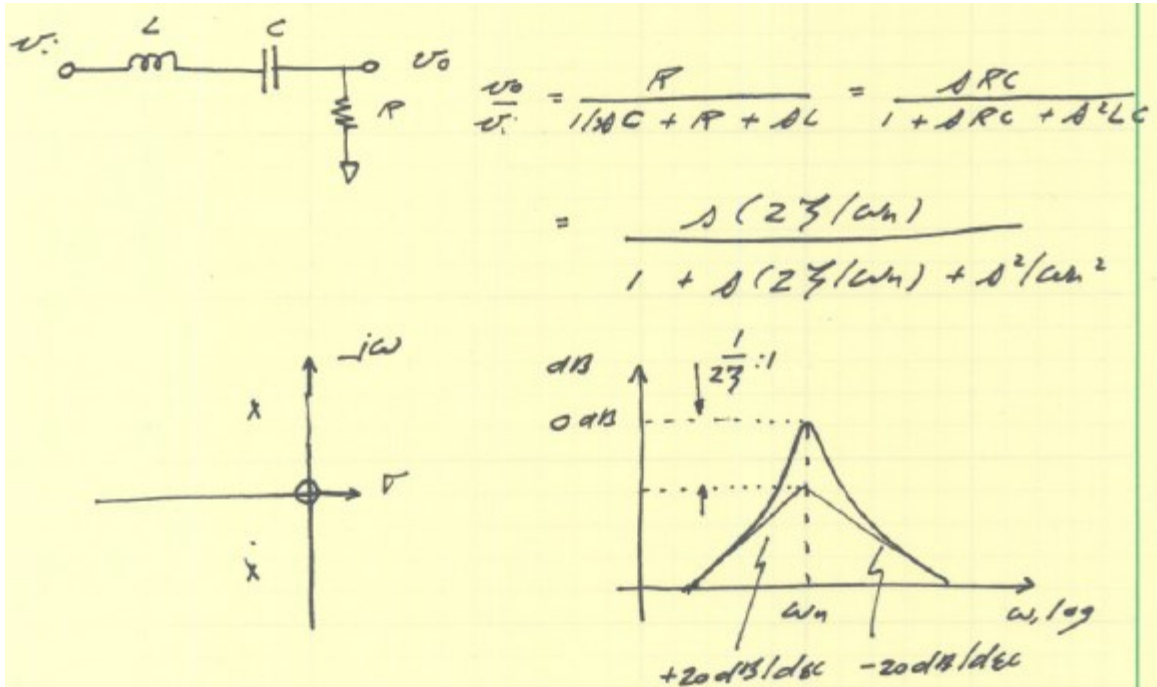


$$|v_o/v_i| = \begin{cases} 2\zeta \cdot \omega/\omega_n & (+20 \text{ dB/dec}) \text{ for } \omega \ll \omega_n \\ 1 & \text{for } \omega = \omega_n \\ 2\zeta \cdot \omega_n/\omega & (-20 \text{ dB/dec}) \text{ for } \omega \gg \omega_n \end{cases}$$

band pass form of "resonator"  
one zero, two complex poles.

# High-Pass 2nd-Order Filters

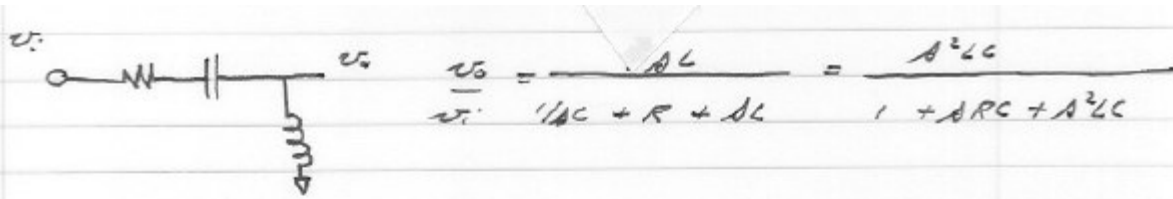
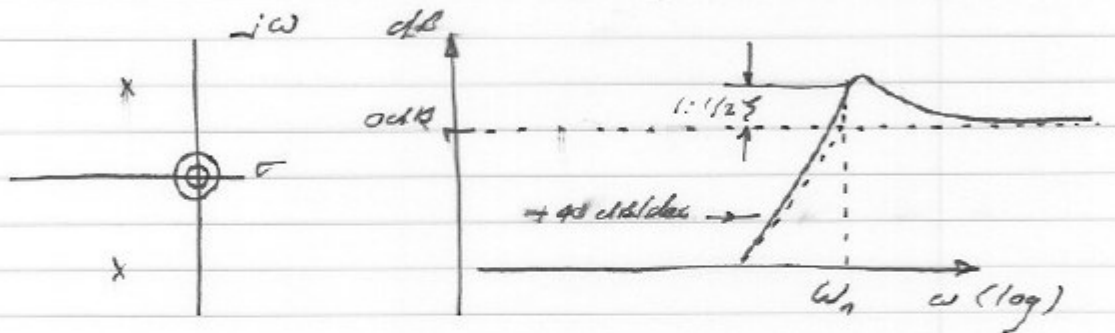
$$= \frac{A^2/\omega_n^2}{1 + A(2\zeta/\omega_n) + A^2/\omega_n^2}$$




$$\frac{v_o}{v_i} = \begin{cases} \omega^2/\omega_n^2 & (+40 \text{ dB/dec}) \text{ for } \omega \ll \omega_n \\ 1/(2\zeta) & \omega = \omega_n \\ 1 & \omega \gg \omega_n \end{cases}$$

High pass form

two zeros, 2 complex poles

# Impulse Response

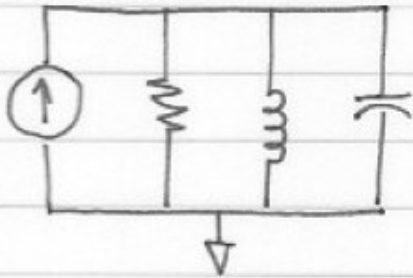

$$i(t) = g_0 \cdot \delta(t)$$

$$V(s)/I(s) = R \frac{s(2\zeta\omega_n)}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

$$\text{but } I(s) = g_0$$


$$\Rightarrow V(s) = g_0 R \frac{s(2\zeta\omega_n)}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

$$= g_0 R 2\zeta\omega_n \left[ \frac{s + \zeta\omega_n}{(s + \zeta\omega_n)^2 + \omega_d^2} + \frac{(-\zeta\omega_n/\omega_d) \cdot \omega_d}{(s + \zeta\omega_n)^2 + \omega_d^2} \right]$$

$$\text{but } (\omega_n/\omega_d) = 1/\sqrt{1-\zeta^2}$$
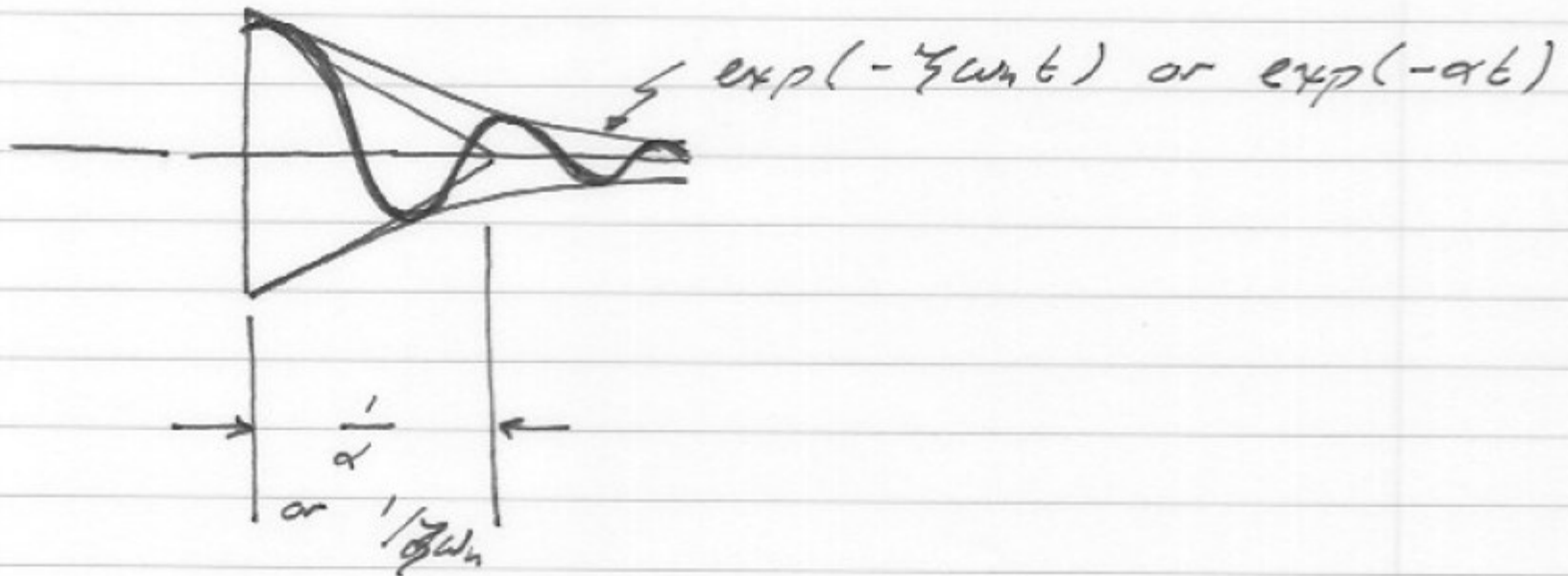
# Impulse Response

$$v(t) = g_0 R(2\zeta\omega_n) \left[ e^{-\zeta\omega_n t} \right] \left[ \cos(\omega_d t) - \frac{\zeta}{\sqrt{1-\zeta^2}} \sin(\omega_d t) \right]$$




- rings at a frequency  $\omega_d$


- decays at a rate  $\exp(-\alpha t)$



# Impulse Response

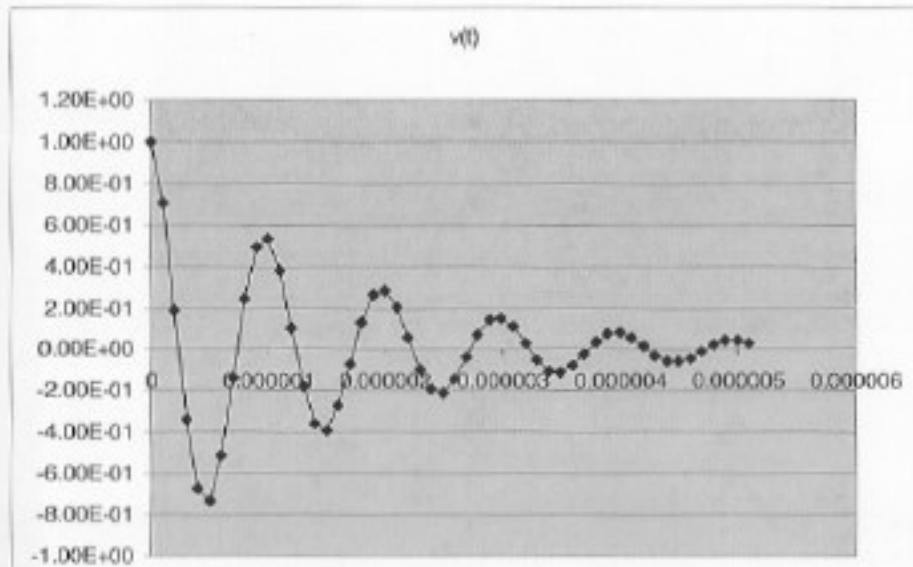


$$\zeta = 0.1$$

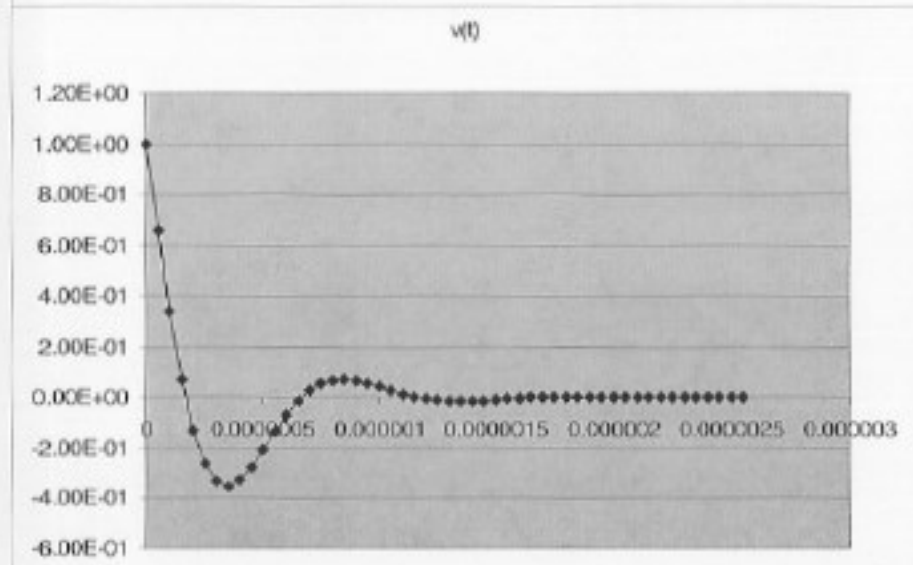

$$\zeta = 0.5$$

# Step Response of 2nd Order Systems

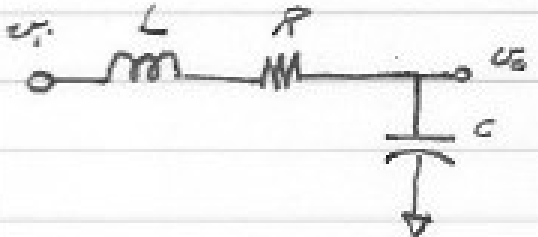

$$\frac{u_o}{u_i} = \frac{1/sC}{1/sC + R + sL} = \frac{1}{1 + sRC + s^2LC}$$

$$= \frac{1}{1 + s(2\zeta/\omega_n) + s^2/\omega_n^2}$$

What would be the step response?

# Step Response of 2nd Order Systems

$$H(s) = \frac{1}{1 + j\omega(2\zeta/\omega_n) + \omega^2/\omega_n^2}$$

$$= \frac{\omega_n^2}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

so, if  $v_{in}(t) = v_k \cdot u(t) \rightarrow V_{in}(s) = v_k/s$

then:  $V_{out}(s) = v_k \frac{\omega_n^2/s}{(s + \zeta\omega_n)^2 + \omega_d^2}$

$$\frac{1/s}{(s + \zeta\omega_n)^2 + \omega_d^2} = \frac{a}{s} + \frac{b s + c}{(s + \zeta\omega_n)^2 + \omega_d^2}$$

$$= a/s + \frac{b s + c}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\rightarrow 1 = a \cdot [s^2 + 2\zeta\omega_n s + \omega_n^2] + b s^2 + c s$$

$$s^0: \quad 1 = a \omega_n^2 \quad \rightarrow \quad a = 1/\omega_n^2$$

$$s^1: \quad 0 = 2\zeta\omega_n a + c \quad \rightarrow \quad c = -2\zeta/\omega_n$$

$$s^2: \quad 0 = a + b \quad \rightarrow \quad b = -1/\omega_n^2$$

# Step Response of 2nd Order Systems

$$\text{so: } V_0(s) = \frac{V_k}{s} + \frac{-V_k \cdot s - 2\zeta \omega_n V_k}{(s + \zeta \omega_n)^2 + \omega_d^2}$$

$$= \frac{V_k}{s} - V_k \frac{s + 2\zeta \omega_n}{(s + \zeta \omega_n)^2 + \omega_d^2}$$


$$\text{note that: } \frac{V_k \cdot (s + \zeta \omega_n)}{(s + \zeta \omega_n)^2 + \omega_d^2} \Rightarrow V_k \cdot e^{-\zeta \omega_n t} \cos \omega_d t \cdot u(t)$$

$$\text{and that: } \frac{V_k \cdot \zeta \omega_n}{(s + \zeta \omega_n)^2 + \omega_d^2} \Rightarrow V_k \zeta \frac{\omega_n}{\omega_d} e^{-\zeta \omega_n t} \sin \omega_d t \cdot u(t)$$

$$\text{this used: } \omega_n = \omega_d \cdot \sqrt{1 - \zeta^2}$$

# Low-Pass, 2nd-Order Filters: Its step response:

So:

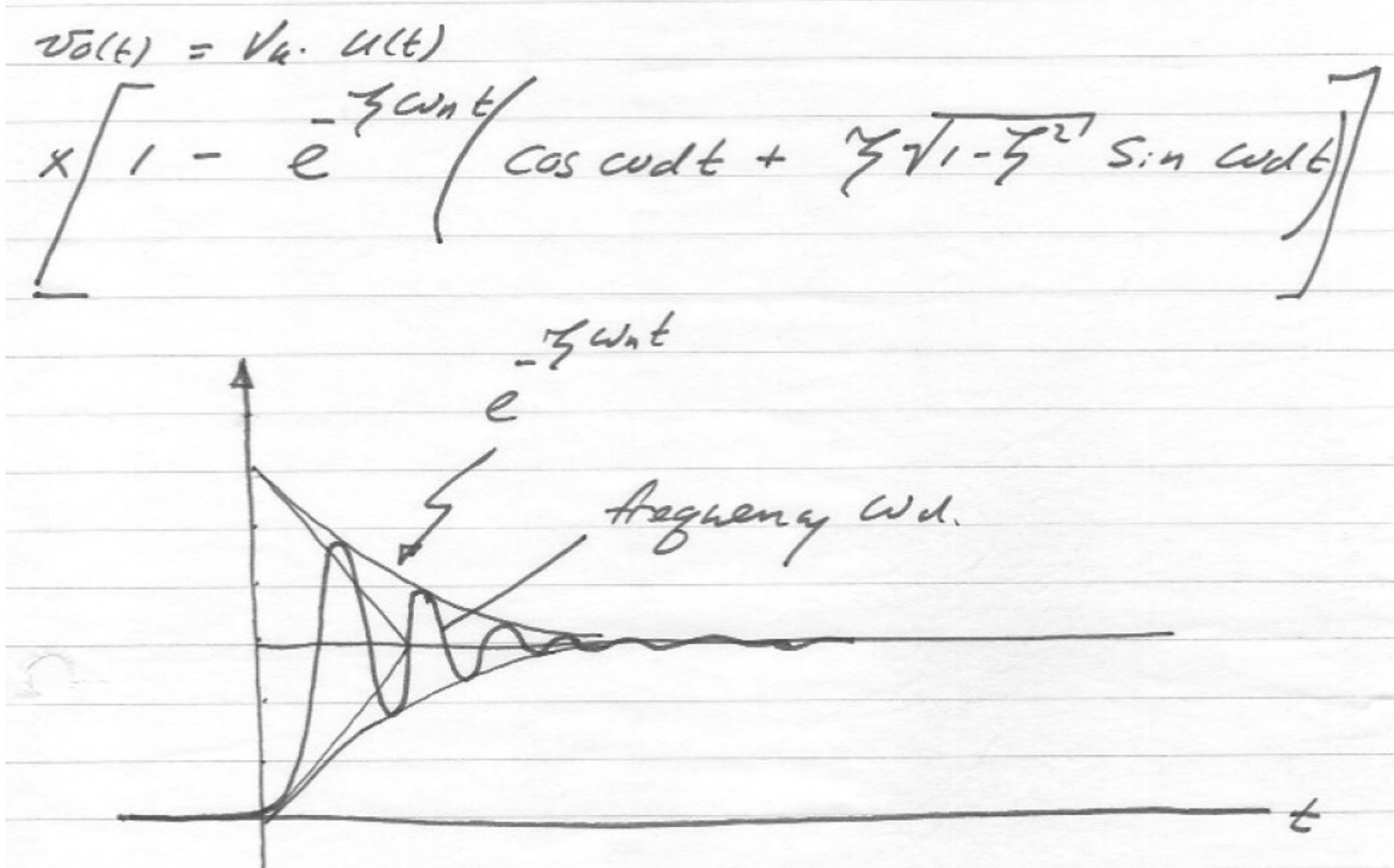

# Low-Pass, 2nd-Order Filters: Its step response:

The\*\*\*key observation\*\*\*

