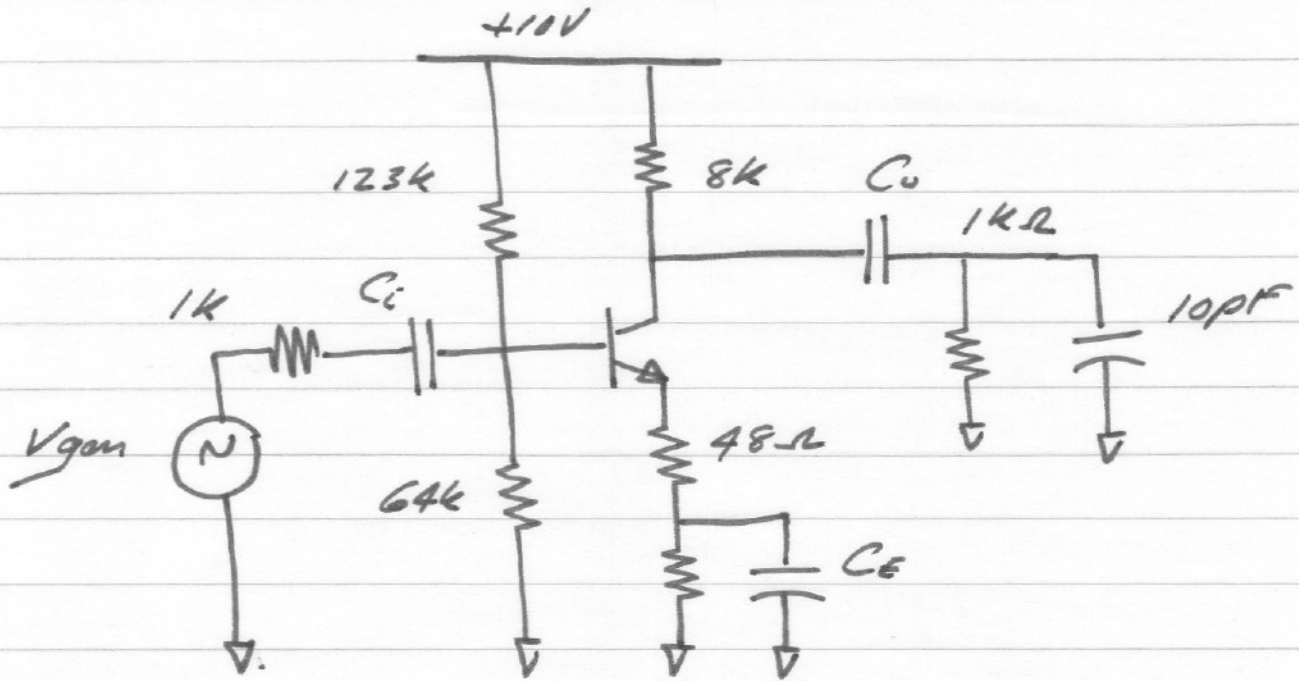


ECE137B Notes Set 4

Amplifier pulse response:



we had found earlier:

$$v_o/v_{gen}(s) = \frac{-8.9 (1 - s \cdot 1ns)}{(1 + s \cdot 0.11\mu s)(1 + s \cdot 2.1ns)}$$

Let us approximate:

$$v_o/v_{gen}(s) = \frac{-8.9}{(1 + s \cdot 0.11\mu s)(1 + s \cdot 2.1ns)}$$

Step response: $v_i(t) = IV \cdot u(t) \rightarrow V_i(s) = IV/s$

$$v_o/v_{gen} = \frac{A_0}{(1 + A\tau_1)(1 + A\tau_2)} \quad v_i(s) = \frac{B}{s} \quad ; B = IV$$

$$v_o(s) = \frac{A_0 B}{A(1 + A\tau_1)(1 + A\tau_2)}$$

$$= \frac{K_1}{1 + A\tau_1} + \frac{K_2}{1 + A\tau_2} + \frac{K_3}{A}$$

let A approach $-1/\tau_1$:

$$\frac{A_0 B}{(-1/\tau_1)(1 - \tau_2/\tau_1)} = K_1 = A_0 B \cdot \frac{\tau_1}{\tau_2 - \tau_1} \cdot \tau_1$$

let A approach $-1/\tau_2$:

$$K_2 = \frac{A_0 B}{(-1/\tau_2)(1 - \tau_1/\tau_2)} = A_0 B \frac{\tau_2}{\tau_1 - \tau_2} \cdot \tau_2$$

let A approach zero:

$$K_3 = A_0 B$$

$$U_0(s) = A_0 B \left(\frac{\tau_1}{\tau_2 - \tau_1} \right) \frac{\tau_1}{1 + s\tau_1} + A_0 B \left(\frac{\tau_2}{\tau_1 - \tau_2} \right) \frac{\tau_2}{1 + s\tau_2} + \frac{A_0 B}{A}$$

$$V_0(t) = A_0 B \left[u(t) - u(t) \frac{\tau_1}{\tau_1 - \tau_2} e^{-t/\tau_1} - u(t) \frac{\tau_2}{\tau_2 - \tau_1} e^{-t/\tau_2} \right]$$

$$A_0 B = -8.9V \quad \tau_1 = 0.11\mu s \quad \tau_2 = 2.1\mu s$$

$$V_{out}(t) = -8.9V \left[u(t) \right] \left[1 - 1.02 \cdot e^{-t/0.11\mu s} + 0.02 e^{-t/2.1\mu s} \right]$$

= this term, due to the 2nd pole in the frequency response

1) Is really small if $\tau_2 \ll \tau_1$

2) Dies down much more quickly if $\tau_2 \ll \tau_1$

Conclusion: pulse response is dominated by

the effect of the dominant pole

(4)


so we could have done this more quickly:

$$v_o/v_{gen}(s) \approx \frac{-8.9}{(1 + s \cdot 0.11 \mu s)}$$

2nd pole neglected;

$$V_o(s) = \frac{-8.9 \cdot 1V}{s \cdot (1 + s \cdot 0.11 \mu s)} = -8.9 \left[\frac{1}{s} - \frac{0.11 \mu s}{1 + s(0.11 \mu s)} \right]$$

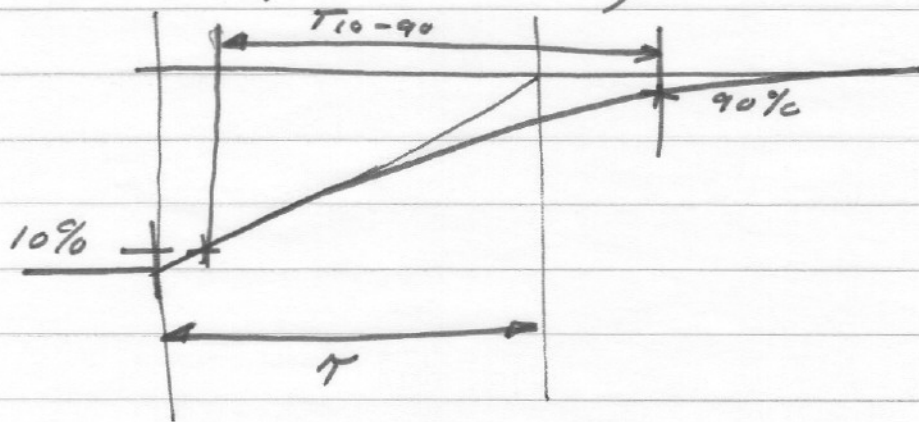
$$v_{out}(t) = -8.9 \cdot \left(1 - e^{-t/0.11 \mu s} \right) \cdot u(t)$$



$$T_{10-90} = \tau \cdot [\ln 0.9 - \ln 0.1] = 2.2\tau = 23045$$


LOW Frequency response

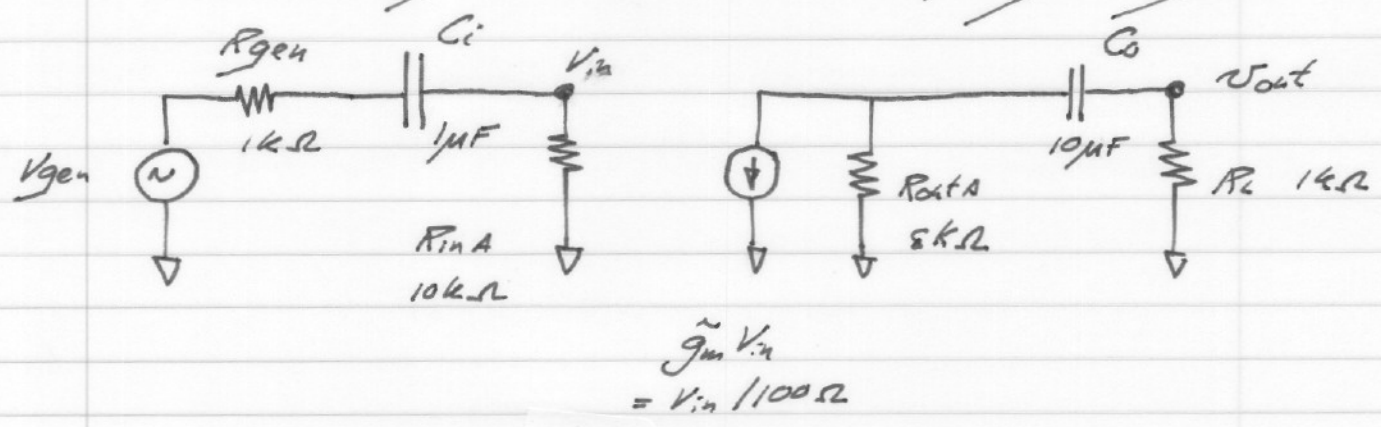Ignore C_E for now. This is not reasonable, but is necessary at present to simplify analysis.



$$\frac{v_{in}}{v_{gen}} = \frac{v_{in}}{v_{gen}} \Big|_{MS} \times \frac{1 + A T_{in}}{1 + A T_{in}} ; \quad T_{in} = C_i (R_{gen} + R_{inA}) = 11 \text{ ms}$$

$$= \frac{v_i}{v_{gen}} \Big|_{MS} \frac{j f / f_{low1}}{1 + j f / f_{low1}} ; \quad f_{low1} = 1 / 2\pi T_{in} = 14.4 \text{ Hz}$$

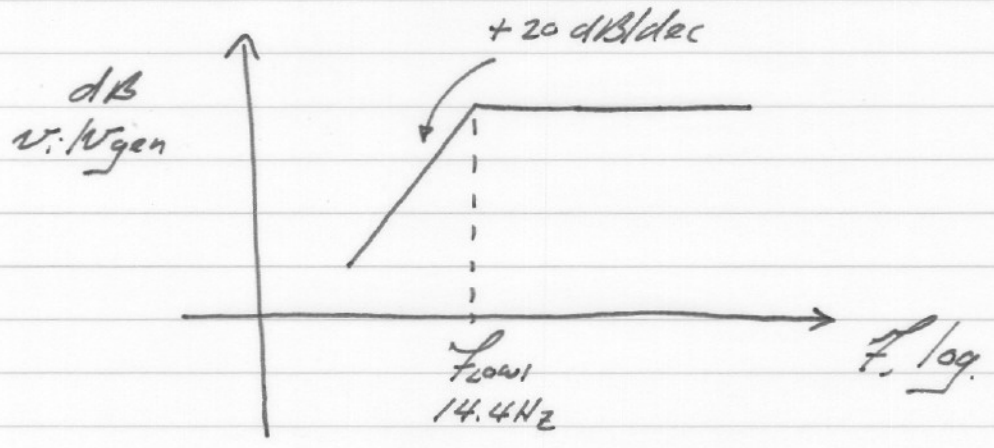


$$v_i / v_{gen} \Big|_{MS} = R_{inA} / (R_{inA} + R_{gen}) = 0.91$$

6


$$\frac{v_o}{v_i} = \frac{v_o}{v_i / M_{13}} \frac{A_{T_{out}}}{1 + A_{T_{out}}} ; T_{out} = C_0 (R_{outA} + R_L) = 90 \text{ ns}$$

$$\frac{v_o/v_i}{M_{13}} = -g_m (R_{outA} \parallel R_L) = -8.9$$
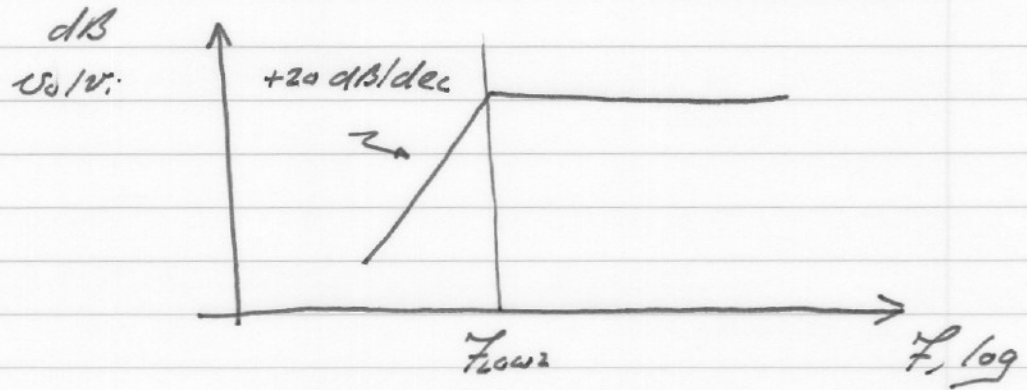
$$\frac{v_o}{v_i} = \frac{v_o}{v_i / M_{13}} \frac{j\omega / f_{low2}}{1 + j\omega / f_{low2}} ; f_{low2} = 1 / 2\pi T_{out} = 1.77 \text{ Hz}$$



Overall low-frequency response

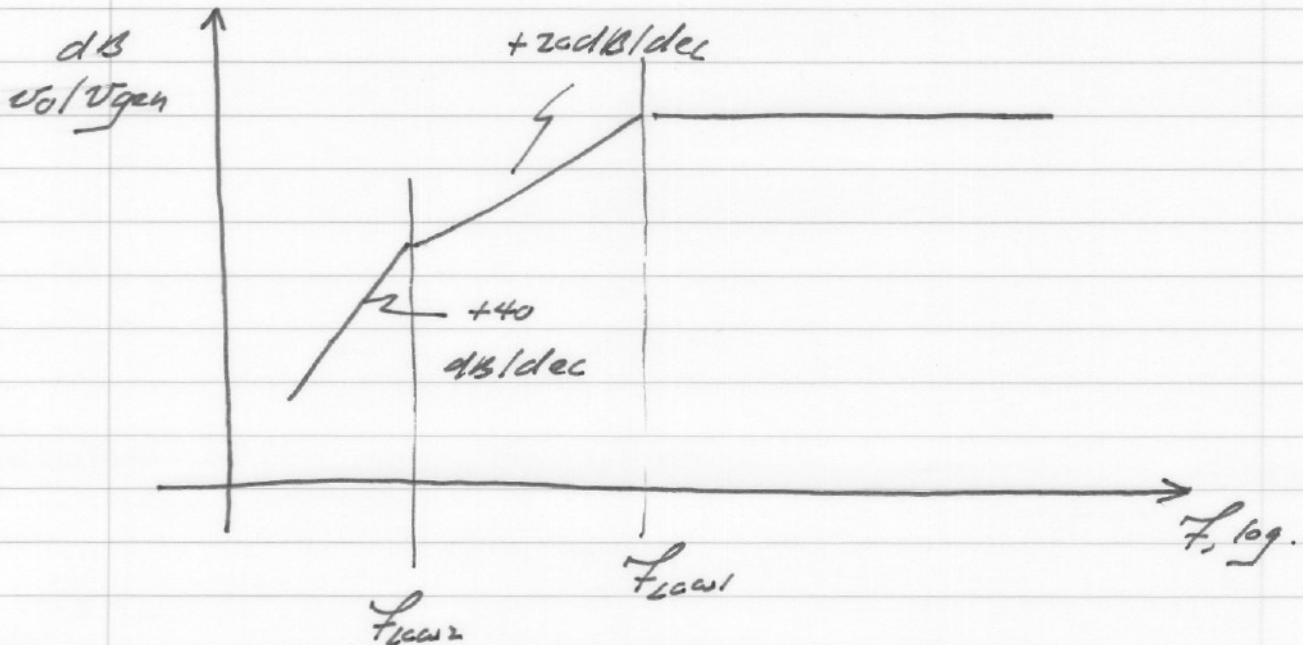

$$\frac{v_o}{v_{gen}} = \frac{v_o}{v_{gen}} \cdot \frac{A_{mb}}{A_{mb}} \cdot \frac{A \tau_{in}}{1 + A \tau_{in}} \cdot \frac{A \tau_{out}}{1 + A \tau_{out}}$$

- this ignores the high frequency rolloff

Step Response of amplifier

$v_{gen}(t) = v_x / A$ e.g. $v_{gen}(t) = v_x \cdot u(t)$

$$v_{out}(s) = \frac{\tau_o}{1 + A \tau_o} \cdot \frac{\tau_i}{1 + A \tau_i} \cdot A \cdot A_{mb} \cdot v_x$$

$$= A_{mb} v_x \left[\frac{\tau_{in}}{\tau_{in} - \tau_{out}} \cdot \frac{\tau_{out}}{1 + A \tau_{out}} + \frac{\tau_{out}}{\tau_{out} - \tau_{in}} \cdot \frac{\tau_{in}}{1 + A \tau_{in}} \right]$$



↘
↘
↘

-0.14
1.14


$$v_{out}(t) = A_{mb} v_x \left[\frac{\tau_{in}}{\tau_{in} - \tau_{out}} u(t) e^{-t/\tau_{out}} + \frac{\tau_{out}}{\tau_{out} - \tau_{in}} u(t) e^{-t/\tau_{in}} \right]$$

$\tau_{in} = 11 \text{ ms}$

$\tau_{out} = 90 \text{ ms}$

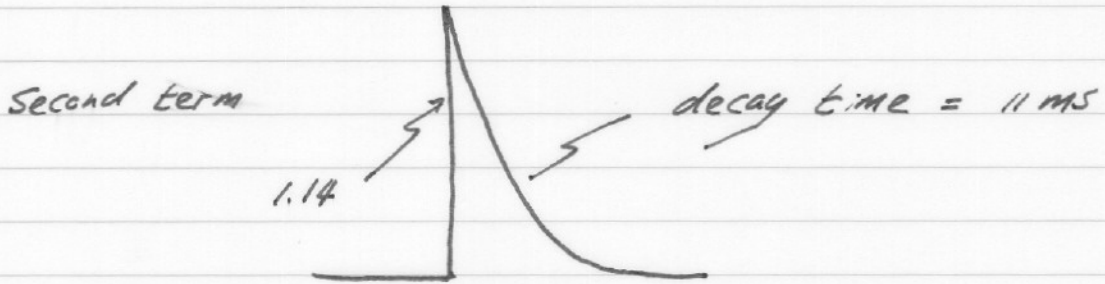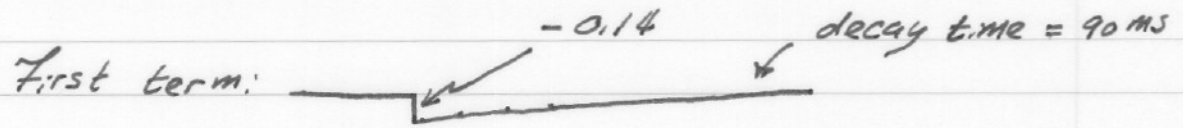


total response (normalized to $Ambv_x$):

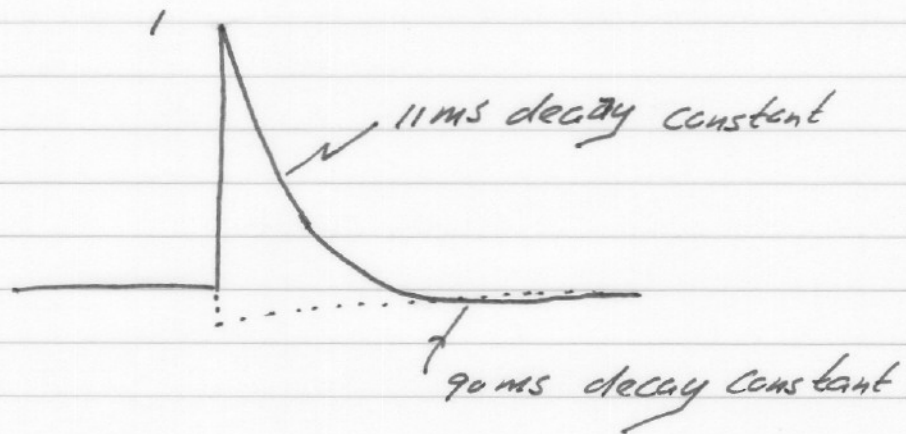


Again, the lower of the two low-frequency poles contributes only a small amount to the step response and decays away more slowly.

⇒ step response dominated by highest of high frequency poles.

overall frequency response

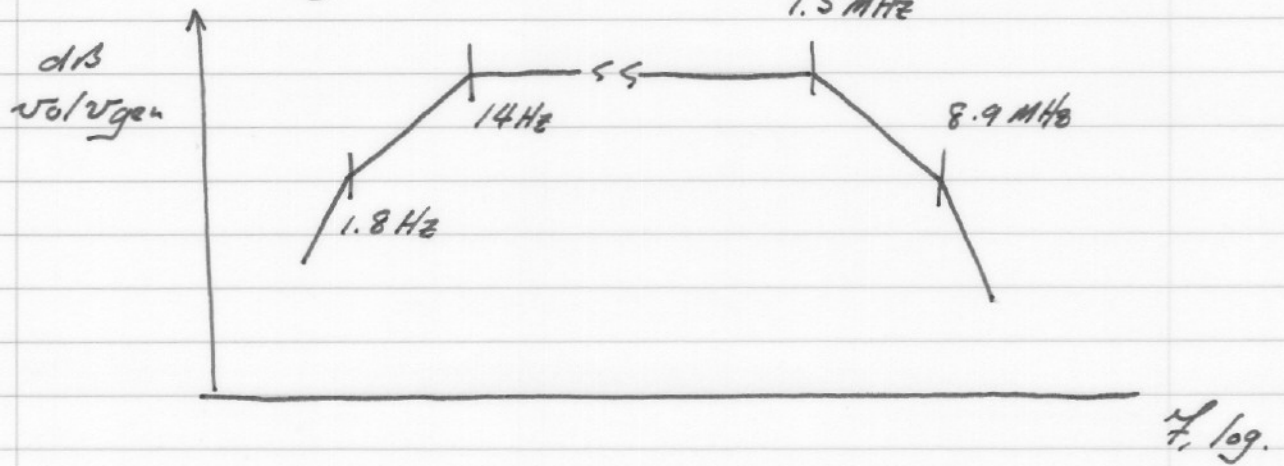

overall unit-step response

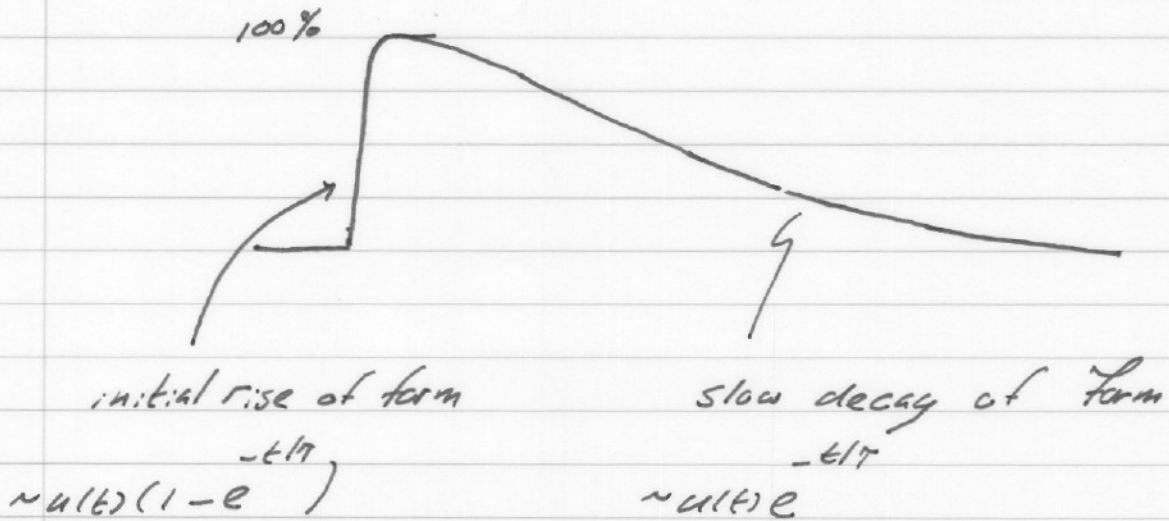

$T = 103 \text{ ns}$

$T = 11 \text{ ms}$

$T_{10-90} = 226 \text{ ns}$