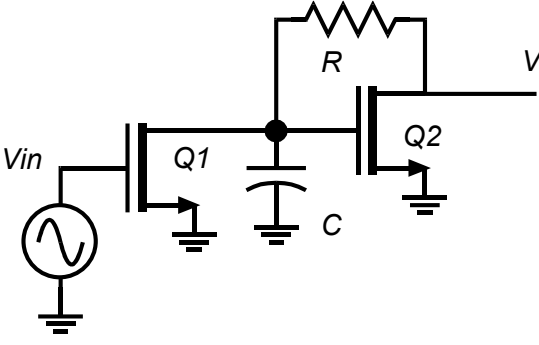
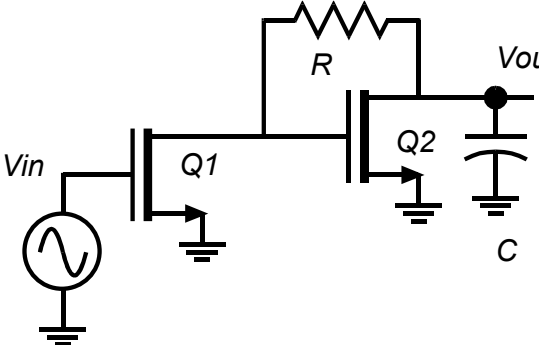
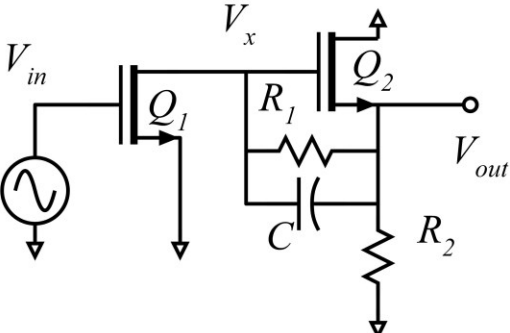
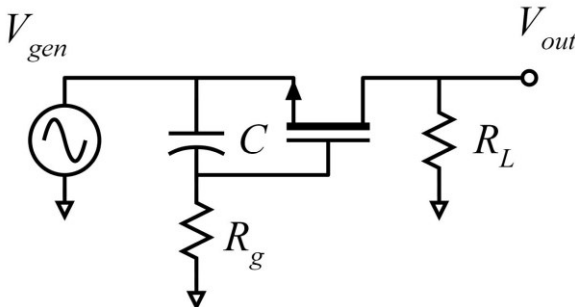
	<p>The problems below will use the following small signal model for the mosfet.</p>
	<p>Problem 1: This is a transconductance-transimpedance amplifier. Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>g_{m1}</math> and <math>g_{m2}</math> respectively. Their output resistances <math>R_{ds1}</math> and <math>R_{ds2}</math> are both infinity. <math>g_{m1}=40 \text{ mS}</math>. <math>g_{m2}=30 \text{ mS}</math>. <math>R=10\text{k}\Omega</math>. <math>C=100 \text{ fF}</math>, <math>C_{gs}=0 \text{ fF}</math></p> <p>a) Draw a small-signal equivalent circuit of the circuit</p> <p>b) Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math></p> <p>c) Find any/all pole and zero frequencies of the transfer function, in Hz:</p> <p>d) Draw a clean Bode Plot of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes</p>
	<p>Problem 2: Here again is a transconductance-transimpedance amplifier. Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>g_{m1}</math> and <math>g_{m2}</math> respectively. Their output resistances <math>R_{ds1}</math> and <math>R_{ds2}</math> are both infinity. <math>g_{m1}=40 \text{ mS}</math>. <math>g_{m2}=30 \text{ mS}</math>. <math>R=10\text{k}\Omega</math>. <math>C=100 \text{ fF}</math>, <math>C_{gs}=0 \text{ fF}</math></p> <p>(a) Draw a small-signal equivalent circuit of the circuit</p> <p>b) Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math></p> <p>c) Find any/all pole and zero frequencies of the transfer function, in Hz:</p> <p>d) Draw a clean Bode Plot of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains</p>

	<p>and pole or zero frequencies, Label Slopes</p>
 <p>Problem 3: Ignore DC bias analysis. You don't need it. The FETs have <math>\lambda=0</math> hence <math>G_{ds}=0</math>. further, <math>C_{gs}=C_{gd}=0</math> fF. But, <math>C, R_1, R_2</math> are all nonzero</p> <p>(a) Replacing the transistors with high frequency small-signal model, draw a small-signal equivalent circuit diagram.</p>	<p>(b) USING NODAL ANALYSIS, compute <math>V_{out}(s)/V_{in}(s)</math> in ratio-of-polynomials form</p> $V_{out}(s)/V_{in}(s) = A_{v, mid-band} \times (s\tau)^m \times \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$ <p>here <math>m</math>, an integer, can be positive or negative or zero.</p> <p>(c) <math>g_{m1}=10</math> mS. <math>g_{m2}=5</math> mS <math>R_1 =10</math> kOhm, <math>R_2=20</math> kOhm, <math>C=0.1</math>pF</p> <p>Find the frequencies of any zeros (there may be zero, one or two present ) in <math>V_{out}(s)/V_{in}(s)</math>:</p> <p>(d) Find any/all pole and zero frequencies of the transfer function, in Hz: Draw a clean Bode Plot on semilog paper of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes (d) <math>V_{in}(t)</math> is a 100 mV amplitude step-function Find <math>V_{out}(t)</math>, and plot it below. Label axes, show initial and final values, show time constants</p>
 <p>Problem 4: Ignore DC bias analysis. You don't need it. The transistor has transconductance <math>g_m</math>. Its output resistance <math>R_{ds}</math> is infinity. (a) Draw a small-signal equivalent circuit of the circuit. (b) <math>g_m=1</math> mS. <math>C=10</math> pF. . Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math></p> <p>(c) Find any/all pole and zero frequencies of the transfer function, in Hz: Draw a clean Bode Plot on semilog paper of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes (d) <math>V_{in}(t)</math> is a 100 mV amplitude step-function Find <math>V_{out}(t)</math>, and plot it below. Label axes, show initial and final values, show time constants</p>	<p>Problem 4: Ignore DC bias analysis. You don't need it. The transistor has transconductance <math>g_m</math>. Its output resistance <math>R_{ds}</math> is infinity. (a) Draw a small-signal equivalent circuit of the circuit. (b) <math>g_m=1</math> mS. <math>C=10</math> pF. . Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math></p> <p>(c) Find any/all pole and zero frequencies of the transfer function, in Hz: Draw a clean Bode Plot on semilog paper of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes (d) <math>V_{in}(t)</math> is a 100 mV amplitude step-function Find <math>V_{out}(t)</math>, and plot it below. Label axes, show initial and final values, show time constants</p>

	<p>Problem 5: Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>g_{m1}</math> and <math>g_{m2}</math> respectively. Their drain-source resistances <math>R_{ds1}</math> and <math>R_{ds2}</math> are both infinity. (a) Draw a small-signal equivalent circuit of the circuit (t) Find, by nodal analysis, a small-signal expression for <math>V_{out}/V_{in}</math></p>
	<p>Problem 6: <math>R_1=1\text{ k}\Omega</math>, <math>R_2=4\text{ k}\Omega</math>, <math>R_3=6\text{ k}\Omega</math>, <math>R_4=8\text{ k}\Omega</math>, <math>C_1=1\text{ fF}</math>, <math>C_2=2\text{ fF}</math>  Using Nodal analysis, find the transfer function <math>V_{out}(s)/V_{gen}(s)</math>. Give the answer in standard form</p> $\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big _{DC} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$