
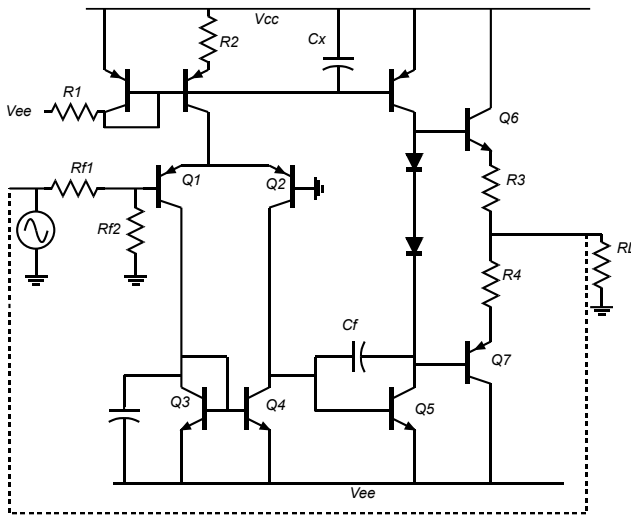


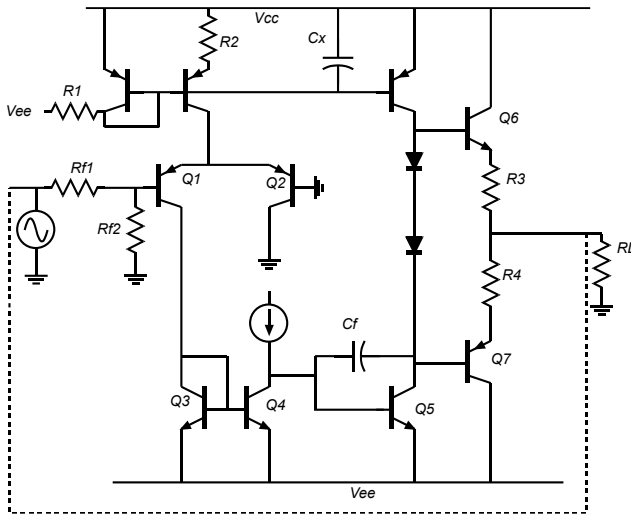Problem 1. All transistors except the output transistors have $C_{je}=10$ fF, $C_{cb}=40$ fF and $\tau_f=0.75$ ps. The push pull output transistors have $C_{je}=100$ fF, $C_{cb}=400$ fF and $\tau_f=1$ ps. All transistors have infinite beta, and infinite V_a , EXCEPT Q4 and Q5, giving them infinite beta but $V_a=100$ Volts. The 2 diodes have I_{se} 10:1 smaller than the 2 output transistors. The load resistance is 1000 Ohm. C_x is infinity, which AC grounds the bases of the 3 transistors connected to it. The supplies are + and - 3.3 volts. Q6 and Q7 are biased at 2 mA. All transistors are matched in I_s , except Q6 and Q7, which have 10:1 larger I_s . Choose R1 so that Q5 is biased at 2 mA emitter current. Choose R2 so that Q1 and Q2 are biased at 0.25 mA each. $R_{f1}=100$ Ohm, $R_{f2}=10$ Ohm. a) Find the DC bias conditions. Find the open-loop (Differential) gain of the operational amplifier. Choose C_f so that the loop bandwidth is 1 GHz.





b) High Frequency analysis. Assume Q7 is on and Q6 is off. With an infinite capacitor shorting Q3's collector and emitter, use the MOTC to find a_1 and a_2 associated with Q1 and Q2's input. (the high frequency analysis splits at Q2, because it is operating as a common base stage). Then, using the approximation that the time constant associated with $(C_{cb5}+C_f)$ is much larger than other time constants in the Q4/Q5/Q7 signal path, find a_1 and a_2 associated with this part of the circuit. Find the overall transfer function of the form

- Draw Bode plots (Magnitude and phase) of $A_d(f)$ and $\beta(f)$
- Find the loop bandwidth and estimate from this the bandwidth of V_{out}/V_{gen} .
- Find the gain margin and the phase margin of the feedback loop. Is the amplifier stable?




(Note that there is a second signal path through the amplifier, as illustrated at left. This is somewhat beyond the scope of the class...we will simply assume in 137b that the 2 paths have similar time constants.)

Problem 2:

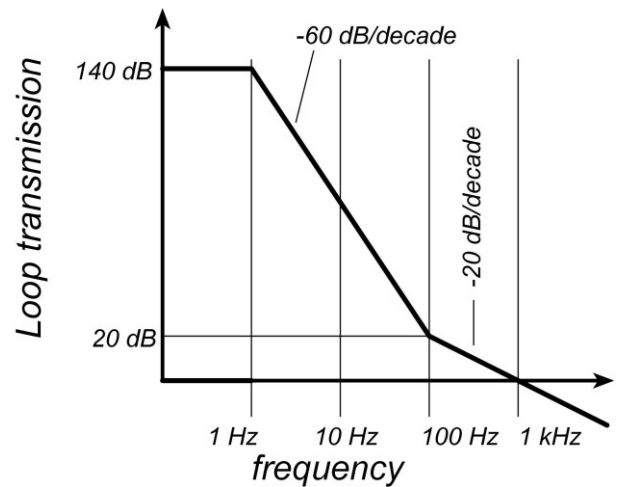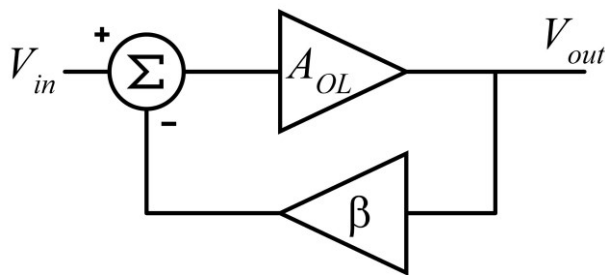

A control system, as sketched above, has a loop transmission with a DC value of 10^7 (140dB), three LHP poles at 1 Hz, and two LHP zeros at 100Hz. The resulting loop bandwidth is 1 kHz.

Make a the Nyquist stability plot below, and from this determine whether the loop is stable. *Very important hint: for the low-frequency portion of the plot (DC to about 500Hz), which will otherwise run off the paper, you can shrink the radial scale of the plot. The *radial scale* of the plot only needs to be accurate at frequencies at which $\|T\|$ is fairly close to 1, let us say between 0.5 and 2.0.*

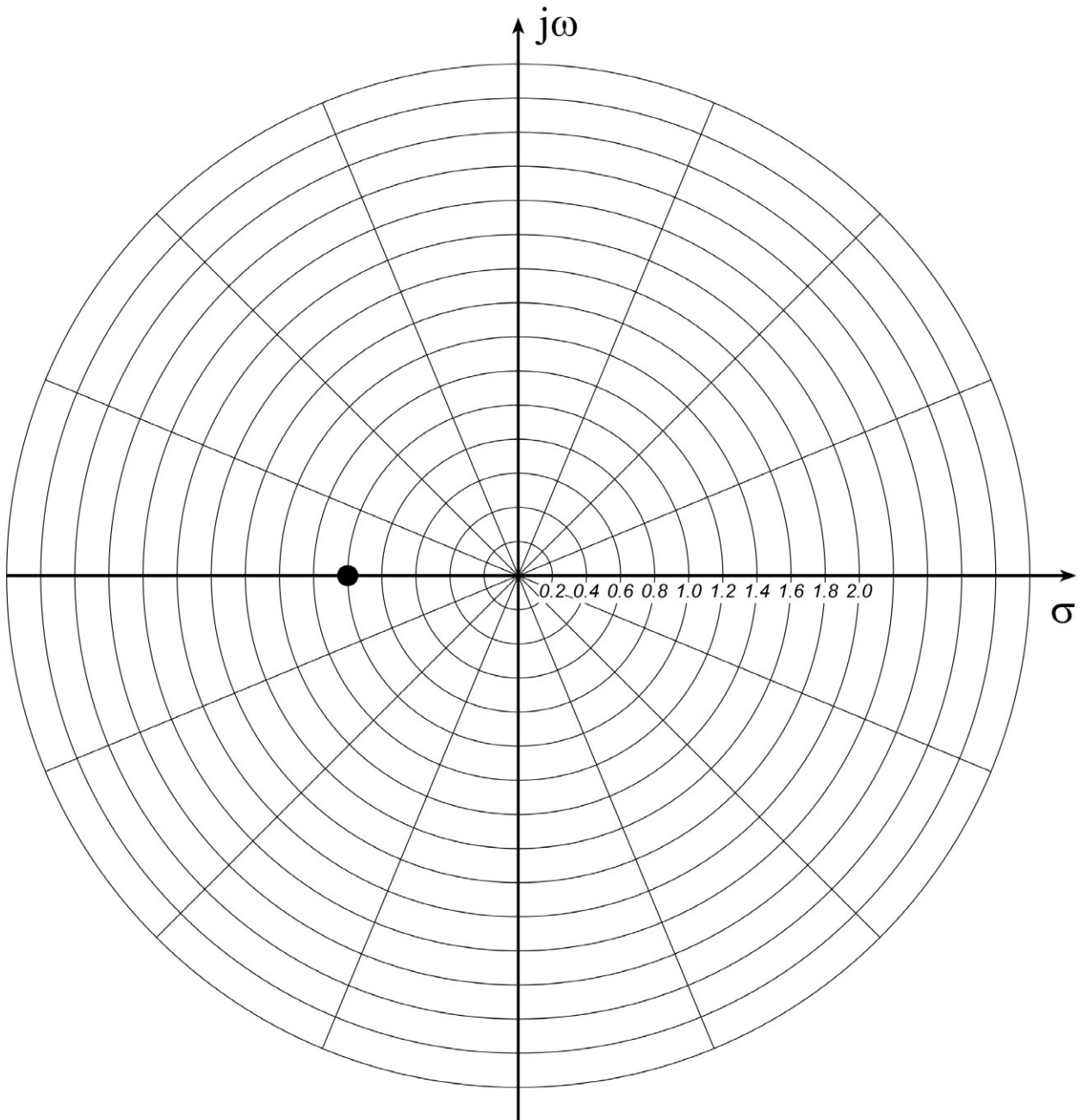

Problem 3

A different feedback loop. To the right is a plot of $T(j\omega)$, with ω plotted over the range from DC to a very high positive frequency. Both $A_{OL}(s)$ and $\beta(s)$ are stable, i.e. the open-loop amplifier and the feedback network are, of themselves, stable before the feedback loop is connected.

Is the loop stable or unstable ?

Yes/No is insufficient: you must clearly state why. If the loop is unstable, how many poles of the closed-loop gain $A_{CL}(s)$ lie in the unstable half of the S-plane ?

