

ECE145a / 218a ***Signal Flow Graphs***

Mark Rodwell

University of California, Santa Barbara

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

Signal Flow Graphs

Mason : control system theory

System of equations


(example : S - parameters)

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

Variables represented as nodes : a_1


Represent as below :

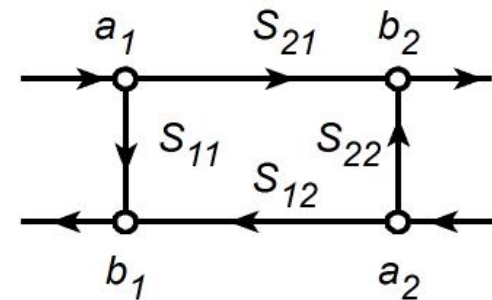

Value of variable = sum of entering branches

= sum of values of connecting nodes

times weight of branches.


Representation of Generator & Load

$$V^+ = T_s V_{gen} + \Gamma_s V^-$$


$$\rightarrow V^+ / \sqrt{Z_0} = T_s V_{gen} / \sqrt{Z_0} + \Gamma_s V^- / \sqrt{Z_0}$$

$$\rightarrow a_1 = a_{gen} + \Gamma_s b_1$$

$$\text{further : } a_2 = \Gamma_L b_2$$

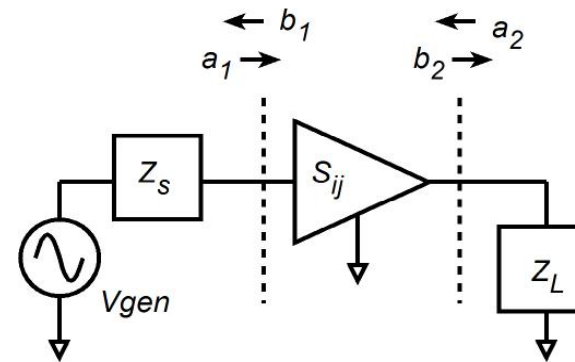


Representation :

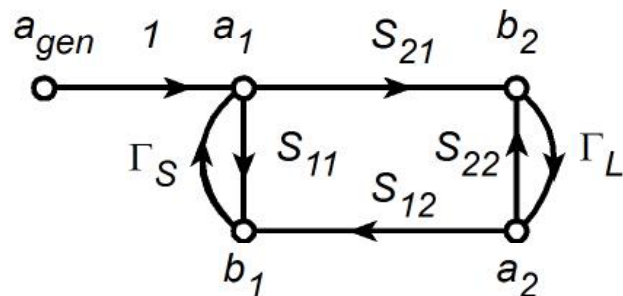


2nd Example: Cascaded Amplifiers

Circuit

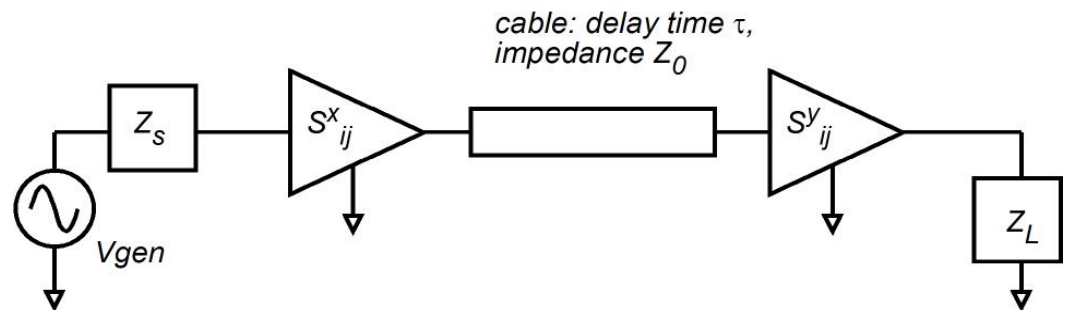

Representation

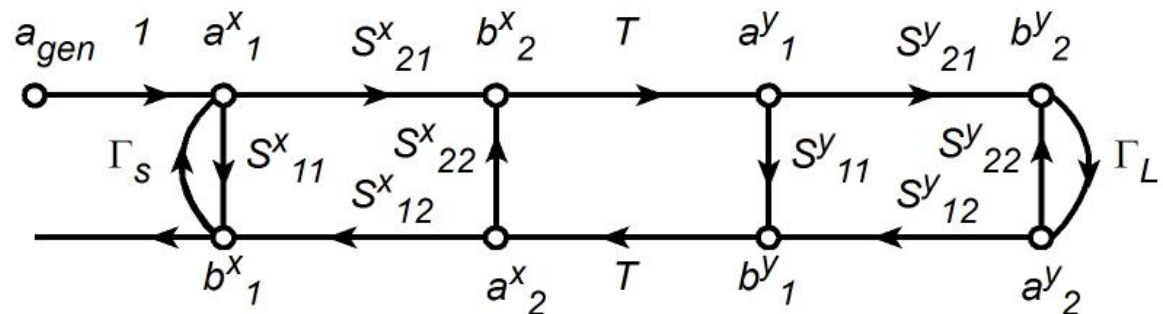

$$T = e^{-j\omega\tau}$$

The signal flow graph compactly and visually represents the many equations describing the system.

Why Use Signal Flow Graphs ?

Signal flow graphs most heavily used in control system theory :







- Organizes the representation of a set of linear equations
- Lends visual intuition in analysis.
- Provides efficient solution through * Mason's Gain Rules *

S.J. Mason : " Feedback theory – Some Properties of Signal Flow Graphs"
Proc. IRE, 41, p.1141, Sept. 1953.

or : Many texts on control system theory.


Manipulating Signal Flow Graphs

Elementary manipulations:

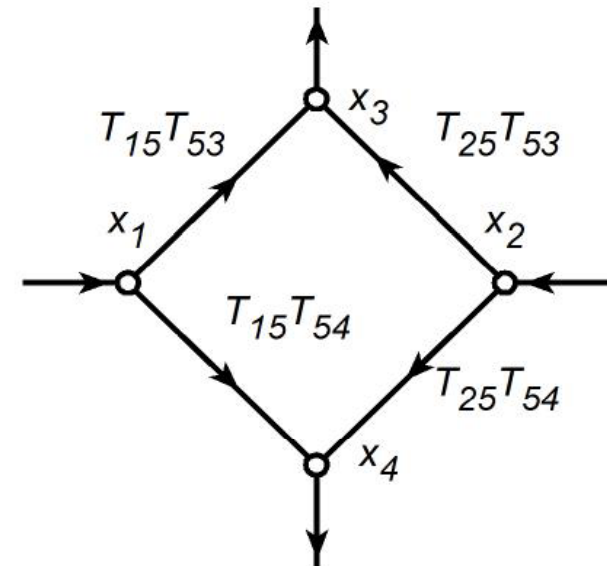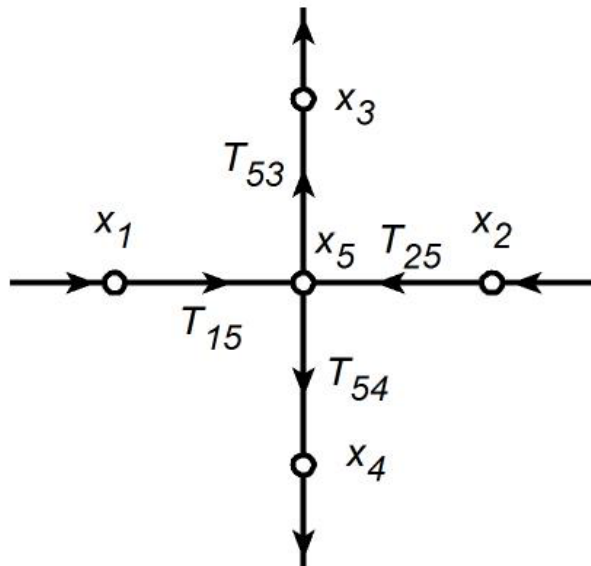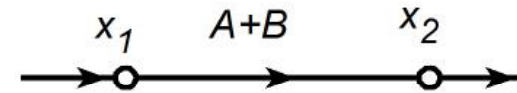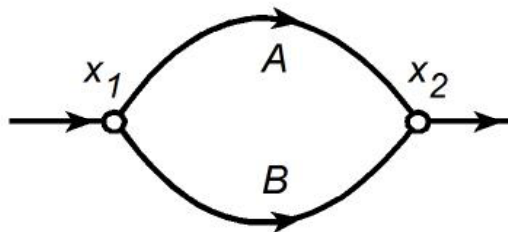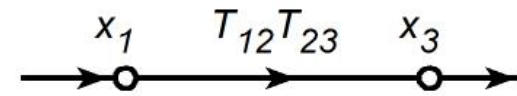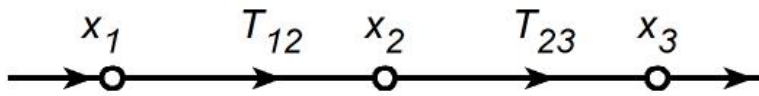

Reducing a Feedback Loop


System with feedback :

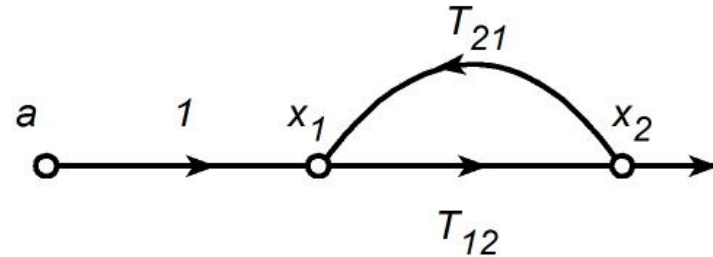

$$x_2 = T_{12}x_1$$


$$x_1 = a + T_{12}x_2$$
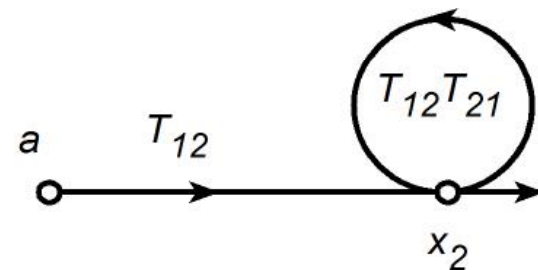
$$\rightarrow x_2 = T_{12}a + T_{12}T_{21}x_2$$



$$x_2 = T_{12}a + T_{12}T_{21}x_2$$
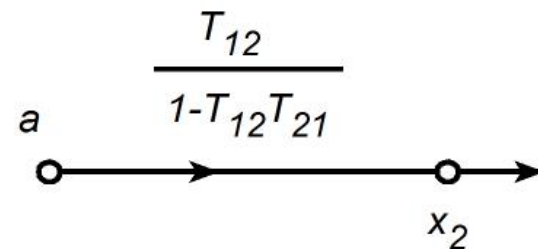
$$\rightarrow x_2 = \frac{T_{12}}{1 - T_{12}T_{21}} a$$





Mason's Gain Rule

Define $T = b/a =$ "transmission"

How do we find T ?

Define a path P_i as any route from a to b which does not go through any node twice.

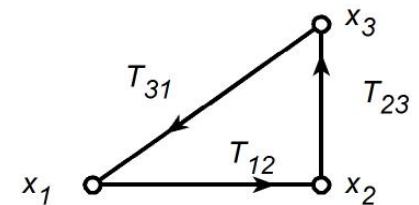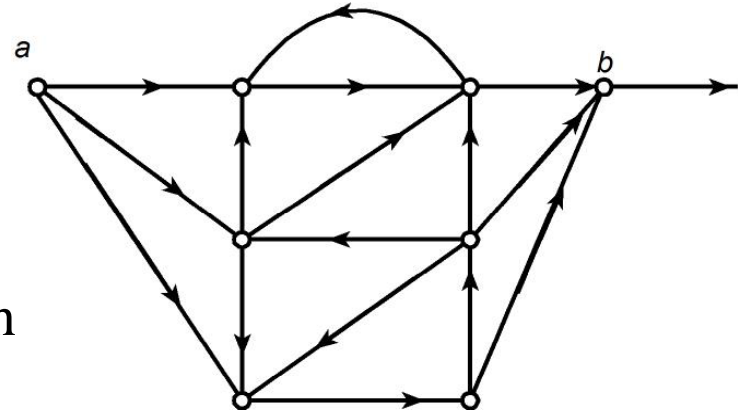Define a loop coefficient L_i as the product $(T_{12}T_{23}T_{31})$ of the transmission coefficients around any closed loop.



Mason's Gain Rule

$$T = \frac{b}{a} = \frac{P_1 \left[1 - \sum L(1)^{(1)} + \sum L(2)^{(1)} - \dots \right] + P_2 \left[1 - \sum L(1)^{(2)} + \sum L(2)^{(2)} - \dots \right] + \dots}{1 - \sum L(1) + \sum L(2) - \sum L(3) + \dots}$$

Where :

$\sum L(1)$ = sum of all loop coefficients


$\sum L(1)^{(1)}$ = sum of all loop coefficients for loops
which do not touch path P_1

$\sum L(2)$ = sum of all second - order loops

A second - order loop is the product of the coefficients of any pair of non - touching loops.


$\sum L(2)^{(1)}$ = sum of all second - order loops which do not touch path P_1 .

etc.

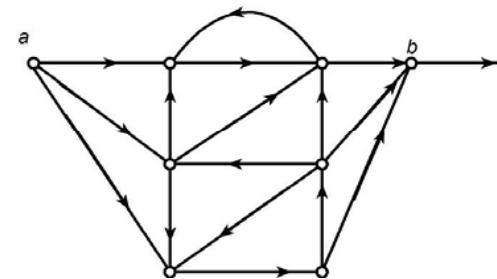

Analysis of Simple Amplifier

Find $T = b_2 / a_{gen}$

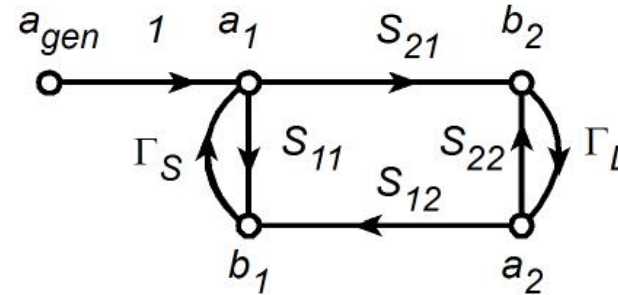


$$T = \frac{P_1 [1 - \cancel{\sum L(1)^{(1)}} + \cancel{\sum L(2)^{(1)}} - \dots]}{1 - \sum L(1) + \sum L(2)}$$

$$= \frac{S_{21}}{1 - \underbrace{\Gamma_s S_{11} - \Gamma_l S_{22} - \Gamma_s \Gamma_l S_{21} S_{12}}_{\sum L(1)} + \underbrace{\Gamma_s S_{11} \Gamma_l S_{22}}_{\sum L(2)}}$$


= easy !

Input Reflection Coefficient
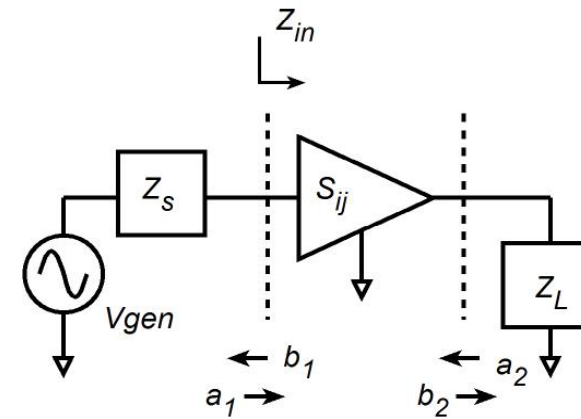
$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$



Overall Representation

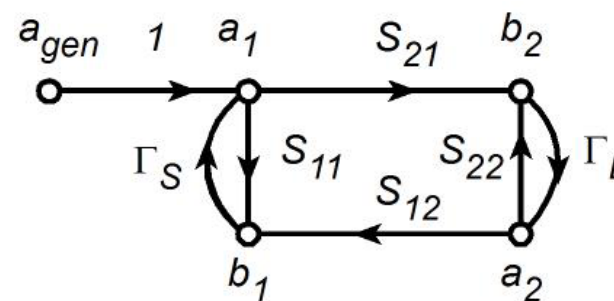


Input Reflection Coefficient

Relationship between incident and reflected waves at input :

$$T = \frac{b_1}{a_1} = \Gamma_{in} = \frac{S_{11}[1 - S_{22}\Gamma_L] + S_{21}\Gamma_L S_{12}}{1 - S_{22}\Gamma_L}$$
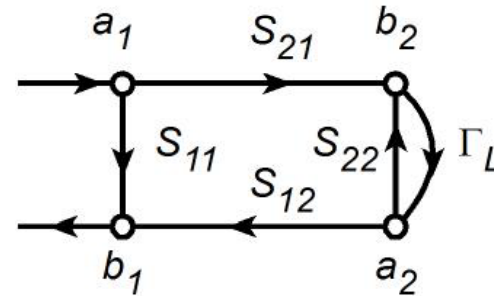
$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L}$$




Input $\left\{ \begin{array}{l} \text{impedance} \\ \text{reflection coefficient} \end{array} \right\}$ depends upon

load $\left\{ \begin{array}{l} \text{impedance} \\ \text{reflection coefficient} \end{array} \right\}$ unless $S_{12}S_{21} = 0$.

Output Reflection Coefficient

Relationship between incident and reflected waves at output :
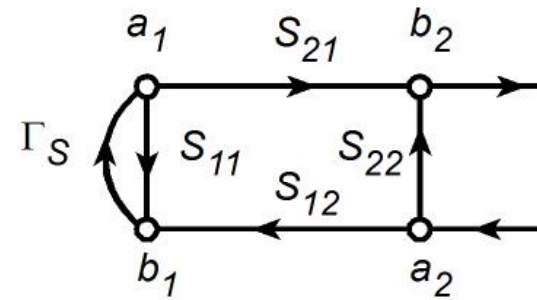
$$T = \frac{b_2}{a_2} = \Gamma_{out} = \frac{S_{22}[1 - S_{11}\Gamma_S] + S_{21}\Gamma_S S_{12}}{1 - S_{11}\Gamma_S}$$



$$\Gamma_{out} = S_{22} + \Gamma_S \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_S}$$

Output $\left\{ \begin{array}{l} \text{impedance} \\ \text{reflection coefficient} \end{array} \right\}$ depends upon

source $\left\{ \begin{array}{l} \text{impedance} \\ \text{reflection coefficient} \end{array} \right\}$ unless $S_{12}S_{21} = 0$.

Implication for Impedance Matching

$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L}$$

$$\Gamma_{out} = S_{22} + \Gamma_S \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_S}$$

If $S_{12}S_{21} = 0$, then either $S_{12} = 0$ or $S_{21} = 0$.

In either case, the amplifier cannot pass signals in both directions.

If $S_{12}S_{21} = 0$, the amplifier is * unilateral *.

Unilateral amplifiers have $\Gamma_{in} = S_{11}$ and $\Gamma_{out} = S_{22}$.

In this case, tuning the input match does not disturb the output tuning, nor does tuning the output match disturb the input tuning.

In bilateral amplifiers ($S_{12}S_{21} \neq 0$), input and output tuning are interactive.

Interactive tuning \rightarrow at a minimum: design is more difficult.

If $S_{12}S_{21}$ is sufficiently large, we will find that matching is not possible.


Origin of Nonzero $S_{12}S_{21}$

Reverse coupling in common-source FETs : C_{gd}

Reverse coupling in common-emitter BJT : C_{cb}

Reverse coupling in common-gate FETs : L_g, C_{ds}

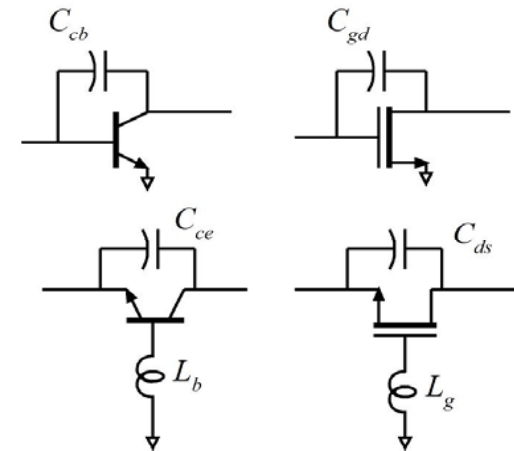Reverse coupling in common-base BJT : L_b, C_{ce}




Some of these are device parasitics, some arise only from poor interconnect design near the device terminals.

High reverse isolation (low S_{12}) increases amplifier stability and (usually) increases device maximum stable gain.

Available Source Power


$$P_{AV,G} = \|V_{gen}\|^2 / 4 \cdot \text{Re}\{Z_{gen}\}$$

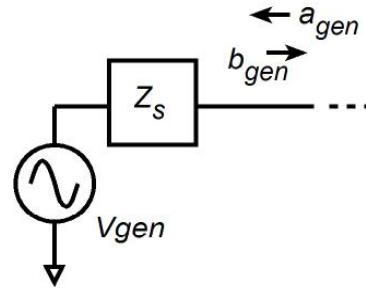

$$b_{gen} = T_s V_{gen} / \sqrt{Z_0} + \Gamma_s a_{gen}$$


$$b_{gen} = b_s + \Gamma_s a_{gen}$$

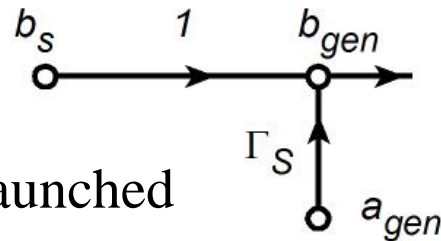note that b_s is the wave amplitude launched into a load $Z_L = Z_0$



Now : connect conjugate - matched load
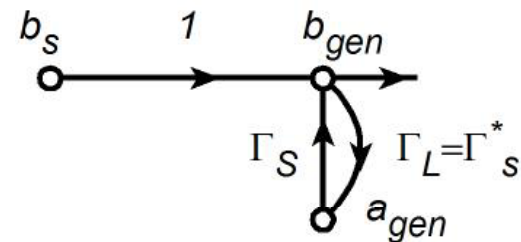
$$Z_L = Z_S^* \text{ i.e. } \Gamma_L = \Gamma_S^*$$



Available Source Power

$$\text{Reverse Power} = \|b_s\|^2 \frac{\|\Gamma_L\|^2}{[1 - \|\Gamma_S\|^2]^2} = \|b_s\|^2 \frac{\|\Gamma_S\|^2}{[1 - \|\Gamma_S\|^2]^2}$$

$$\text{Forward Power} = \|b_s\|^2 \frac{1}{[1 - \|\Gamma_S\|^2]^2}$$

$$\text{Load Power} = \text{Available Power} = \|b_s\|^2 \frac{1}{1 - \|\Gamma_S\|^2}$$

$$P_{AVG} = \frac{\|b_s\|^2}{1 - \|\Gamma_S\|^2} \text{ where } \|b_s\|^2 \text{ is the power delivered to } Z_L = Z_0$$

