

***ECE145a / 218a***

***Tuned Amplifier Design***

***-basic gain relationships***

***-design in the (simple) unilateral limit***

***Mark Rodwell***

***University of California, Santa Barbara***

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax


# Generator Wave Relationships

Recall from last notes set :

$$V^+ = T_s V_{gen} + \Gamma_s V^-$$

$$\rightarrow V^+ / \sqrt{Z_0} = T_s V_{gen} / \sqrt{Z_0} + \Gamma_s V^- / \sqrt{Z_0}$$
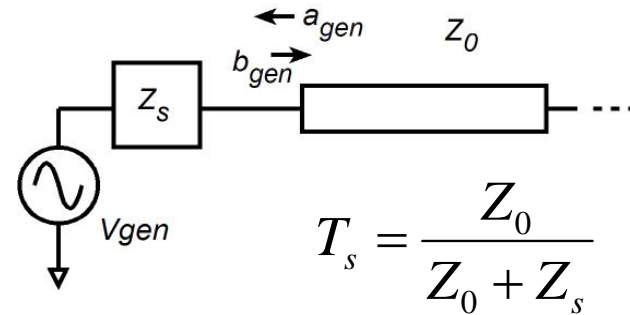
$$\rightarrow b_{gen} = b_s + \Gamma_s a_{gen}$$



$$b_{gen} = b_s + \Gamma_s a_{gen}$$

$$\text{where } b_s = \frac{\sqrt{Z_0}}{Z_0 + Z_s} \cdot V_{gen}$$

$$\text{and } \Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$$

# Generator Wave Relationships: Load Power



$$b_{gen} = b_s + \Gamma_s a_{gen}$$

$$\text{Power delivered to } Z_0 : P_{Z_0} = \|b_{gen}\|^2$$

$$\text{Power delivered to } \Gamma_L : P_{Load} = \|b_{gen}\|^2 - \|a_{gen}\|^2$$

$$b_{gen} = b_s / (1 - \Gamma_S \Gamma_L) \quad \text{and} \quad a_{gen} = \Gamma_L b_{gen}$$

$$\text{so: } \|b_{gen}\|^2 = \frac{\|b_s\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \quad \text{and} \quad \|a_{gen}\|^2 = \|\Gamma_L\|^2 \cdot \|b_{gen}\|^2$$

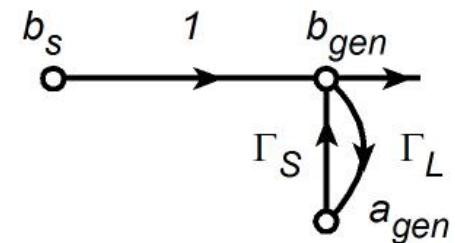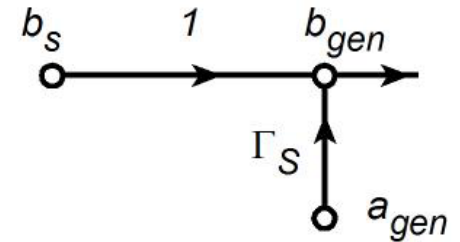


Power delivered to an arbitrary load

$$P_{load} = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot \|b_s\|^2 = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot P_{Z_0}$$

# Generator Wave Relationships: Available Power

Power delivered to an arbitrary load


$$P_{load} = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot \|b_s\|^2 = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot P_{Z_0}$$

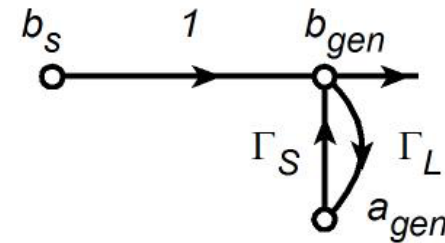

Power delivered to a matched load  $\Gamma_L = \Gamma_S^*$



$$P_{AVG} = \frac{1 - \|\Gamma_S\|^2}{\|1 - \Gamma_S \Gamma_S^*\|^2} \cdot \|b_s\|^2 = \frac{1 - \|\Gamma_S\|^2}{\|1 - \|\Gamma_S\|^2\|^2} \cdot \|b_s\|^2$$

$$= \frac{\|b_s\|^2}{1 - \|\Gamma_S\|^2}$$

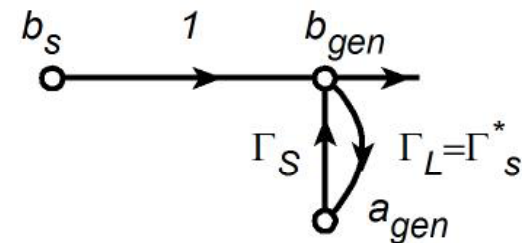

$$P_{AVG} = \frac{\|b_s\|^2}{1 - \|\Gamma_S\|^2} = \frac{P_{Z_0}}{1 - \|\Gamma_S\|^2}$$

# Transducer Gain

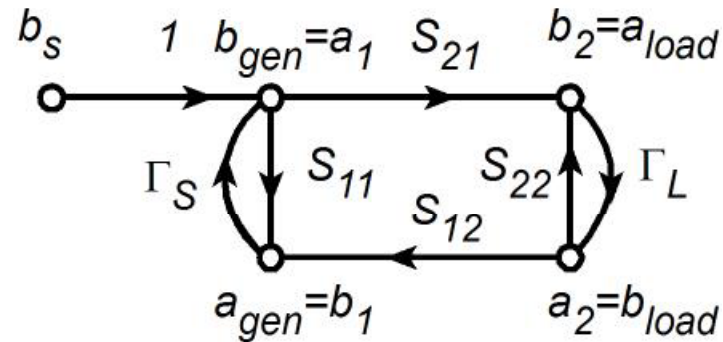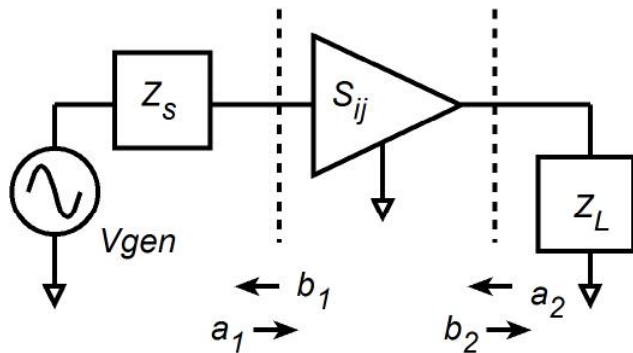

$$\frac{a_{load}}{b_s} = \frac{S_{21}}{1 - \Gamma_s S_{11} - \Gamma_L S_{22} - \Gamma_s \Gamma_L S_{21} S_{12} + \Gamma_s S_{11} \Gamma_L S_{22}} = \frac{S_{21}}{(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - \Gamma_s \Gamma_L S_{21} S_{12}}$$

Transducer Gain :  $G_T = P_{load} / P_{AVG}$

$$P_{AVG} = \frac{\|b_s\|^2}{1 - \|\Gamma_s\|^2}$$

$$\text{while } P_{load} = \|a_{load}\|^2 - \|b_{load}\|^2 = \|a_{load}\|^2 \cdot [1 - \|\Gamma_{load}\|^2]$$

# Transducer Gain

$$G_T = \frac{P_{load}}{P_{AVG}} = \frac{[1 - \|\Gamma_s\|^2]}{\|b_s\|^2} \cdot \|a_{load}\|^2 \cdot [1 - \|\Gamma_{load}\|^2] = \frac{\|a_{load}\|^2}{\|b_s\|^2} \cdot [1 - \|\Gamma_{load}\|^2] \cdot [1 - \|\Gamma_s\|^2]$$

$$\text{but } \frac{a_{load}}{b_s} = \frac{S_{21}}{(1 - \Gamma_s S_{11})(1 - \Gamma_l S_{22}) - \Gamma_s \Gamma_l S_{21} S_{12}}$$

$$\Rightarrow G_T = \frac{\|S_{21}\|^2 \cdot [1 - \|\Gamma_{load}\|^2] \cdot [1 - \|\Gamma_s\|^2]}{\|(1 - \Gamma_s S_{11})(1 - \Gamma_l S_{22}) - \Gamma_s \Gamma_l S_{21} S_{12}\|^2}$$

This is the general bilateral expression for transducer gain.



It depends upon,  $\Gamma_s, \Gamma_{load}$ , and  $\{S_{21}, S_{12}, S_{11}, S_{22}\}$ .

# Input and Output Impedance Relationships

Recall that

$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L}$$
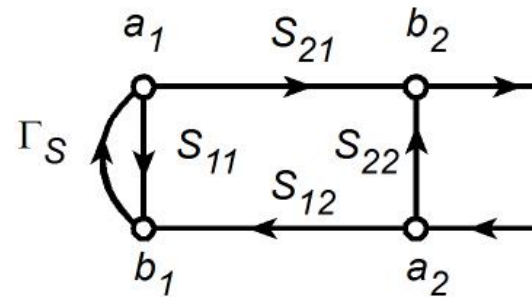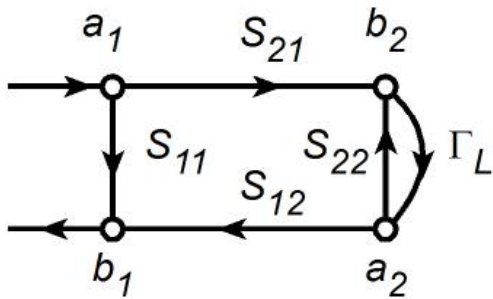
$$\Gamma_{out} = S_{22} + \Gamma_S \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_S}$$



# Input and Output Impedance Relationships

$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} \quad \text{and} \quad G_T = \frac{\|S_{21}\|^2 \cdot [1 - \|\Gamma_{load}\|^2] \cdot [1 - \|\Gamma_s\|^2]}{\|1 - \Gamma_s S_{11} - \Gamma_l S_{22} + \Gamma_s S_{11} \Gamma_l S_{22} - \Gamma_s \Gamma_l S_{21} S_{12}\|^2} = \frac{N}{D}$$

$$\begin{aligned} D &= \left\| 1 - \Gamma_s \left( \Gamma_{in} - \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} \right) - \Gamma_l S_{22} + \Gamma_s \Gamma_l S_{22} \left( \Gamma_{in} - \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} \right) - \Gamma_s \Gamma_l S_{21} S_{12} \right\|^2 \\ &= \left\| 1 - \Gamma_s \Gamma_{in} + \Gamma_s \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} - \Gamma_l S_{22} + \Gamma_s \Gamma_l S_{22} \Gamma_{in} - \Gamma_s \Gamma_l S_{22} \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} - \Gamma_s \Gamma_l S_{21} S_{12} \right\|^2 \\ &= \left\| 1 - \Gamma_s \Gamma_{in} - \Gamma_l S_{22} + \Gamma_s \Gamma_l S_{22} \Gamma_{in} + \Gamma_s \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} - \Gamma_s \Gamma_l S_{22} \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} - \Gamma_s \Gamma_l S_{21} S_{12} \right\|^2 \\ &= \left\| 1 - \Gamma_s \Gamma_{in} - \Gamma_l S_{22} + \Gamma_s \Gamma_l S_{22} \Gamma_{in} + \Gamma_s \Gamma_L S_{21} S_{12} \left( \frac{1}{1 - S_{22}\Gamma_L} - \frac{S_{22}\Gamma_L}{1 - S_{22}\Gamma_L} - 1 \right) \right\|^2 \\ &= \left\| 1 - \Gamma_s \Gamma_{in} - \Gamma_l S_{22} + \Gamma_s \Gamma_l S_{22} \Gamma_{in} \right\|^2 = \left\| (1 - \Gamma_s \Gamma_{in})(1 - \Gamma_l S_{22}) \right\|^2 \\ &= \left\| 1 - \Gamma_s \Gamma_{in} \right\|^2 \cdot \left\| 1 - \Gamma_l S_{22} \right\|^2 \quad \dots \text{tedious, but not hard.} \end{aligned}$$



# Transducer Power Gain

Therefore

$$G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_{in}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22}\Gamma_L\|^2}$$

$$\text{where } \Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L}$$

By a similar substitution

$$G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - S_{11}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_{out}\Gamma_L\|^2}$$

$$\text{where } \Gamma_{out} = S_{22} + \Gamma_S \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_S}$$

Look carefully at these expressions :

the input - output bilateral interaction is hidden in either the  $\Gamma_{in}$  or  $\Gamma_{out}$  terms.

We will use these to derive various power gains.

# Operating Power Gain: Gain with Input Matched

$$G_p = \frac{P_{load}}{P_{in}} \xrightarrow{\text{iff } P_{in}=P_{AVG}} \frac{P_{load}}{P_{AVG}} = G_T$$

$$P_{in} = P_{AVG} \text{ implies } \Gamma_s = \Gamma_{in}^*$$

$$\text{Since } G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_{in} \Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22} \Gamma_L\|^2}$$

$$G_P = \frac{1 - \|\Gamma_{in}^*\|^2}{\|1 - \Gamma_{in} \Gamma_{in}^*\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22} \Gamma_L\|^2}$$

$$G_P = \frac{1}{1 - \|\Gamma_{in}\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22} \Gamma_L\|^2}$$

$$\text{where } \Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21} S_{12}}{1 - S_{22} \Gamma_L}$$

$G_p$  is used to examine the variation in transistor gain as we vary the output match.

$G_p$  is computed with the input matched.

# Available Power Gain: Gain with Output Matched

$$G_A = \frac{P_{AVA}}{P_{AVG}} \xrightarrow{\text{iff } P_{AVA}=P_{load}} \frac{P_{load}}{P_{AVG}} = G_T$$

$$P_{AVA} = P_{load} \text{ implies } \Gamma_L = \Gamma_{out}^*$$

$$\text{Since } G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - S_{11}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_{out}\Gamma_L\|^2}$$

$$G_A = \frac{1 - \|\Gamma_s\|^2}{\|1 - S_{11}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_{out}^*\|^2}{\|1 - \Gamma_{out}\Gamma_{out}^*\|^2}$$

$$G_A = \frac{1 - \|\Gamma_s\|^2}{\|1 - S_{11}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1}{1 - \|\Gamma_{out}^*\|^2}$$

$$\text{where } \Gamma_{out} = S_{22} + \Gamma_s \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_s}$$

$G_A$  is used to examine the variation in transistor gain as we vary the input match.

$G_A$  is computed with the output matched.

# How About Maximum Available Gain ?

$$G_{\max} = \frac{P_{AVA}}{P_{in}} \xrightarrow{\text{iff } P_{AVA}=P_{load} \text{ and } P_{in}=P_{AVG}} \frac{P_{load}}{P_{AVG}} = G_T$$

we now need  $\Gamma_L = \Gamma_{out}^*$  and  $\Gamma_s = \Gamma_{in}^*$

we must simultaneously solve

$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} = \Gamma_s^* \text{ and } \Gamma_{out} = S_{22} + \Gamma_s \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_s} = \Gamma_L^*$$

and then substitute into

$$G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_{in}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22}\Gamma_L\|^2}$$

This is, at a minimum, mathematically tedious.

Worse, there may be no solution...

...more on this later.

# **Unilateral Amplifier Design**

# Unilateral Amplifier Design

---

We will now consider the various gain relationships under the simplifying case of  $S_{12} = 0$ .

We do this to develop better our understanding of these gains.

The unilateral expressions are not to be used for real amplifier design, or real transistor gain calculations.

Warning : the expressions are gains for a device which happens to \* be \* unilateral, not the gain of a bilateral device after we provide feedback to \* make it \* unilateral. The latter quantity is Mason's invariant, the unilateral gain, and is described elsewhere.

# Unilateral Amplifier Design

Suppose we have a device with  $S_{12} = 0$ .

$$G_T = \frac{\|S_{21}\|^2 \cdot [1 - \|\Gamma_{load}\|^2] \cdot [1 - \|\Gamma_s\|^2]}{\|(1 - \Gamma_s S_{11})(1 - \Gamma_l S_{22}) - \Gamma_s \Gamma_l S_{21} S_{12}\|^2} \Rightarrow \frac{[ ] \cdot [1 - \|\Gamma_s\|^2]}{\|(1 - \Gamma_s S_{11})(1 - \Gamma_l S_{22})\|^2}$$

$$G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_s S_{11}\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_L S_{22}\|^2}$$

Simple and easy to recognize!

$$G_T = G_S \cdot \|S_{21}\|^2 \cdot G_L \quad \text{where } G_S = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_s S_{11}\|^2} \quad \text{and} \quad G_L = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_L S_{22}\|^2}$$



$G_S$  is the fraction of gain lost/gained due to input mismatch/match

$G_L$  is the fraction of gain lost/gained due to output mismatch/match

# Power Wasted Due to Mismatch

Recollect the power relationships for a generator

$$P_{load} = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot \|b_s\|^2 = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_S \Gamma_L\|^2} \cdot P_{Z_0}$$

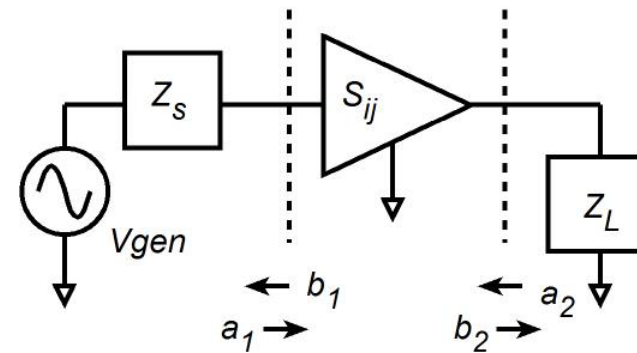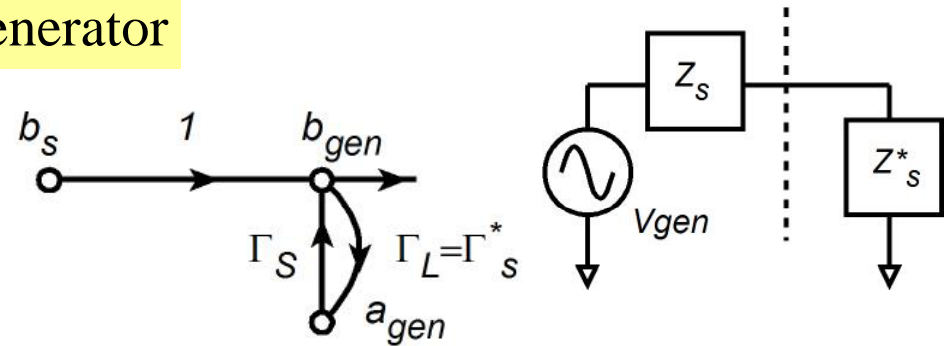

Recognize the same terms in

$$G_T = G_S \cdot \|S_{21}\|^2 \cdot G_L \quad \text{where} \quad G_S = \frac{1 - \|\Gamma_S\|^2}{\|1 - \Gamma_S S_{11}\|^2} \quad \text{and} \quad G_L = \frac{1 - \|\Gamma_L\|^2}{\|1 - \Gamma_L S_{22}\|^2}$$

Given that  $S_{12}S_{21} = 0$ ,  $S_{11}$  and  $S_{22}$  are the input and output reflection coefficients.


Hence  $G_S$  and  $G_L$  just represent impedance mismatch terms at input and output.



# Maximum Power Transfer, Maximum Available Gain

Recollect the power relationships for a generator


$$P_{AVG} = \frac{\|b_s\|^2}{1 - \|\Gamma_s\|^2} = \frac{P_{Z_0}}{1 - \|\Gamma_s\|^2}$$

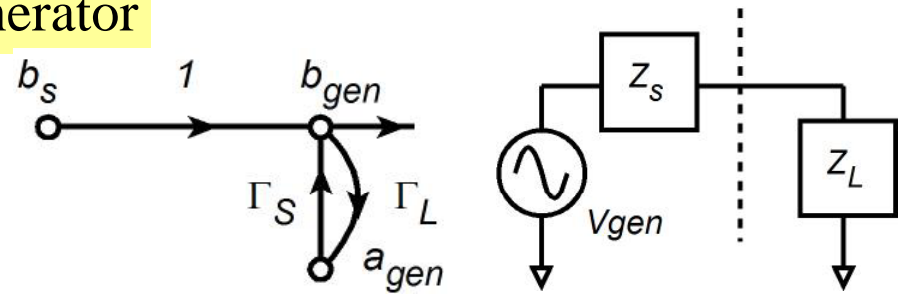

We must now match on input and output:  $\Gamma_s = S_{11}^*$  and  $\Gamma_L = S_{22}^*$

Recognize the same terms in

$$G_{\max} = \frac{1}{1 - \|S_{11}\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1}{1 - \|S_{22}\|^2}$$

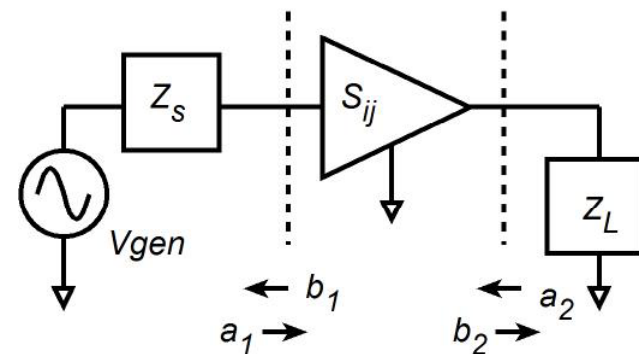

Can we make sense of this expression ?

# Impedance matching = Recycling the Reflections !


Suppose we have an amplifier with  $S_{11} = 0.5 + j0$ .

Given a  $50\Omega$  generator, 25% of the available input power is reflected and lost.

If we could recycle this power,

the input power would be increased in proportion to  $\frac{1}{1-0.25}$

which is to say, in proportion to  $\frac{1}{1-\|\Gamma_{in}\|^2}$ .

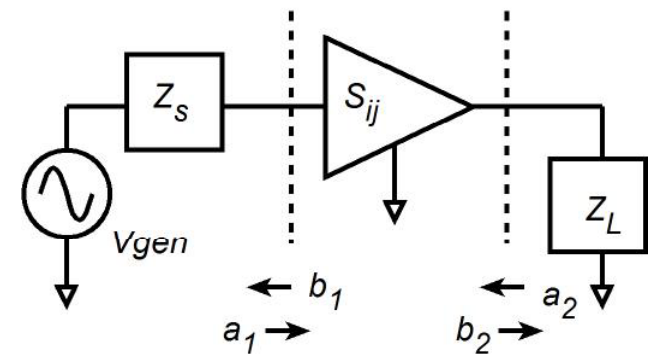

Impedance - matching recycles the reflected power.