

ECE 202A

Nov. 8, 1989

①

General Comments about (unilateral)
Matched amplifier design.

If unilateral

$$G_T = \frac{P_{load}}{P_{avs}} = G_S |S_{21}|^2 G_L$$


$$= \frac{1 - |I_S|^2}{|1 - S_{11} I_S|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - S_{22} I_L|^2}$$

$$G_{MAX} = \left(\frac{1}{1 - |S_{11}|^2} \right) |S_{21}|^2 \left(\frac{1}{1 - |S_{22}|^2} \right)$$

⇒ Concept of Matching on input & output to attain G_{max} .

Lets look @ G_{max} for a highly simplified device

Model:

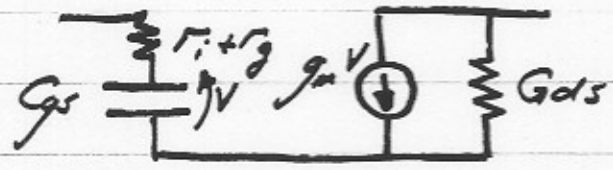


(no r_s , no C_{gd})

This is the simplest model for a FET to have non-infinite F_{max} .

$$G_{max} = \frac{P_{AVA}}{P_{in}} = \frac{P_{load}}{P_{in}} \quad \text{if output is matched}$$

available output power

power absorbed in input

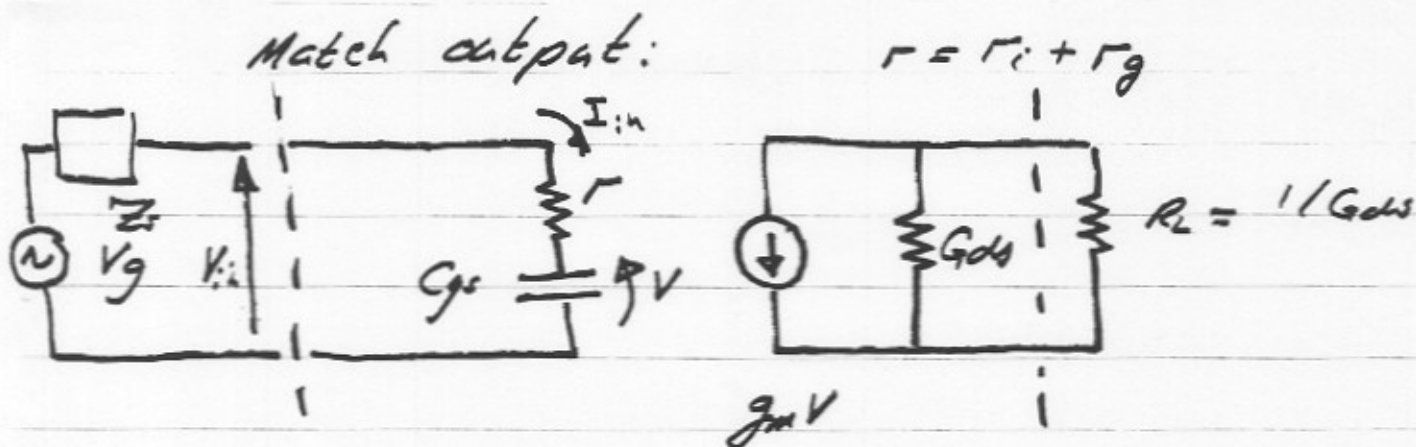

$$P_{load} = \left((g_m V) \times \frac{1}{2} \right)^2 R_L = \frac{g_m^2}{4 G_{ds}} \cdot |V|^2$$

$$P_{in} = |I_{in}|^2 r$$

$$\text{But } |V|^2 = |I|^2 / \omega^2 C_{gs}^2$$


$$\Rightarrow \frac{P_{load}}{P_{in}} = \frac{P_{AVA}}{P_{iL}} = G_{MAX} = \frac{g_m^2}{4 G_{ds}} \frac{1}{\omega^2 C_{gs}^2} \frac{1}{r}$$

(4)

$$G_{\max} = \frac{g_m^2 / \omega^2 C_{gs}^2}{4 G_{ds}(\tau_i + \tau_g)} = \frac{g_m^2 / (2\pi f)^2 C_{gs}^2}{4 G_{ds}(\tau_i + \tau_g)}$$

but $f_T = g_m / 2\pi C_{gs}$
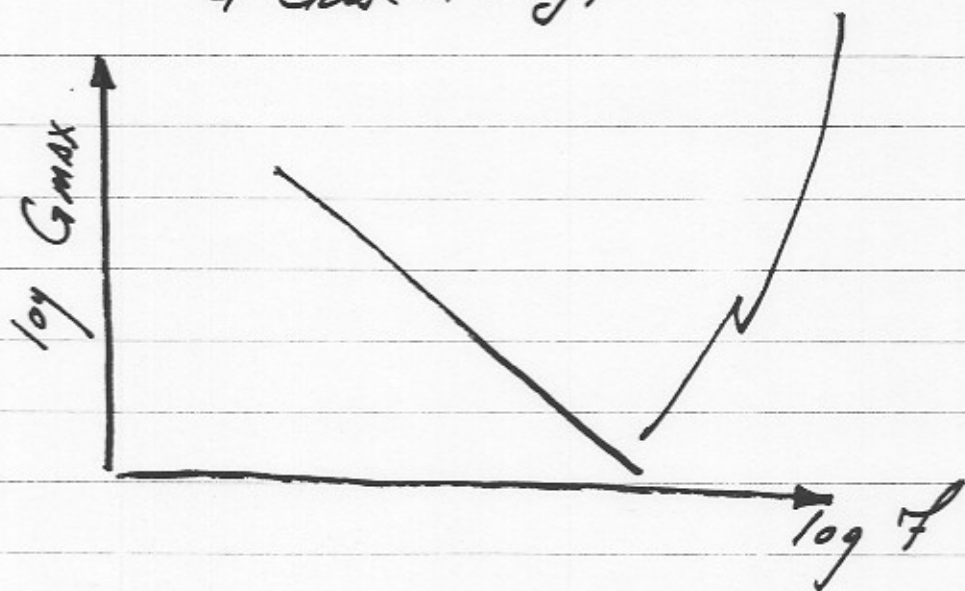
$$G_{\max} = \frac{f_T^2 / f^2}{4 G_{ds}(\tau_i + \tau_g)} = 1 \text{ when } f = \frac{f_T}{2\sqrt{G_{ds}(\tau_i + \tau_g)}}$$



so $G_{\max} = \frac{f_{\max}^2}{f^2}$ where $f_{\max} = \frac{f_T}{2\sqrt{G_{ds}(\tau_i + \tau_g)}}$

This in general can be carried out (with much more pain) for the more complete device models:

Recall

FET:

$$f_{max} \approx \frac{f_T}{2\sqrt{(r_g + r_s + r_i) G_{ds} + 2\pi f_T r_g C_{gd}'}}$$

BJT:


$$f_{max} \approx \frac{f_T}{2\sqrt{(r_e + r_{b'b}) / \beta_{ce} + 2\pi f_T r_{b'b} C_{bc}'}}$$

$$\approx \sqrt{\frac{f_T}{8\pi r_{b'b} C_{bc}'}}$$

Again, be aware that these are only approximate expressions based on "typical" parameters.

If you put the device model into Touchstone, it will plot G_{MAX}

so, with our unilateral device model :

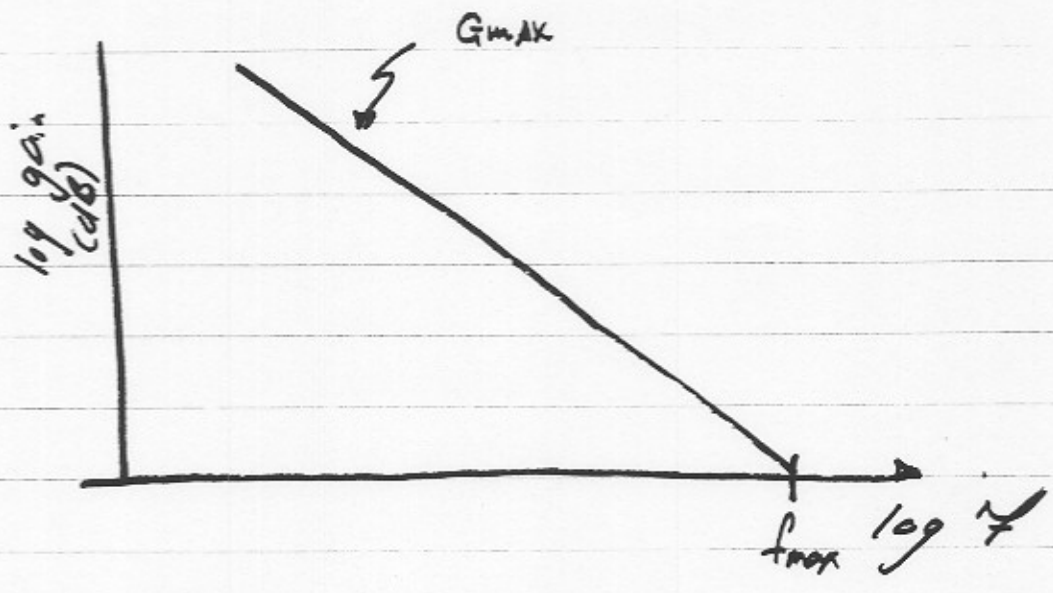


$$G_T = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$G_T = G_{MAX} \cdot \frac{(1 - |S_{11}|^2)(1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2} \cdot \frac{(1 - |S_{22}|^2)(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2}$$

$$= G_{MAX} \text{ if SWR } \Gamma_S = \Gamma_{in}^* \\ \Gamma_L = \Gamma_{out}^*$$

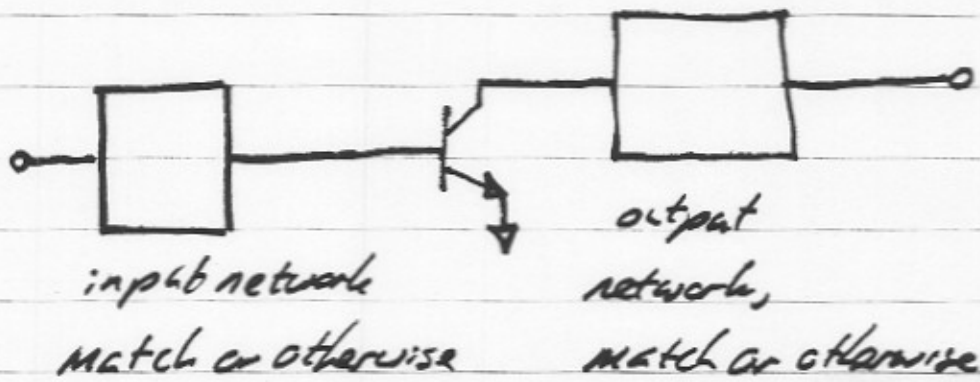So: picture of amplifier circuit of any type, but no feedback.




overall power gain must be $\leq G_{MAX}$

is equal to G_{MAX} iff input & output are matched

using lossless matching networks.

Why not lossy networks?

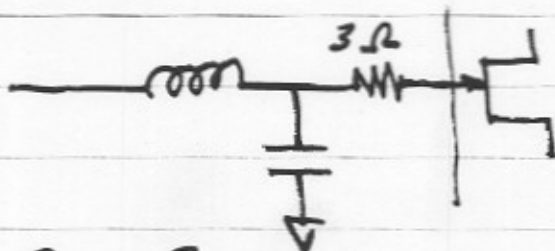


$G < G_{MAX}$ because $P_{in\ device} = P_{gen} - P_{resistor} < P_{generator}$.


So, amplifiers fail to attain G_{MAX} because:

- 1) They fail to match on both input & output
- 2) They use lossy elements (resistors) to attain a match.

or both.


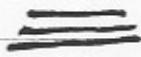


ex: matched amplifier

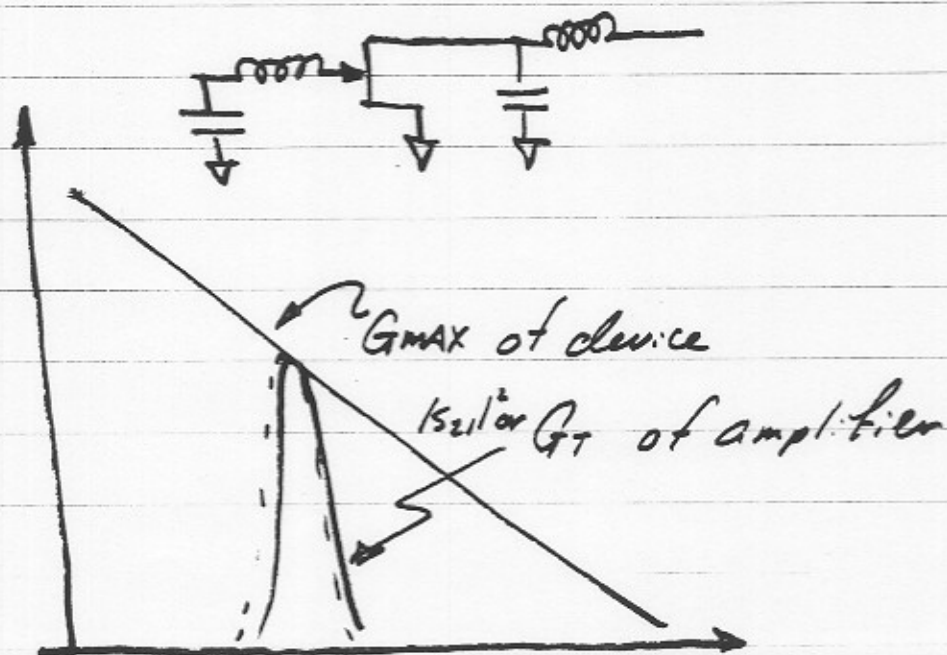

This is desirable for a tuned system (radio receiver, etc)

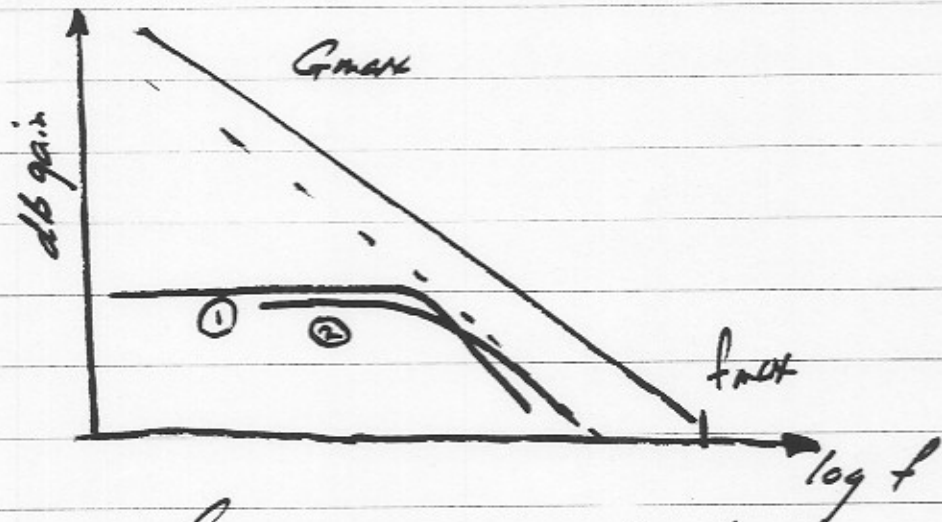
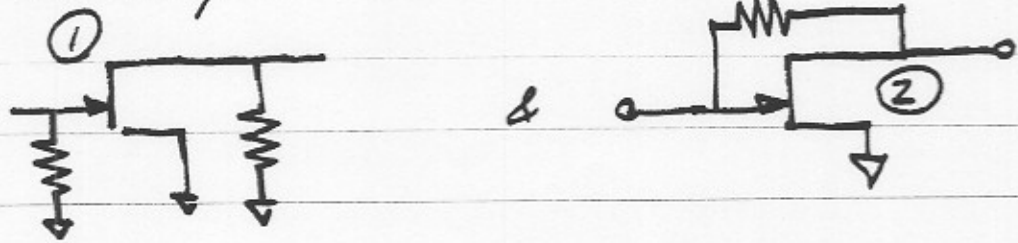
ex: resistively-terminated and feedback amplifiers.



The gain-frequency curve clearly has to lie under the G_{MAX} curve. In fact, the gain-frequency curve may be constrained well below this by the $(f_T/f)^2$ line, or even lower.

⇒ Flat gain, but at the expense of performance far below the fundamental limit (G_{MAX}) of the device.

Ex: Travelling-wave Amp

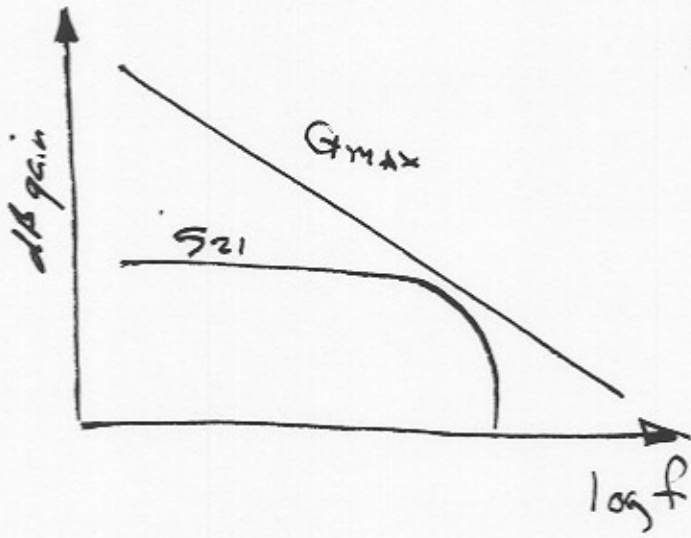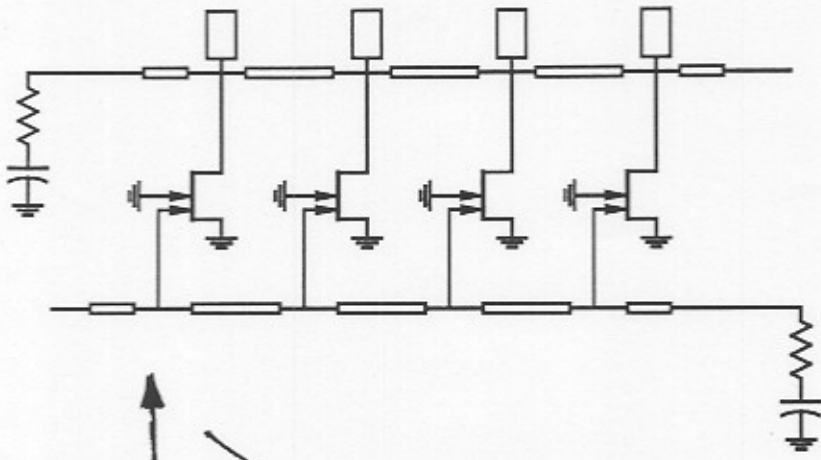

so a general question is "how well are we using the available power gain of the device?"

Real-world issues:

Cost - related to die area. Here the TWA, "optimum" in one sense, is really lousy. Eats die area. F.B. Amps win due to small area.

Parameter sensitivity: Here TWA's & F.B. Amps do well, but Tuned amps (i.e. "optimum") do badly.

Stability The engineer's nightmare. Need to watch with all designs. F.B. amp probably best.

Noise Performance, Power output: Very important, but discuss later.

also Power supplies, power consumption