
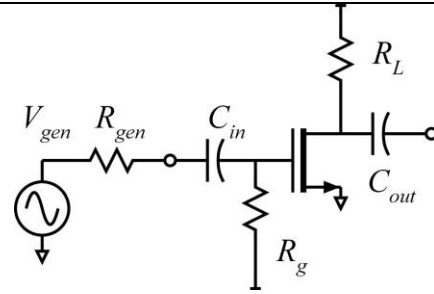


ECE 145b problem set (noise)

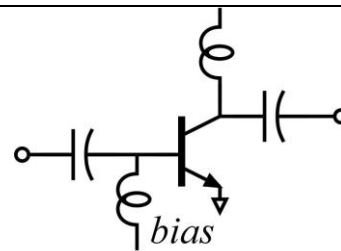Problem 1: Microphone preamplifier. The microphone generates 1 mV, RMS, from a voice signal which is uniformly distributed in frequency over 400 Hz-4 kHz. $R_{gen}=600$ Ohms, $R_g=100$ MOhm (treat as infinite), $R_L=10$ kOhm. The FET has zero parasitic capacitances, infinite R_{ds} , and zero parasitic resistances R_g , R_s , R_d , and R_i . The blocking capacitors are infinite. The FET channel noise parameter is $\Gamma=1.0$, and $g_m=5$ mS. (a) Find the total input referred noise voltage and (b) find the system signal/noise ratio over the 400 Hz-4 kHz bandwidth.




Problem 2: The bipolar Transistor has $\beta=200$ and $R_{bb}=50$ Ohms. All other parasitic elements are zero. It is biased at 1mA collector current. The L's and C's shown here are bias T elements, and are infinite. Find (a) the spectral densities of the input referred noise voltage and current generators E_n and I_n , and their cross spectral density, (b) The total amplifier input noise voltage given a 500 Ohm generator (c) the noise figure given a 500 Ohm generator and (d) the minimum noise figure and optimum generator impedance.




ECE 218B problem set (noise)

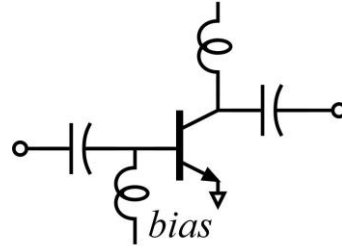
Problem 1: The bipolar Transistor has $\beta=200$ and $R_{bb}=50$ Ohms. All other parasitic elements are zero. It is biased at 1mA collector current. The L's and C's shown here are bias T elements, and are infinite. find (a) the spectral densities of the input referred noise voltage and current generators E_n and I_n , and their cross spectral density, (b) The total amplifier input noise voltage given a 500 Ohm generator (c) the noise figure given a 500 Ohm generator and (d) the minimum noise figure and optimum generator impedance.



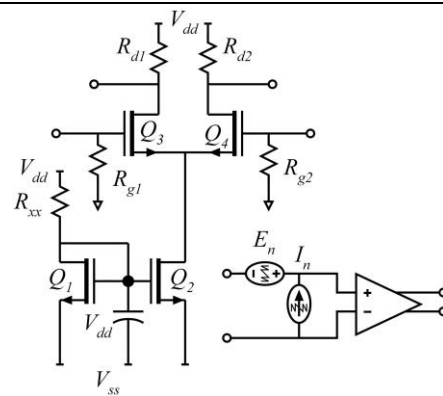
Problem 2: Differential amplifier. The FETs have zero parasitic capacitances, infinite R_{ds} , and zero parasitic resistances R_g , R_s , R_d , and R_i . Assume square-law models for the FETs with $I_d = K_1 \cdot (V_{gs} - V_{th})^2$, with $K_1 = (1\text{mA/V}^2)$, with a 0.3 V threshold. Assume power supplies of ± 2 Volts, and $R_{g1}=R_{g2}=1$ MegOhm. Q_3 and Q_4 are to be biased with 200 microamps drain current, and the DC voltage drops across R_{d1} and R_{d2} are each 0.5 Volts. The current mirror bypass capacitor is infinite. (a) Find all component values and DC bias voltages and currents. (b) find the small signal differential voltage gain. (c) Assuming a FET channel noise parameter $\Gamma = 0.75$, find the spectral densities of E_n and I_n . (d) If the generator impedances for V_+ and V_- , the two input signal generators, are each 10 kOhm, find the total input-referred noise voltage spectral density, and the RMS noise voltage in a DC-1MHz bandwidth. (e) Find the noise spectral density of the drain current of Q_2



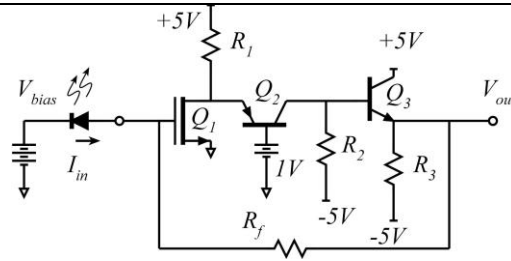Problem 4: This is a transimpedance optical preamp. V_{out} is at zero volts. Q_2 and Q_3 have infinite β . Q_1 -3 have zero parasitic resistances and capacitances. Q_3 is biased at 10 mA, Q_2 at 5 mA, Q_1 at 5 mA; this will allow you to find the resistor values. Q_1 has 20 mS transconductance and $\Gamma=1$. R_f is 10kOhm. Find the input-referred noise current.



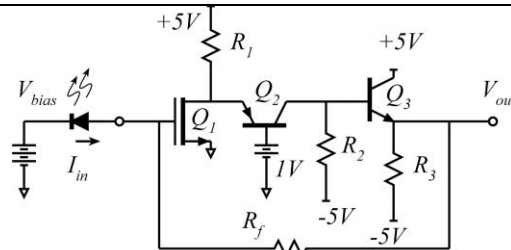Problem 5: With the same parameters as problem 4, now ignore the noise sources of R_1 , R_2 , R_3 , Q_2 , and Q_3 , so that you are only considering the noise of Q_1 and R_f . The FET has infinite R_{ds} , and zero parasitic resistances R_g , R_s , R_d , and R_i . The FET has $C_{gd}=C_{ds}=0\text{fF}$, however C_{gs} is nonzero and is determined from $f_{\tau} = g_m/2\pi C_{gs}=100$ GHz. Find the input-referred noise current spectral density



as a function of frequency. This is a classic optical receiver sensitivity calculation.
