

# ECE 145C / 218C, notes set xx: Automatic Gain Control (very quick summary)

***Mark Rodwell***

***Doluca Family chair***

***University of California, Santa Barbara***

rodwell@ece.ucsb.edu


# Power detectors & peak detectors

Square-wave drive (easy analysis)

$$\exp\left(\frac{V_{out}}{nkT/q}\right) = \left( \exp\left(\frac{V_{pp}}{2nkT/q}\right) + \exp\left(\frac{-V_{pp}}{2nkT/q}\right) \right)^{-1}$$

$$V_{out} \approx \begin{cases} -\left(\frac{V_{pp}}{2} - \frac{nkT}{q} \ln(2)\right) \text{ (peak detection)} & \text{if } V_{pp} \gg \frac{nkT}{q} \\ -\frac{V_{pp}^2}{2nkT/q} \text{ (power detection)} & \text{if } V_{pp} \ll \frac{nkT}{q} \end{cases}$$

This will be derived in lecture

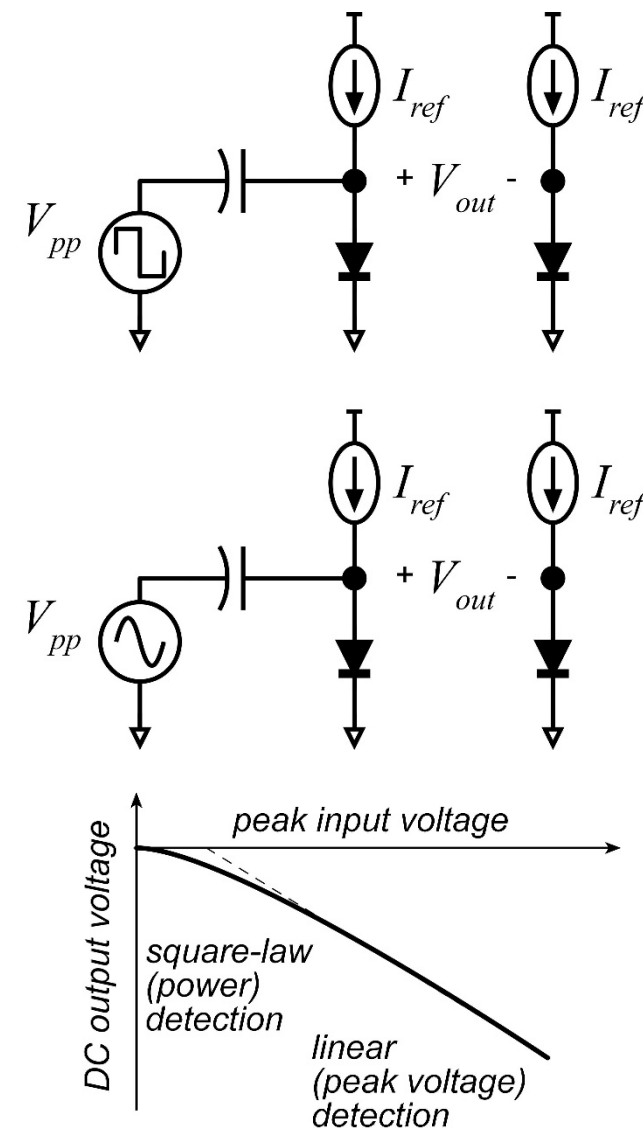


# Power detectors & peak detectors

Sinusoidal drive (more difficult analysis)

$$V_{out} \approx -\frac{V_{peak}^2}{4nkT/q} \text{ (power detection) if } V_{pp} \ll \frac{nkT}{q}$$

this will again be derived in lecture

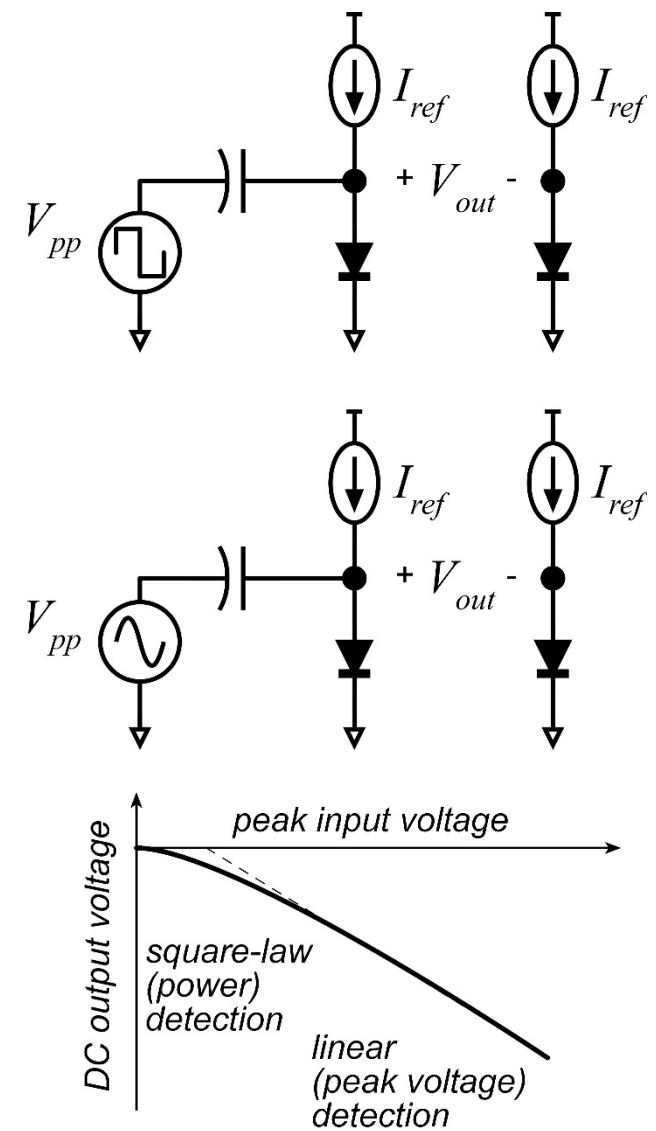

# AGC detector, set point, and AGC loop amplifier

$$I_{REF1} / I_{REF2} = R_2 / R_1$$

So, if  $V_{pp} = 0$  V,

$$V_{DET} = \frac{nkT}{q} \ln(R_2 / R_1)$$

Given sinusoidal drive with  $V_{pp} \ll nkT / q$

$$V_{DET} \approx \frac{nkT}{q} \ln(R_2 / R_1) - \frac{V_{peak}^2}{4nkT / q}$$


Loop stabilizes when  $V_{DET} = 0$  V, hence

$$V_{peak} = 2 \frac{nkT}{q} \sqrt{\ln(R_2 / R_1)}$$

Need  $R_1, R_2$ , and  $R_3$  all  $\gg nkT / qI_{REF}$

If needed, exchange the polarity of the connection to  $V_{DET}$

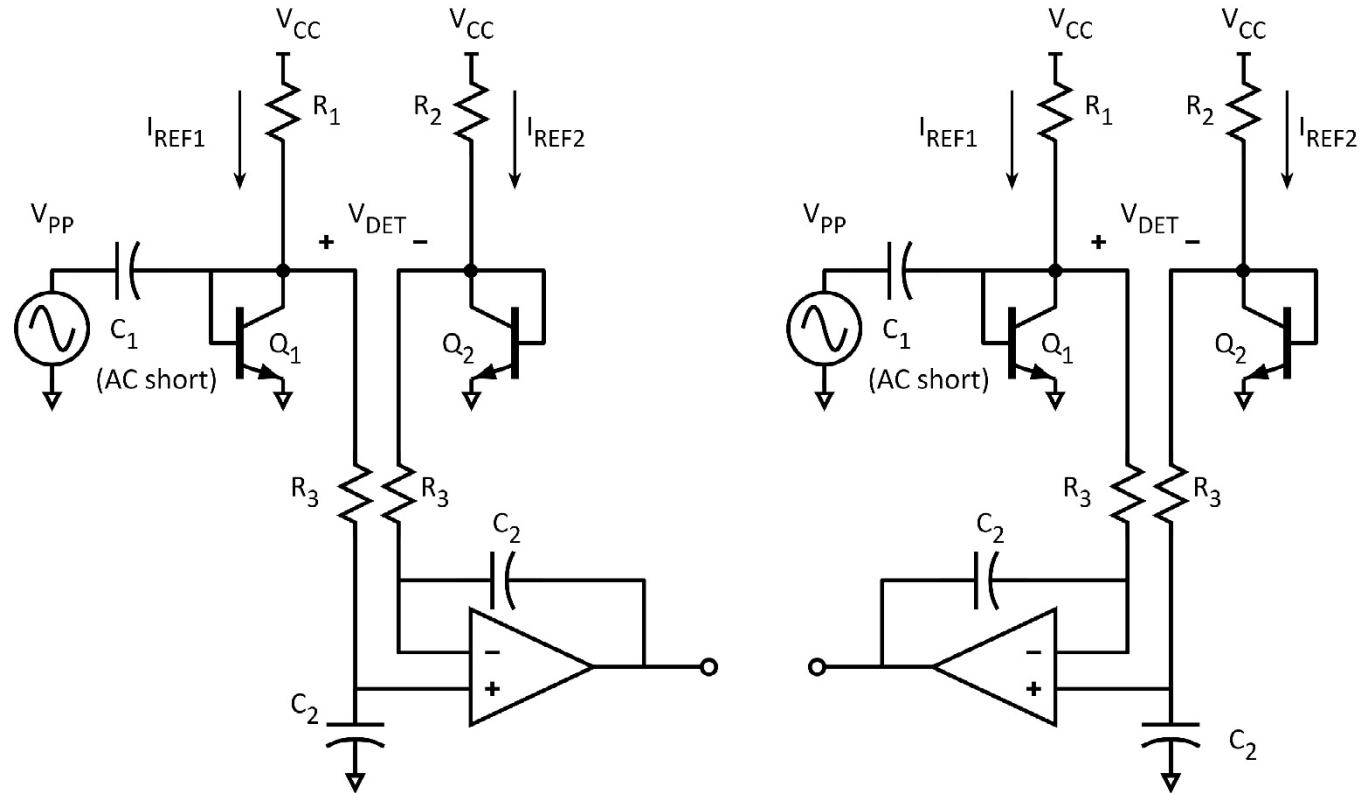to obtain the correct sign of AGC loop gain



# AGC detector, set point, and AGC loop amplifier

You can also set up an offset like so...

With  $V_{pp} = 0$  V,

$$V_{DET} = I_{REF} R_2$$

Given sinusoidal drive with  $V_{pp} \ll nkT / q$

$$V_{DET} \approx I_{REF} R_2 - \frac{V_{peak}^2}{4nkT / q}$$


Loop stabilizes when  $V_{DET} = 0$  V, hence

$$V_{peak}^2 = (I_{REF} R_2)(4nkT / q)$$

Need  $R_1, R_2$ , and  $R_3$  all  $\gg nkT / qI_{REF}$

If needed, exchange the polarity of the connection to  $V_{DET}$

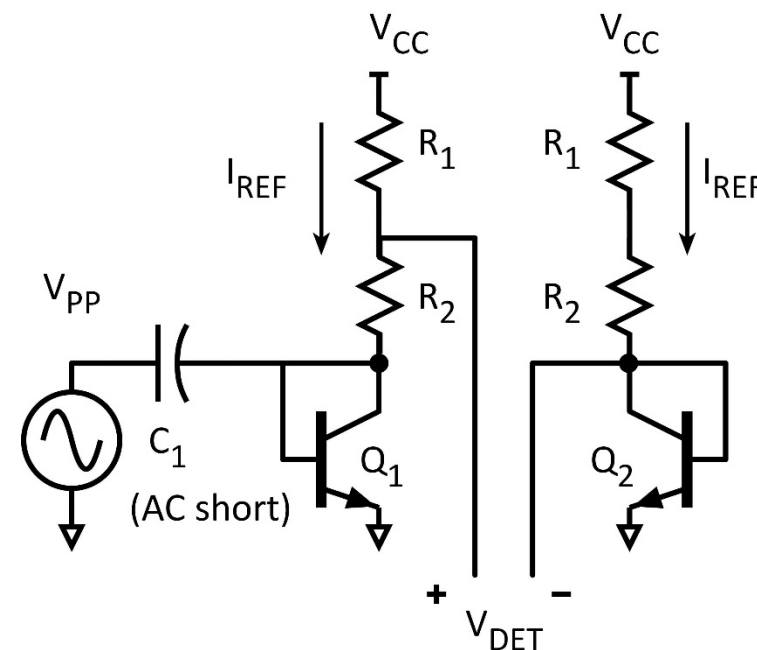to obtain the correct sign of AGC loop gain



# Mixer vs. variable-gain amplifier


## Mixer

$$V_{out} = \kappa V_{RF} V_{LO} \text{ for some constant } \kappa$$

For large positive  $V_{LO} : V_{out} = \kappa V_{RF}$

For large negative  $V_{LO} : V_{out} = -\kappa V_{RF}$

AGC loop will not function correctly

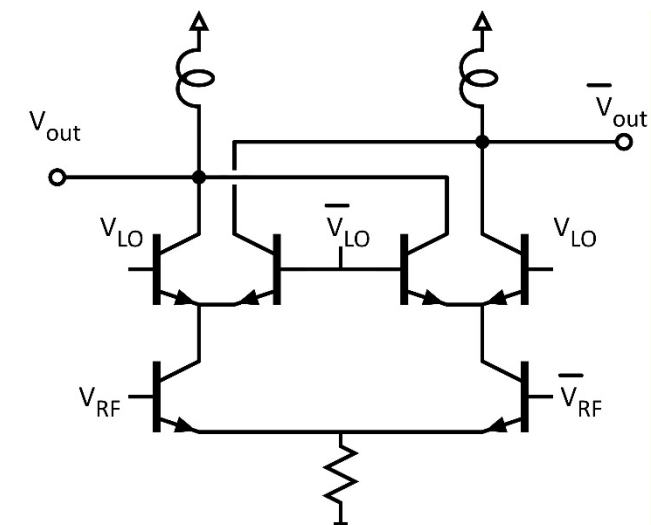


## Variable-gain amplifier

$$V_{out} = A_v V_{RF}$$

For large positive  $V_{AGC} : A_v$  is large

For large negative  $V_{AGC} : A_v$  is zero

AGC loop will function correctly

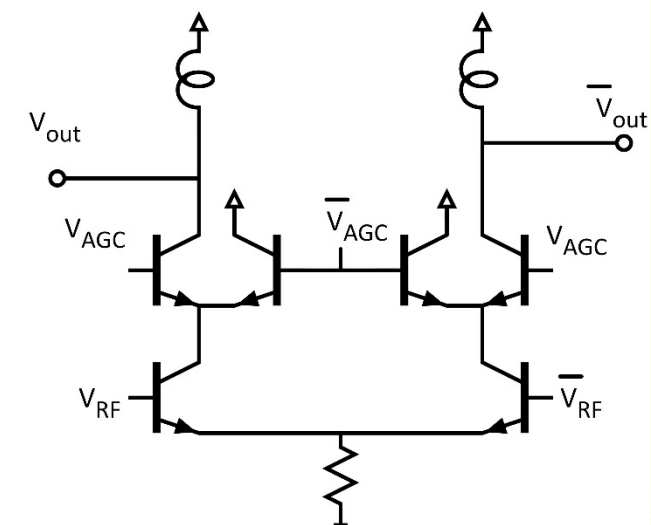


# Simpler variable-gain amplifiers

The top circuit is complex  
but has stable DC bias


The middle circuit is less complex  
but bias currents vary strongly with  $\beta$ .

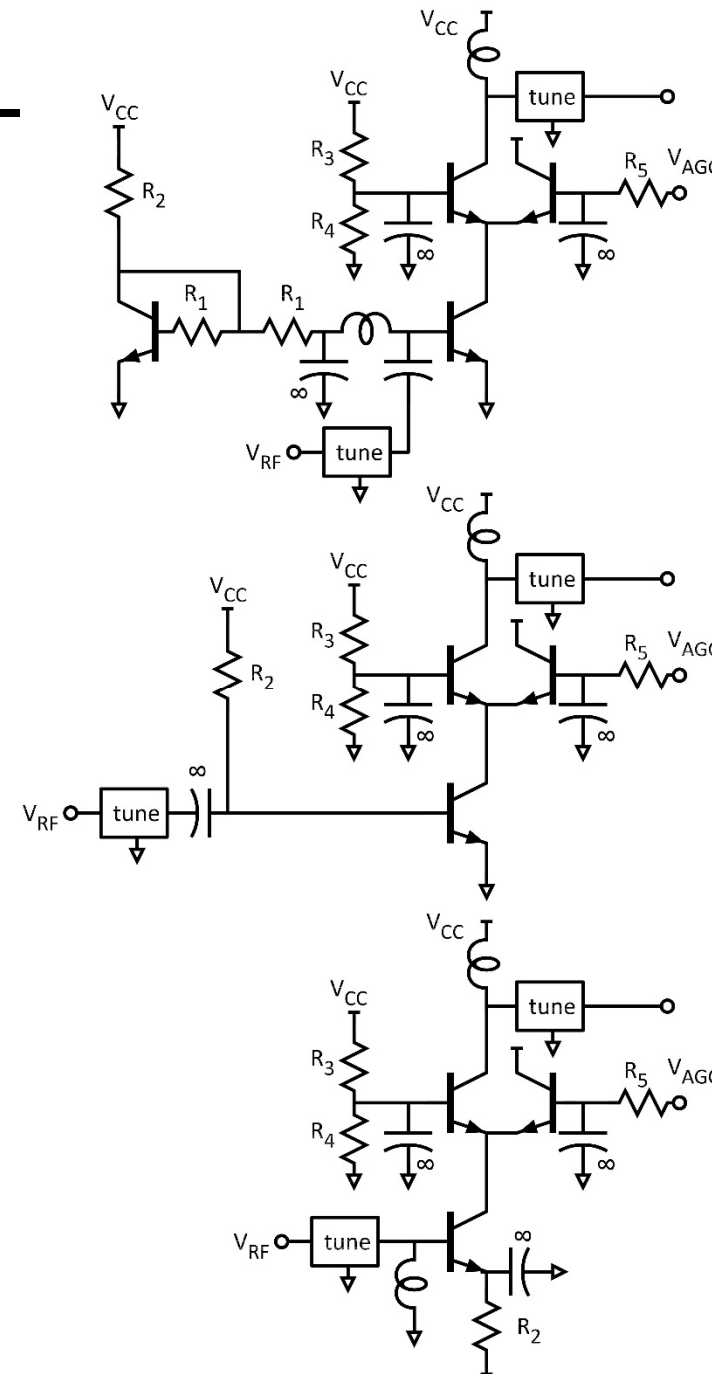The bottom circuit has stable DC bias,  
and has clean RF layout parasitics  
(with micro-X bjt packages),  
but requires + and - supplies.



# Simpler variable-gain amplifiers

Two more  
single-supply  
options...

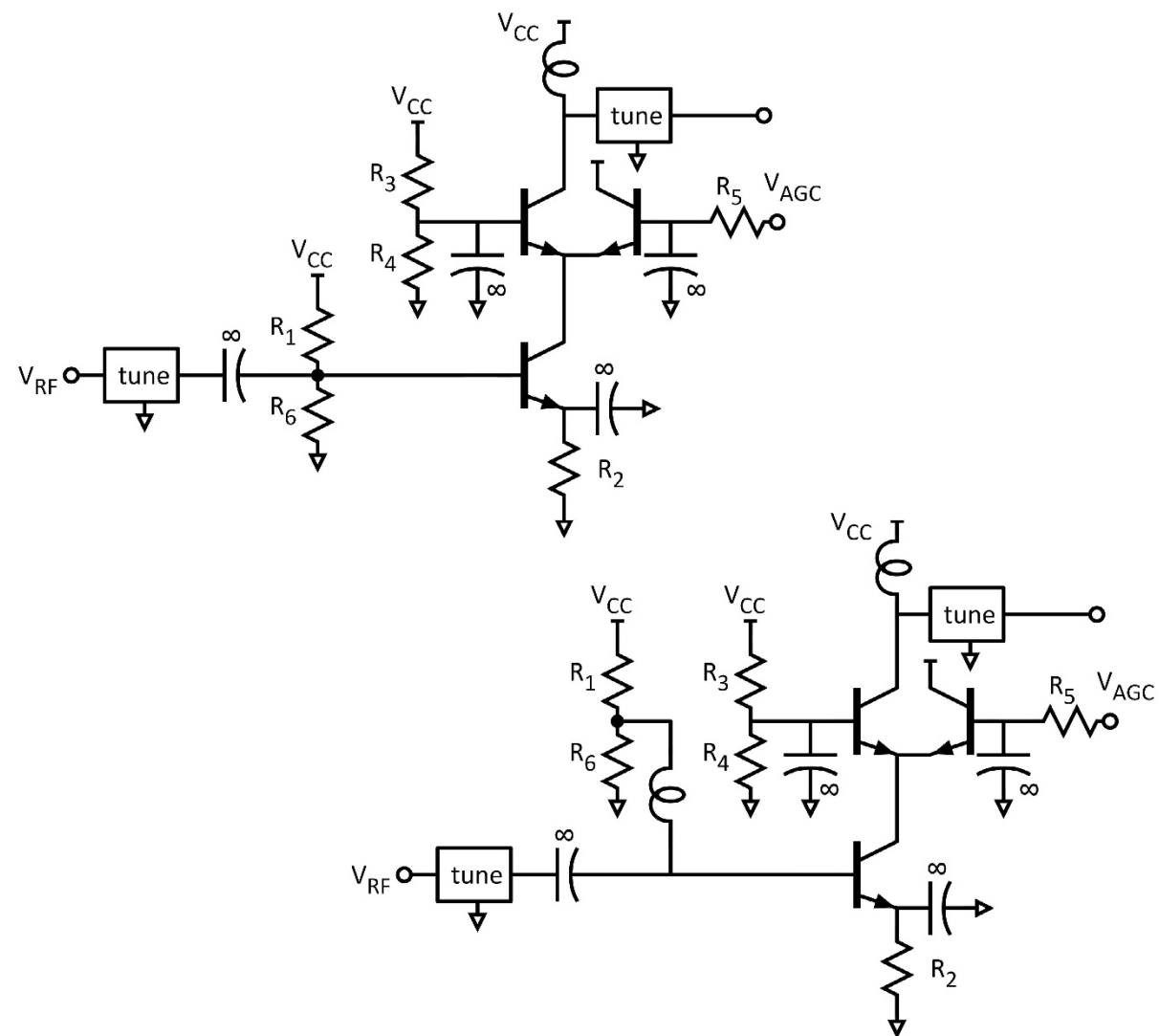



# Even simpler variable-gain amplifiers

This is a common-base stage  
with a variable-current shunt

By adding  $R_5$  and  $R_6$ , the input and  
output networks become  
lossy matching networks.

Lower gain, higher noise figure  
broader bandwidth  
easier matching network design

