

- **Notes Set 14: Circuit noise analysis methods**

- Method of transposition of sources. Many examples worked
- En-In model of FET. Noise figure circles. Strong discrepancy between impedance and noise-matching.

Circuit noise examples

Circuit noise Methods


First, an analytic technique which is very efficient for some noise problems.

... and very inefficient for others...

Rodwells (unpublished) method of transposition of sources

Rule:


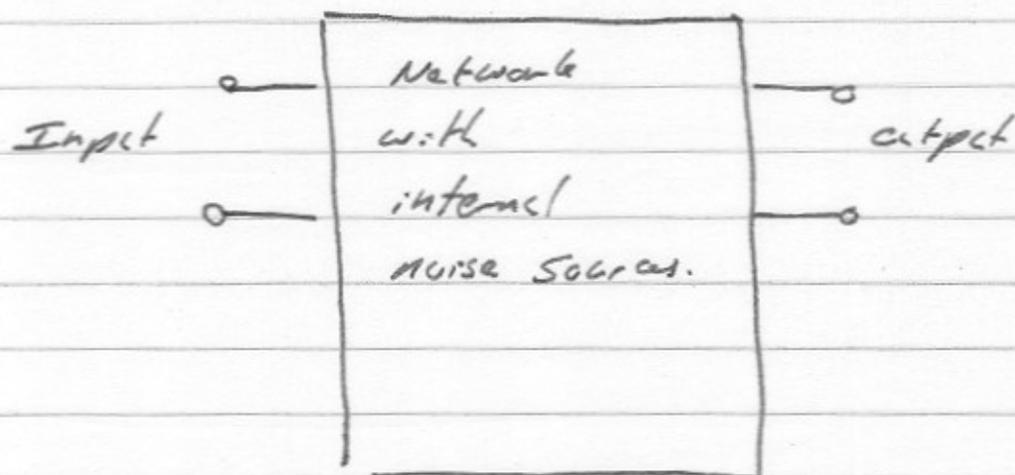
Separate problem into a generator (input) and an output, and an amplifier.



We desire to analyze the network to find the input-referred noise (voltage/current/power etc)


We can do this by a series of transformations to the internal network, transformations which may change many of the internal node voltages & branch currents, but which do not change the input or output node voltages or currents.

allowed transformations:

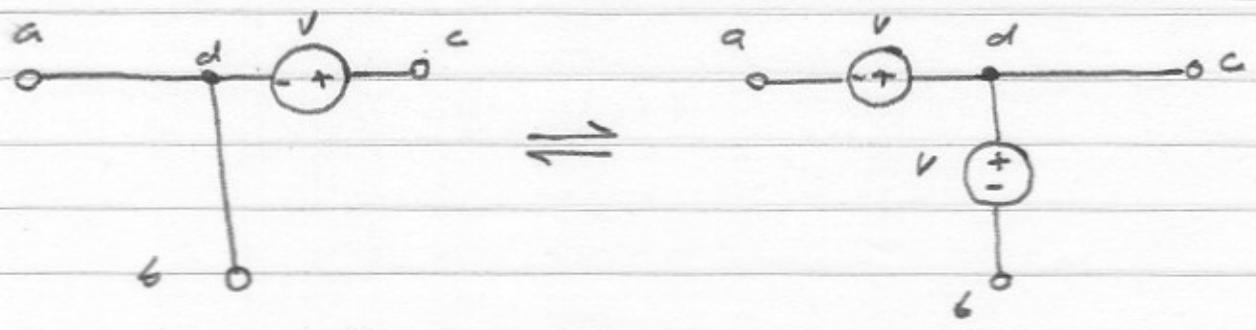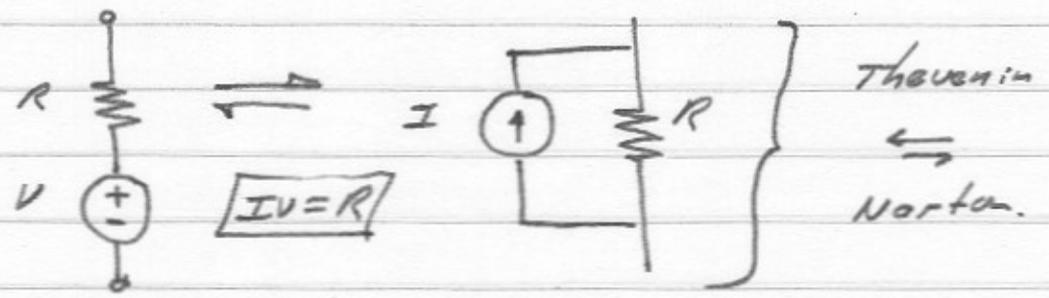



— pushing a voltage through a node —

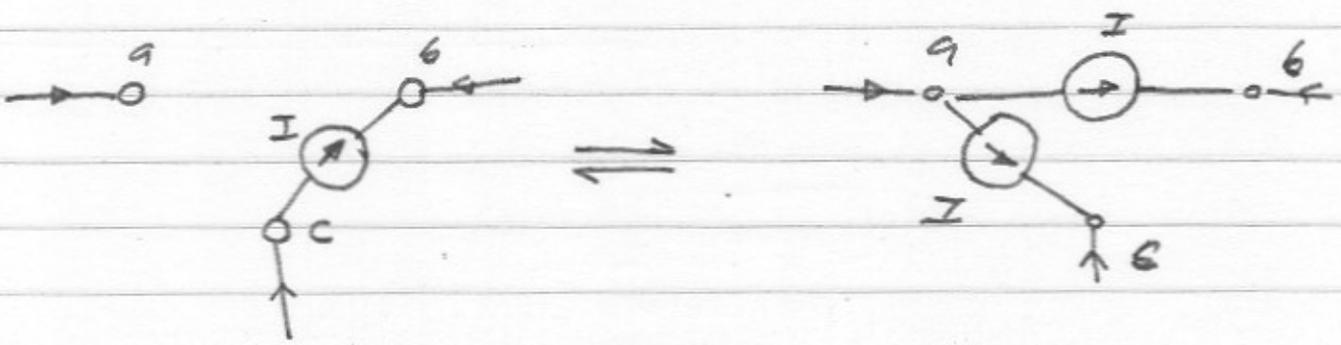only the node "d" voltage has changed; allowable unless "d" is the input or output node.



Pushing a current across a branch.

---

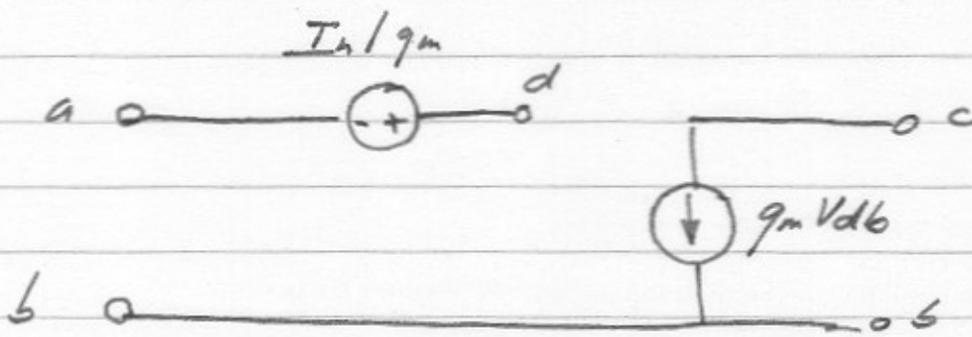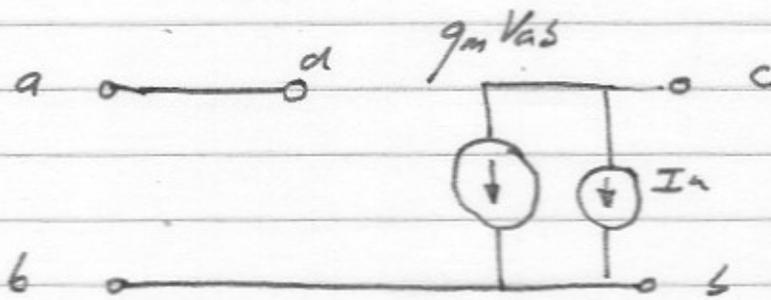


- Pushing a voltage through a transconductance -  
 Only the node "d" (a newly created node) voltage  
 has changed



---

There are other transformations, but they should now be obvious.

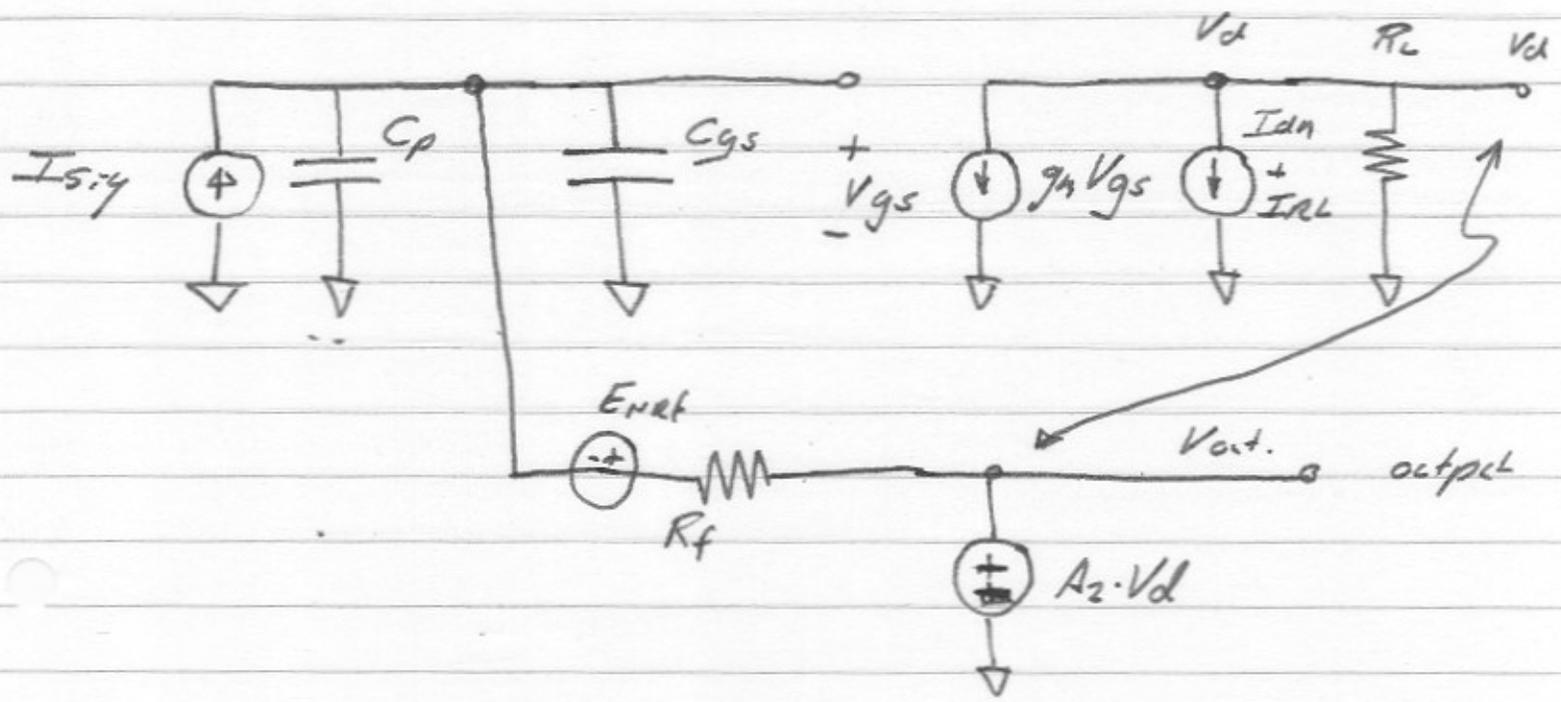Example (only 1 given; Method will appear repeatedly in circuit lectures)



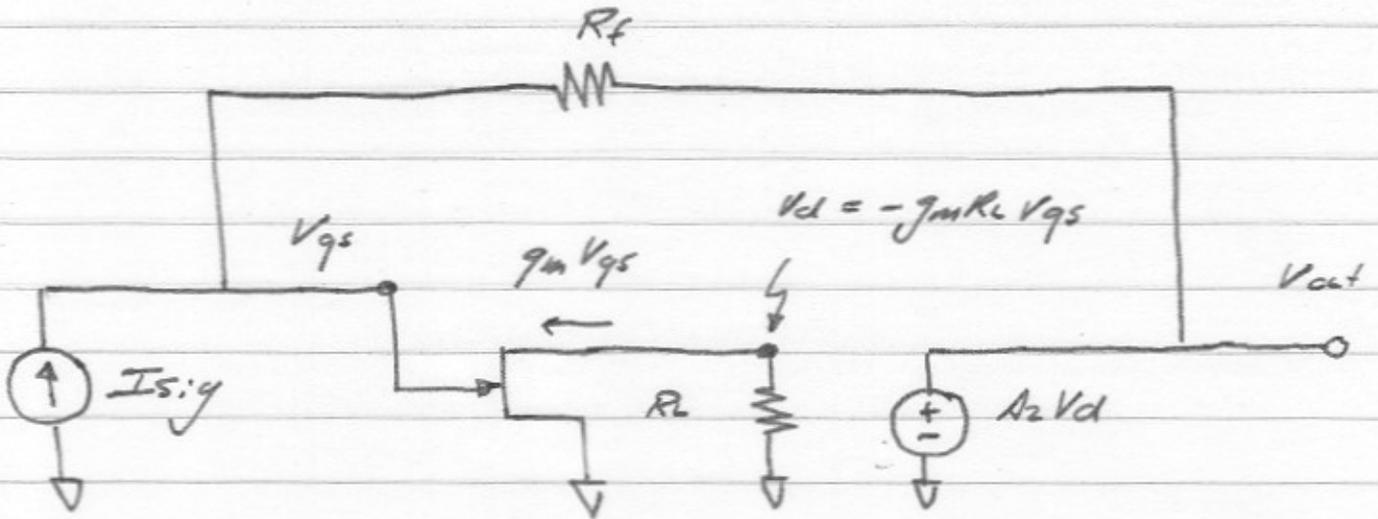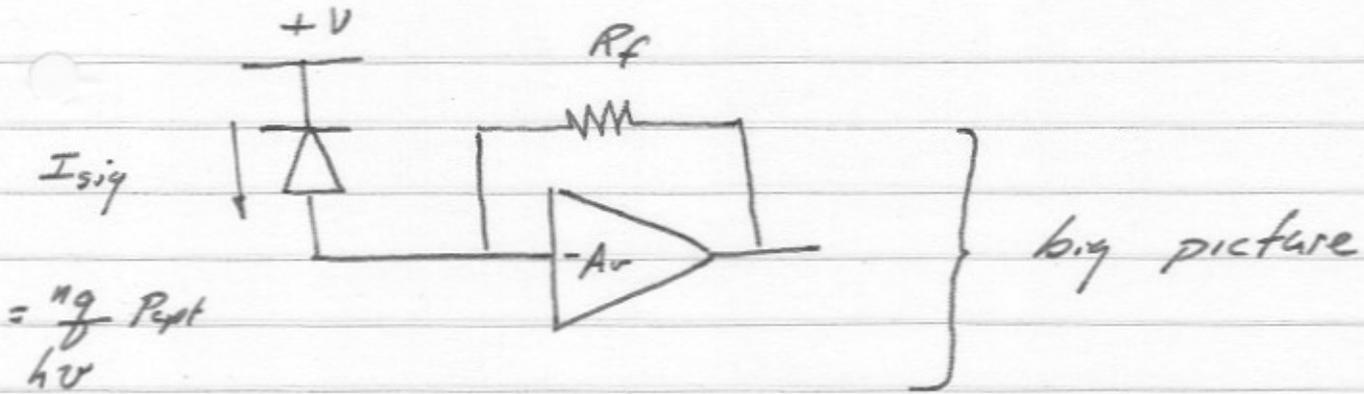
This is the model of a pin-fet optical receiver preamplifier.



amplifier 1<sup>st</sup> stage  
detailed model

amplifier 2<sup>nd</sup> stage  
highly idealized.


$$A_v = A_2 \cdot (g_m R_L)$$



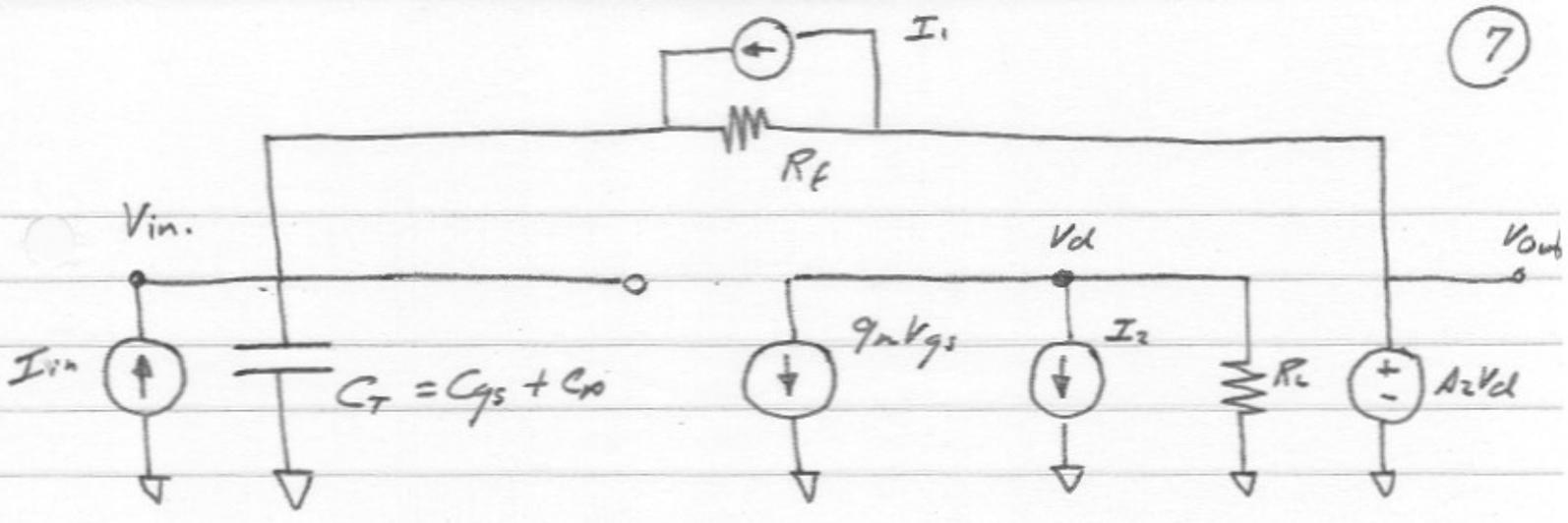


$I_1: S_{I_1 I_1} = 4kT/R_f$

$I_2: S_{I_2 I_2} = 4kT/g_m + 4kT/R_L$

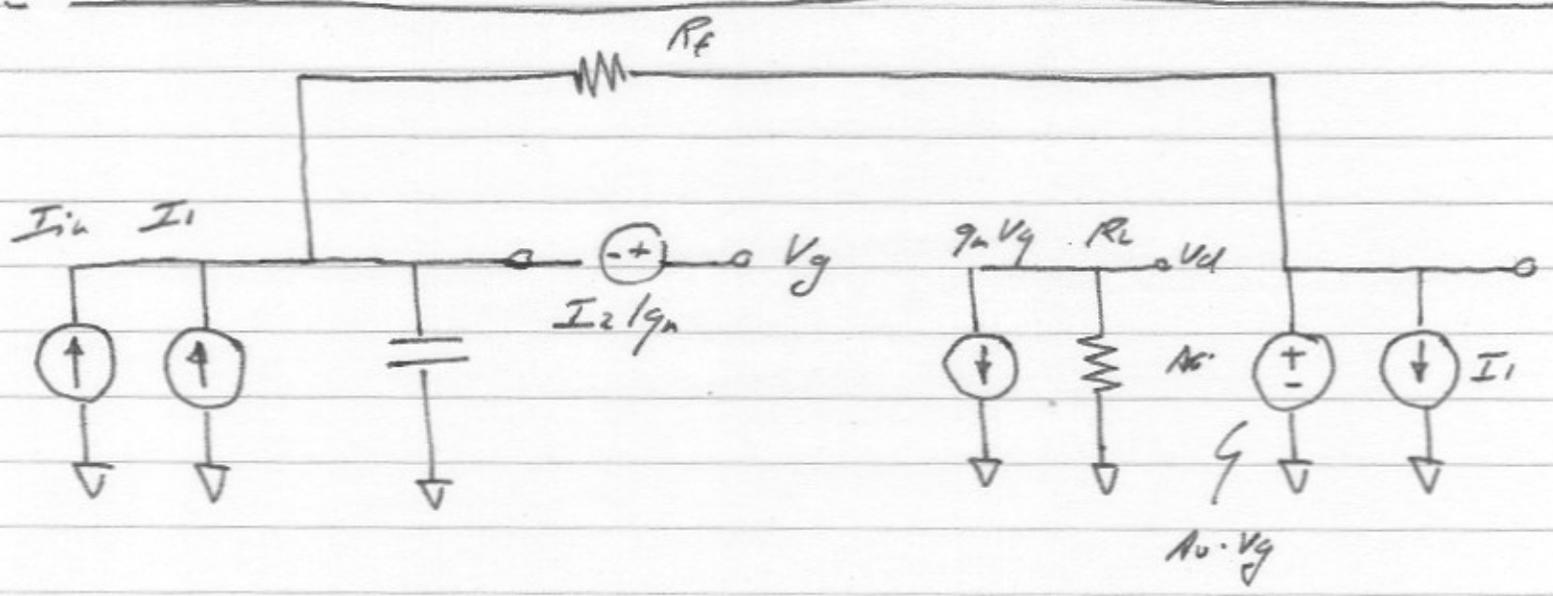apply transformations which do not change  $V_{in}$  or  $V_d$



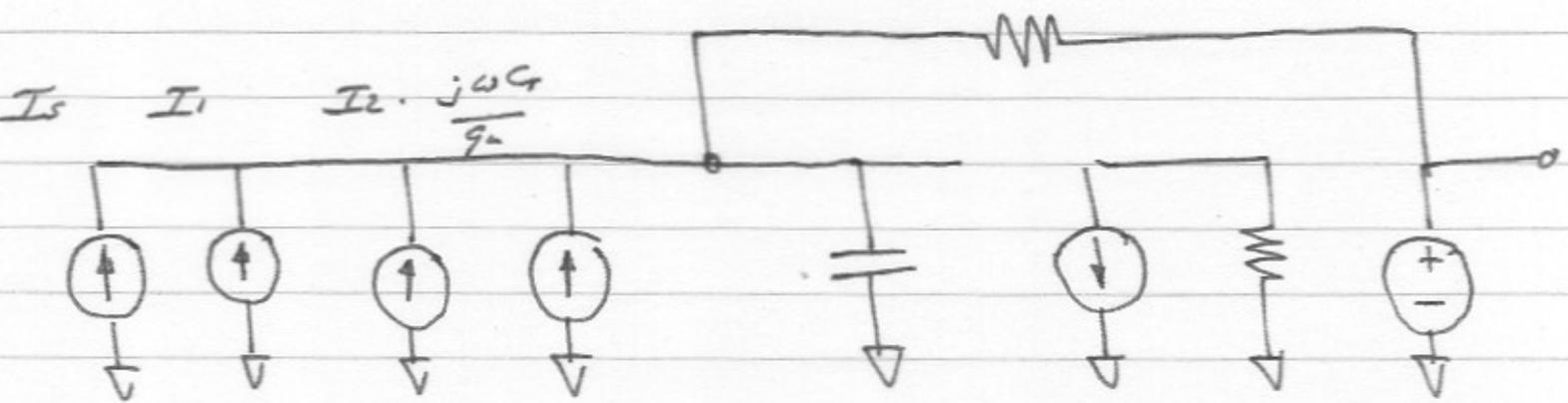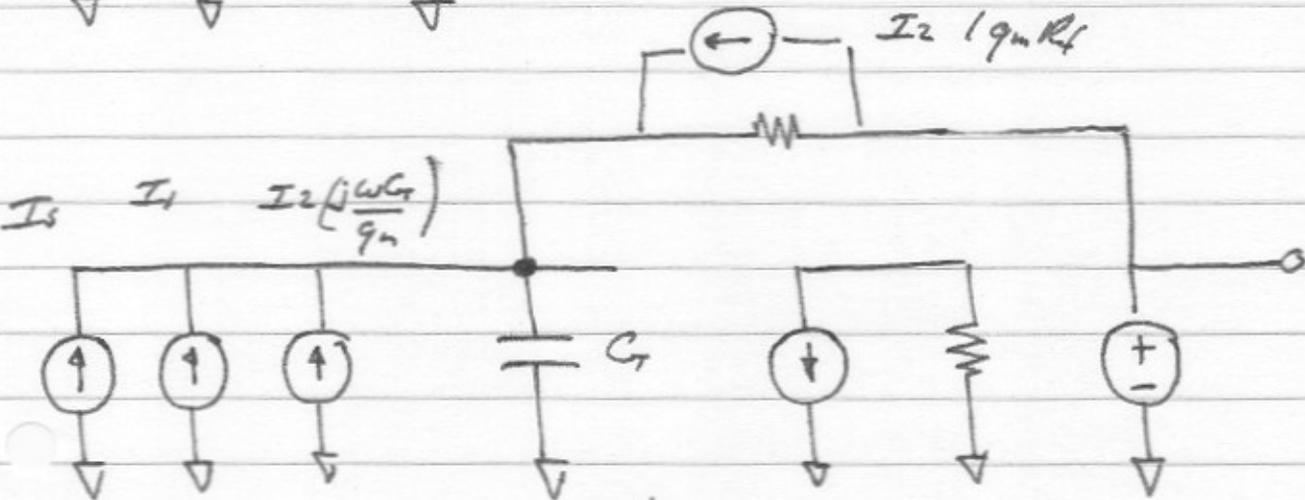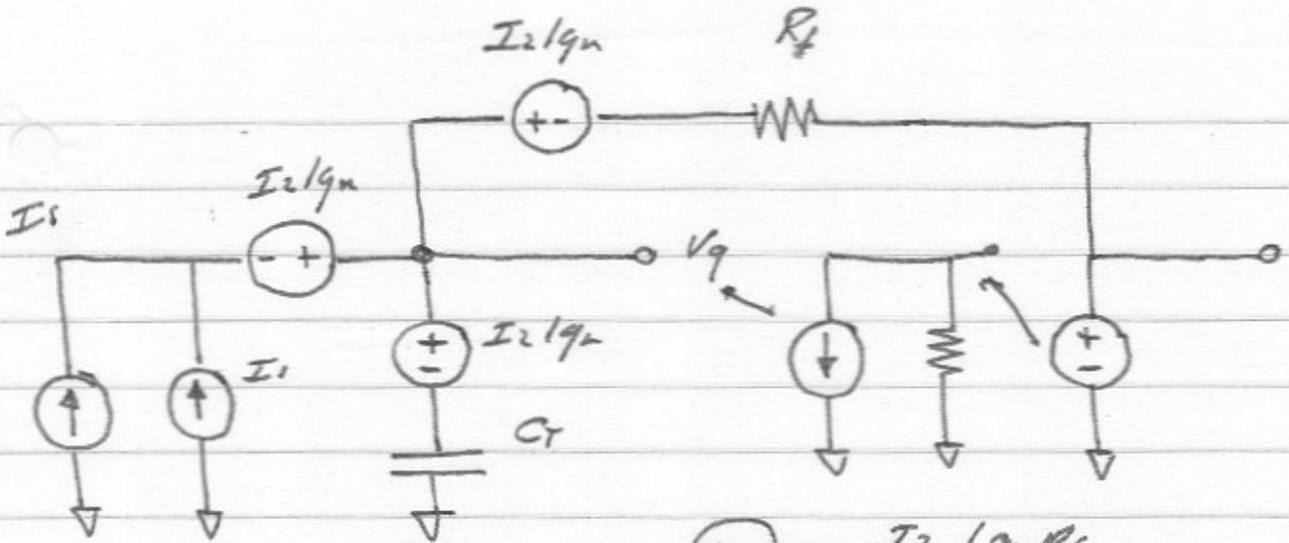

$I_2 / g_n R_f$

(9)

So the total input-referred noise-current spectral density is

$$\frac{d \langle I_T I_T^* \rangle}{df} = \frac{4kT}{R_f}$$


$$+ 4kT \Gamma g_m \left[ \frac{\omega^2 C_T^2}{g_m^2} + \frac{1}{g_m^2 R_f^2} \right]$$

$$= \frac{4kT}{R_f} + \frac{4kT \Gamma}{g_m} \left[ \omega^2 C_T^2 + \frac{1}{R_f^2} \right]$$

[ ... the method is faster than the lecture showed, as we can move generators on 1 drawing ... ]


## Cautionary Comment about Biasing

bias fees are noiseless:

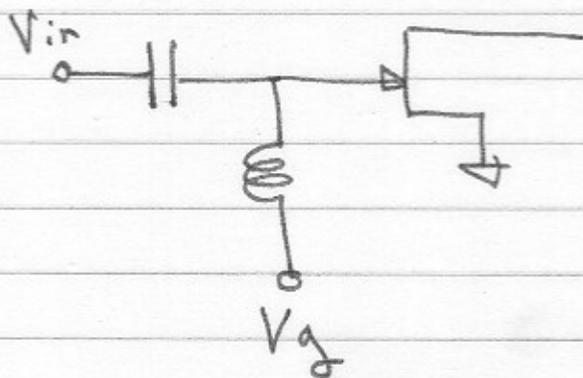


... but their low-frequency cutoff precludes their use in a number of applications.

IF we need a bias current  $I$ :

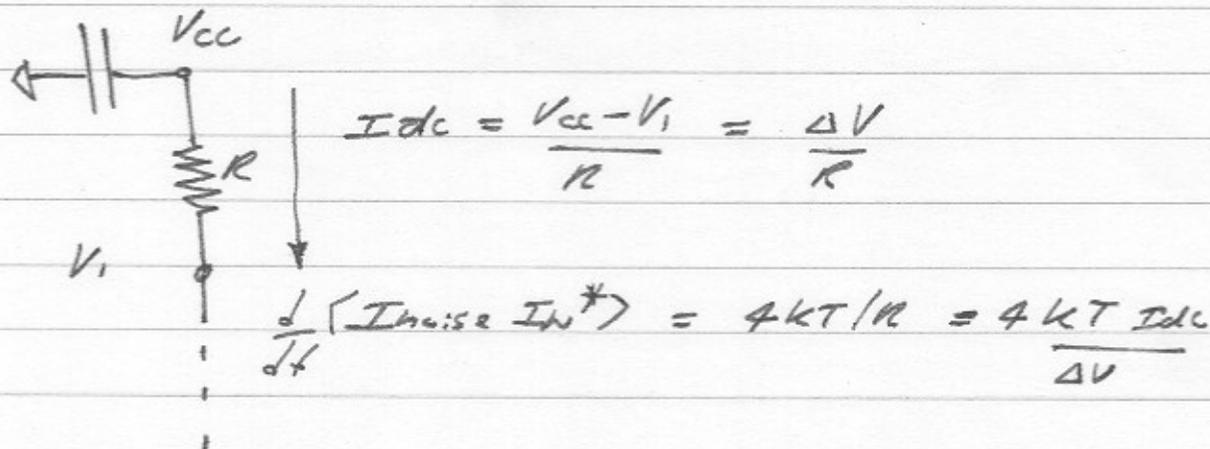

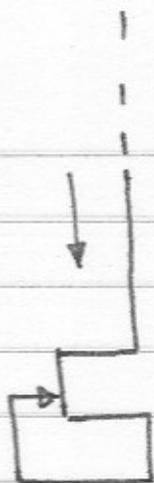Make  $\Delta V$  big to make the current source noiseless.



Fet Constant-current source

at low frequencies:

$$\frac{d}{df} \langle I_n I_n^* \rangle = 4kT \Pi g_m$$

$$= 4kT \Pi \cdot \left( \frac{g_m}{I_{dc}} \right) \cdot I_{dc}$$


Since  $(g_m I_{dc})^{-1} \sim O(V_p)$ , ...

$$\frac{d}{df} \langle I_n I_n^* \rangle \sim O \left[ 4kT \Pi \frac{I_{dc}}{V_p} \right]$$

... this is noisier than the resistor by the


$$\text{ratio} \sim \left( \Delta V \cdot \frac{\Pi}{V_p} \right)$$

ouch !

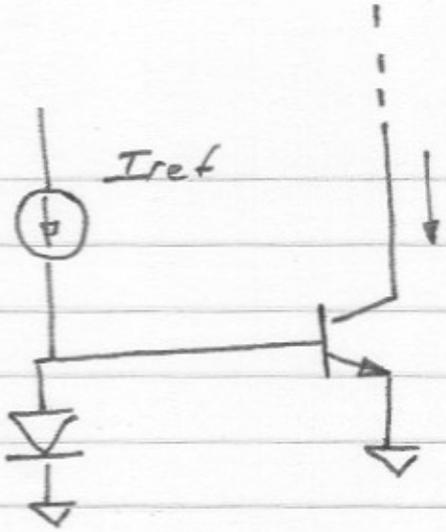

Bipolar current mirror

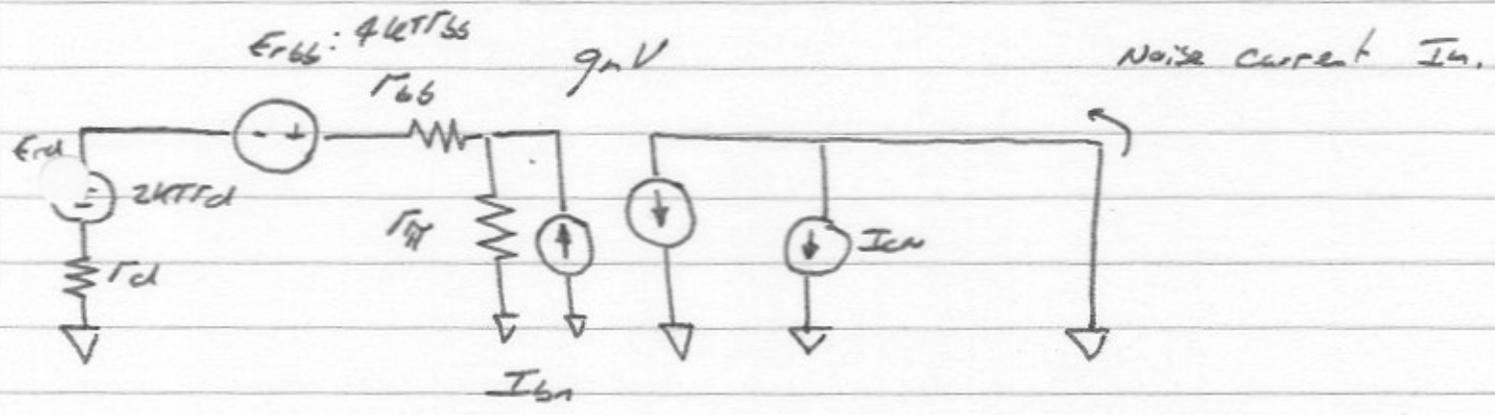$I_{ref}$  noiseless (?)  $\rightarrow$  (really  $4kT I_{ref} / \Delta V$ )



$$I_n = (E_{rd} + E_{rs}) \cdot \frac{r_{\pi}}{r_{\pi} + r_d + r_{bb}} \cdot g_m$$

$$+ (r_{bb} + r_d) \frac{r_{\pi}}{r_{\pi} + r_d + r_{bb}} \cdot I_{bn} \cdot g_m + I_{cn}$$

use  $\beta / g_m = r_{\pi}$ :

$$S_{I_n I_n}(f) = 4KT \left( r_{bb} + \frac{r_d}{2} \right) \left( \frac{\beta}{r_{bb} + r_d + \beta / g_m} \right)^2$$

$$+ 2g I_b \left( \frac{\beta}{r_{bb} + r_d + \beta / g_m} \right)^2 (r_{bb} + r_d)^2$$

$$+ 2g I_{dc}$$


This gets complicated. The last term alone ( $2g I_c$ )

is bigger than resistor-current-source noise by

the ratio  $\left[ \Delta V / 2(KT/g) \right]$


- oach!

### Simple Common-source amplifier:

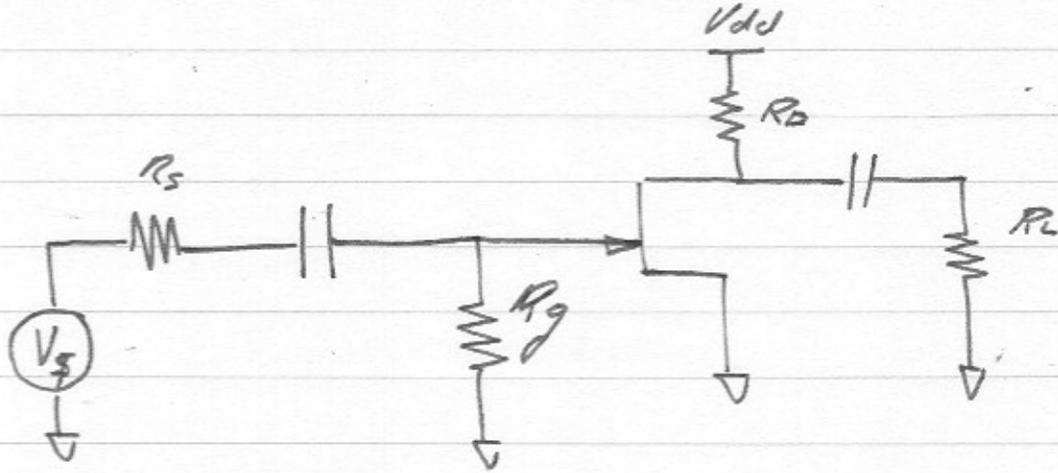


Since this is just an example, pick a simplified

### FET Model

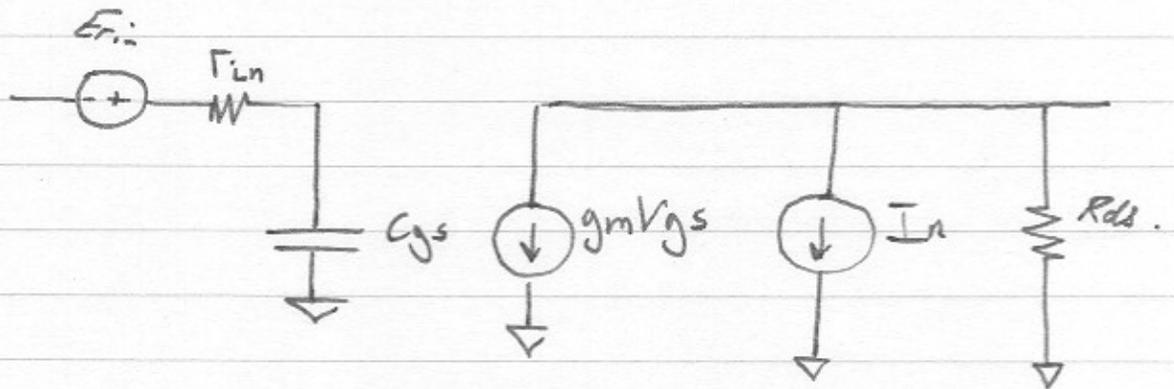
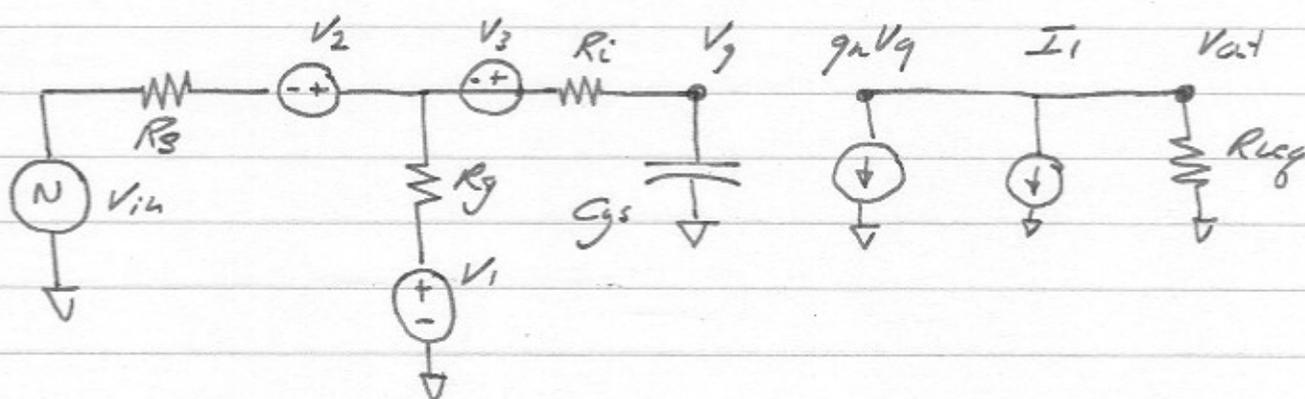
$$\left. \begin{aligned} E_{r,i}: S &= 4kT\Gamma_{L,i} \\ I_n: S &= 4kT\Gamma_{I_n}g_m \end{aligned} \right\} \text{zero cross-spectral density.}$$



$$V_1: 4kTR_g$$

$$V_2: 4kTR_s$$

$$V_3: 4kTR_i$$

$$I_1: 4kT[7g_m + 4kT(1/R_s + 1/R_i)] : R_{eq}^{-1} = R_{ds}^{-1} + R_d^{-1} + R_i^{-1}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_g}{R_g + R_s} \frac{1}{1 + j\omega C_{gs}(R_i + R_s \parallel R_g)} \cdot (-g_m R_{eq})$$


Most efficient to work this by a mixture of methods.

\*  $V_2$  already at input: leave it there...


$$\frac{V_{out}}{I_1} = R_{eq}$$

So, we can Model  $I_1$  by an input voltage of


$$V_{eq|I_1} = \frac{-I_1}{g_m} \cdot \frac{R_g + R_s}{R_g} (1 + j\omega C_{gs}(R_i + R_s || R_g))$$

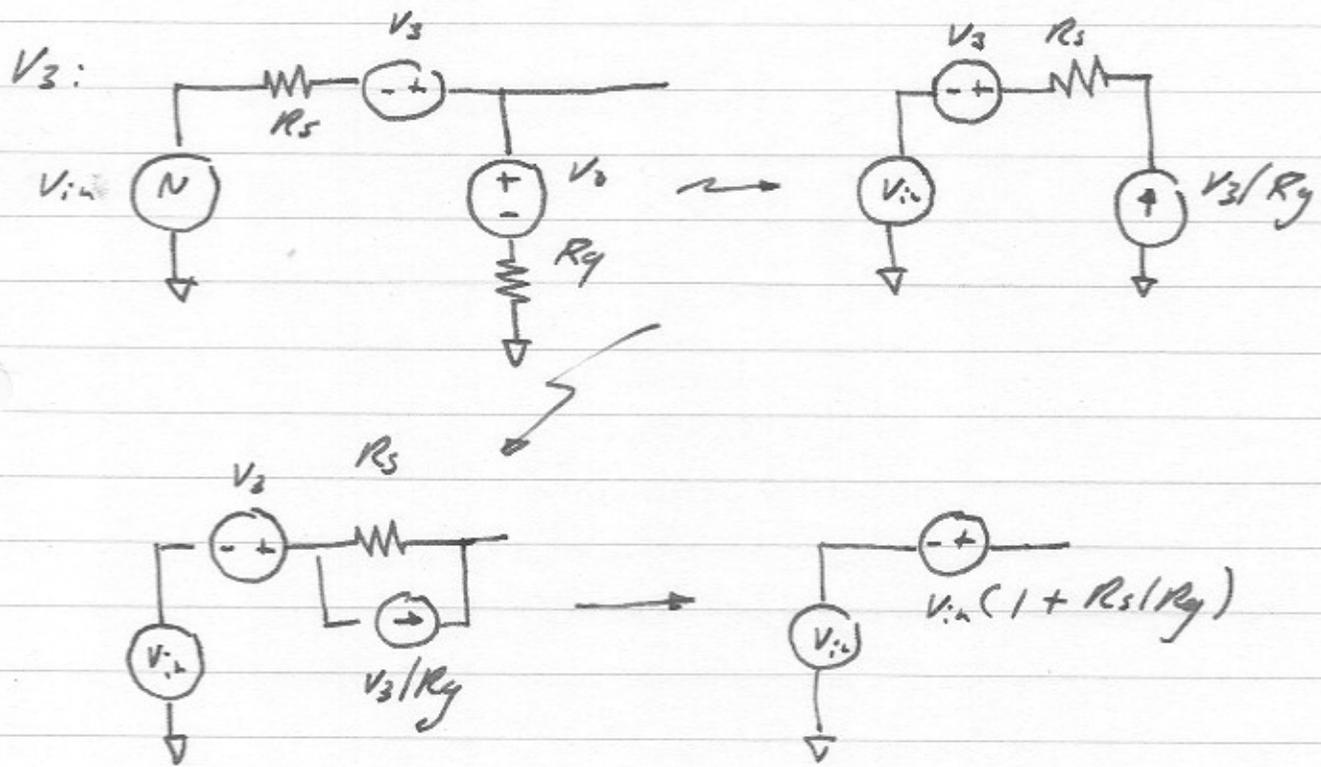

... easier to do than draw ...

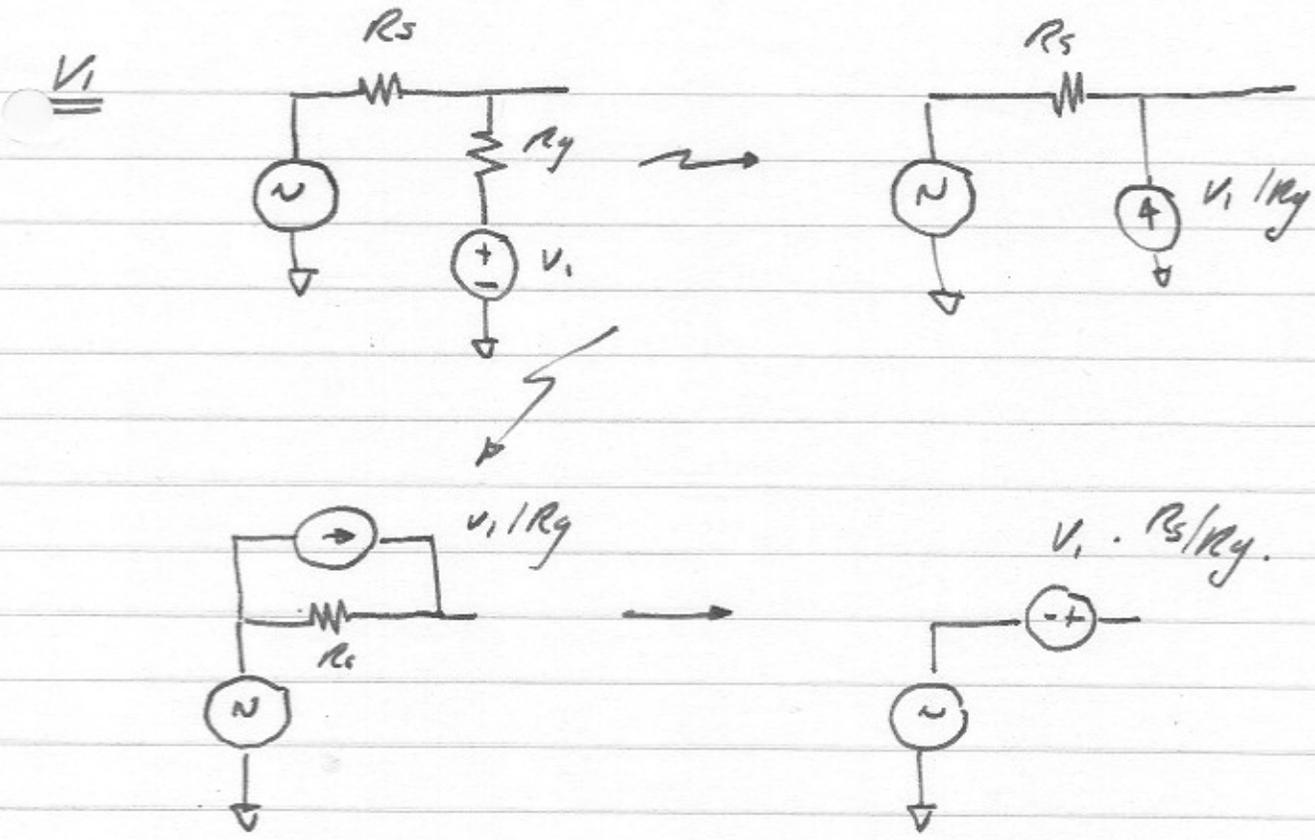

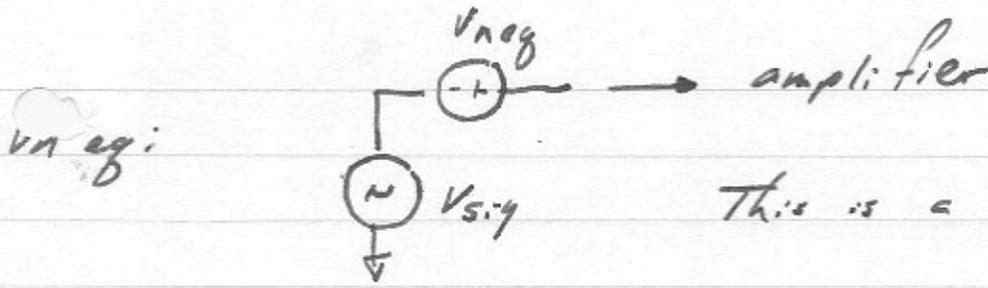So we can now gather terms & write the input-referred noise voltage ...



This is a total noise voltage model

$$S_{v_{n,eq}}(f) = 4kT \Gamma g_m \cdot \left[ \frac{R_g + R_s}{g_m R_g} \right]^2 \left[ 1 + \omega^2 C_{gs}^2 \cdot (R_i + R_s \parallel R_g) \right]^2$$


$$+ 4kT R_s$$

$$+ 4kT R_i \left[ 1 + R_s \parallel R_g \right]^2$$

$$+ 4kT R_g \cdot \left[ R_s \parallel R_g \right]^2$$


you may simplify further...

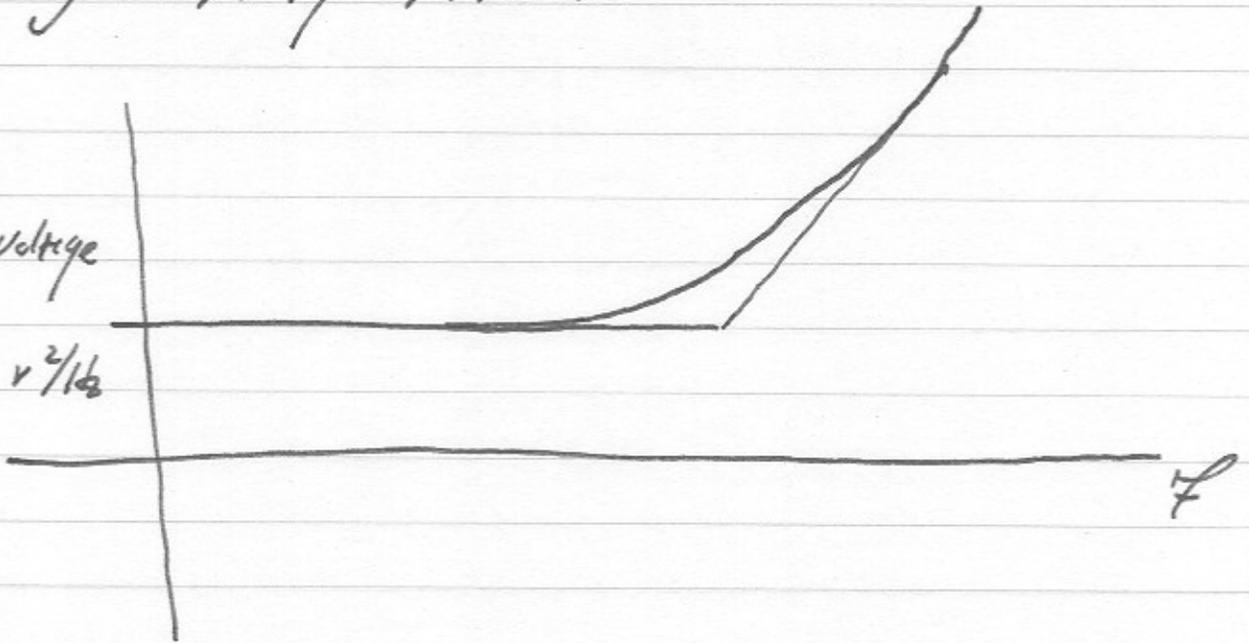input  
referred  
total noise voltage  
spectral  
density,  $v^2/Hz$




~~18~~

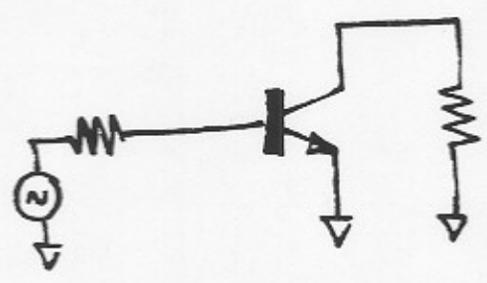
can do same analysis for bipolar c-e amplifier:



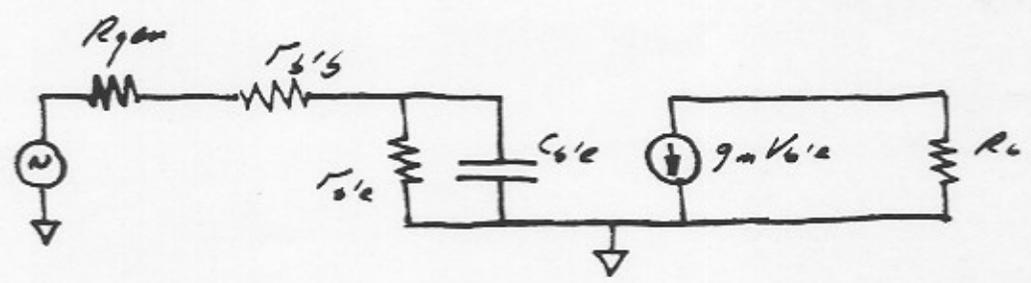neglect  $R_{ce}$  (b.c.)  
neglect  $R_E$  &  $C_{cb}$  just to  
make the problem tractable



add noise sources:

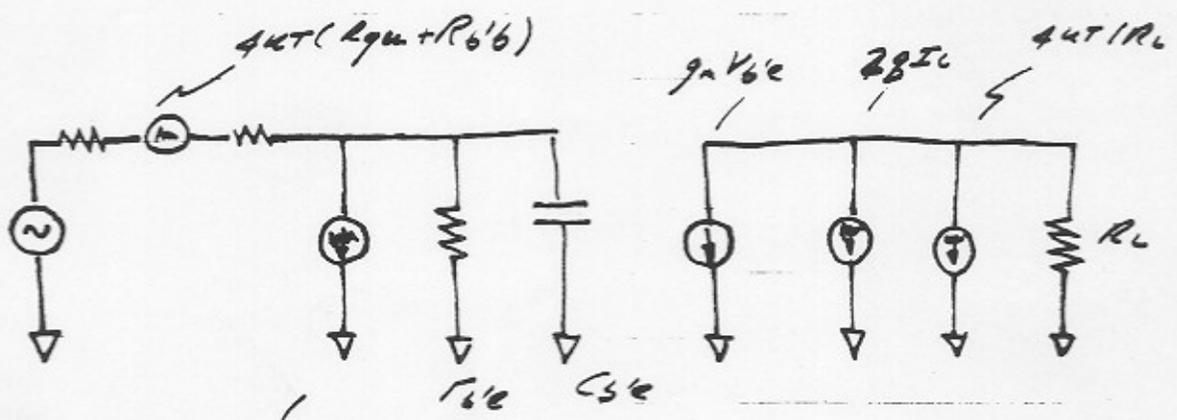

$$\frac{d\langle i^2 \rangle}{dt} = 2q I_B$$

$$= \frac{2q I_C}{\beta}$$

Following similar steps, the input-referred noise voltage can be found:

$$\frac{d\langle E_{in}^2 \rangle}{df} = 4KT(R_{gen} + R_{b'c}) + \frac{2qI_c}{\beta} (R_{gen} + R_{b'c})^2 + \frac{1}{g_m^2} \left( 2qI_c + \frac{4KT}{R_L} \right) \left( 1 + (2\pi f C_{b'e})^2 [r_{b'e} \parallel (r_{b'c} + r_{gen})]^2 \right) \times \left( \frac{r_{b'e} + r_{b'c} + R_g}{r_{b'e}} \right)^2$$

complex: If  $\beta$  is reasonably large, so that  $r_{b'e} \gg R_{gen} + r_{b'c}$

$$\frac{d\langle E_{in}^2 \rangle}{df} \approx 4KT(R_{gen} + R_{b'c}) + \frac{2qI_c}{\beta} (R_{gen} + R_{b'c})^2 + \frac{1}{g_m^2} \left( 2qI_c + \frac{4KT}{R_L} \right) \left( 1 + (2\pi f C_{b'e})^2 (r_{b'c} + r_{gen})^2 \right)$$

optimization: note that  $g_m = kT/qI_C$  & ~~is~~

$$C_b'e = C_b'e_{\text{depl}} + g_m(\tau_b + \tau_c)$$

↑  
base, collector  
transit times

by varying  $I_C$ , an optimum is found with lowest noise.

In general for bipolar:

At lower frequencies: low device noise depends on having high  $\beta$ , low  $\tau_b$ 's, and optimum bias.


At very low frequencies ( $< 10 \text{ kHz}$ ), 1/f noise processes become important.

At high frequencies: (high  $\beta$ ), low  $\tau_b$ 's, low base and collector transit times, optimum bias

similar but not exactly the same parameters as for power gain.

Another example: . . . Develop an  $E_n - I_n$  Model of a fet

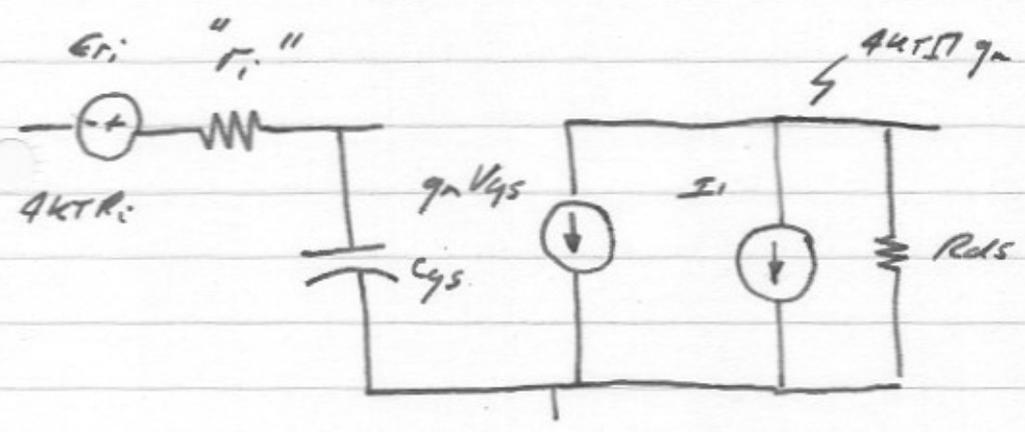Comment: Again, I will simplify the FET noise Model. I am teaching methods here, so you can generalize as you wish.








this model lumps  $r_i + r_s + r_y \rightarrow r_i$

$$\frac{g_m}{1 + g_m R_{ds}} \rightarrow g_m$$


and small correction to  $I_1$

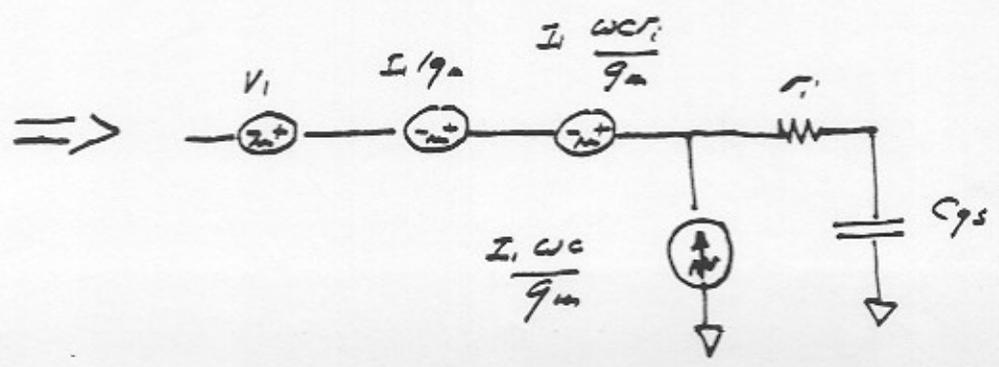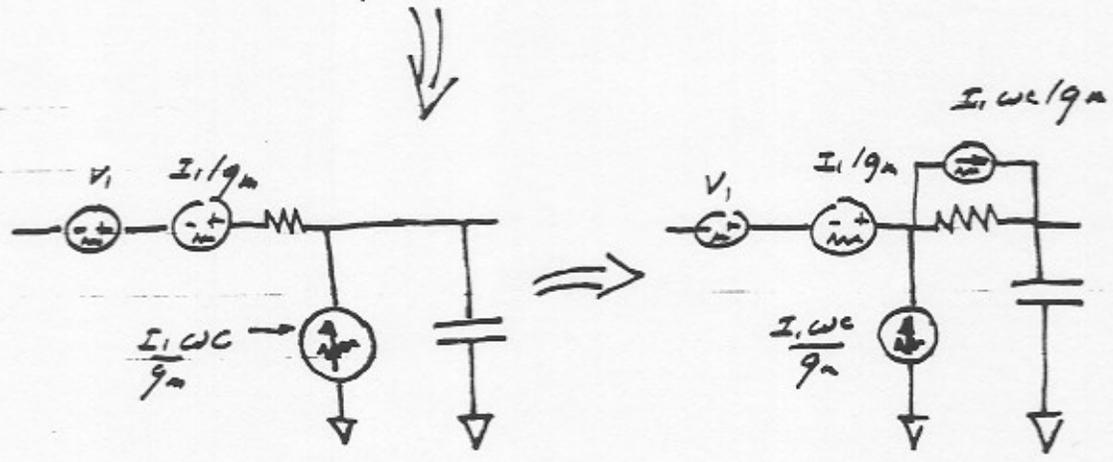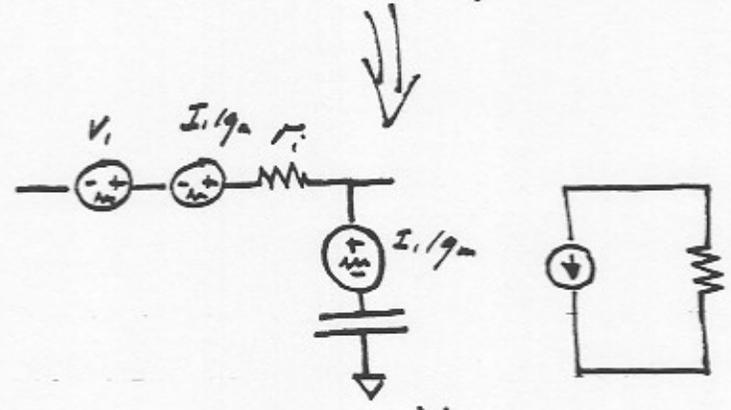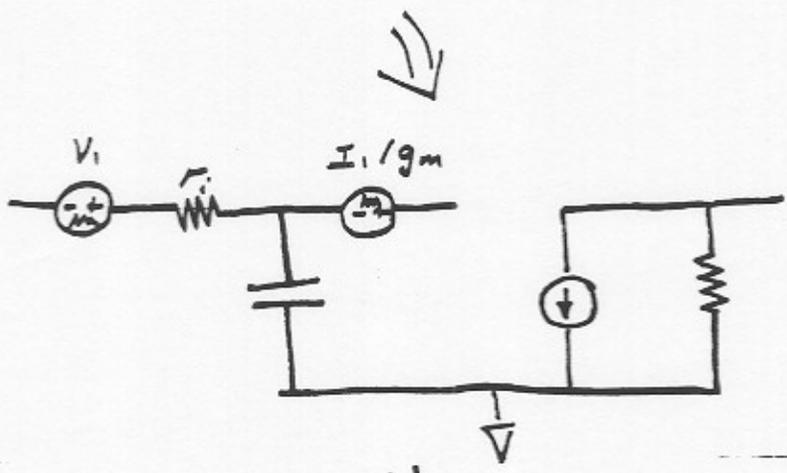... in order to obtain the "hand analysis" fet noise Model.



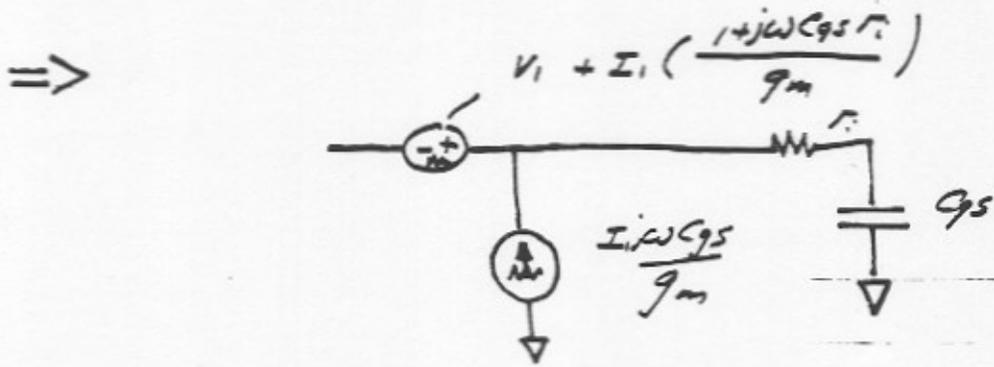

⇒ FET noise Model:

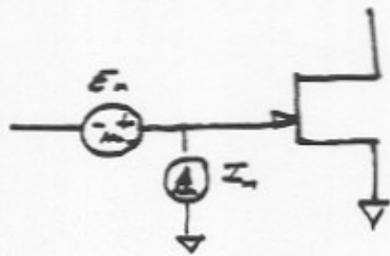

~~$\frac{d\langle E_n^2 \rangle}{df} = 4KT r_1 + \frac{4KT \Gamma}{g_m} (1 + (2\pi f C_{gs})^2 r_1^2)$~~

$$\frac{d\langle I_n^2 \rangle}{df} = \frac{4KT \Gamma}{g_m} (2\pi f C_{gs})^2$$

and  $\frac{d\langle E_n I_n^* \rangle}{df} = 4KT \Gamma g_m \left[ \frac{1 + j\omega C_{gs} r_1}{g_m} \right] \left[ \frac{j\omega C_{gs}}{g_m} \right]^*$

↑  
cross-spectral density

Making the substitution  $r_i \rightarrow r_i + r_g + r_s$ ;

$$\frac{d}{df} \langle E_n E_n^* \rangle = 4kT(r_i + r_g + r_s) + \frac{4kT\Gamma}{g_m} \left[ 1 + (2\pi f C_{gs}(r_i + r_s + r_g))^2 \right]$$

$$\frac{d}{df} \langle I_n I_n^* \rangle = \frac{4kT\Gamma}{g_m} (2\pi f C_{gs})^2$$

$$\frac{d}{df} \langle E_n I_n^* \rangle = \frac{4kT\Gamma}{g_m} \left[ 1 + j2\pi f C_{gs}(r_i + r_s + r_g) \right] \left[ j2\pi f C_{gs} \right]^*$$

It is important to understand that this correlation is arising from circuit analysis, starting with a device model having uncorrelated physical random processes.

Poor papers in the literature get confused regarding this point.


## Noise Figure Again

Earlier we had shown:

$$F = 1 + \frac{S_{vv}(f) + \|Z_g\|^2 S_{II}(f) + 2 \operatorname{Re} [Z_g^* S_{vI}^*(f)]}{4KT \operatorname{Re} [Z_g]}$$

... and had found a minimum noise figure  
and an optimum generator impedance.

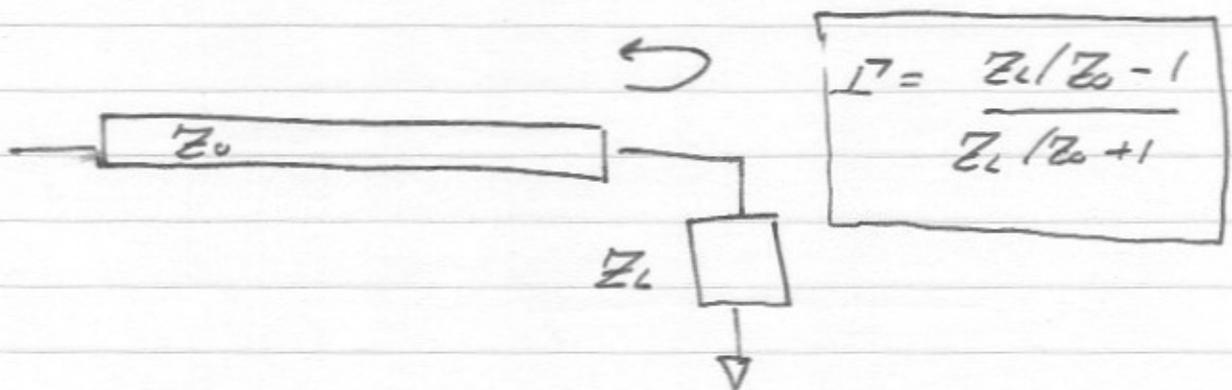Microwave designers usually work with impedances indirectly, writing them as a function of reflection coefficients which would arise if that impedance were to terminate a transmission line:



From this the noise figure can be written in terms of the reflection coefficients, thus:

$$F = F_{min} + 4 \cdot \frac{R_n}{Z_0} \frac{\| \Gamma_g - \Gamma_{opt} \|^2}{(1 - \|\Gamma_g\|^2) \|1 + \Gamma_{opt}\|^2}$$

where

$F_{min}$  as before:




$$\Gamma_{opt} = \frac{Z_{opt}/Z_0 - 1}{Z_{opt}/Z_0 + 1} \quad \Gamma_g = \frac{Z_g/Z_0 - 1}{Z_g/Z_0 + 1}$$

$$\frac{R_n}{Z_0} = \frac{[F(Z_g=Z_0) - F_{min}]}{4 |\Gamma_{opt}|^2}$$

where  $F(Z_g=Z_0)$  is the noise figure with  $Z_g=Z_0$ .

with some effort we can write  $\Gamma_{opt}$  &  $R_n$  directly in terms of the  $(E_n, I_n)$  spectral densities.

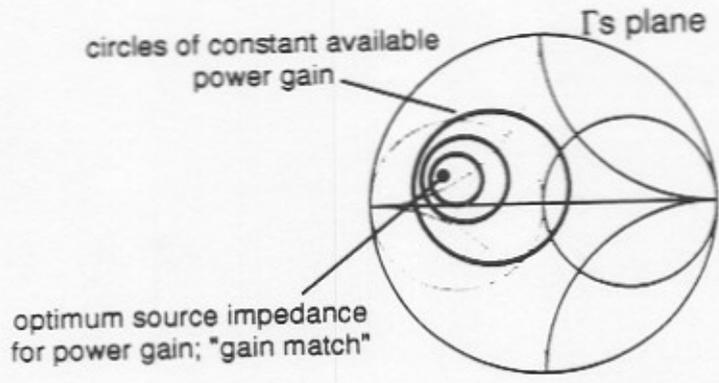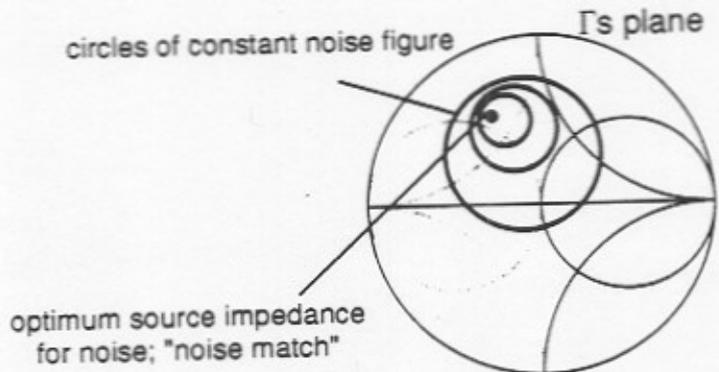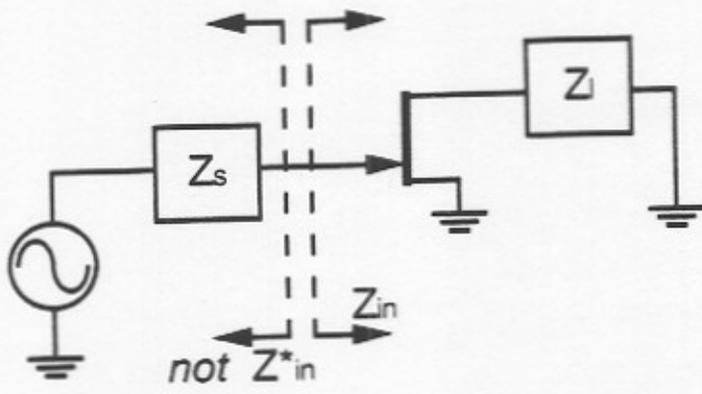don't bother, <sup>this</sup> math best left to a computer & there are no new concepts involved.




*note that the match conditions are different!!!*

Now note the following point:


$Z_s$  for optimum noise is not the (matched)  $Z_s$  for optimum gain.

Many people are troubled by this; they should not be.


Simple example: FET

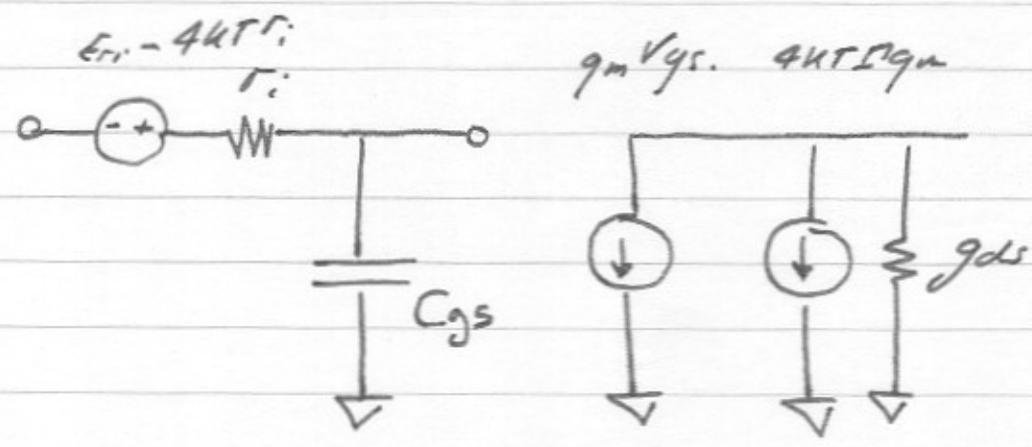

Lets impedance match on input:

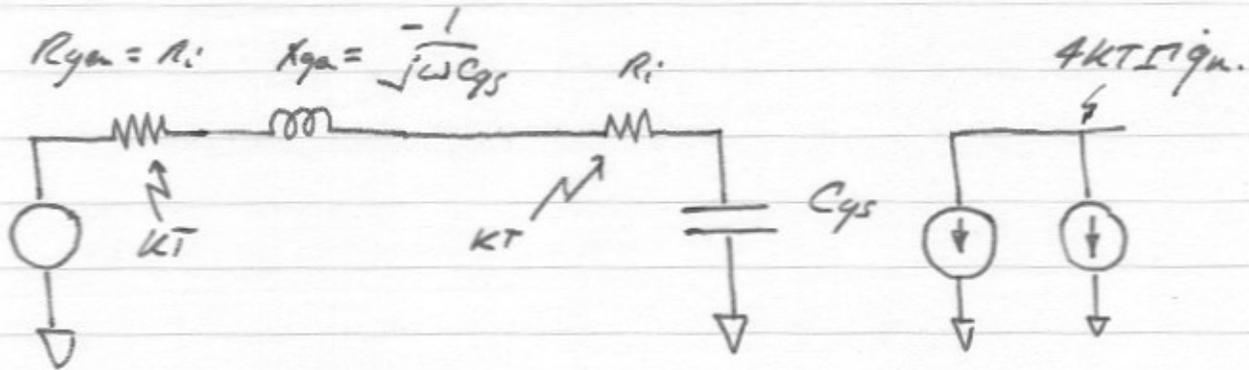

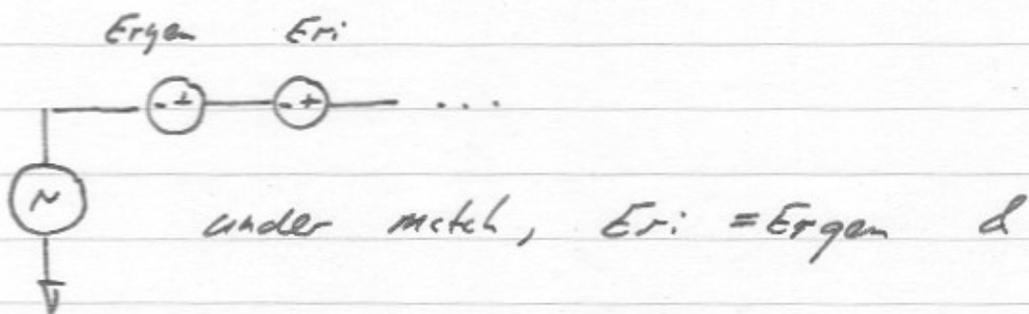Lets not even consider the drain noise  $4kT\Gamma_{gm}$ .



$$F = 1 + 1 + \text{terms due to } 4kT\Gamma_{gm}$$

↑  
noise due to  $R_i$

Matching has made F at least 3dB because  $R_i$  &  $R_{gen}$  contribute equally to the output. Low noise clearly requires a mismatch such that  $R_i$  contributes less strongly!!!