

- Notes Set 16: Bipolar Noise  
analysis topics

- noise figure of BJT at low frequencies.
- resistive feedback amplifier noise figure

Consisting of:

1. Noise figure relationships for bipolar.


2. A few final "circuits" noise problems/examples.

---

First:

Example for the purpose of showing Method  
Low-Frequency bipolar amplifier.

# Bipolar Transistor Noise Model

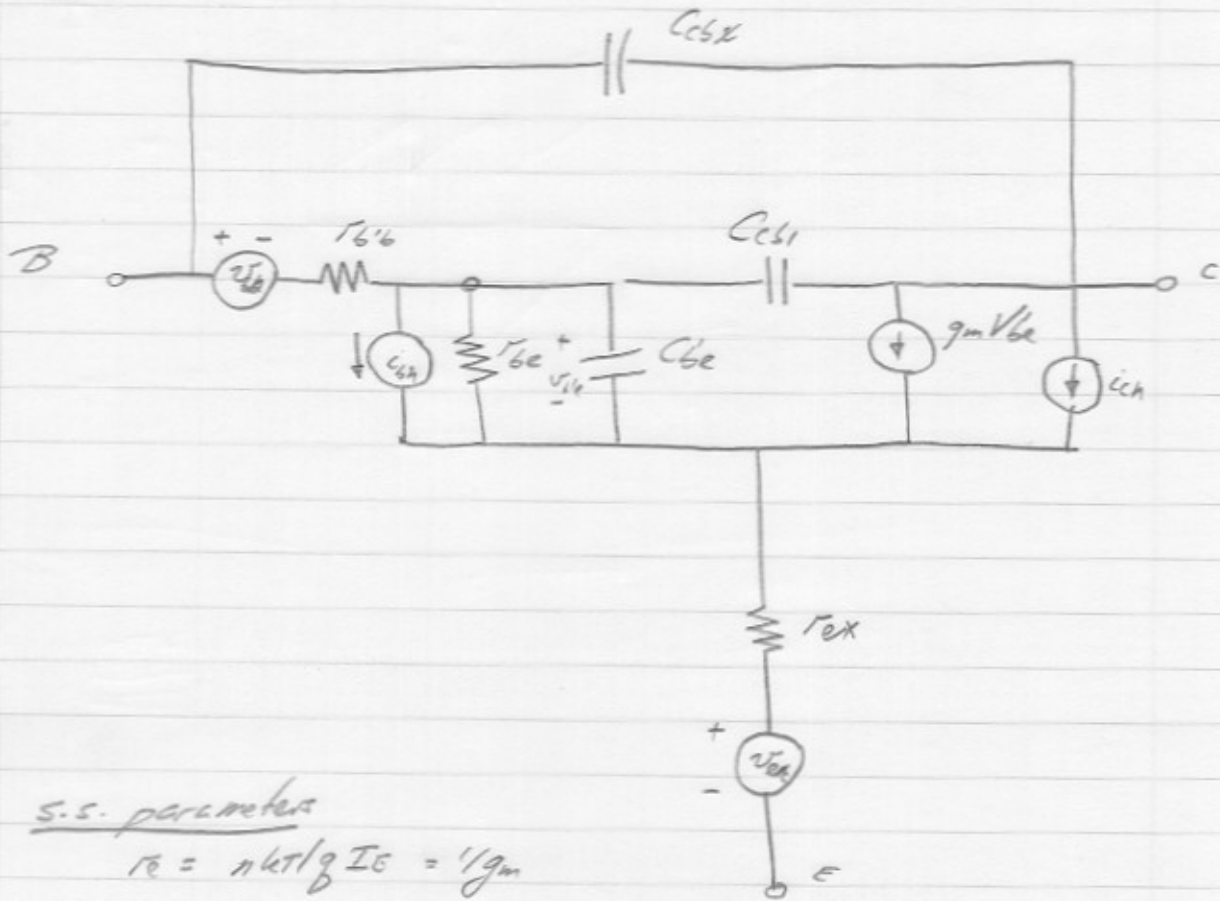

s.s. parameters

$$r_e = n k T / q I_E = 1/g_m$$

$$r_{be} = \beta r_e$$

$$C_{be} = C_{be,depl} + g_m T_f$$

Noise terms: All are statistically independent (uncorrelated)

$$\frac{d}{df} \langle v_{bn}^2 \rangle = 4kT r_{be} \quad \text{base thermal noise.}$$

$$\frac{d}{df} \langle i_{bn}^2 \rangle = 2q I_b \quad \text{base shot noise.}$$


$$\frac{d}{df} \langle i_{cn}^2 \rangle = 2q I_c$$

$$\frac{d}{df} \langle v_{en}^2 \rangle = 4kT r_{ex} \quad \text{thermal noise of the emitter contact resistance.}$$

The advantage of the hybrid- $\pi$  noise model is precisely that the noise terms are uncorrelated.
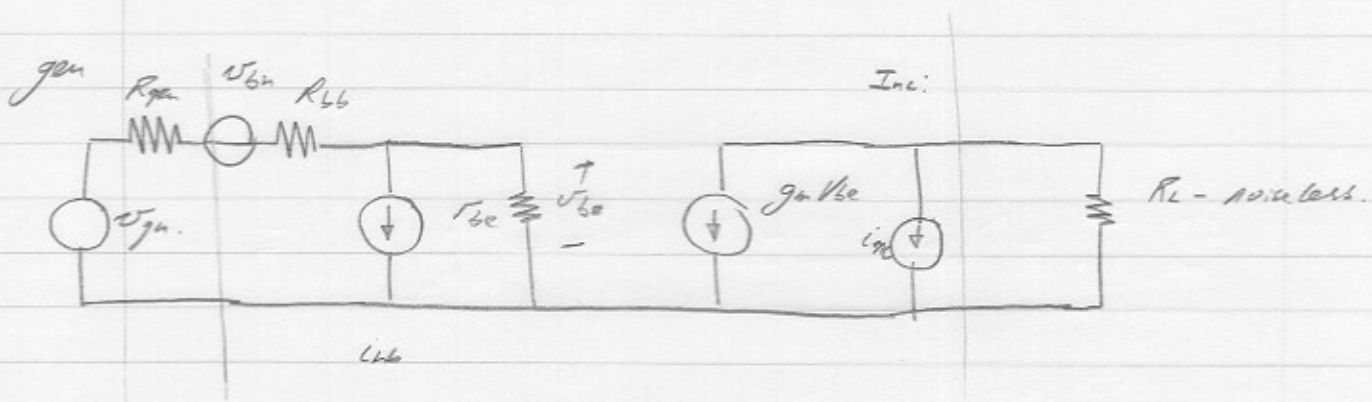
### Noise figure at low frequencies:

initially - omit the base emitter contact resistance:



$F = \frac{\text{total noise power at output, with noisy device}}{\text{" " " " " " " " noiseless device.}}$

$v_{gn} = \text{generator noise} \Rightarrow \text{spectral density } \frac{d}{df} \langle v_{gn}^2 \rangle = 4kT R_{gn}$

$v_{bn} = \text{base thermal noise: } \rightarrow \frac{d}{df} \langle v_{bn}^2 \rangle = 4kT R_{bb}$

$i_{bn} = \text{base shot noise: } \frac{d}{df} \langle i_{bn}^2 \rangle = 2q I_B$

$i_{cn} = \text{collector shot noise: } \frac{d}{df} \langle i_{cn}^2 \rangle = 2q I_c$

output noise due to generator:

$$v_{out} = v_{gn} \cdot \frac{r_{be}}{r_{be} + r_{gen} + r_{be}} \cdot g_m R_L$$

$$\frac{d \langle v_{out}^2 \rangle}{df} = \frac{d P_{out}}{df} = 4kT r_{gen} \cdot \left[ \frac{\beta r_e}{\beta r_e + R_{gen} + r_{be}} \cdot \frac{1}{r_e} \right]^2 R_L$$
  
$$r_{be} = \beta r_e \quad g_m = \frac{1}{r_e}$$

output noise due to  $R_{b'}$ 's - same analysis as above:

$$\frac{d P_{out}}{df} = 4kT R_{b'6} \left[ \frac{\beta r_e}{\beta r_e + R_{gen} + R_{b'6}} \cdot \frac{1}{r_e} \right]^2 R_L$$

clearly must make  $r_{b'6} \ll r_{gen}$ !

output noise due to  $in_b$ :

$$v_{out} = in_b \cdot \left[ \frac{R_{gen} + R_{b'6}}{r_{be}} \right] \cdot \frac{R_L}{r_e}$$

$$\frac{d P_{out}}{df} = \frac{v_{out}^2}{R_L} = 2g I_b \left[ \frac{\beta r_e}{\beta r_e + R_{gen} + R_{b'6}} \cdot \frac{1}{r_e} \cdot (R_{gen} + R_{b'6}) \right]^2 R_L$$

$$= 2g \frac{I_c}{\beta} \left[ R_{gen} + R_{b'6} \right]^2 \left[ \frac{\beta r_e}{\beta r_e + R_{gen} + R_{b'6}} \cdot \frac{1}{r_e} \right]^2 R_L$$

now use  $I_c \approx I_e$  &  $\frac{1}{I_e} = \frac{kT}{g I_e} = r_e$

$$= \frac{2kT}{\beta r_e} \cdot \left[ R_{gen} + R_{b'6} \right]^2 \left[ \frac{\beta r_e}{\beta r_e + R_{gen} + R_{b'6}} \cdot \frac{1}{r_e} \right]^2 R_L$$

output noise due to inc- collector shot noise

$$\frac{P_{out}}{P_{in}} = 2q I_c \cdot R_L =$$

now use  $kT/qI_c = r_e$  &  $I_c \approx I_E$

$$= \frac{2kT}{r_e} \cdot R_L$$

Noise figure, again, takes the ratio of these...

$$F = 1 + \frac{R_{b'6}}{R_{gen}} + \frac{2kT}{\beta r_e} [R_{gen} + R_{b'6}]^2 \frac{1}{4kT R_{gen}}$$

$$+ \frac{2kT/r_e}{4kT R_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{b'6}}{\beta r_e} \cdot r_e \right]^2$$

$$\equiv$$

$$F = 1 + \frac{R_{b'6}}{R_{gen}} + \frac{1}{2\beta} \frac{1}{r_e} \frac{[R_{gen} + R_{b'6}]^2}{R_{gen}}$$

$$+ \frac{1}{2} \frac{r_e}{R_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{b'6}}{\beta r_e} \right]^2$$

noise figure, at low frequencies, with no emitter contact resistance

F = 1 generator term!

+  $\frac{1}{2\beta} \frac{1}{r_e} \frac{[R_{gen} + R_{b'c}]^2}{R_{gen}}$  base shot noise

+  $\frac{R_{b'c}}{R_{gen}}$  base thermal noise

+  $\frac{1}{2} \frac{r_e}{r_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{b'c}}{\beta r_e} \right]^2$  collector shot noise.


now clearly at low frequencies one uses a sufficiently large device to ensure  $R_{b'c} \ll R_{gen}$ . Examine also the other terms:

A =  $\frac{1}{2\beta r_e} \frac{[R_{gen} + R_{b'c}]^2}{R_{gen}} = \frac{1}{2} \frac{1}{\beta r_e}$

B =  $\frac{1}{2} \frac{r_e}{r_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{b'c}}{\beta r_e} \right]^2 \approx \frac{1}{2} \frac{r_e}{r_{gen}}$  if  $\beta r_e \gg R_{gen} + R_{b'c}$   
=  $\frac{1}{2} \frac{r_e}{r_{gen}}$

The sum A+B is minimized by choosing  $\frac{1}{2} \frac{1}{\beta r_e} = \frac{1}{2} \frac{r_e}{r_{gen}}$ , e.g.  
 $r_e = \sqrt{\frac{r_{gen}}{\beta}}$  = ...
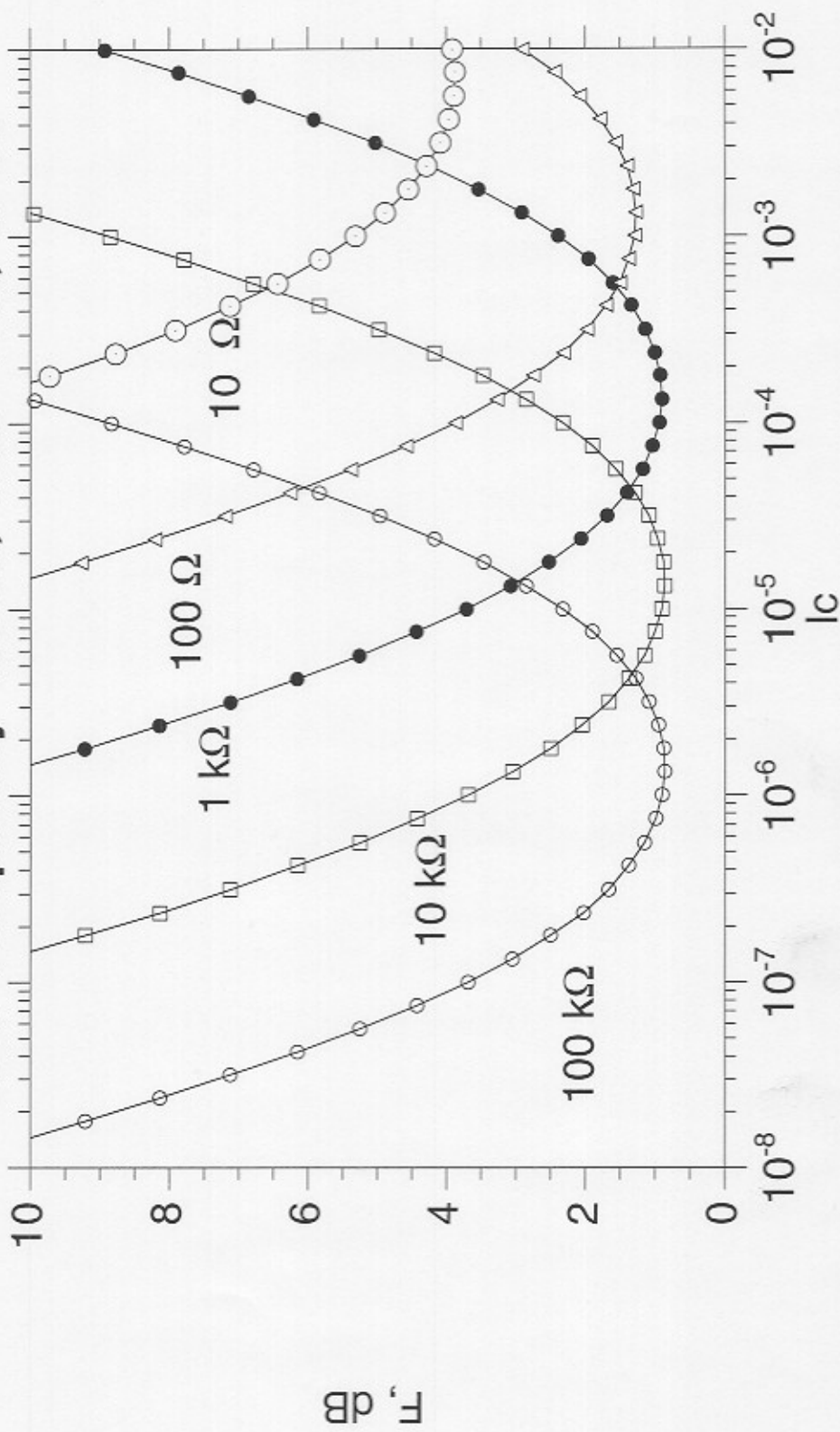
# Low Frequency Noise, $R_{bb}=10\Omega$ , $\beta=30$





opt. max bias - low frequency, idealized

$$r_{e,opt} = \sqrt{\frac{1}{2\beta} \left[ \frac{R_{gen} + R_{bb}}{R_{gen}} \right]^2 \cdot \frac{1}{2\beta} R_{gen}} = \frac{[R_{gen} + R_{bb}]}{\sqrt{\beta}}$$

$$\boxed{r_{e,opt} = \frac{R_{gen} + R_{bb}}{\sqrt{\beta}}}$$

$$F_{max} = 1 + \frac{R_{bb}}{R_{gen}} + \frac{1}{2\sqrt{\beta}} \frac{R_{gen} + R_{bb}}{R_{gen}}$$

$$+ \frac{1}{2\sqrt{\beta}} \frac{R_{gen} + R_{bb}}{R_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{bb}}{\beta r_e} \right]^2$$

Now, note that the last term is problematic (messy).

However, when we plug into the expression for  $r_{e,opt}$ , the fraction becomes  $\left[ \frac{\sqrt{\beta} + 1}{\sqrt{\beta}} \right]^2$

$$F_{min} = 1 + \frac{R_{b'6}}{R_{ga}} + \left( \frac{R_{gen} + R_{b'6}}{R_{gen}} \right) \frac{1}{\sqrt{\beta'}} \cdot \left( 1 + \frac{\left( \frac{\sqrt{\beta'} + 1}{\sqrt{\beta'}} \right)^2}{2} \right)$$

so for  $\beta$  reasonably large, this is

$$F_{min} \approx 1 + \frac{R_{b'6}}{R_{gen}} + \frac{R_{gen} + R_{b'6}}{R_{gen}} \cdot \frac{1}{\sqrt{\beta'}}$$

$F_{min} \approx \left( 1 + \frac{1}{\sqrt{\beta'}} \right) \left( 1 + \frac{R_{b'6}}{R_{gen}} \right)$	$\tau_{opt} \approx \frac{R_{gen} + R_{b'6}}{\sqrt{\beta'}}$
---------------------------------------------------------------------------------------------------------	--------------------------------------------------------------

again this assumes:


- no emitter resistance
- low frequency model.

conclusions for the mid-band analysis are the usual ones:

- Need  $R_{b'6} \ll R_{gen}$
- Need  $\beta \gg 1$

At low frequencies, if we choose a big device, we should be able to attain  $F \approx 0.7 \text{ dB}$

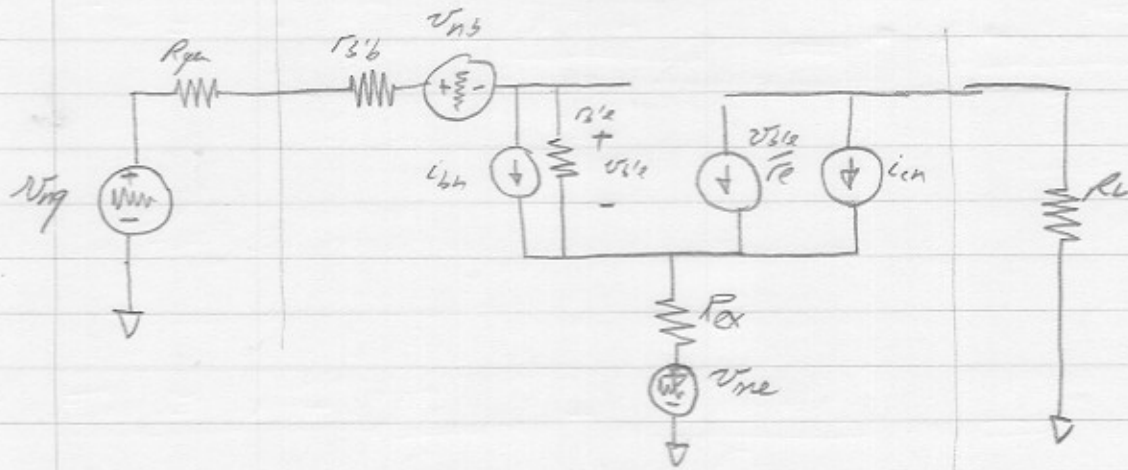Now let's look at the effect of emitter resistance:



I will immediately start using degenerated gain expressions, or the analysis will be intractable.


output power due to generator:

$$\frac{dP_{out}}{df} = 4kT R_{gen} \cdot \left[ \frac{\beta(r_e + R_{ex})}{\beta(r_e + R_{ex}) + R_{gen} + R_{b6}} \cdot \frac{1}{r_e + R_{ex}} \right]^2 \cdot R_L$$

output power due to base thermal noise

$$\frac{dP_{out}}{df} = 4kT R_{b6} \left[ \frac{\beta(r_e + R_{ex})}{\beta(r_e + R_{ex}) + R_{gen} + R_{b6}} \cdot \frac{1}{r_e + R_{ex}} \right]^2 \cdot R_L$$

output power due to  $i_{nb}$ :

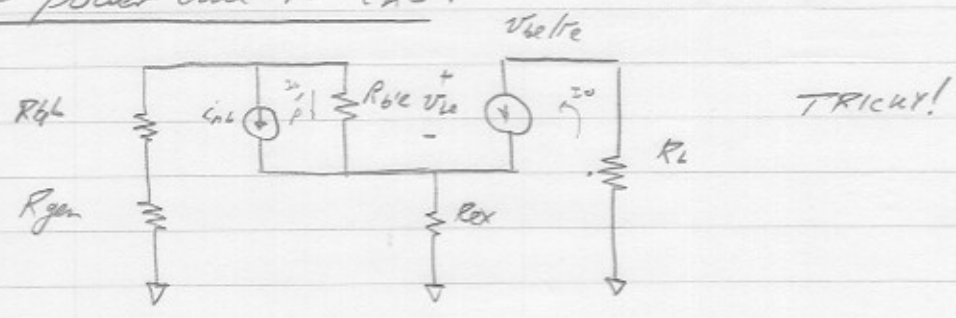

$$v_o \cong i_{nb} \cdot (R_{b6} + R_{gen}) \parallel (\beta R_{ex} + \beta r_e) \cdot \frac{R_L}{r_e + R_{ex}}$$


$$+ \frac{R_{ex}}{r_e + R_{ex} + \frac{R_{b6} + R_{gen}}{\beta}} \cdot R_L \cong i_{nb} \cdot R_L$$

$$\frac{i_o}{i_{nb}} = \left[ \frac{\beta (R_{ex} + r_e)}{R_{gen} + R_{b6} + \beta (R_{ex} + r_e)} \cdot \frac{1}{r_e + R_{ex}} \cdot (R_{b6} + R_{gen}) \right] + \frac{\beta R_{ex}}{R_{gen} + R_{b6} + \beta (r_e + R_{ex})}$$

$$= \frac{\beta (R_{ex} + R_{b6} + R_{gen})}{R_{gen} + R_{b6} + \beta (r_e + R_{ex})}$$

$$\frac{dP_{out}}{df} = 2g I_b \cdot \left[ \frac{\beta R_{ex} + \beta R_{b6} + \beta R_{gen}}{R_{gen} + R_{b6} + \beta r_e + \beta R_{ex}} \right]^2 \cdot R_L$$

output power due to  $I_{ac}$

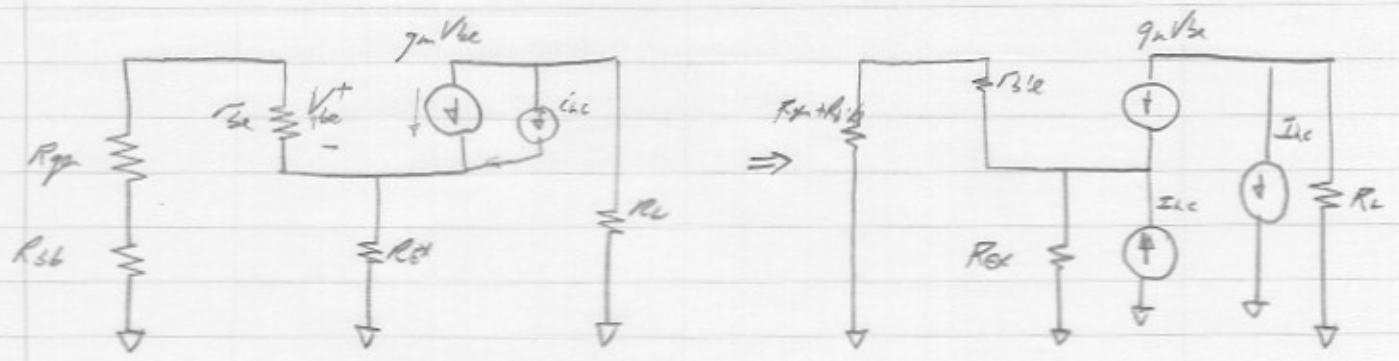

$$\frac{d}{dt} \langle I_{ac}^2 \rangle = 2g I_c$$

$$\frac{I_{out}}{I_{ac}} = 1 - \frac{R_{ex}}{R_{ex} + r_e + \frac{R_{qm} + R_{L'}^2}{\beta}}$$

$$\begin{aligned} \frac{dP_{out}}{dt} &= \left[ \frac{r_e + \frac{R_{qm} + R_{L'}^2}{\beta}}{r_e + R_{ex} + \frac{R_{qm} + R_{L'}^2}{\beta}} \right]^2 \cdot R_L \cdot 2g I_c \\ &= \left[ \frac{\beta r_e + R_{qm} + R_{L'}^2}{(\beta r_e + R_{ex}) + R_{qm} + R_{L'}^2} \right]^2 \cdot R_L \cdot 2g I_c \end{aligned}$$

output power due to  $I_{ne}$

$$\frac{I_{out}}{I_{ne}} = \frac{R_{ex}}{R_{ex} + r_e + R_{gs} + \frac{R_L' L}{\beta}} \quad ; \quad \frac{d(I_{ne}^2)}{df} = \frac{4kT}{R_{ex}}$$

$$\frac{dP_{out}}{df} = \frac{4kT}{R_{ex}} \left[ \frac{R_{ex}}{R_{ex} + r_e + \frac{R_{gs} + R_L'}{\beta}} \right]^2 \cdot R_L$$


---

Noise figure

$$F = 1 + \frac{R_{L'}' b}{R_{gs}}$$

$$+ \frac{2g_m I_b}{4kT R_{gs}} \left[ \frac{\beta r_e + \beta R_{ex} + R_{gs} + R_L'}{\beta r_e + \beta R_{ex} + R_{gs} + R_L'} \cdot \frac{\beta R_{ex} + \beta R_L' + \beta R_{gs}}{\beta} \right]^2$$

$$+ \frac{2g_m I_c}{4kT R_{gs}} \left[ \frac{\beta r_e + R_{gs} + R_L' b}{\beta} \right]^2$$

$$+ \frac{4kT/R_{ex}}{4kT R_{gs}} \left[ \frac{\beta^2 R_{ex}^2}{\beta} \right]^2$$

Noise Figure Low frequency including external emitter resistance.

$$F = 1 + \frac{R_{b'6}}{R_{gen}} \quad \text{generator \& base thermal noise terms}$$

$$+ \frac{1}{2\beta} \frac{1}{r_e} \left[ \frac{R_{b6} + R_{ex} + R_{gen}}{R_{gen}} \right]^2 \quad \text{base shot noise}$$

$$+ \frac{1}{2} \frac{r_e}{R_{gen}} \left[ \frac{\beta r_e + R_{gen} + R_{b'6}}{\beta r_e} \right]^2 \quad \text{collector shot noise}$$

$$+ \frac{1}{2} \frac{R_{ex}}{R_{gen}} \quad \text{external emitter resistance noise!}$$

This is a nice simple expression, but it does not reduce the answer into the form which I was looking for! Let's see what happens if we try to lump the emitter resistance noise together with the collector shot noise.


external:  $4kT R_{ex}$

internal:  $2kT r_e$

I also include an  
 example problem for mid-band noise analysis.

- This will not be worked in lecture -

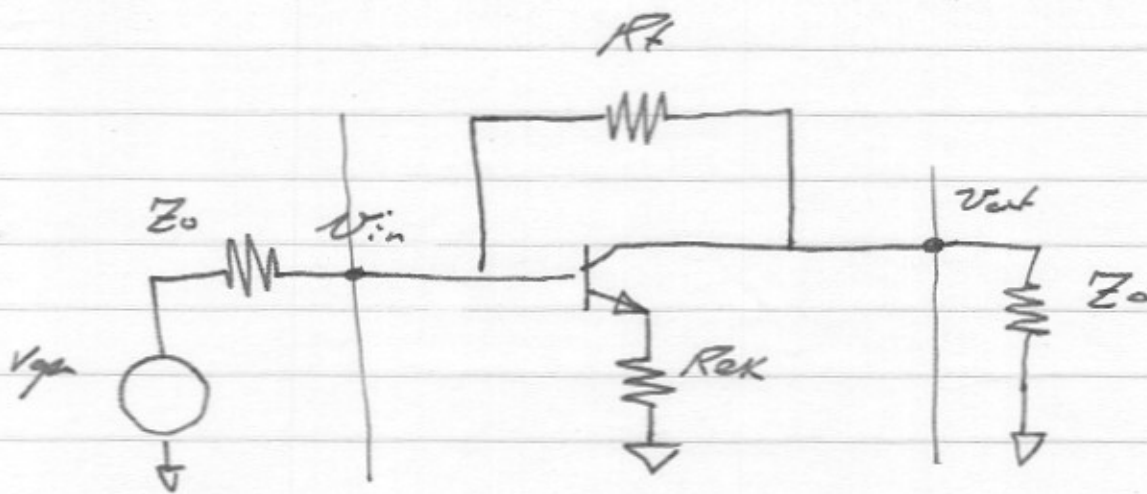- Circuit is Resistive Feedback amplifier



defining:  $\tilde{g}_m = \frac{1}{kT/q I_E + R_{EK}}$


then if we desire  $Z_{in} = Z_{out} = Z_0$   
 and  $\frac{v_{out}}{v_{in}} = -A$ .

$$\tilde{g}_m = \frac{1-A}{Z_0} \quad \text{and} \quad R_f = Z_0 (1-A)$$

For  $\beta$  large.



Feedback Amplifier noise analysis:

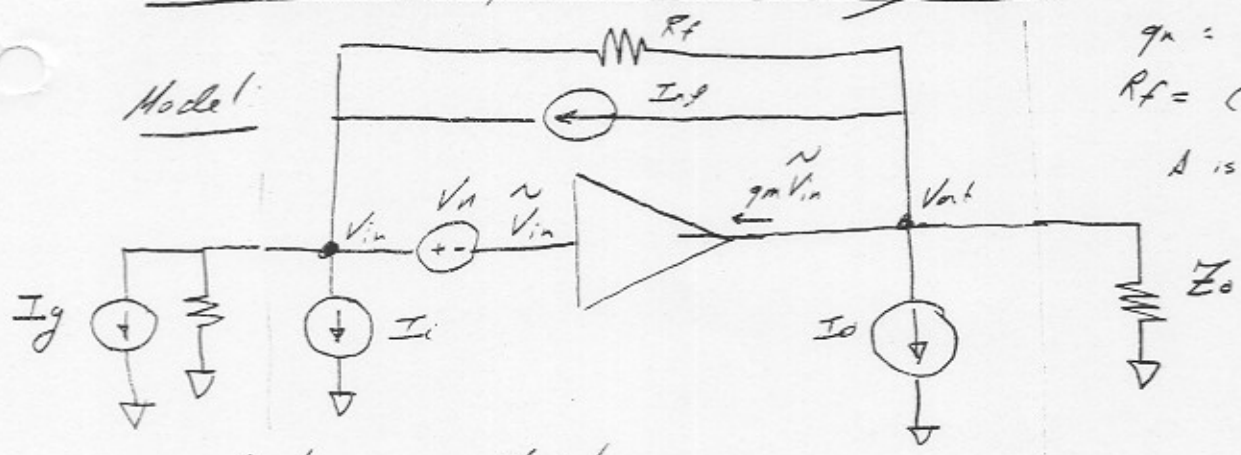

$$g_m = \frac{1+A}{Z_o}$$

$$R_f = (1+A) Z_o$$

A is voltage gain

Work by superposition:

Ig: generator noise:

$$V_o = +A \frac{Z_o}{2} I_g; \quad \int \langle I_g^2 \rangle / df = 4kT/Z_o$$

$$\frac{\int \langle V_o \rangle}{df} = A^2 \frac{Z_o^2}{Z_o^2} \frac{1}{Z_o} \frac{4kT}{Z_o} = A^2 kT \quad \text{of course.}$$

Ii - input noise of amplifier:

$$V_o = (+A Z_o / 2) I_i$$

Io: output noise current:


$$V_o = -I_o Z_o / 2$$

Vn: input noise voltage

Vn on input can be treated as a current  $I_n = V_n g_m$  on the output, so output noise voltage is

$$V_o = +V_n [g_m Z_o / 2] = V_n \frac{[1+A]}{2}$$

RF - feedback resistor noise:

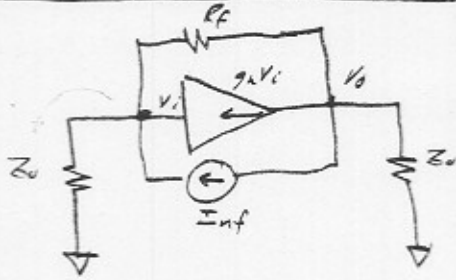

$$V_i \left[ \frac{1}{Z_0} + \frac{1}{Z_o} \frac{1}{1+A} \right] + V_o \left[ \frac{-1}{Z_o} \frac{1}{1+A} \right] = I_{nf}$$

$$V_i \left[ \frac{1+A}{Z_o} - \frac{1}{Z_o} \frac{1}{1+A} \right] + V_o \left[ \frac{1}{Z_o} + \frac{1}{Z_o} \frac{1}{1+A} \right] = -I_{nf}$$

$$-\frac{V_o}{Z_o I_{nf}} = \frac{\left(1 + \frac{1}{1+A}\right) + \left(1+A - \frac{1}{1+A}\right)}{\left(1 + \frac{1}{1+A}\right)^2 - \left(1+A - \frac{1}{1+A}\right)\left(-\frac{1}{1+A}\right)}$$

$$= \frac{(1+A+1) + (1+A^2+2A-1)}{(1+A+1)^2 + (1+A^2+2A-1)} \cdot (1+A)$$

$$= \frac{2+3A+A^2}{A^2+4A+4+A^2+2A} \cdot (1+A)$$

$$= \frac{(A+1)^2(A+2)}{2A^2+6A+4} = \frac{(A+1)^2(A+2)}{2[A^2+3A+2]}$$

$$= \frac{1}{2} \frac{(A+1)^2(A+2)}{(A+1)(A+2)} = \frac{1}{2} (A+1) !$$


$$\Rightarrow \boxed{V_o = -(1+A) \cdot \frac{Z_o}{2} \cdot I_{nf}}$$

$$\begin{aligned} \frac{d\langle P_o \rangle}{df} &= \frac{1}{Z_o} \frac{d\langle V_o^2 \rangle}{df} = \frac{1}{Z_o} \left[ (1+A)^2 \frac{Z_o^2}{4} \right] \left[ 4kT/R_f \right] \\ &= \frac{1}{Z_o} \left[ 1+A \right]^2 \frac{Z_o^2}{4} \frac{4kT}{Z_o} \frac{1}{1+A} = kT[1+A] \end{aligned}$$

$$\boxed{\frac{d\langle P_o \rangle}{df} = kT[1+A]} \quad \text{due to } R_f$$


Note particularly that since  $A$  is the voltage gain, not the power gain, that the relative noise contribution of  $R_f$  becomes minor for high amplifier gains.

Effect of Collector shot noise:

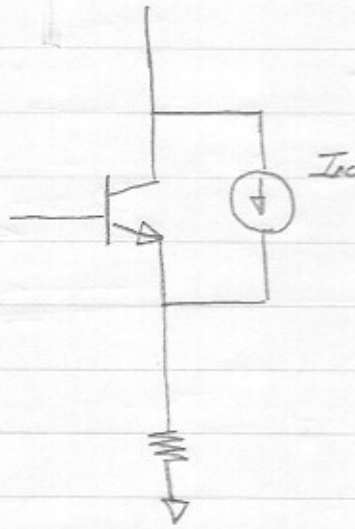


$$\frac{d \langle I_{c0}^2 \rangle}{df} = 2q I_{c0} = 2kT/r_e$$

$\Rightarrow$

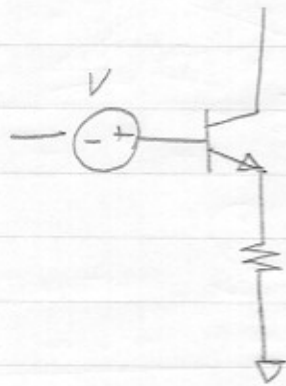

$$V = I_{c0} \cdot r_e$$


$\Rightarrow$

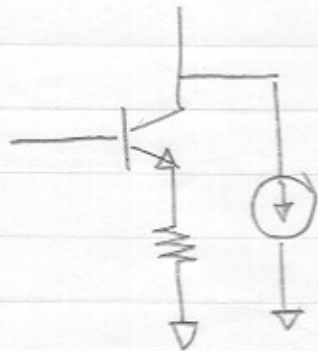

$$\tilde{I} = \frac{V}{r_e + R_{ex}} = I_{c0} \cdot \frac{r_e}{r_e + R_{ex}}$$

$$\frac{d \langle \tilde{I}^2 \rangle}{df} = 2kT \frac{r_e}{(r_e + R_{ex})^2}$$


Effect of  $R_{EX}$  thermal noise:

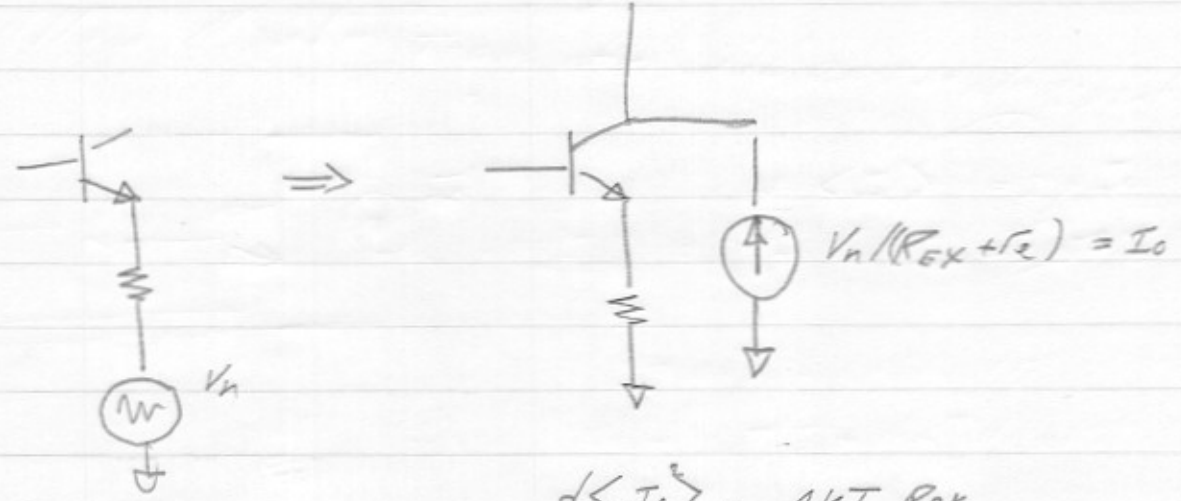


$$\frac{d\langle I_0 \rangle}{df} = \frac{4kT R_{EX}}{(R_{EX} + r_e)^2}$$

Base shot noise?

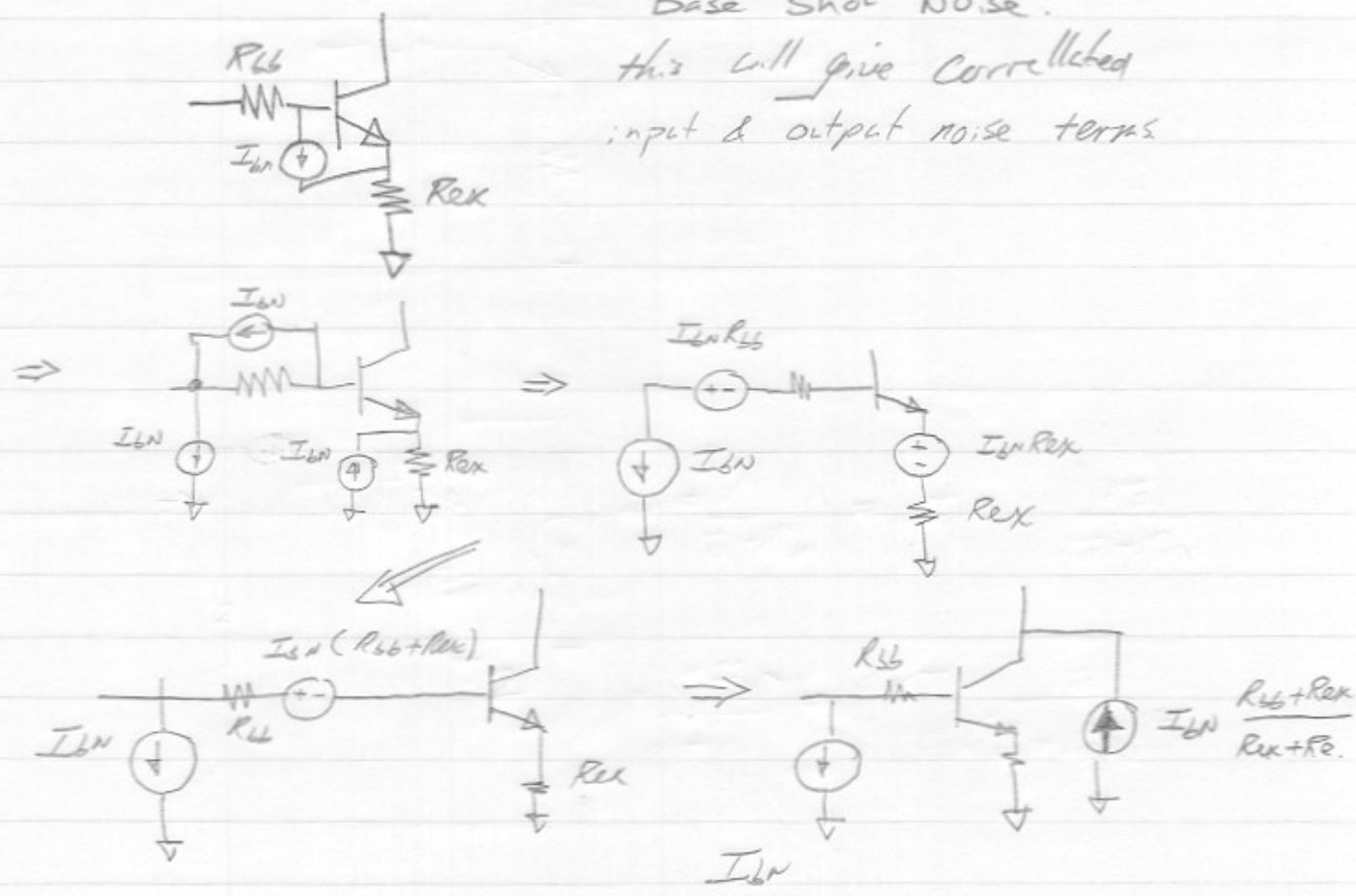this will give correlated input & output noise terms



So Mid-band transistor noise Model is:

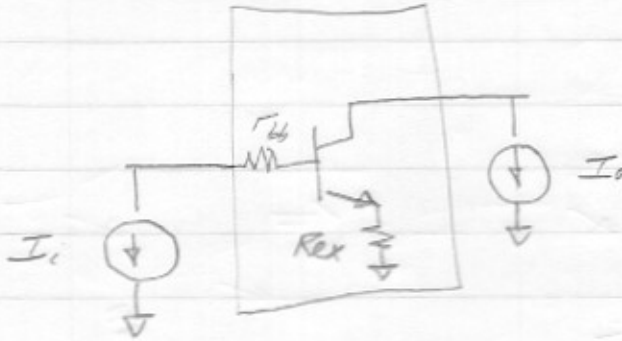

$$\frac{d\langle I_i^2 \rangle}{df} = 2g I_b = \frac{2kT}{\beta I_e}$$

$$\frac{d\langle I_o^2 \rangle}{df} = \frac{4kT[R_{bb} + R_{ex}]}{(R_{ex} + I_e)^2} + \frac{2kT I_e}{R_{ex} + I_e} + 2g I_b \left( \frac{R_{bb} + R_{ex}}{R_{ex} + I_e} \right)^2$$

$= 2kT / \beta I_e$

$$\frac{d\langle I_i I_o \rangle}{df} = - \left( \frac{R_{bb} + R_{ex}}{R_{ex} + I_e} \right) \cdot 2g I_b$$

so now substitute these back into the amplifier

output noise terms:

generator:  $\frac{d\langle P_{out} \rangle}{df} = A^2 kT$  / feedback resistor  $\frac{d\langle P_b \rangle}{df} = kT[1+A]$

amplifier input noise current:

$$\frac{d\langle P_{out} \rangle}{df} = A^2 \frac{Z_o^2}{4} \cdot \frac{2kT}{\beta I_e} \frac{1}{Z_o} = A^2 \frac{Z_o}{I_e} \frac{2kT}{4\beta}$$

but  $g_m Z_o = \beta I_e Z_o = 1+A$

$$= A^2 \frac{Z_o}{4} \cdot \frac{2kT}{\beta I_e} = \frac{A^2 Z_o}{4} \frac{2g_m I_b}{\beta}$$

amplifier output noise current

$$\frac{d\langle P_{out} \rangle}{df} = \left[ \frac{4kT Z_o (R_{bb} + R_{ex}) + 2kT I_e}{(R_{ex} + I_e)^2} + \frac{2kT}{\beta I_e} \left( \frac{R_{bb} + R_{ex}}{R_{ex} + I_e} \right)^2 \right] \cdot Z_o / 4$$

$$\frac{d\langle P_{out} \rangle}{df} = kT \frac{Z_o}{R_{ex} + I_e} \left[ \frac{R_{bb} + R_{ex} + I_e / 2}{R_{ex} + I_e} + \frac{2g_m I_b}{4\beta} \frac{(R_{bb} + R_{ex})^2}{R_{ex} + I_e} \right]$$

correlation term (negative)

$$\frac{d\langle P_{out} \rangle}{df} = 2 \frac{d\langle I_{in} \rangle}{df} \cdot \frac{A Z_o}{2} \cdot \left( \frac{-Z_o}{2} \right) \frac{1}{Z_o}$$

$$= + \left( \frac{R_{bb} + R_{ex}}{R_{ex} + I_e} \right) \frac{A Z_o}{2}$$

Total output noise power:

$$\frac{d \langle P_o \rangle}{df} = A^2 kT + [1+A] kT$$

generator,  $R_f$

$$+ 2g I_b \left[ \frac{A^2 E_o}{4} + \frac{Z_o}{4} \left( \frac{R_{bb} + R_{ex}}{R_{ex} + r_e} \right)^2 + \frac{A E_o}{2} \left( \frac{R_{bb} + R_{ex}}{R_{ex} + r_e} \right) \right]$$

base shot noise

$$+ kT \frac{Z_o}{R_{ex} + r_e} \left[ \frac{R_{bb} + R_{ex} + r_e/2}{R_{ex} + r_e} \right]$$

base thermal

$R_{ex}$

collector shot

$$\frac{d \langle P_o \rangle}{df} = A^2 kT + [1+A] kT$$

generator,  $R_f$

$$+ 2g I_b Z_o \frac{1}{4} \left[ A + \frac{R_{bb} + R_{ex}}{R_{ex} + r_e} \right]^2$$

(of course)

base shot.

$$+ kT (1+A) \left[ \frac{R_{bb} + R_{ex} + r_e/2}{R_{ex} + r_e} \right]$$

base,  $R_{ex}$  thermal

collector shot.

To get noise figure, divide by  $A^2 kT \dots$



## Noise Figure

$$F = 1 + \left[ \frac{1+A}{A^2} \right] + \frac{2g I_b Z_0 / 4}{2\beta I_K T} \left[ 1 + \frac{1}{A} \frac{R_{bb} + R_{ex}}{R_{ex} + r_e} \right]^2$$

generator,  $R_f$       Base shot

$$+ \left[ \frac{1+A}{A^2} \right] \left[ \frac{R_{bb} + R_{ex} + r_e / 2}{R_{ex} + r_e} \right]$$

base thermal,  $R_{ex}$  thermal, collector shot.

The above is written in physical form. To get the result in terms of  $r_e$ , use  $2g I_b = 2kT / \beta r_e$

$$F = 1 + \left[ \frac{1+A}{A^2} \right] + \frac{1}{2\beta} \frac{Z_0}{r_e} \left[ 1 + \frac{1}{A} \frac{R_{bb} + R_{ex}}{R_{ex} + r_e} \right]^2$$

$$+ \left[ \frac{1+A}{A^2} \right] \left[ \frac{R_{bb} + R_{ex} + r_e / 2}{R_{ex} + r_e} \right]$$

we also end up with more "useful" expressions if we use  $(R_{ex} + r_e)^{-1} Z_0 = 1 + A \Rightarrow (R_{ex} + r_e)^{-1} = Z_0 (1 + A)$

$$F = 1 + \left[ \frac{1 + A}{A^2} \right] \quad \text{generator, } R_f$$

$$+ \frac{2q I_b Z_0 / 4}{kT} \left[ 1 + \frac{1 + A}{A} \frac{R_{bb} + R_{ex}}{Z_0} \right]^2 \quad \text{base shot}$$

$$+ \left[ \frac{1 + A}{A} \right]^2 \frac{R_{bb} + R_{ex} + r_e / 2}{Z_0} \quad \text{base thermal, } R_{ex} \text{ thermal, collector shot.}$$

Again use  $2q I_b = 2kT / \beta r_e$  to get another useful form:

$$F = 1 + \left[ \frac{1 + A}{A^2} \right] + \frac{1}{2\beta} \frac{Z_0}{r_e} \left[ 1 + \frac{1 + A}{A} \frac{R_{bb} + R_{ex}}{Z_0} \right]^2$$

$$+ \left[ \frac{1 + A}{A} \right]^2 \frac{R_{bb} + R_{ex} + r_e / 2}{Z_0}$$

finally, start approximating:

if  $R_{ex}$  is larger than  $r_e$ , then  $R_{ex} + r_e \cong r_e + R_{ex}$ .

we then get:

$$F \cong 1 + \left[ \frac{1+A}{A^2} \right] + \frac{1}{2\beta} \frac{Z_0}{r_e} \left[ 1 + \frac{1+A}{A} \frac{R_{bb} + R_{ex}}{Z_0} \right]^2$$

$$+ \left[ \frac{1+A}{A} \right]^2 \frac{R_{bb}}{Z_0} + \left[ \frac{1+A}{A^2} \right]$$

$R_{bb}$  thermal. ←  $R_{ex}$  thermal + collector shot

this is

$$F \cong 1 + 2 \left[ \frac{1+A}{A^2} \right] + \frac{1}{2\beta} \frac{Z_0}{r_e} \left[ 1 + \frac{1+A}{A} \frac{R_{bb} + R_{ex}}{Z_0} \right]^2$$

$$+ \left[ \frac{1+A}{A} \right]^2 \frac{R_{bb}}{Z_0}$$

if we can approximate that  $A+1 \cong A$ , we have:

$$F \cong 1 + \frac{2}{A} + \frac{Z_0}{2\beta r_e} \left[ 1 + \frac{R_{bb} + R_{ex}}{Z_0} \right]^2 + \frac{R_{bb}}{Z_0}$$

now, the findings here can be quite profound!