

## • Notes Set 7: First Look at Noise in Circuits

- pre-introduction of transistor noise models.
- circuit noise analysis.
- Total input referred noise voltage, total input referred noise current
- Short circuit input noise voltage. Open circuit input noise current,
- Noise figure, minimum noise figure and optimum source impedance.
- Friss Formula, available gain, noise measure, noise temperature.

ECE Notes Set 7

Now do

First look at noise in circuits


we have not yet finished noise  
in devices, so why the division?

Will want to talk about quantities  
like noise figure, etc; when we do  
talk about device noise.

So, will need to do initial treatment  
of noise in circuits now.

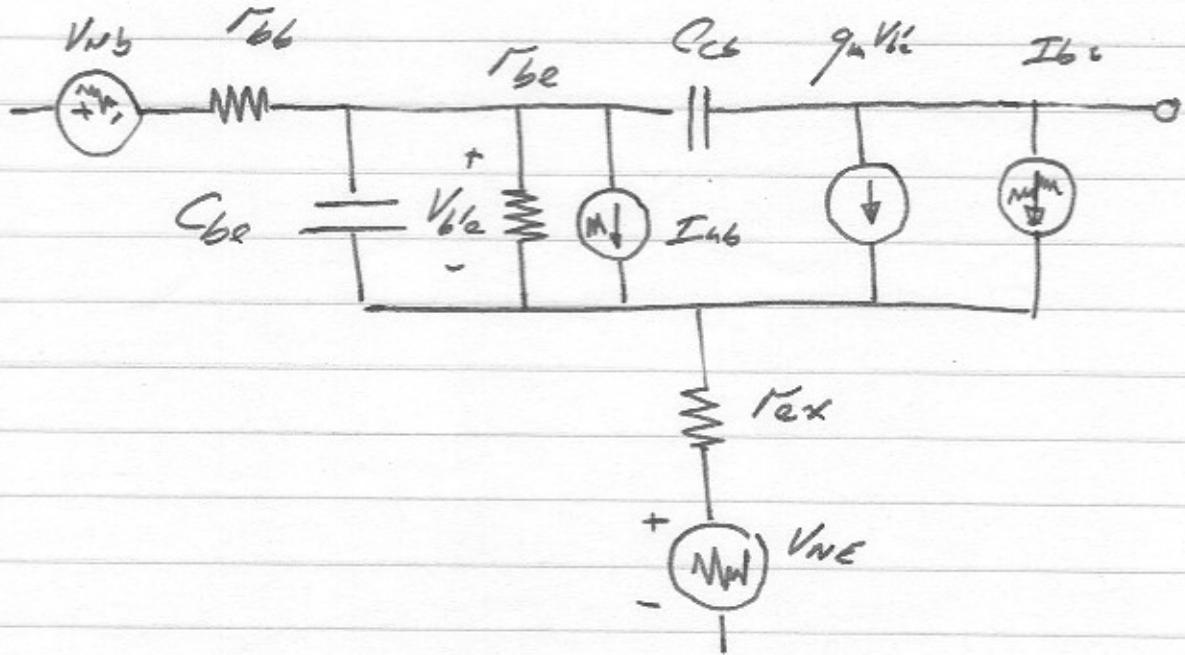(2)

We will show later that bipolar transistors have noise models like so:



where  $V_{Nb}$  &  $V_{ne}$  are the thermal noise


generators of  $R_{be}$  &  $R_{ex}$

&  $I_{nb}$  &  $I_{nc}$  are shot noise (later)

generators for the base & collector DC currents.

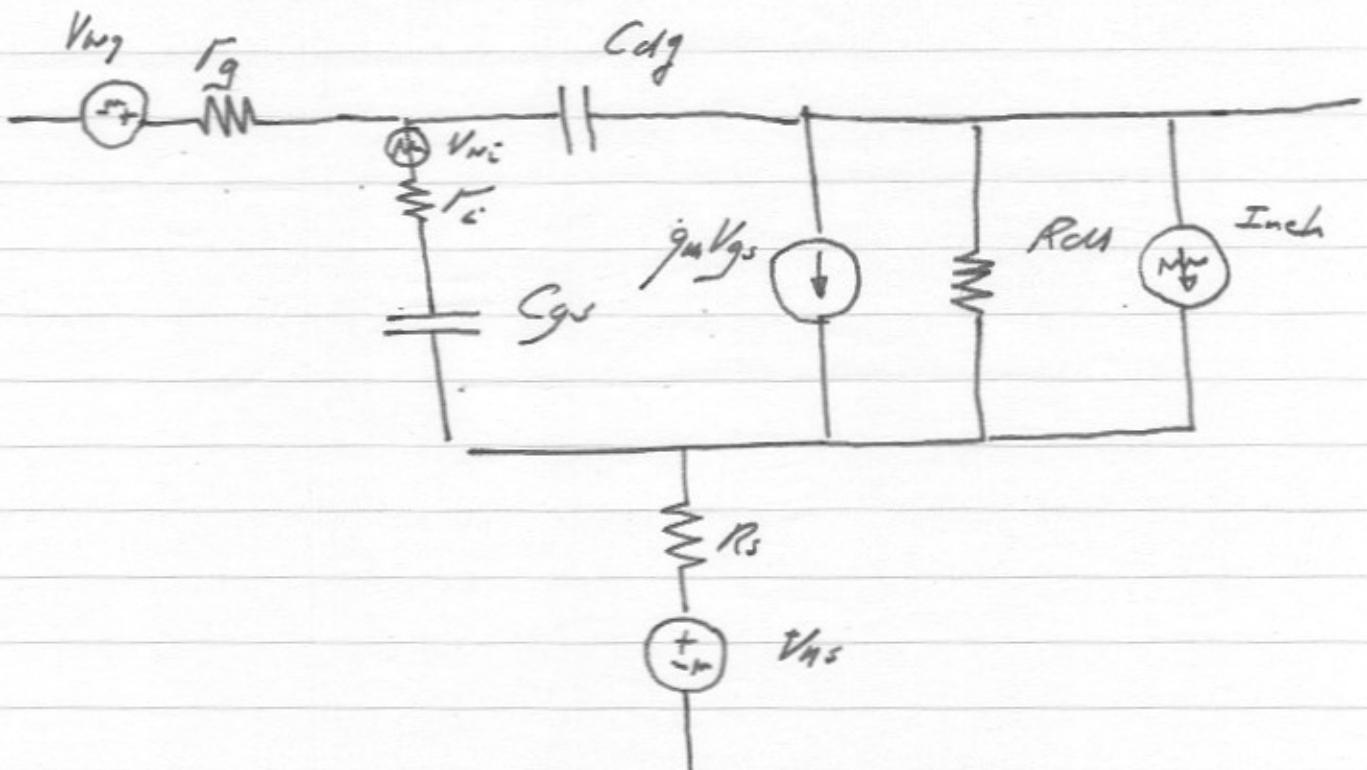(3)

Similarly, we will show that an FET  
can often be modelled like so:




where  $V_{ng}$ ,  $V_{ns}$ , are thermal noise generators for  
 $R_s$  &  $r_g$ .

$V_{in}$ , &  $V_{ni}$  are not strictly equilibrium noise  
sources & have perhaps a small correlation.


Again, we will develop these noise models soon. I need some device models now to support the circuit example which follows.
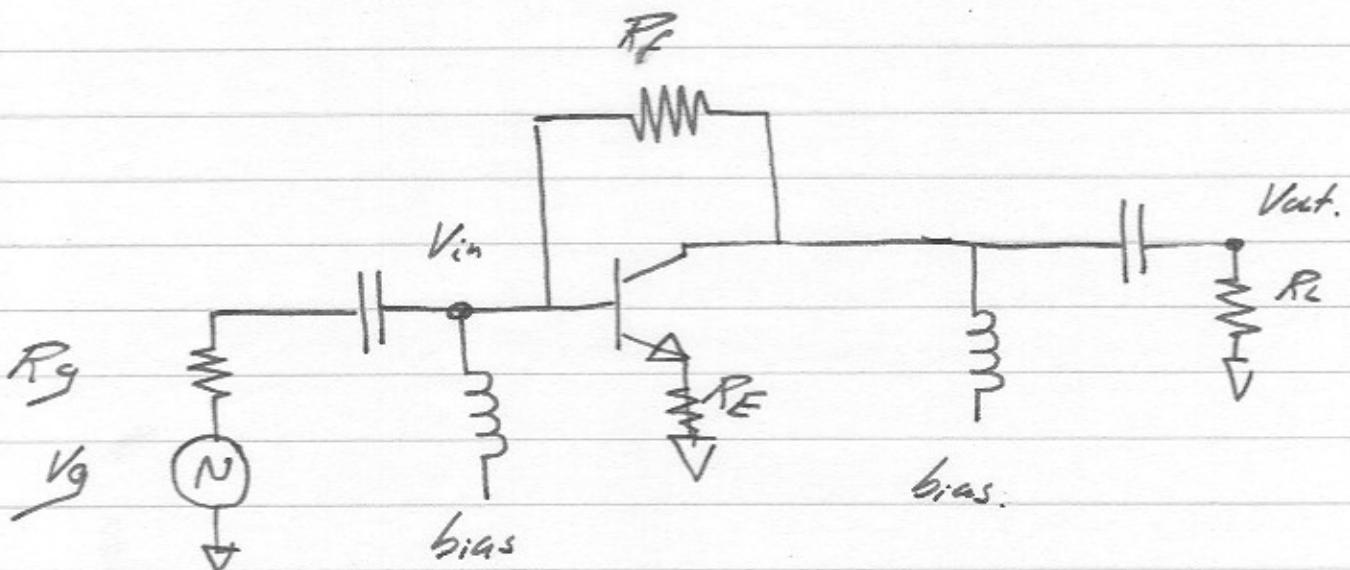
### Introduction to noise analysis in circuits:



The noise model of this circuit is as below:

- Small-Signal model shown -

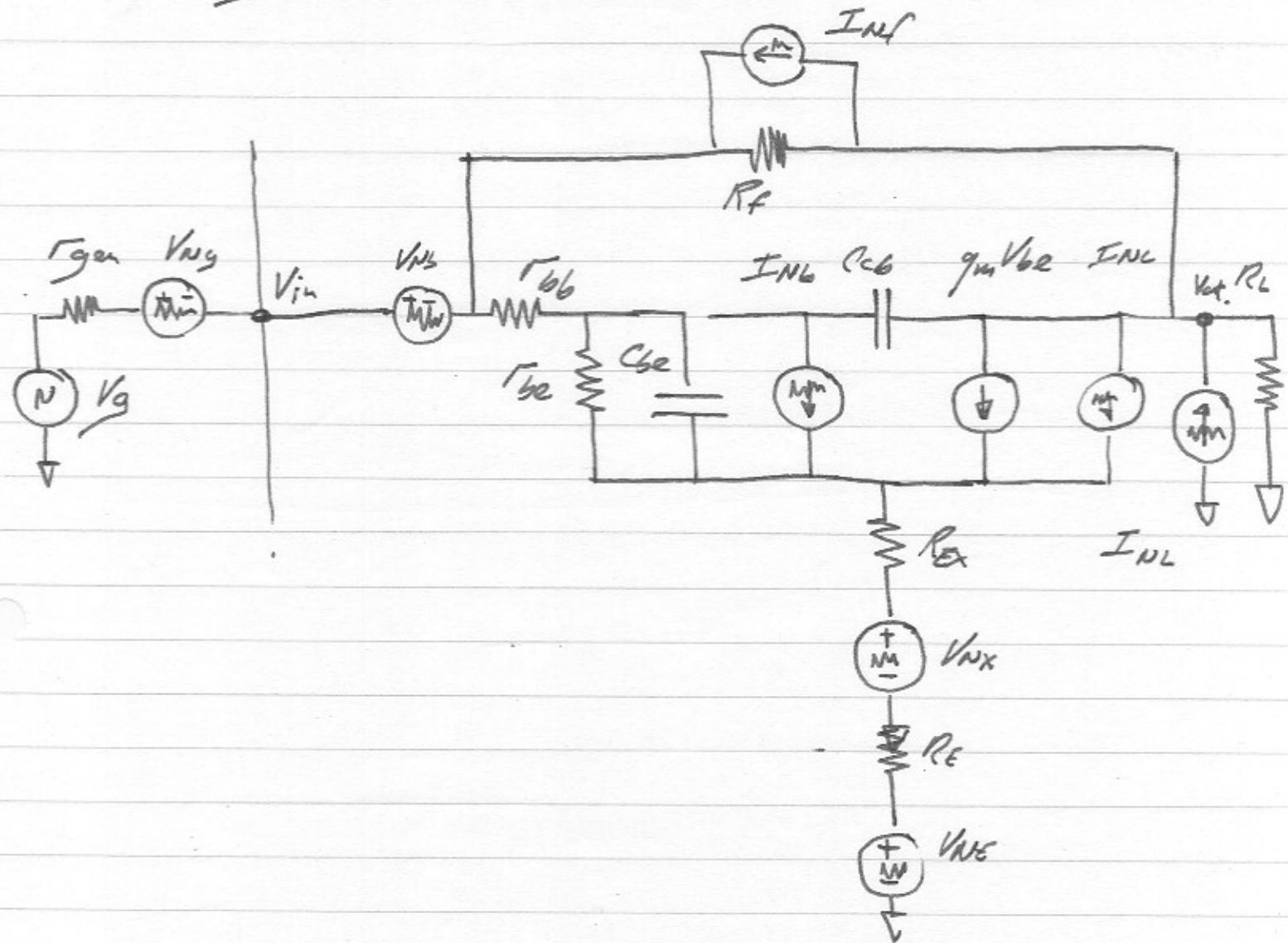

(6)

$V_{N\pi}$  thermal noise of  $R_E$

$V_{NG}$  " " "  $R_E$

$V_{Ng}$  " " "  $R_{gen}$

$I_{NL}$  " " "  $R_F$

$I_{NL}$  " " "  $E_{BE} R_L$

$V_{NG}$  " " "  $R_{bb}$

$I_{Ns}$  shot noise of base current

$I_{NC}$  " " " collector "

2 Noise sources are of particular sign.ificance:

$V_{Ng}$ : belongs to the generator.


#  $I_{NL}$ : belongs to the load

(7)

Again, it is not our purpose here today  
to learn how to solve this problem ~~effec-~~  
efficiently, or to make performance optimizations.

Instead, right now we are setting up  
some circuit noise definitions which  
we will need shortly...

## General Model:

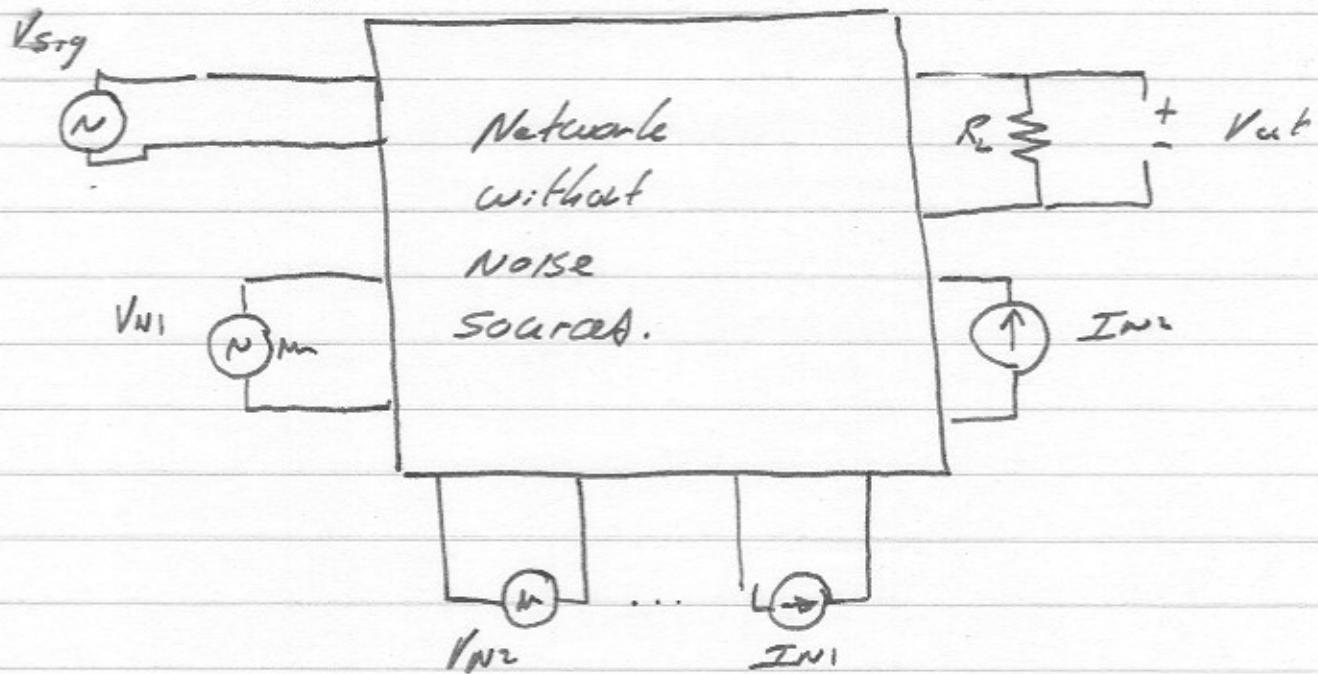

Here,

$$V_{out} = A V_{S,y} + A_1 V_{N1} + A_2 V_{N2} + \dots$$

$$+ Z_1 I_{in1} + Z_2 I_{in2} + \dots$$

This relationship is found by arduous circuit analysis. The first term is output signal, the remainder is output noise.

(9)

so, the output noise voltage is

$$V_{N, \text{out}} = A_1 V_{N1} + A_2 V_{N2} + \dots$$

$$+ Z_1 I_{M1} + Z_2 I_{M2} + \dots$$

now form

$$\frac{d}{dt} \langle V_{N, \text{out}} V_{N, \text{out}}^* \rangle$$

by multiplying the above by its complex conjugate

(10)

5c

$$\frac{\partial}{\partial f} \langle V_{\text{ault}} V_{\text{ault}}^* \rangle$$

 $\|A_i\|^2$ 

$$= \frac{\partial}{\partial f} \langle V_{N1} V_{N1}^* \rangle \quad . \quad A_1 A_1^*$$

$$+ \frac{\partial}{\partial f} \langle V_{N2} V_{N2}^* \rangle \quad . \quad A_2 A_2^*$$

+ ...

$$+ Z_1 Z_1^* \frac{\partial}{\partial f} \langle I_{N1} I_{N1}^* \rangle$$

$$+ Z_2 Z_2^* \frac{\partial}{\partial f} \langle I_{N2} I_{N2}^* \rangle$$

+ ...

$$\left\{ + A_1 Z_1^* \frac{\partial}{\partial f} \langle V_{N1} I_{N1}^* \rangle + Z_1 A_1^* \frac{\partial}{\partial f} \langle I_{N1} V_{N1}^* \rangle \right.$$

+ ...

(these  $(N^2-N)$  cross terms are zero if the noise sources are uncorrelated.)

At 5° we have (after substantial effort)

$$\text{calculated } \frac{2}{2f} \langle V_{\text{out}} V_{\text{noise}}^* \rangle$$

\* We also have determined that

$$V_{\text{out}} / \text{signal} = A \underline{V_{\text{gen}}}.$$


So we can lump all the noise generators

together into a single, fictitious, input.

referred total noise voltage

$$\frac{2}{2f} \langle V_{\text{in}, \text{in}} V_{\text{noise}}^* \rangle \stackrel{\Delta}{=} \frac{1}{AA^*} \frac{2}{2f} \langle V_{\text{out}}, V_{\text{noise}}^* \rangle$$

The picture is as follows:-

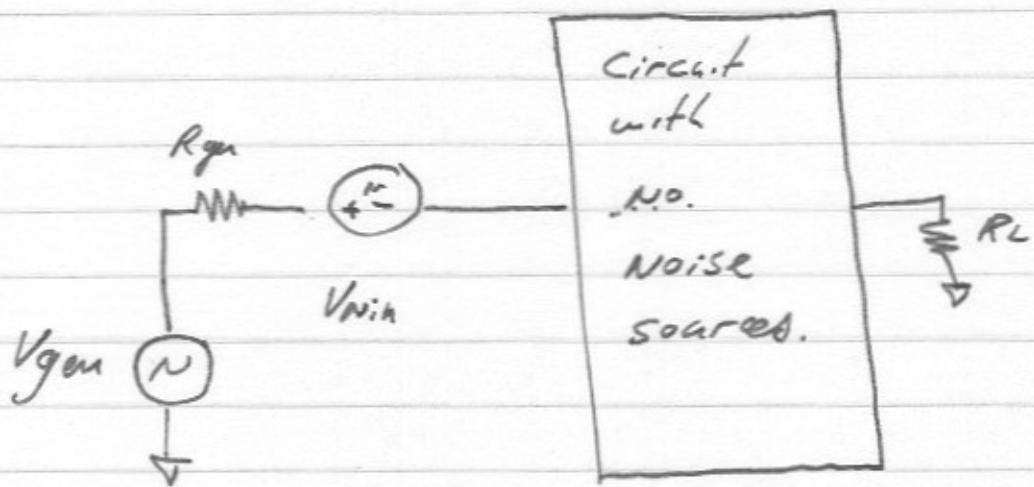

$V_{Nin}$  keeps together

all amplifier noise terms

the generator noise


the noise of the load.

Further,  $V_{Nin}$  as given depends explicitly on

$R_{gen}$ .


[This description may or may not be useful...]

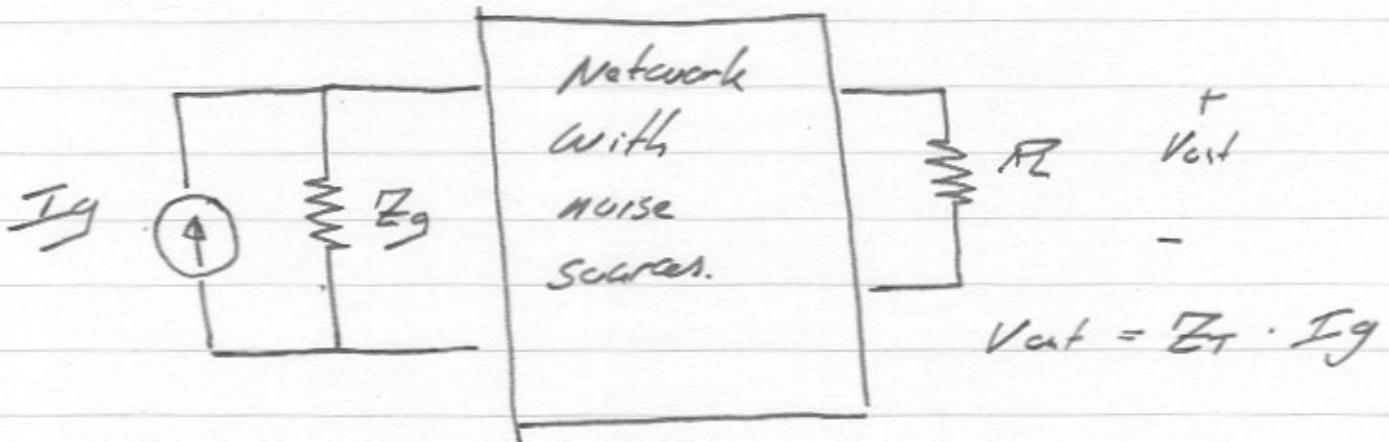In a similar way, if the input signal source is a current source:



We can define an output referred noise current:
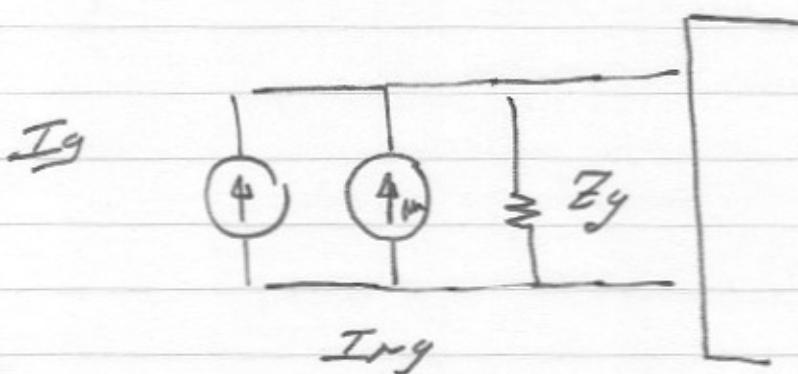
$$\frac{\partial}{\partial f} \langle I_{in} I_{in}^* \rangle = \frac{1}{Z_T Z_T^*} \frac{\partial}{\partial f} \langle V_{out} V_{out}^* \rangle$$



Again note that:

- \*  $I_{in}$  defined above is the total input-referred noise current
- \*  $I_{in}$  includes the noise of the generator, amplifier, and load.
- \*  $I_{n, in}$  depends explicitly on the generator impedance.

$I_{N,in}$ , the total input noise current will be useful when the generator is a current  $I$  when we have a known & specified generator impedance.

$V_{N,in}$ : similar applicability, but when generator is a voltage...


---

We will also want descriptions of circuit noise which are useful over the range of possible generator impedances.


This model should therefore not include the generators' noise.

~~Cleaning up from last time:~~

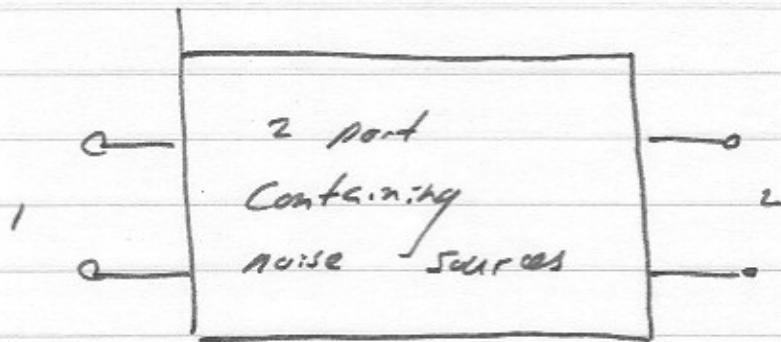From Thvenin's formula, a 2-port with  
many noise sources:



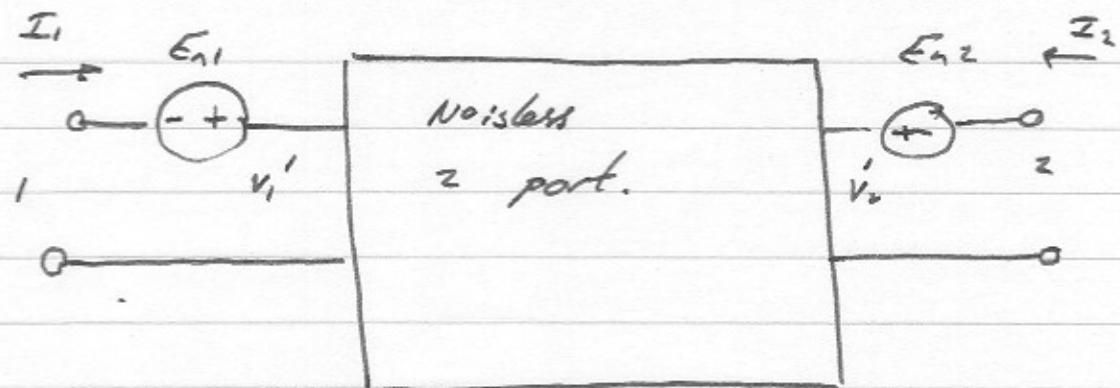can be modelled as a sourceless network with  
open-circuit noise voltages at each port.  
These will be possibly correlated.



If the noiseless 2-port has:


$$\begin{bmatrix} V_1' \\ V_2' \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

and  $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_1' \\ V_2' \end{bmatrix} + \begin{bmatrix} E_{n1} \\ E_{n2} \end{bmatrix}$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 = E_{n1}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 = E_{n2}$$

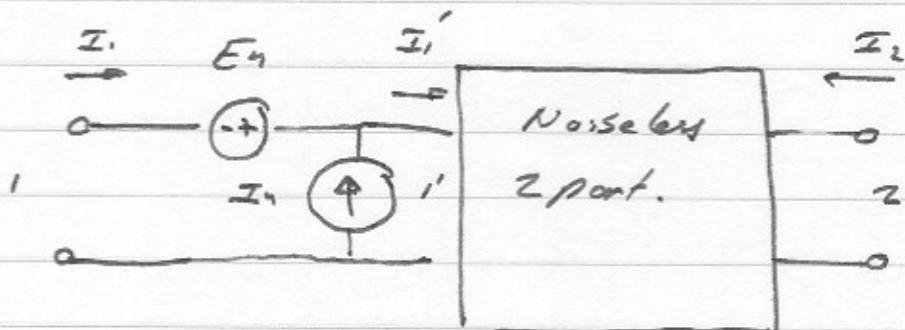Can we instead model the 2-port as below:



15c

~~16~~

This would give

$$V_1 = Z_{11}(I_1 + I_4) + Z_{12}I_2 - E_h$$

$$V_2 = Z_{21}(I_1 + I_4) + Z_{22}I_2$$

which is the same if we set

$$I_4 = -\frac{E_h}{Z_{21}}$$

and


$$E_h = E_{h1} + \frac{Z_{11}}{Z_{21}} E_{h2}$$

.. This proves that the  $(E_h, I_4)$  model

is completely general for a 2-port.

To create this model, look at a range of generator impedances:

First short the input

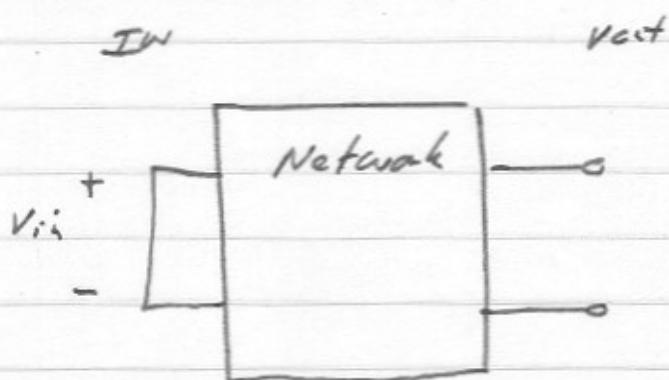


- and measure or calculate  $V_{out}$

Divide by the voltage gain from input to output:  $V_{out} = A_V \cdot V_{in}$  to get

$$\frac{2}{2f} \langle V_N V_N^* \rangle = \frac{1}{A_V A_V^*} \left[ \frac{2}{2f} \langle V_{out} V_{out}^* \rangle \right]_{\text{input open}}$$

This is called the equivalent short circuit input noise voltage

Then make the input an open:

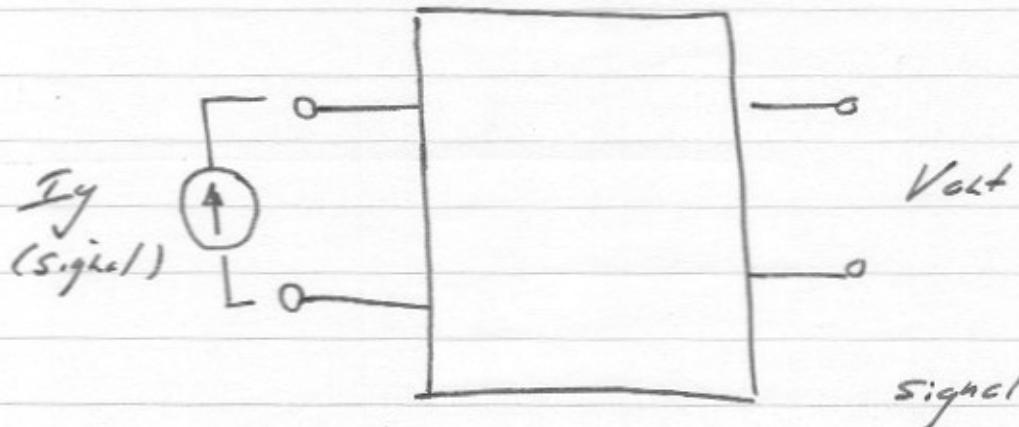

$$\text{signal: } V_{\text{out}} = Z_T I_g$$

... and measure or calculate  $V_{\text{out}}$ .

Divide by the gain from input to output to get

$$\frac{2}{2f} \langle I_{\text{in}} I_{\text{in}}^* \rangle = \frac{1}{Z_T Z_T^*} \left[ \frac{2}{2f} \langle V_{\text{out}} V_{\text{out}}^* \rangle \right]$$

input shorted.

This is called the equivalent open circuit input noise current.


We will also find that these two quantities (noise generators) are correlated.

With the tools I have given you thus far, finding this correlation would require some inefficient method, such as applying a 1Ω generator impedance.

We will cover better methods later.

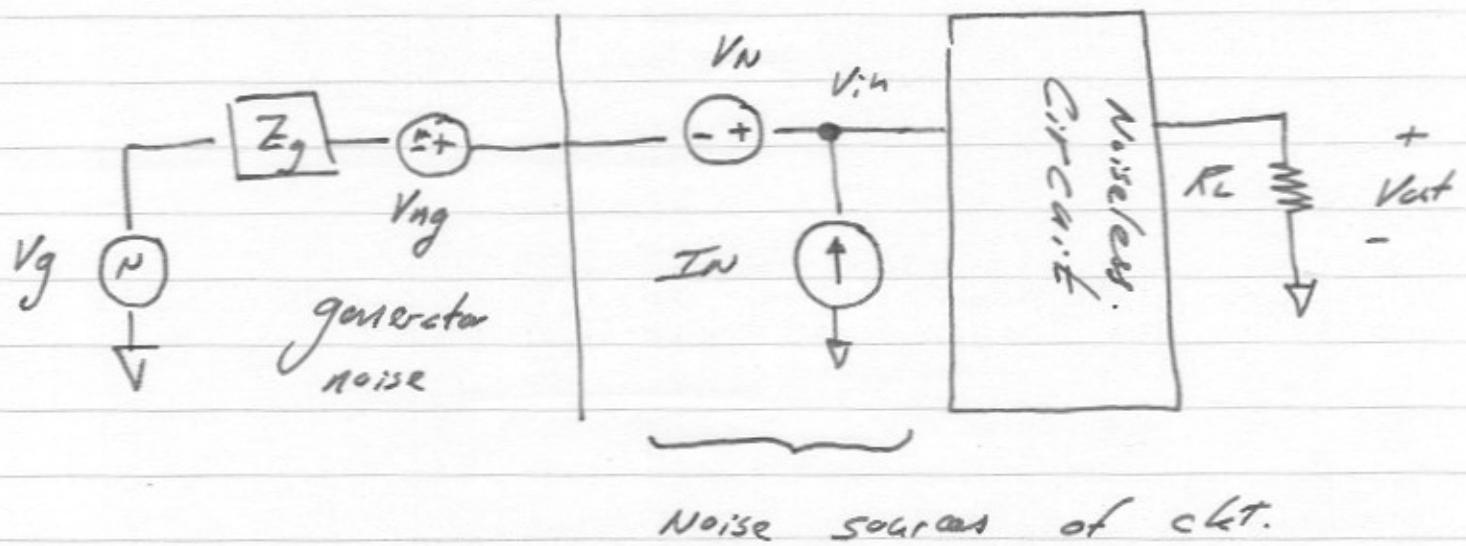(19)

so, in general we can model the amplifier noise as below:



required parameters:

$$\frac{\partial}{\partial f} \langle V_N V_N^* \rangle, \frac{\partial}{\partial f} \langle I_N I_N^* \rangle, \frac{\partial}{\partial f} \langle V_N I_N^* \rangle$$

We can now calculate the input noise voltage  
generator noise.

$$V_{in} = \left\{ V_g + V_{Ng} + V_N + IN Z_g \right\} \cdot \frac{Z_{in}}{Z_{in} + Z_{gen}}$$

↑                      ⌊ Total input referred  
 Signal                  noise voltage  
 V<sub>NT</sub>

So, the total input referred noise voltage is:


$$\begin{aligned}
 \frac{2}{2f} \langle V_{NT} V_{NT}^* \rangle &= \frac{2}{2f} \langle V_N V_N^* \rangle \\
 &\quad + Z_g Z_g^* \frac{2}{2f} \langle IN I_N^* \rangle \\
 &\quad + 2 \cdot R_E \left[ \frac{2}{2f} \langle V_N I_N^* \rangle \cdot Z_g^* \right]
 \end{aligned}$$

which shows explicitly the dependence upon  $Z_g$ .

(21)
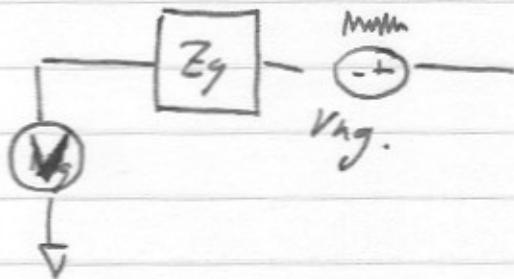
## Noise Figure

A measure of the change in signal/noise ratio incurred in using an amplifier.



Available signal power from generator is

$$P_{AV,S} = \frac{V_g V_g^*}{4 \cdot \text{Re}\{Z_g\}}$$

Available noise power from generator is:

$$\frac{2}{2f} \langle P_{AV,N} \rangle = kT = \frac{2}{2f} \langle V_{ng} V_{ng}^* \rangle \cdot \frac{1}{4 \cdot \text{Re}\{Z_g\}}$$


The Signal/Noise ratio of the generator is:

$$\frac{P_{AV, S}}{\left[ \frac{2}{\Delta f} \langle P_{AV, N} \rangle \right]} = \frac{S}{N_{gen}}$$

units are  $\frac{W}{W/Hz} \rightarrow Hz$

[usually stated as dB in a 1Hz noise bandwidth]  
 "5/W" = 30 dB (1Hz)"

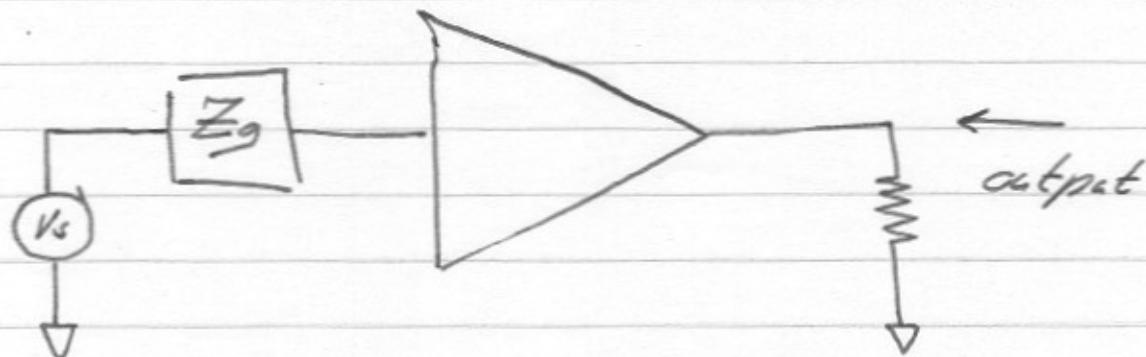Connect the Signal Generator to an amplifier:



there will be some output signal power  $P_{out,S}$

& some output noise power spectral dens.t:  $\frac{2}{2f} \langle P_{out,N} \rangle$

The output S/N ratio is:

$$\frac{S}{N}_{out} = \frac{P_{out,S}}{\frac{2}{2f} \langle P_{out,N} \rangle}$$

Hz.

The Noise figure is:

$$F = \left( \frac{S}{N} \Big|_{\text{generator}} \right) \parallel \left( \frac{S}{N} \Big|_{\text{out}} \right)$$


with the generator being a thermal noise source at temperature  $T$ .

Noise figure is usually set up so that the noise of the load is not calculated in the calculations.

Noise figure is a prime measure of the loss in signal quality due to the amplifier.

Let's calculate the noise figure:

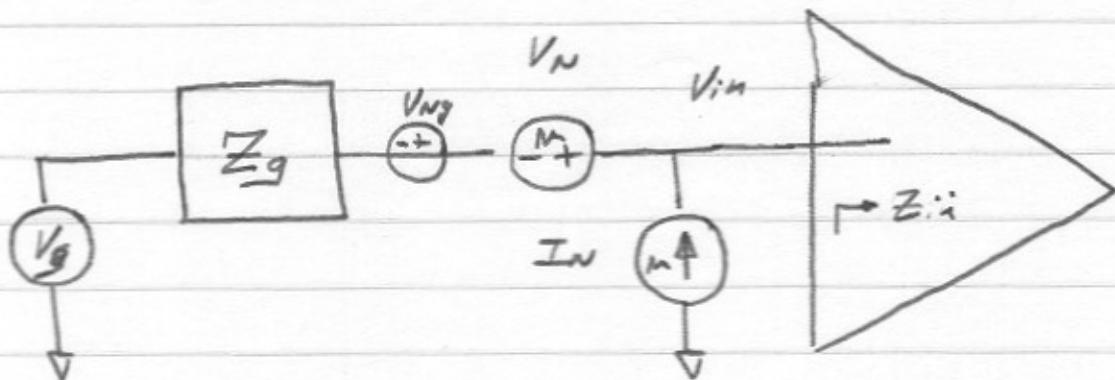start from  $V_N \cdot I_N$  description:



$$V_{in} = \underbrace{(V_g + V_{Ng} + V_N + Z_g I_N)}_{V_{Th}} \cdot \frac{Z_{in}}{Z_{in} + Z_g}$$

$$V_{Th} = \underbrace{V_g}_{\text{Signal}} + \underbrace{V_{Ng}}_{\text{noise}} + \underbrace{V_N}_{\text{amplifier}} + \underbrace{Z_g I_N}_{\text{noise}}$$

Signal gen  
noise  
amplifier  
noise.

$$\text{Av. Signal power} = V_s V_s^* / 4 R_L \{ Z_g \}$$

$$\text{Av. Noise power, generator} = kT = [4 R_L \{ Z_g \}]^{-1} \cdot \frac{d}{df} \langle V_{Ng} V_{Ng}^* \rangle$$

Total Noise power:

$$\frac{d \langle P_{RF} \rangle}{dt} = \left[ \frac{\partial}{\partial t} \langle V_{Ng} V_{Ng}^* \rangle + \frac{\partial}{\partial t} \langle V_N V_N^* \rangle \right] \\ + \frac{\partial}{\partial t} \langle I_N I_N^* \rangle Z_g Z_g^* + 2 \operatorname{Re} \left[ Z_g^* \frac{\partial}{\partial t} \langle V_N I_N^* \rangle \right] \\ \times \left[ 4 \operatorname{Re}[Z_g] \right]^{-1}$$

Since I have input referred all quantities,

I Need look at only the ratio of generator to total noise:

---


$$F = 1 + \frac{\frac{\partial}{\partial t} \langle V_N V_N^* \rangle + Z_g Z_g^* \frac{\partial}{\partial t} \langle I_N I_N^* \rangle + 2 \operatorname{Re} \left[ Z_g^* \frac{\partial}{\partial t} \langle V_N I_N^* \rangle \right]}{4 \cdot K \cdot T \operatorname{Re}[Z_g]}$$


---

This noise figure is clearly a function of

- the amplifier

$$\left[ \frac{2}{2f} \langle V_n V_n^* \rangle, \frac{d \langle V_n I_n^* \rangle}{df} \right]$$

$$+ \frac{d}{df} \langle I_n I_n^* \rangle$$

- and the generator impedance  $Z_g$ .

... This noise figure will vary with generator impedance  $Z_g$ .

$\left[ \begin{matrix} \text{There is a minimum noise figure \&} \\ \text{an optimum source impedance} \end{matrix} \right]$

what are these?

If we write  $Z_g = R_g + jX_g$ , then

$$4kT(F-1) = \frac{1}{R_g} \frac{\partial}{\partial f} \langle V_h V_h^* \rangle + R_g \cdot \frac{\partial}{\partial f} \langle I_h I_h^* \rangle$$

$$+ \frac{X_g^2}{R_g} \cdot \frac{\partial}{\partial f} \langle I_h I_h^* \rangle$$

$$+ 2 \cdot \operatorname{Re} \left[ \frac{\partial}{\partial f} \langle V_h I_h^* \rangle \right]$$

~~$$= 2 \frac{X_g}{R_g} \cdot I_h \left[ \frac{\partial}{\partial f} \langle V_h I_h^* \rangle \right]$$~~

Taking derivatives, w.r.t  $X_g$ ,  $F$  is minimal

when

$$X_{g_{opt}} = - \operatorname{Im} \left[ \frac{\partial}{\partial f} \langle V_h I_h^* \rangle \right] / \frac{\partial}{\partial f} \langle I_h I_h^* \rangle$$

which leaves the noise figure as:

$$4kT(F-1) = \frac{1}{R_g} \left[ \frac{2}{2f} \langle v_n v_n^* \rangle - \frac{\left[ I_m \cdot \frac{2}{2f} \langle v_i i^* \rangle \right]^2}{\frac{2}{2f} \langle i i^* \rangle} \right] + R_g \left[ \frac{2}{2f} \langle i_n i_n^* \rangle \right] + 2 R_i \left[ \frac{2}{2f} \langle v_i i^* \rangle \right]$$

To take derivatives wrt  $R_g$  to find:

$$\begin{aligned} \left( \frac{\partial}{\partial R_g} \right) &= \frac{\left[ \frac{2}{2f} \langle v_n v_n^* \rangle - \frac{\left[ I_m \left[ \frac{2}{2f} \langle v_i i^* \rangle \right] \right]^2}{\frac{2}{2f} \langle i i^* \rangle} \right]}{\frac{2}{2f} \langle i_n i_n^* \rangle} \\ &= \frac{\frac{2}{2f} \langle v_n v_n^* \rangle}{\frac{2}{2f} \langle i_n i_n^* \rangle} - \frac{\left[ I_m \left( \frac{2}{2f} \langle v_i i^* \rangle \right) \right]^2}{\frac{2}{2f} \langle i_n i_n^* \rangle} \end{aligned}$$

And the minimum noise figure is:

$$4K\Gamma(F-1) =$$

$$2 \cdot \sqrt{\frac{2 \langle V_a V_a^* \rangle}{2f} \cdot \frac{2 \langle I_a I_a^* \rangle}{2f} - \left[ \text{Im} \left( \frac{2}{2f} \cdot \langle V I^* \rangle \right) \right]^2} + 2 \cdot \text{Re} \left[ \frac{2}{2f} \langle V I^* \rangle \right]$$


I am not sure what I have accomplished here.  
 and I think I have a sign error  
 on  $\left[ \frac{2}{2f} \langle V I^* \rangle \right]$

Friss Formula for noise figure:

Available gain: power gain of an amplifier with the output matched to the load.

$$G_A = \frac{P_{AVD}}{P_{AVG}}$$

Noise of a cascade of amplifiers:

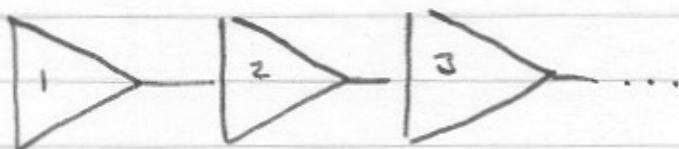

$$F = 1 + F_1 + \frac{F_2 - 1}{G_{AV1}} + \frac{F_3 - 1}{G_{AV1} G_{AV2}}$$

where the noise figures of the individual amplifiers are computed given a generator impedance at the prior state. The available gain of the amplifier in question is also calculated using the generator impedance of the prior stage.

## Noise Measure

One peculiarity of noise figure is that any device has poorer noise figure than a wire. Clearly  $F$  is not a good figure of merit, as minimizing  $F$  is accomplished by never amplifying.

Define  $(1+M)$ , the noise measure, as the noise figure of an  $\infty$  gf chain of amplifiers...


$$\frac{F}{\text{char}} = \sqrt{1 + \frac{F-1}{1 - 1/G_{\text{av}}}} = 1 + M$$

$F_{\text{av}} = 1+M$  is a better measure of quality for low-gain devices.

Again, the Friis Noise formula uses the available gain:

$$G_A = \frac{\text{Power Available from amplifier}}{\text{Power Available from generator.}}$$

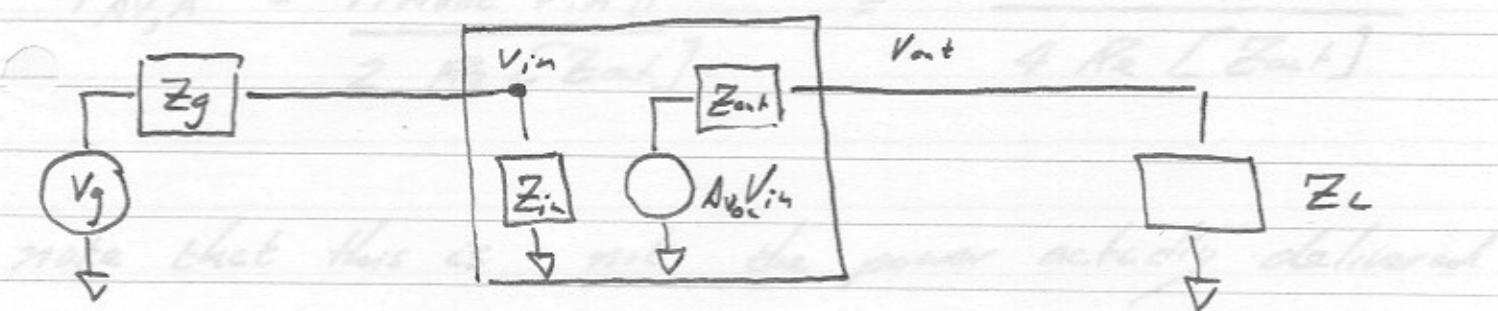Let's derive  $G_A$  for a simple unilateral amplifier.



so the  $Av_{oc}$  is the open-circuit voltage gain.

Power available from generator

$$P_{AV\_g} = \frac{V_g V_g^*}{4 R_e [Z_g]}$$

so:

$$\frac{P_{AV\_g}}{P_{AVG}} = (\text{load}) \parallel Z_m \parallel \frac{R_e [Z_g]}{R_e [Z_g] + R_e} = G_A$$