

• Notes Set 1: Motivation

- scope of topics, from physics, devices, circuits, to systems

ECE 594, Lecture Notes set 1

Motivation Lecture: Agenda of Course.

Noise is not a secondary topic
the fundamental factor in

determining communication system,
measurement system, & control system
performance.

Noise, as a topic, is too broad to consider in a single course:

math

physics

device theory

circuits

systems: hardware perspective

system: analytical perspective.

Interaction theory.

our agenda in the course will be as below:

- * Enough math to be competent.
- * A quick skim-through of physics of noise.
- * Noise models of semiconductor devices.
- * Heavy emphasis on circuits.
- * Heavy emphasis on systems' hardware.
Comm. systems, instrumentation.
- * Re-visiting noise models of T_k and noise in physics later in term.
- * In the last 1-2 lectures, skim other related topics.


(4)

What is the course really about?

Here are some examples of problems we would like to find easy to solve once the term is over:


First Problem:

bipolar transistor:

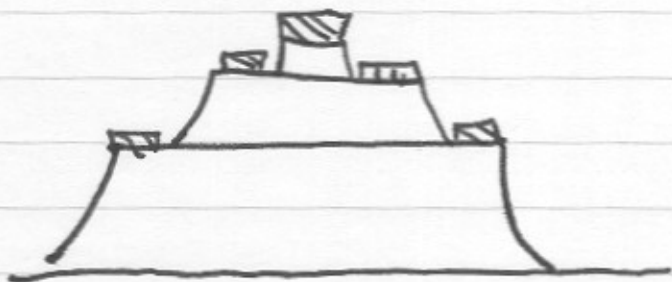

- how does impedance-matching network on input change S/N ratio?
- how does base resistance, transit times?
- how would we design for best noise?

Microphone preamplifier

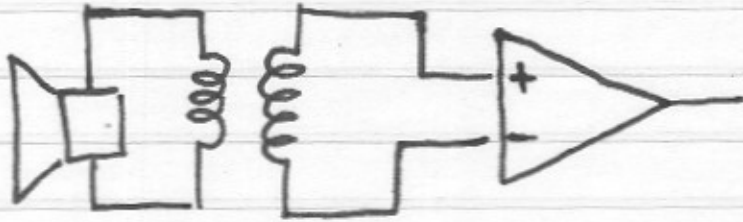


Why is a transformer used?

What ratio?

← What signal levels from microphone
might we reasonably detect?

Optical receiver:

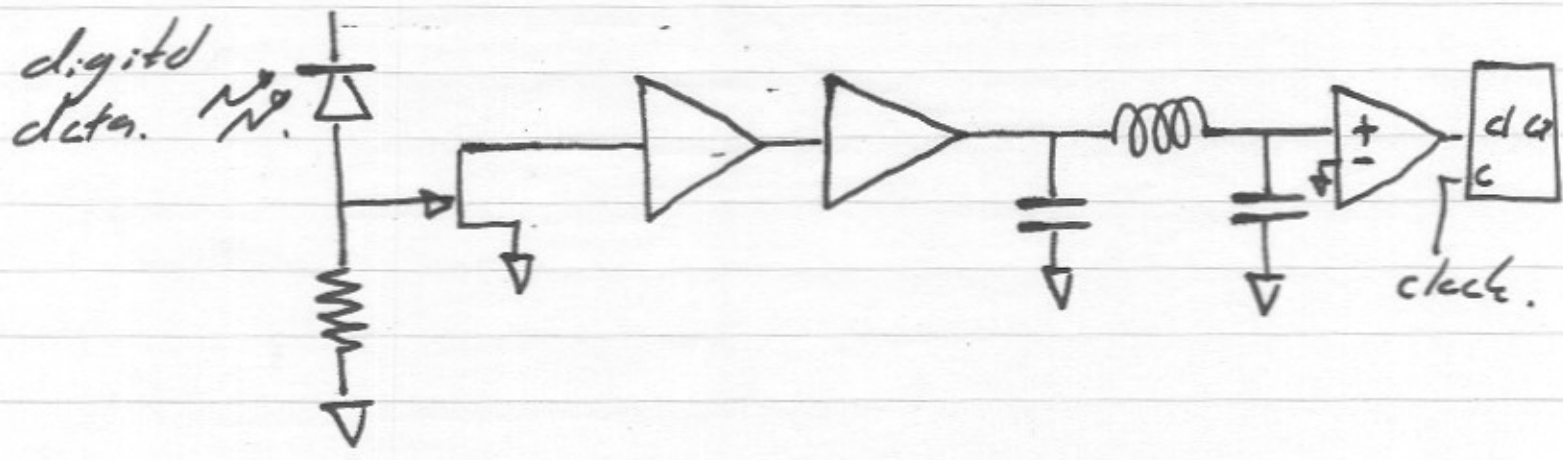


|| what is the minimum detectable power?

|| How does error rate change with power?

|| How to design preamplifier for best sensitivity?

|| what are the filter, comparator, & flip-flop for?

Electro-optic Sampling:

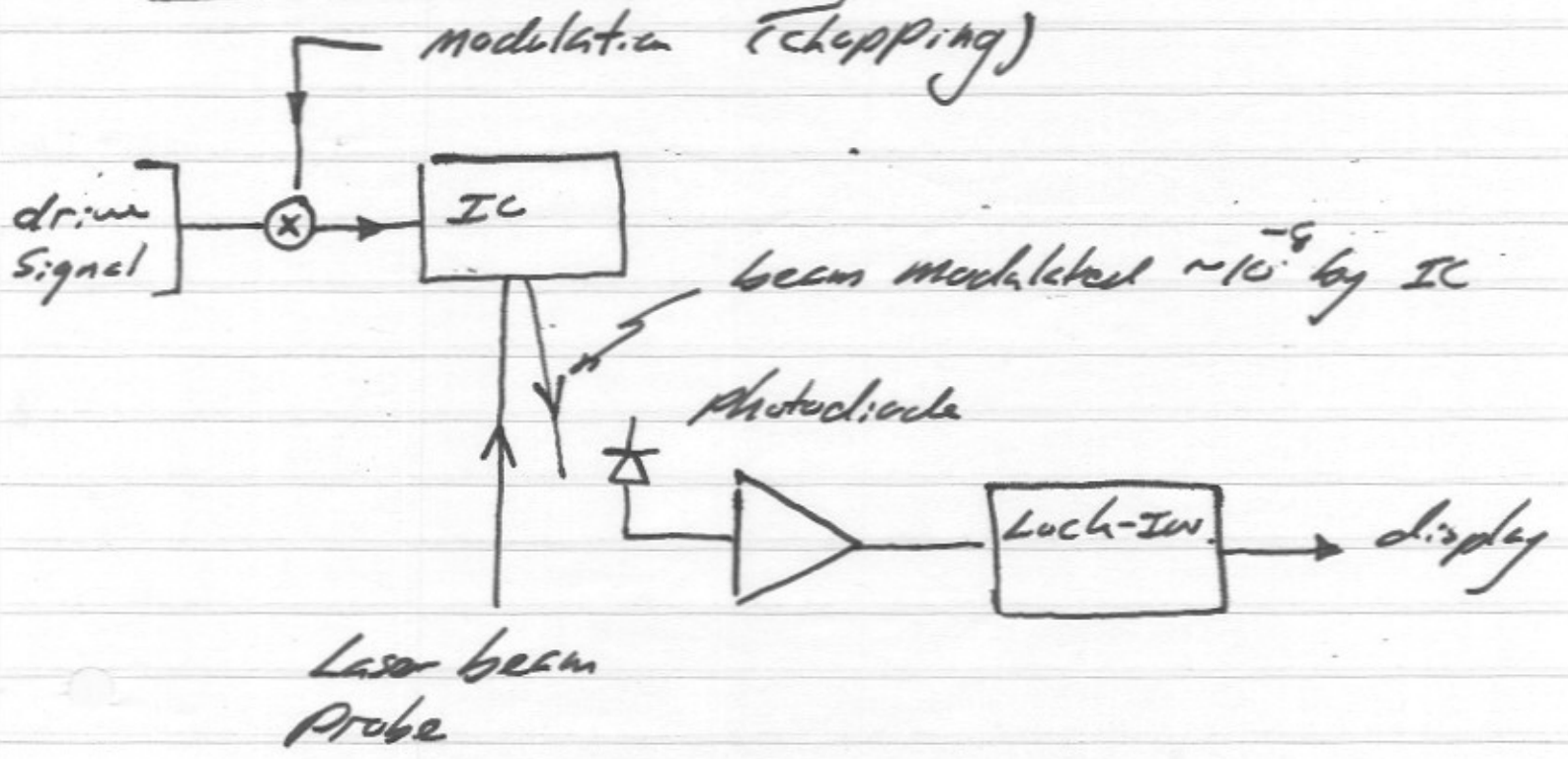


why are we modulating the signal?

what is a lock-in amplifier?

How small a signal can we measure?

Phase locked Loop

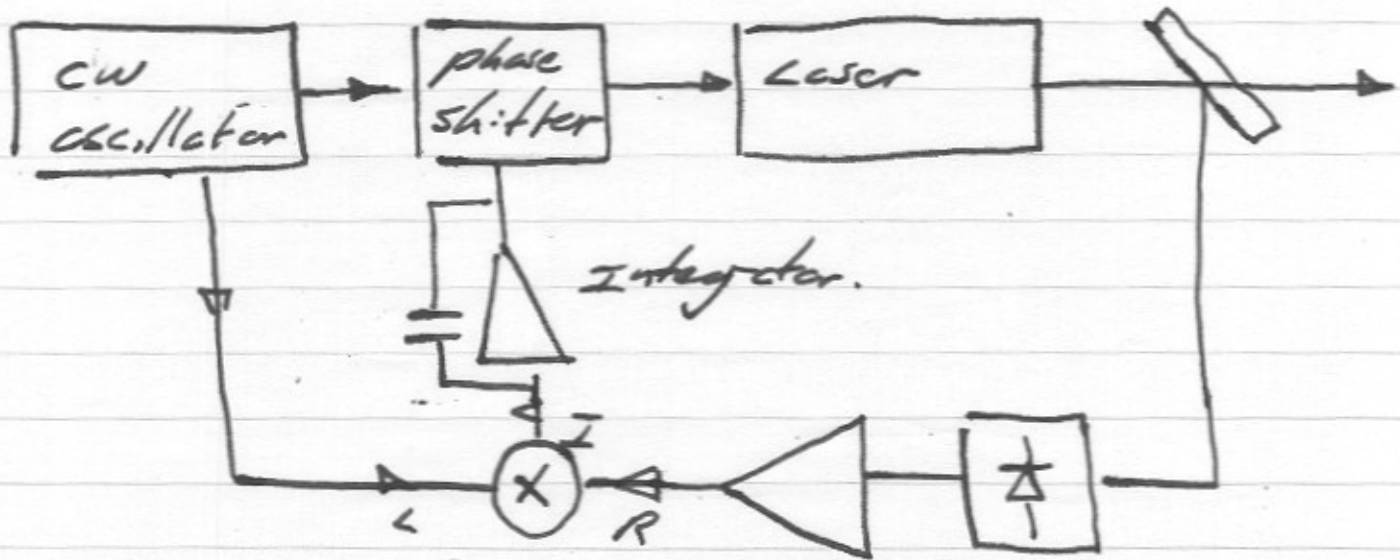

Laser has timing jitter,


phase lock loop suppresses it.

How do we measure / describe "jitter"

How much does loop suppress it?

How does mixer & amplifier noise figure impact system?


Photon Number Amplifier

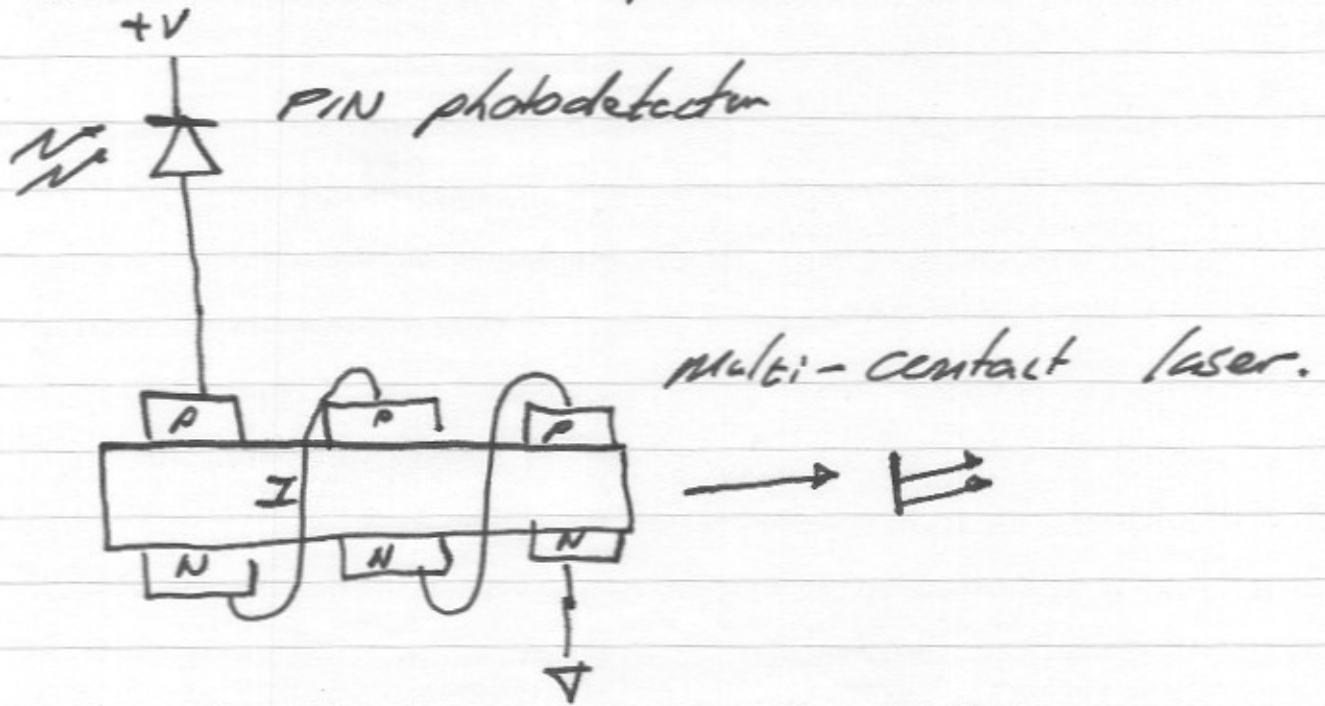

how does optical SN ratio change from input to output?


Is this a noiseless amplifier?

Resonant-tunnel-diode:

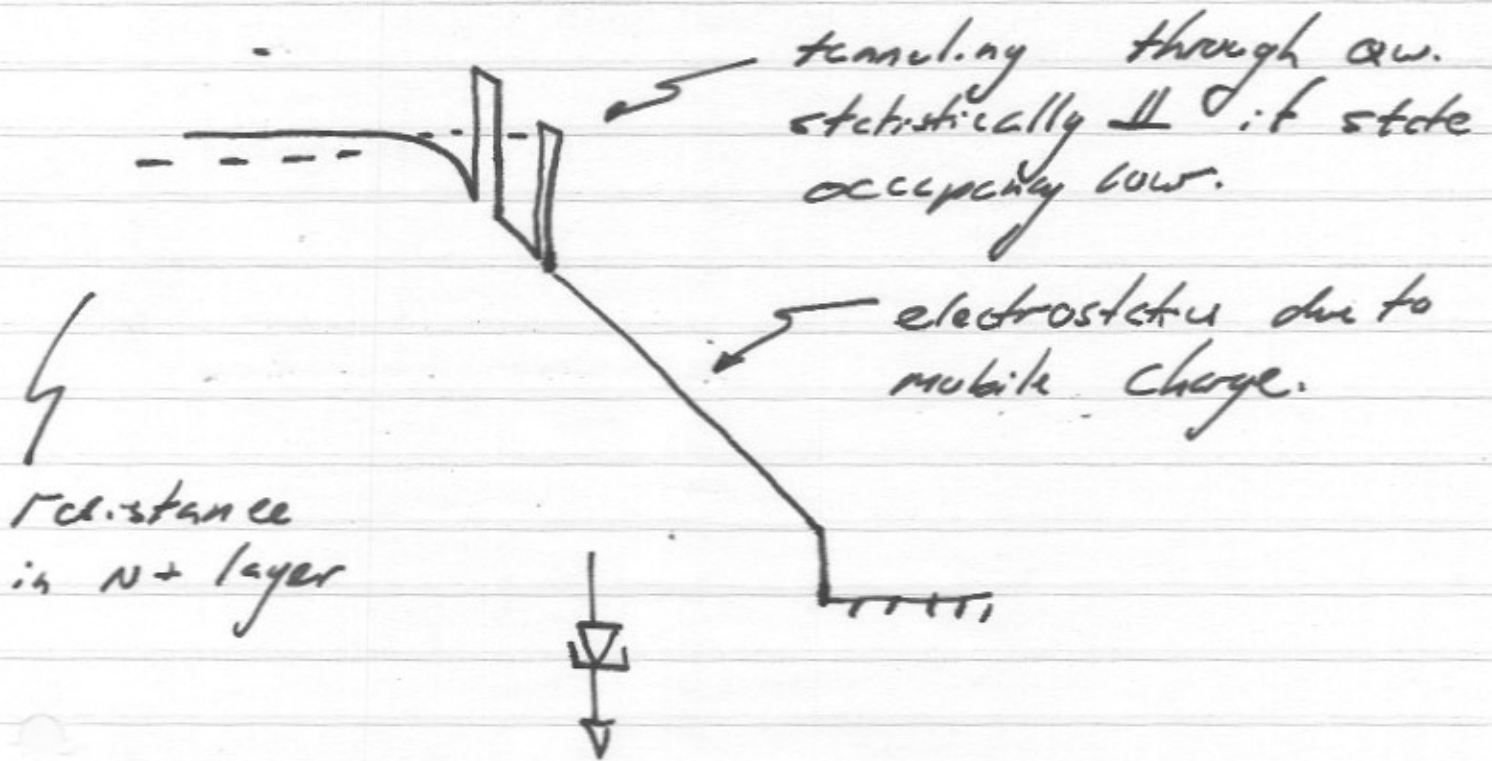

How do we predict the noise contribution of this device?

Input

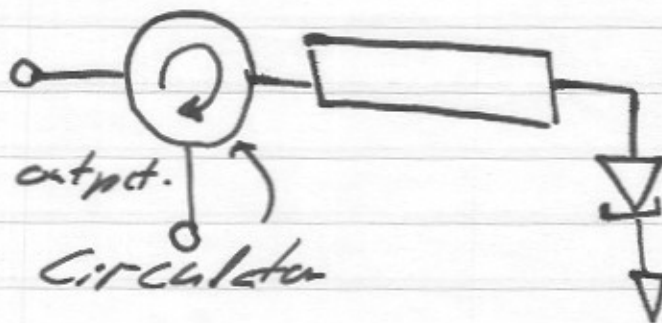


what are the noise properties of this amplifier?

Our objective is to study underlying material with enough detail to be able to confidently give the right answer to these types of problems.

This requires more care than a "practical engineers" class.

example:

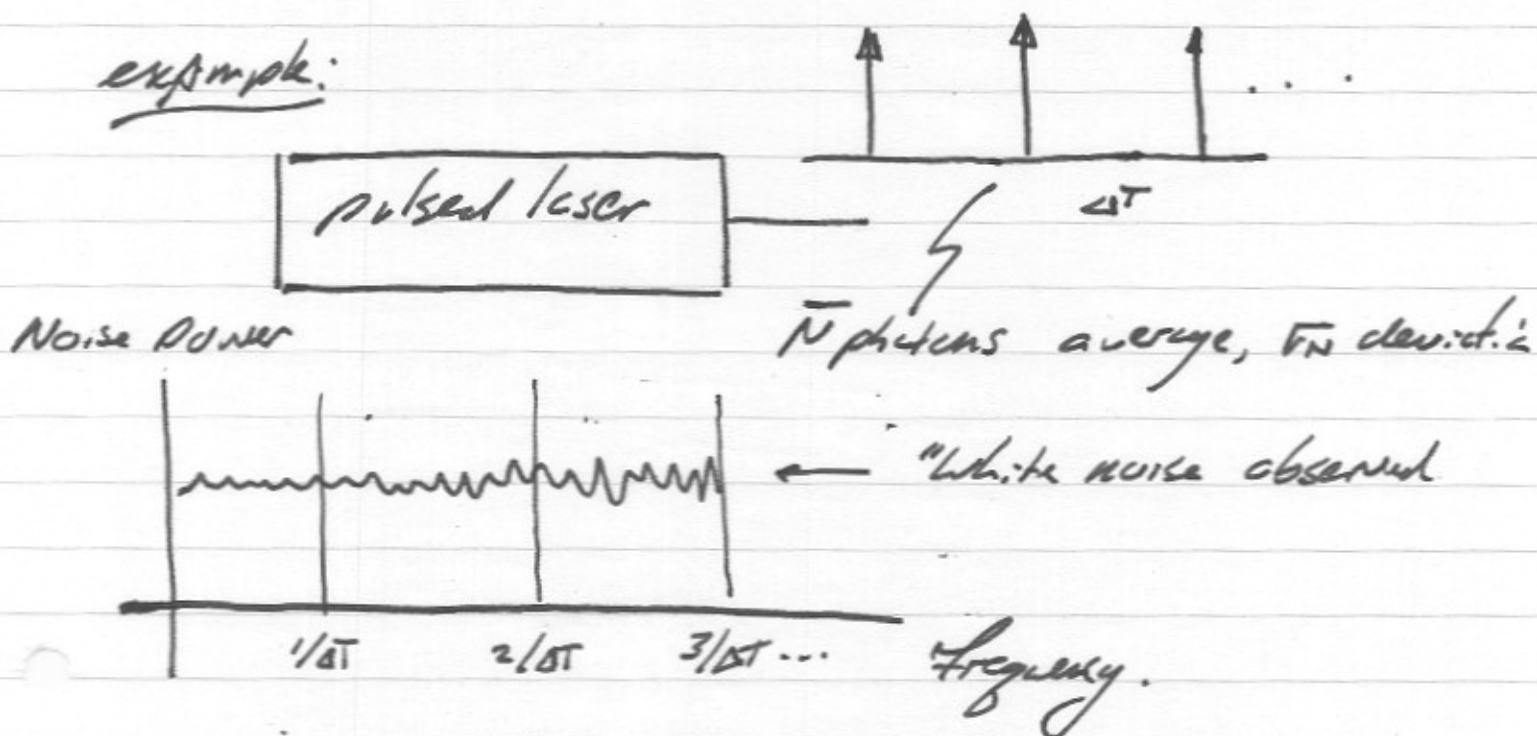

Should receiver bandwidth $\approx 1/\Delta T$??

References we will use cautiously:

Van Der Ziel: Noise in Solid State Devices

Matthienbacher: Low Noise Electronic Design.

Vendelin: Microwave Circuit Design.

Bell Labs: Transmission systems for
communication.

IEEE Paper collections:

Pavel: MMICs

Fukui: Low Noise transistors.

•
••
••• Microwave Digital Radio.

Smith & Personik: Optical Receivers.

Wozencraft & Jacobs:

Principles of Communications
engineering.

Alukhand semiconductor - Linear Applications

Grey & Meyer: Analog IC design.

Papoulis: Probability - random variables.