

*High Speed Mixed Signal IC Design*  
*Notes set 5:*  
*Digital IC design at the Gate level*

*Mark Rodwell*

*University of California, Santa Barbara*

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

# High speed digital IC design at the transistor level

ECL and CML gate designs, DC design

circuit structures for and / or / xor / latches ...


large-signal delay analysis, design for high speed

transmission line interconnects, signal distribution

power-delay relationships


# Basic Gates, Logical Description

And

 

	A=1	A=0
B=1	C=1	C=0
B=0	C=0	C=0

OR

 


	A=1	A=0
B=1	C=1	C=1
B=0	C=1	C=0

XOR  
(exclusive OR)




	A=1	A=0
B=1	C=1	C=0
B=0	C=0	C=1

# ECL gate, circa ~1965

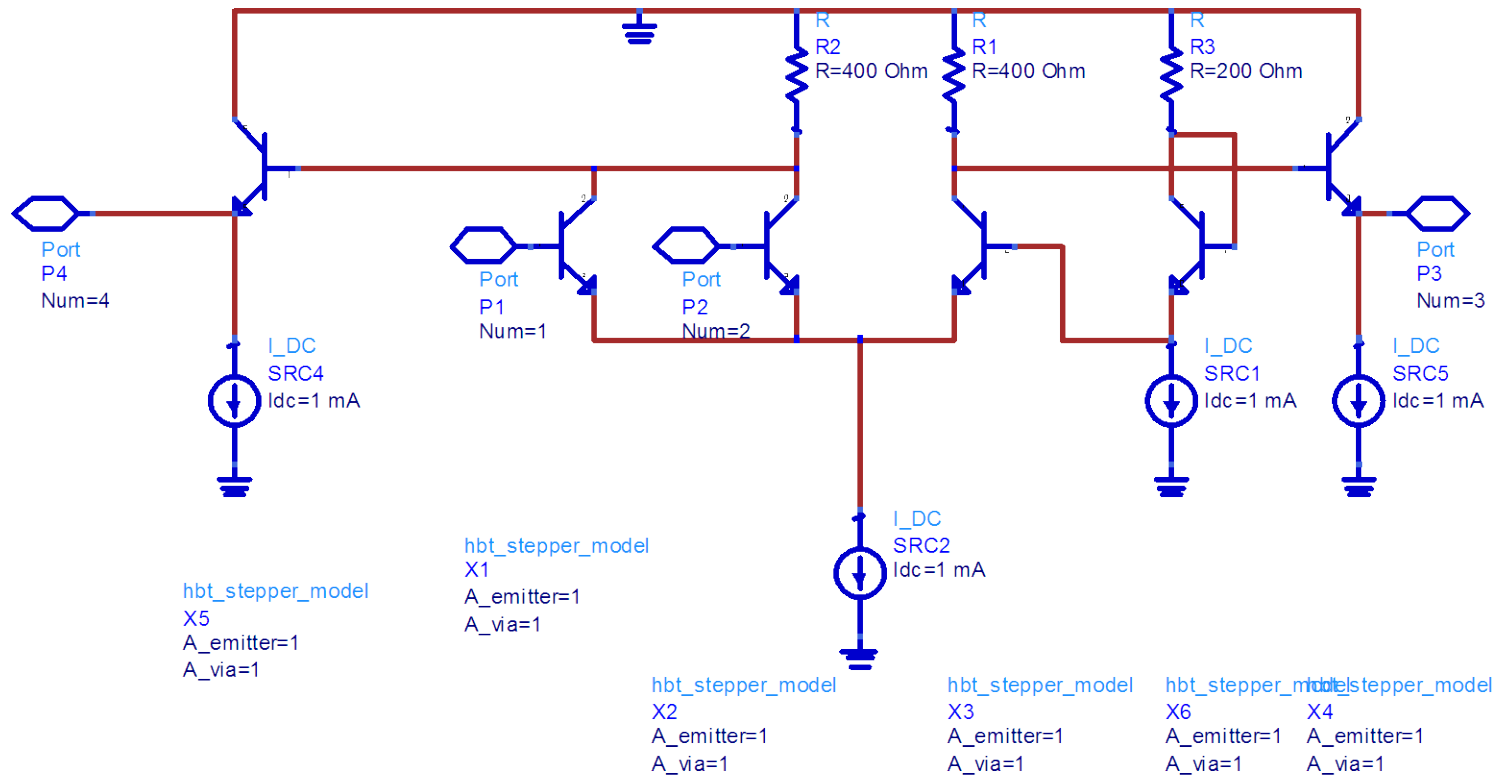

This is an \*OR/NOR gate....port 3 is high if ports 1 or 2 are high  
 ...port 4 is the logical complement of port 3

# ECL gate, circa ~1965

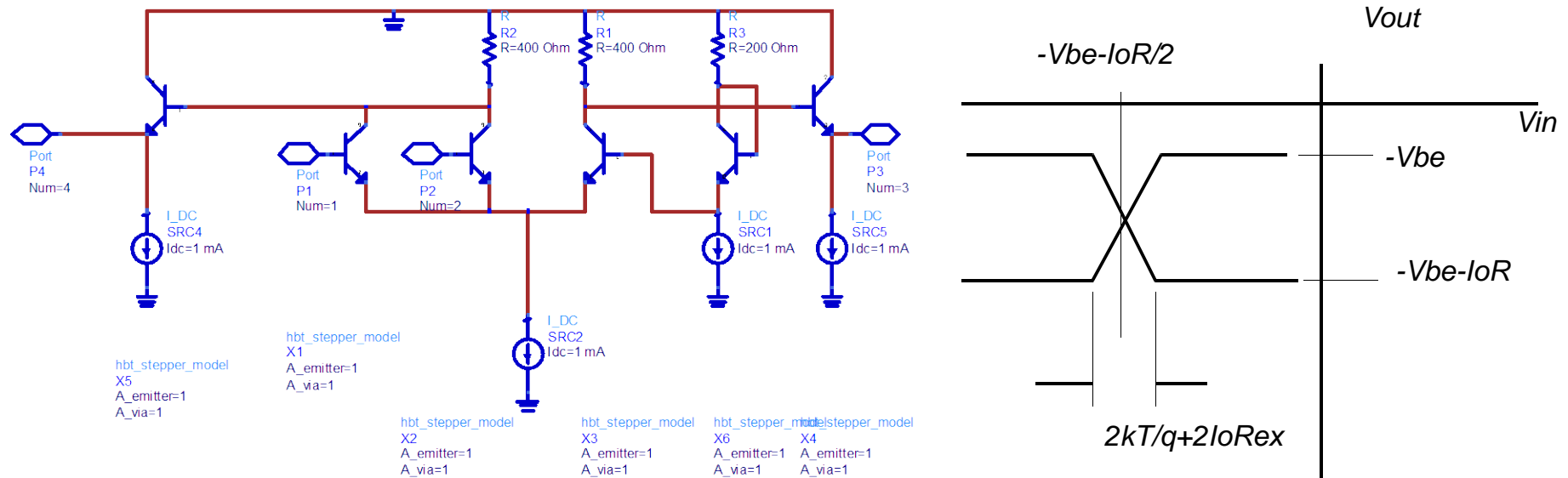

Emitter follower buffering of interconnect capacitance  
(good ? Bad ?)

DC output swing is  $400 \text{ Ohms} * 1 \text{ mA} = 400 \text{ mV} \dots I_o R_L$  in general

Minimum Input voltage swing is  $2kT/q + 2I_o R_{ex}$ .


Need  $I_o R_L \gg (2kT/q + 2I_o R_{ex})$  for adequate noise margin  
...typically 500-600 mV output swing employed

Current sources replaced by resistors or current mirrors
 
## Problems with old-fashioned ECL gate

Gate is single-ended....differential ckt generally preferred  
why ? (standard reasons given are not so convincing...)  
one reason is 2:1 lower permissible logic swing, less power


Gate uses emitter followers on **\*\*output\*\*** ....this can result in strong  
transmission-line ringing....



Output impedance of emitter follower is  
 $Z_{out} \approx 1 / g_m + R_L (jf / f_\tau)$  , which is inductive.


Load on receiving end is capacitive....

Line can ring strongly.

 


Partial mitigation : EF biased by pull - down resistor  
on receiving end of line, biased at e.g. - 2 Volts...this consumes substantial power

# Differential Gates, CML and ECL

 


CML

 

ECL


 
## Differential CML gate, other attributes



Operates with complementary inputs and outputs  
Quite low power consumption, as not many pull-down current sources...



## Differential CML gate, DC operation.

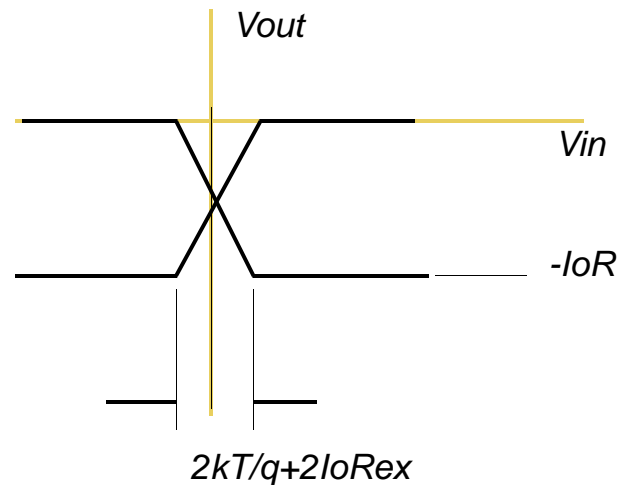 

DC output swing is  $\Delta V_{Logic} = I_o R_L$


DC linear input range is  $\Delta V_{in} = 2kT / q + 2I_o R_{ex}$

Transistor operates at  $V_{ce} = V_{be,on}$  when off

Transistor operates at  $V_{ce} = V_{be,on} - I_o R_L$  when on

Need HBT with LOW  $V_{ce,sat}$


# Differential CML AND / NAND gate

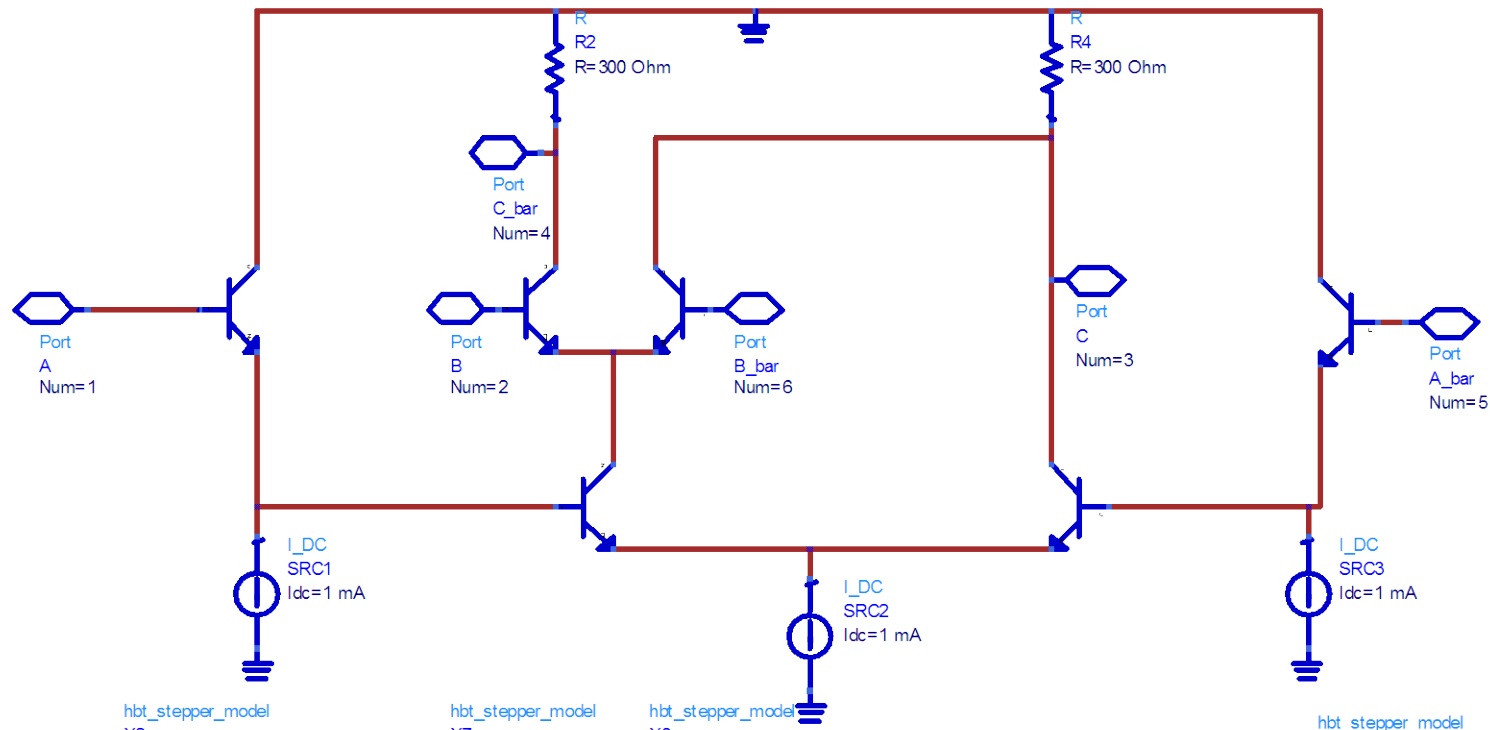


2-input logic gates must be implemented using *series gated current steering*. 3 input gates would require cascading 2-level gates, or 3-level series current steering. 3 level current steering is faster, but needs a more negative supply. OR/NOR gate is created by taking complements of both inputs and output.

# Differential Current-Steering Series-Gated Bipolar Logic Gates

CML

 

ECL

 

# HEMT Logic Gates

## Direct-coupled FET logic

Need enhancement-mode and depletion-mode devices  
 slow driving long wires  
 single-ended...threshold problems with low  $\Delta V$

## Source-Coupled FET logic:

Need a monolithic diode level-shift  
 fairly high power due to source followers  
 Source follows needed for level-shifting


## FET equivalent of CML :

Need a monolithic diode level-shift  
 need enhancement mode device  
 would be best for fast / low-power


Logic family plays strong role in power  
 Need diodes for SCFL

DCFL needs enhancement mode HEMTs:


SCFL

 


DCFL

 

FET equivalent of CML

 


# Differential CML XOR gate

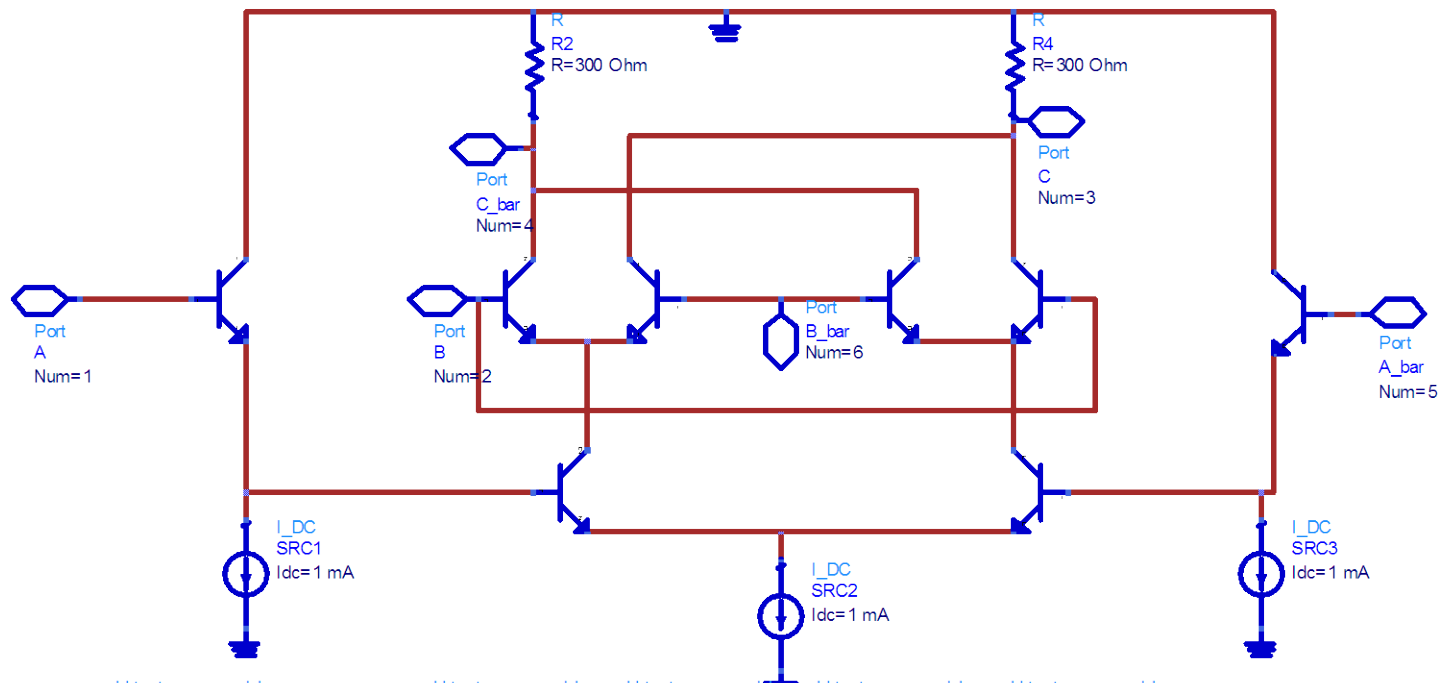

the 6-transistor cell is often referred to as a Gilbert cell (originating with his analog multipliers...). Note that the whole gate requires 3 pull down current sources


## Differential ECL buffer / inverter

 

emitter followers on high "A-level" inputs result in faster gate operation and larger  $V_{ce}$  across switching transistors, at expense of considerably higher current consumption. Emitter followers are usually associated with gate inputs, not outputs.




# Differential ECL XOR gate

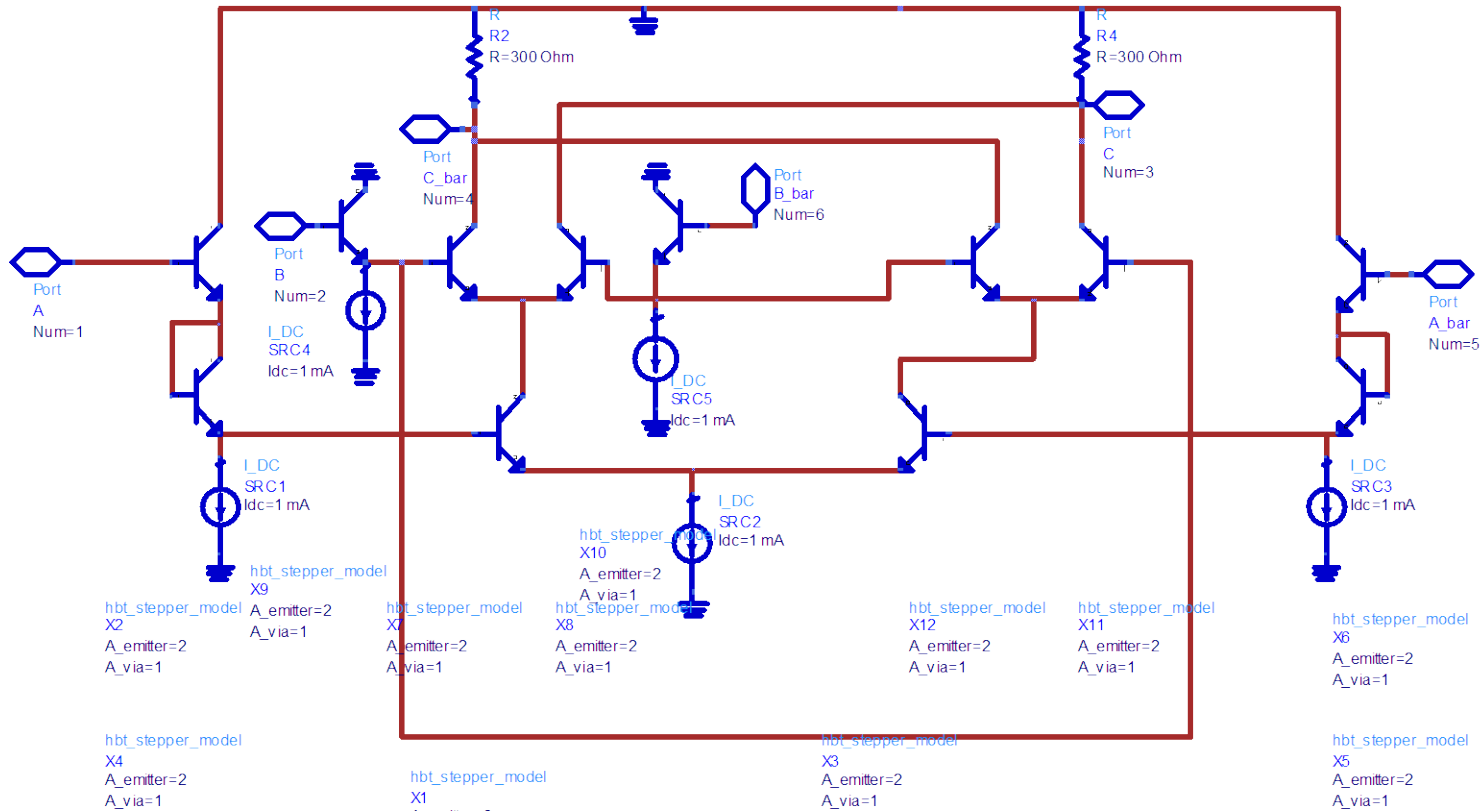

....



 
# Driving Interconnects: EF associated with gate outputs



This can ring quite badly, due to inductive EF output impedance and capacitive CS input impedance.


 
## Driving Interconnects Receiving end termination




receiving end termination....matched termination....

line should not (ideally) ring...actually does due to transistor capacitances ...

logic swing is  $I_o \cdot Z_o$ ...with  $Z_o$  of 100 Ohms typical, this requires 2 mA drive current for 200 mV logic swing in a 100 Ohm environment...


## Double line termination

 

double matched termination....ringing more strongly suppressed, use where needed....

... logic swing is  $I_0 \cdot Z_0 / 2$ ...with  $Z_0$  of 100 Ohms typical, this requires 4 mA drive current for 200 mV logic swing in a 100 Ohm environment...


## unterminated lines

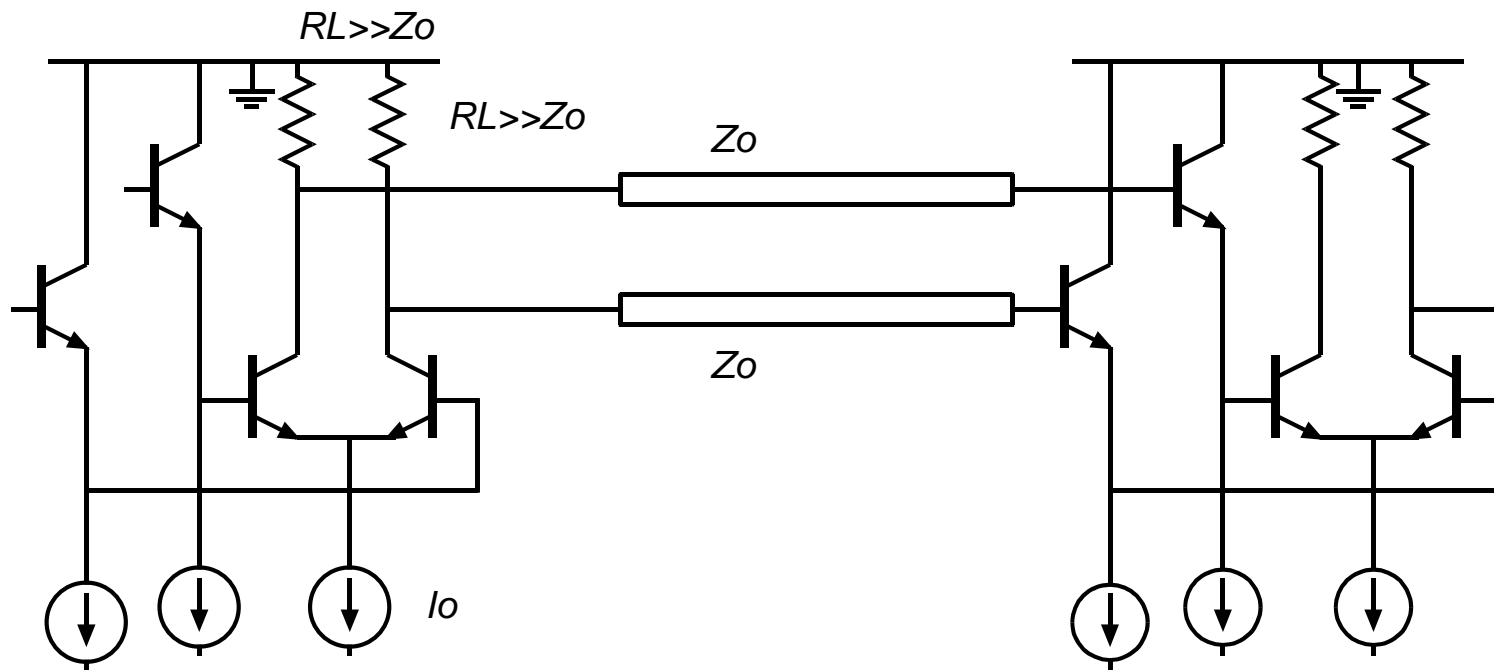

here lines are not terminated. Acceptable only when line delay is short in comparison with risetimes of concern. A short unterminated line will act as a capacitive load; a long unterminated line will ring. More on this in a few slides.

... logic swing is  $I_0 \cdot RL$ ...current consumption greatly reduced (and smaller HBTs used)....
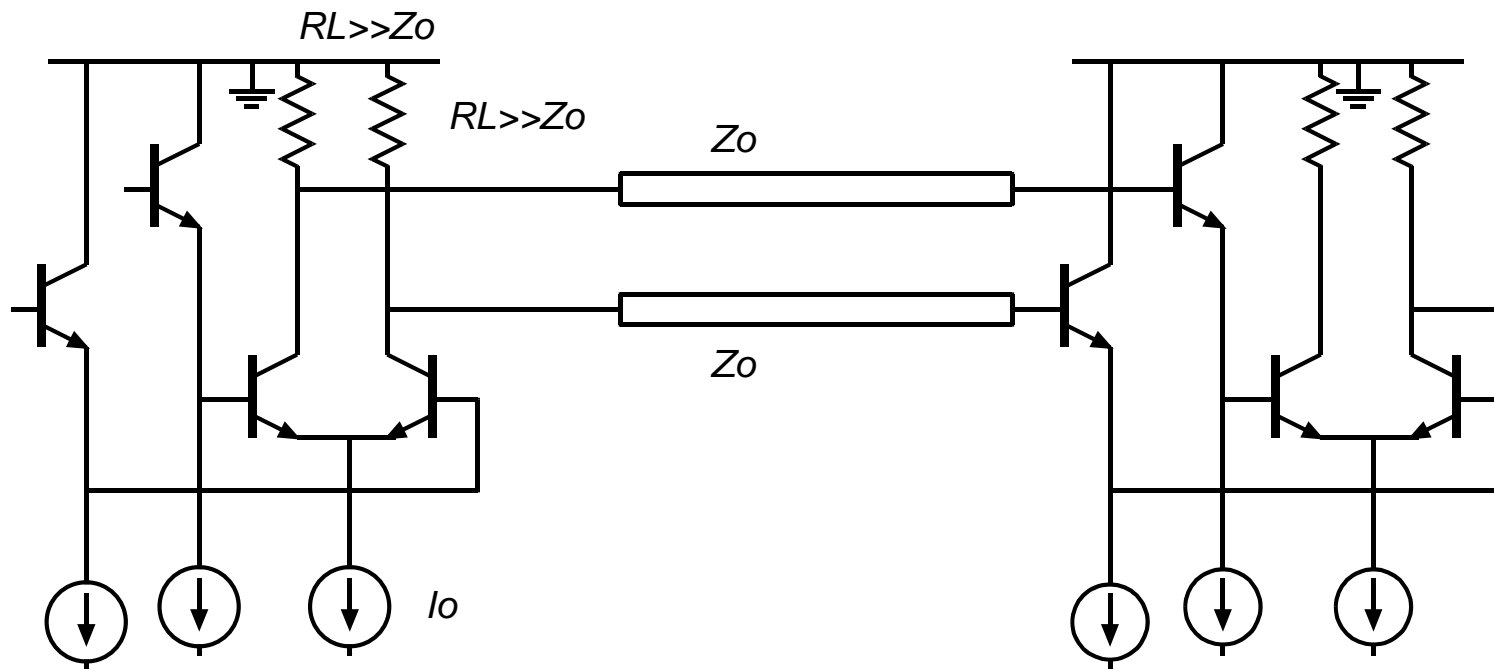
# unterminated lines: delay due to wiring capacitance



If and only if  $\tau_{wire} \ll T_{rise/fall}$ , can treat as lumped interconnect.

If and only if  $R_L \gg Z_{wire}$ , then  $L_{wire} / R_L \ll R_L C_{wire}$  & can ignore wiring inductance

Then :

$$C_{wire} = l_{wire} / v_{wire} Z_{wire} = \tau_{wire} / Z_{wire}$$

Charging time constant :

$$\tau_{interconnect} = R_L C_{wire} = \tau_{wire} (R_L / Z_{wire}) = \tau_{wire} \frac{(\Delta V_{logic} / I_o)}{Z_{wire}}$$

## Power Consumption in ECL and CML with singly-terminated Lines

### CML Gate:

Fast

emitter followers on lower level only  
(level-shifting)

$$V_{cc} = 3V_{be} + 300 \text{ mV} \leftarrow \text{IR drop on mirror resistor}$$

$$I = 3I_{\text{switched}} = 3 \cdot \Delta V_{\text{logic}} / Z_o \quad (\text{approx.})$$

### ECL Gate:

Adds emitter followers on upper level  
Somewhat faster

$$V_{cc} = 4V_{be} + 300 \text{ mV}$$

$$I = 5I_{\text{switched}} = 5 \cdot \Delta V_{\text{logic}} / Z_o \quad (\text{approx.})$$

### E<sup>2</sup>CL Gate:


Double emitter followers driving both levels  
helps with  $f/f_{\tau}$ , higher  $V_{ce}$  for high J/C

$$V_{cc} = 5V_{be} + 300 \text{ mV}$$


$$I = 7I_{\text{switched}} = 7 \cdot \Delta V_{\text{logic}} / Z_o \quad (\text{approx.})$$

**Need to use CML for low power**


CML

 

ECL

 

# Power and Power-Delay Products

 

Device sized for 100  $\Omega$  load:  
(300 mV ECL logic swing)  
0.25  $\mu\text{m}$  x 6  $\mu\text{m}$  emitter  
 $J_{\text{peak}}=2 \text{ mA}/\mu\text{m}^2$   
→ peak speed at 2 mA


Shorter stripe length device:  
0.25  $\mu\text{m}$  x 0.5  $\mu\text{m}$  emitter  
***peak speed at 250  $\mu\text{A}$  bias***

The smaller device consumes 12:1 less power but cannot use terminated lines. The lines then act as capacitive parasitics, and circuit speed is reduced due to the resulting  $\text{RLC}_{\text{wire}}$  time constant.


 
# Power-Delay Product for a “Baseline” Device

1  $\mu\text{m}$  by 1  $\mu\text{m}$  emitter



0.5 mA per transistor, 1.5 mA total for gate. 3.3 V supply

Power consumption:  
- 5 mW @ FO=2


Power-delay product  
(assuming 5 ps delay):  
25 fJ @ FO=2

*Wiring capacitance ignored*

$$P \approx 3 \cdot (3.3\text{V}) \cdot (5 \cdot 10^4 \text{ A/cm}^2) \cdot (1 \mu\text{m})^2 = 5 \text{ mW}$$


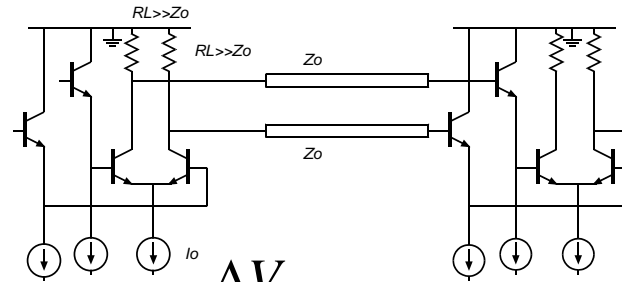
# Low-power gates have large delay from wiring capacitance



$$\tau_{\text{interconnect}} = R_L C_{\text{wire}} / 2 = \tau_{\text{wire}} (R_L / 2Z_{\text{wire}}) = \tau_{\text{wire}} \frac{\Delta V_{\text{logic}}}{2I_o Z_{\text{wire}}}$$

$$\tau_{\text{gate}} = \tau_{\text{interconnect}} + \tau_{\text{transistor terms}} = \tau_{\text{wire}} \frac{\Delta V_{\text{logic}}}{2I_o Z_{\text{wire}}} + \tau_{\text{transistor terms}}$$

$P_{\text{gate}} = V_{ee} N I_o$ , where  $N$  is the number of current sources per gate

$$\tau_{\text{gate}} P_{\text{gate}} = V_{ee} N I_o \tau_{\text{wire}} \frac{\Delta V_{\text{logic}}}{2I_o Z_{\text{wire}}} + V_{ee} N I_o \tau_{\text{transistor terms}}$$

$$= \frac{N V_{ee} (\Delta V_{\text{logic}})}{2} \frac{\tau_{\text{wire}}}{Z_{\text{wire}}} + V_{ee} N I_o \tau_{\text{transistor terms}}$$


As transistors are scaled,  $\tau_{\text{transistor terms}}$  becomes smaller, and power - delay product becomes interconnect - limited

# Minimum allowable logic voltage swing

$$\tau_{\text{gate}} P_{\text{gate}} = \frac{NV_{ee} (\Delta V_{\text{logic}})}{2} \frac{\tau_{\text{wire}}}{Z_{\text{wire}}} + V_{ee} NI_o \tau_{\text{transistor terms}}$$

Interconnect - limited delay becomes smaller as  $\Delta V_{\text{logic}}$  is made smaller.

 What are the limits to reducing  $\Delta V_{\text{logic}}$  ?



Linear input voltage range is  $2kT / q + I_o R_{ex}$

$\Delta V_{\text{logic}}$  must be several times this.

## Minimum Logic Voltage Swing

The linear input voltage range of the gate is

$$\Delta V_{linear} = 2kT / q + 2I_o R_{ex}$$

We need margin against signal degradation due to

signal ringing (interconnects, circuit - level a2)

gate - gate interference due to supply or ground coupling


This safety margin is called "noise" margin

has **\*\*absolutely\*\*** nothing to do with thermal noise  $\sqrt{4kTR\Delta f}$

should instead be called "EMI + ringing" margin



In order to have adequate "noise" margin we need
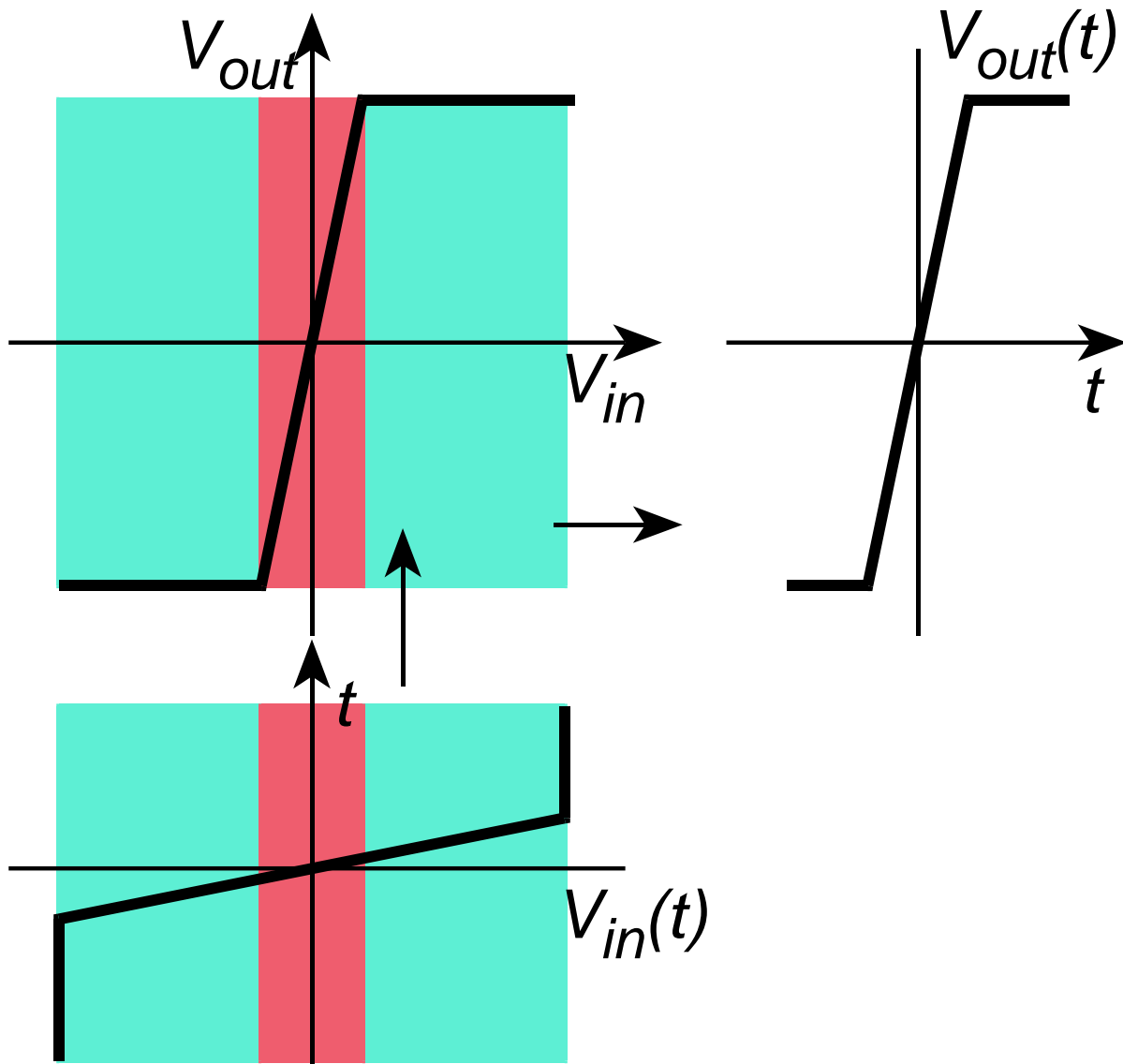
$$\Delta V_{logic} \sim > 3 * \Delta V_{linear} = 6kT / q + 6I_o R_{ex} \sim 150 \text{ mV} + 6I_o R_{ex}$$



$$\Delta V_{linear} = 2kT / q + 2I_o R_{ex}$$
  
$$\Delta V_{logic} > 3 * \Delta V_{linear} = 6kT / q + 6I_o R_{ex}$$



To tolerate ringing and EMI,  
 $\Delta V_{logic}$  must be several times  
 larger than  $\Delta V_{linear}$


# Circuits become interconnect limited

$$\tau_{\text{gate}} P_{\text{gate}} = \frac{NV_{ee}(\Delta V_{\text{logic}})}{2} \frac{\tau_{\text{wire}}}{Z_{\text{wire}}} + V_{ee} NI_o \tau_{\text{transistor terms}}$$

Interconnect limits: as transistors are scaled,  
wiring capacitance dominates

Power•delay becomes dependent only on supply voltage & logic voltage swing

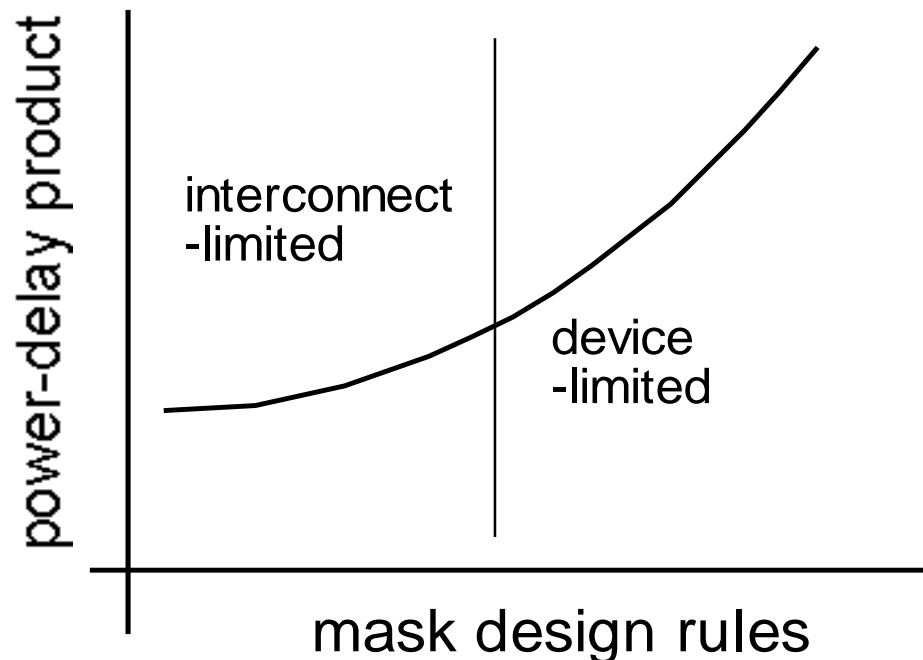independent of design rules, independent of transistor bandwidth





# Power-delay product in interconnect limit

$$P_{gate} T_{prop} = (1/2) C_{wire} V_{cc} \Delta V_{logic}$$

bipolar logic (static power)

$$P_{gate} / f_{clock} = (1/2) C_{wire} V_{cc} \Delta V_{logic}$$

CMOS logic (dynamic power)

$$(T_{prop} f_{clock})^{-1} \sim \text{number gates between latches}$$

For fast, low-power logic: reduce  $V_{cc} \Delta V_{logic}$



# Wiring capacitance ? What if we use terminated transmission lines ? (which we often do...)

$$\Delta V_{\text{logic}} = I_o Z_0 > \text{about } 5 * kT / q$$


$$P_{\text{gate}} = V_{ee} I_o = V_{ee} \Delta V_{\text{logic}} / Z_0$$

$$T_{\text{delay}} = T_{\text{gate}} + T_{\text{wire}}$$

$$T_{\text{wire}} = l_{\text{wire}} / v_{\text{wire}}$$


$$P_{\text{gate}} T_{\text{delay}} = T_{\text{gate}} (V_{ee} \Delta V_{\text{logic}} / Z_0) + T_{\text{wire}} (V_{ee} \Delta V_{\text{logic}} / Z_0)$$
 
$$P_{\text{gate}} T_{\text{delay}} > T_{\text{wire}} (V_{ee} \Delta V_{\text{logic}} / Z_0) = V_{ee} \Delta V_{\text{logic}} (l_{\text{wire}} / v_{\text{wire}} Z_0) = V_{ee} \Delta V_{\text{logic}} C_{\text{wire}}$$



so, even though “wiring capacitance” is no longer an accurate description,  $C V_{cc} \Delta V_{\text{logic}}$  is still an accurate expression for the power-delay limit

# ECL Latch

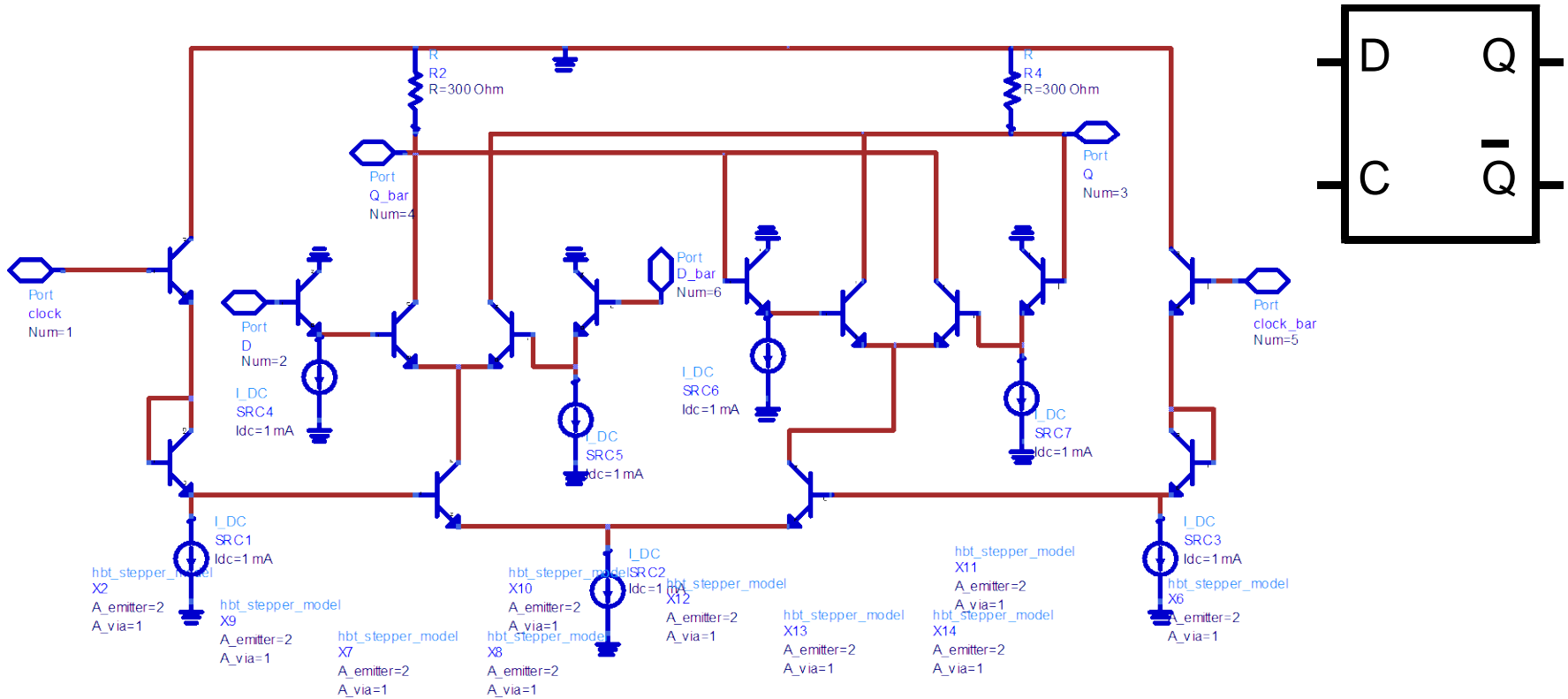


When clock is high, output = input.

When clock is low, output = input at just before clock changed from high to low


Note the positive feedback pair which holds the output level when clock\_bar is high

## Master-Slave Latch

 

Cascading a pair of latches creates a circuit which reads the data input  $D$ , and outputs it as the value  $Q$ , ***Only on a falling edge of clock....output is otherwise held constant....*** MS latch is used as timing control element...output is a version of the input, but sampled only at falling edge of clock

# Master-Slave Latch timing diagram

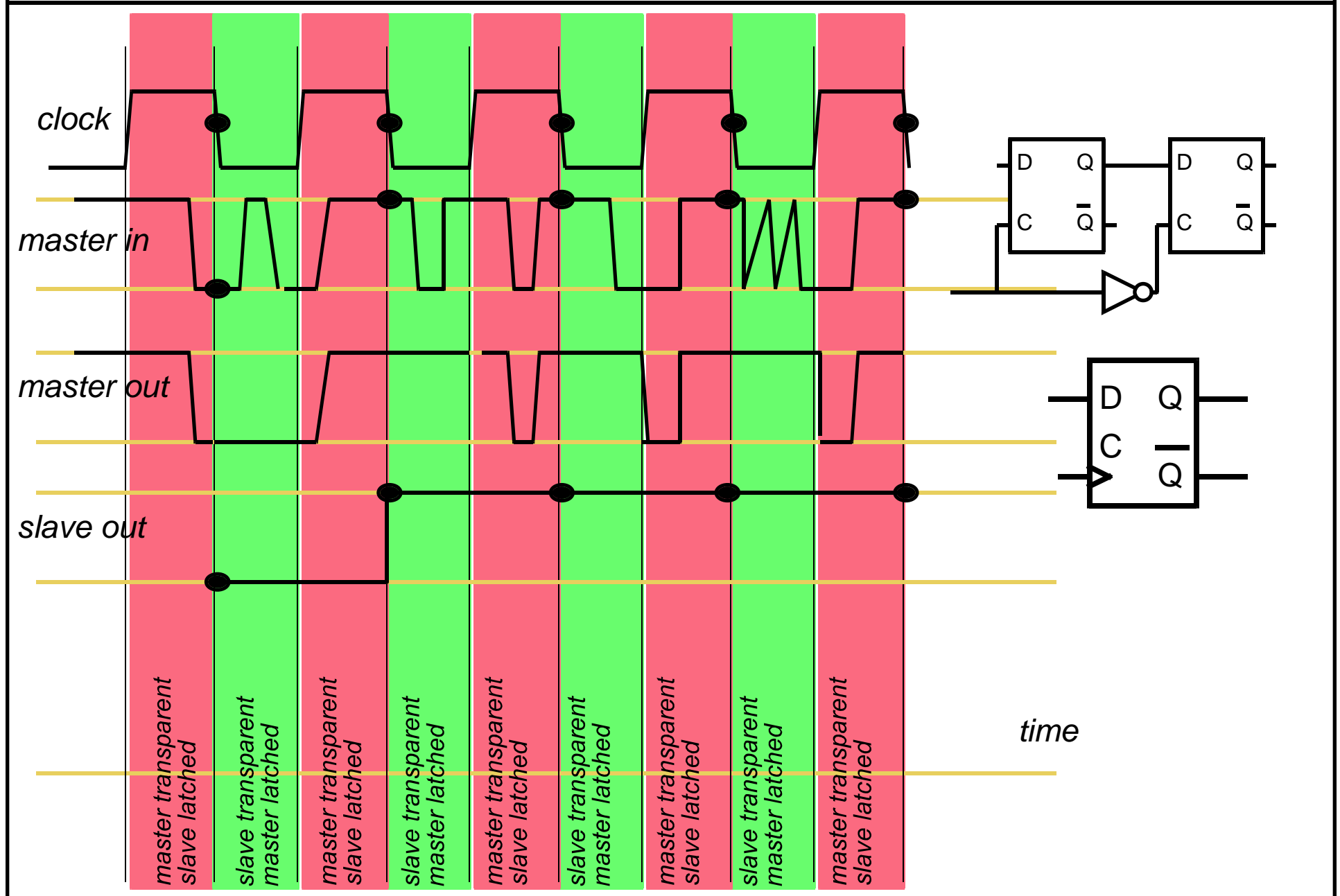

## What are latches and MS latches used for ?


timing control

in logic system, prop delays will be function of transition & critical path.  
timing errors/fluctuations will accumulate...role of latch is to suppress this,  
restore timing.

decision element.

in ADCs and in communications receivers, must decide whether  
a signal exceeds / does not exceed a critical threshold  
***at a particular set of points in time defined by a clock signal.***


## E<sup>2</sup>CL M/S Latch

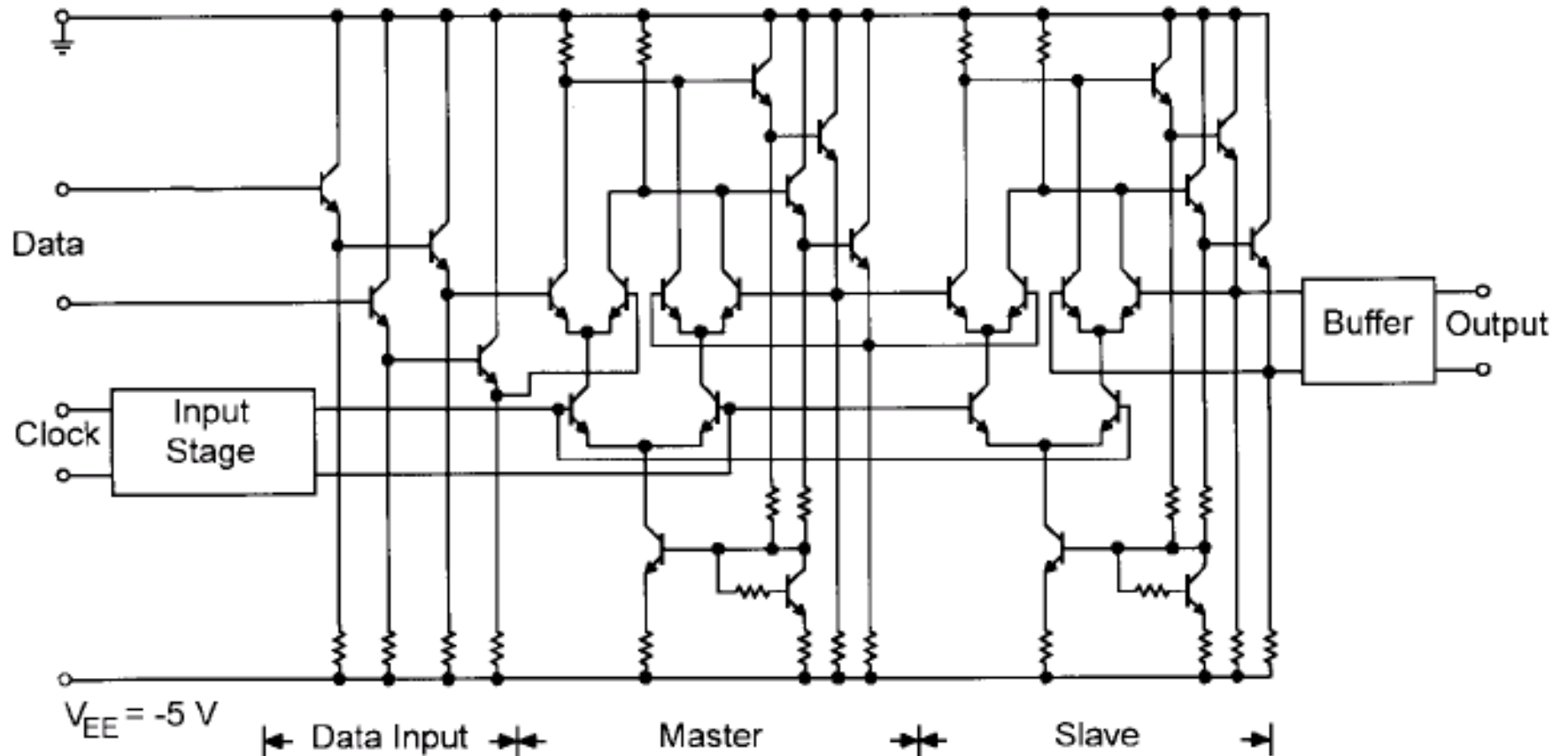


Popular in Si/SiGe due to (1)  $H_{21}^2$  current gain and  
(2) larger  $V_{ce}$  across switching transistors helps  $C_{cb}/I$  ratio


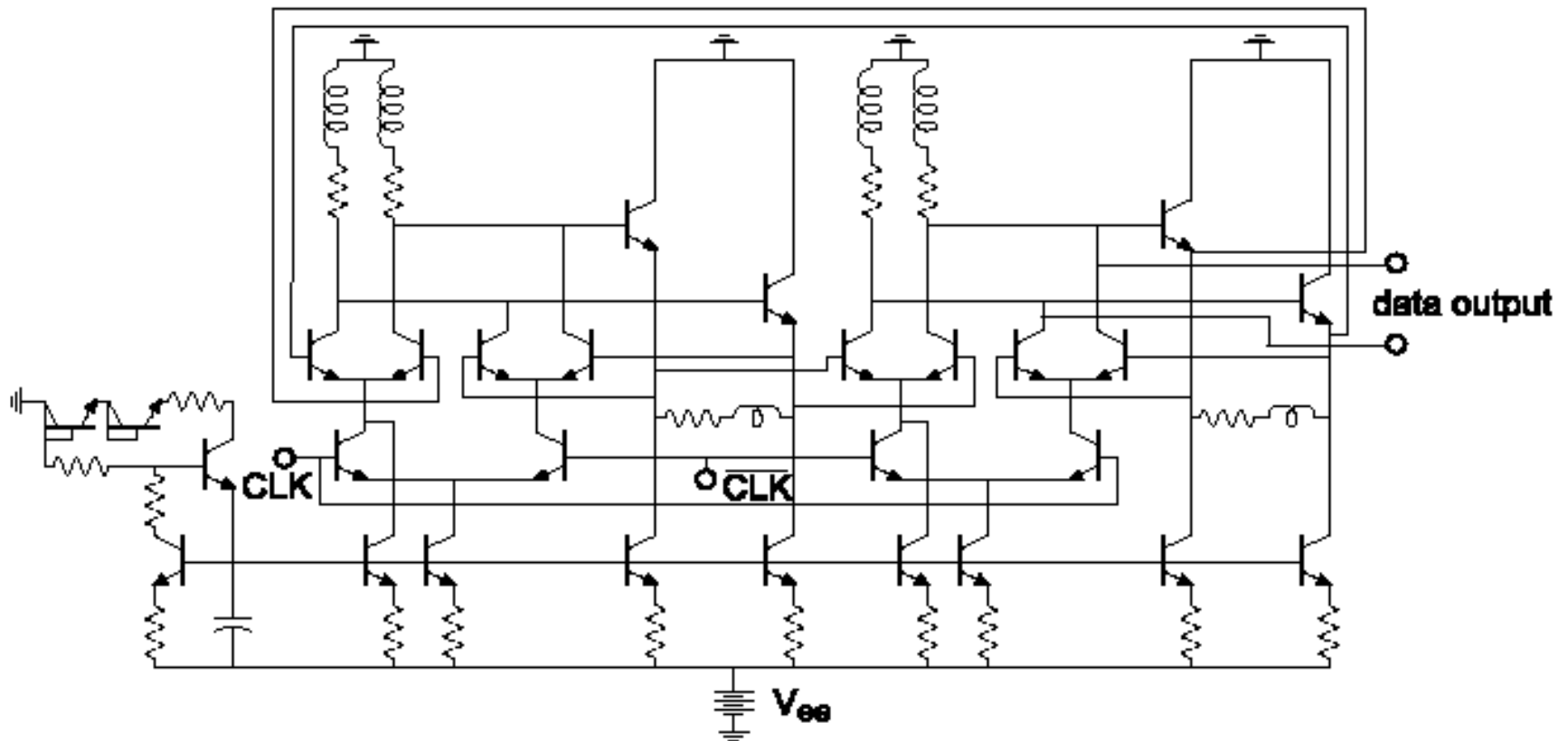
# ECL M/S Latch connected as 2:1 static frequency divider



# Fast ECL 2:1 static frequency divider

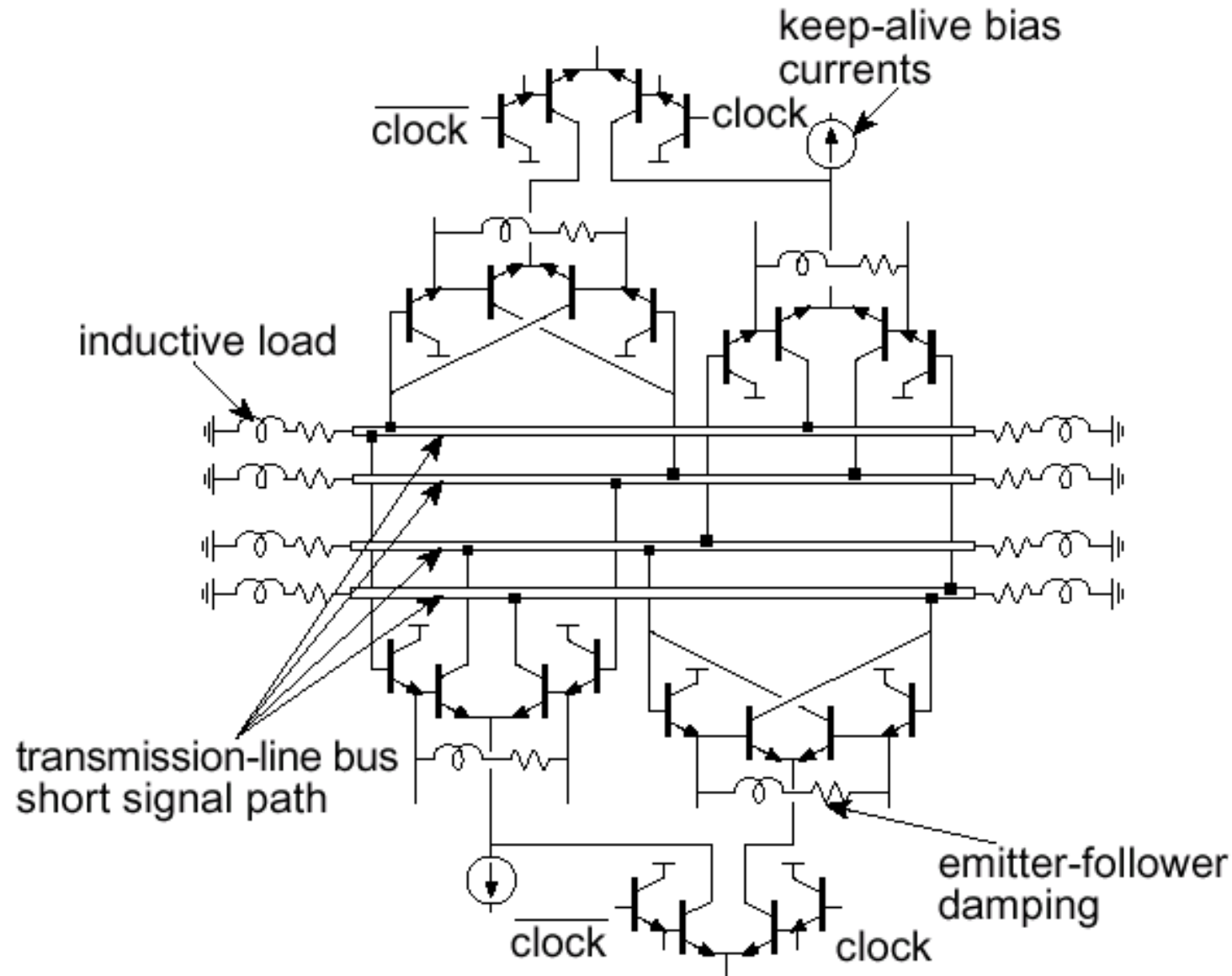

# Logic Propagation delay analysis: start with one-level CML gate

 


Figure 4.1: a) Basic CML gate. b) HBT without parasitics. c) CML equivalent circuit used for calculating propagation delay.

First, basic assumptions: 2:1 fan-out, chain of identical gates

# Basic Assumptions for Propagation delay analysis

 


Figure 4.1: a) Basic CML gate. b) HBT without parasitics. c) CML equivalent circuit used for calculating propagation delay.

Transistor is nonlinear, how do we solve ?

Small - signal analysis :  $C_{s.s.} \equiv dQ / dV$ ,  $g_m \equiv dI / dV$  etc.

Large - signal analysis :  $C_{s.s.} \equiv \Delta Q / \Delta V$ ,  $g_m \equiv \Delta I / \Delta V$  etc.

where  $\Delta V$  is the logic swing.

## Basic Assumptions for Propagation delay analysis

Large - signal analysis :  $C_{s.s.} \equiv \Delta Q / \Delta V$ ,  $g_m \equiv \Delta I / \Delta V$  etc.

This implies :

$$g_m = \Delta I / \Delta V = I_o / I_o R_L = 1 / R_L \ll q I_o / kT$$

$$C_{be,diffusion} = \Delta Q / \Delta V = I_o \tau_f / \Delta V = \tau_f / R_L \ll I_o \tau_f / (kT / q) = g_m \tau_f$$





$$A_v = \Delta V_{out} / \Delta V_{in} = -1$$

$$C_{je,large-signal} = \Delta Q / \Delta V = \left( \int_{V_{be,on} - \Delta V}^{V_{be,on}} C_{je}(v) dV \right) / \Delta V = C_{je,eff}$$

$$C_{cb,large-signal} = \Delta Q / \Delta V = (C_{cb} \Delta V) / \Delta V = C_{cb}$$

Note that large signal operation greatly reduces the effective values of gm and the diffusion capacitance...by roughly a factor of 10. Logic speed is much more controlled by depletion capacitances than it is by HBT base and collector stored charge
  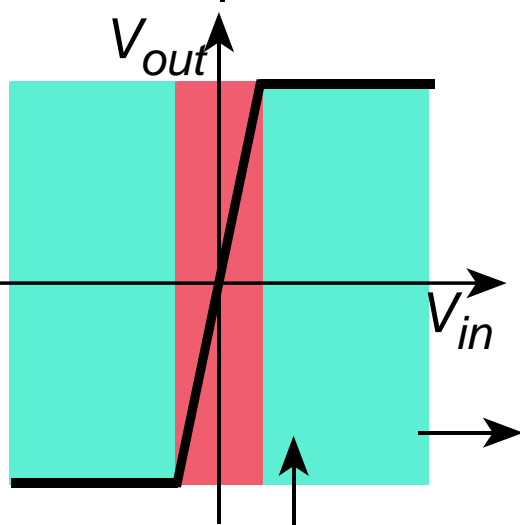 
# Why isn't base+collector transit time so important ?



diffusion + depletion capacitance  
 only depletion capacitance

Diffusion capacitance :

$$\begin{aligned}
 \delta Q_{\text{base}} &= (\tau_b + \tau_c) \delta I_C \\
 &= (\tau_b + \tau_c) \frac{dI_C}{dV_{be}} \delta V_{be} \\
 &= \frac{(\tau_b + \tau_c) I_C}{kT/q} \delta V_{be}
 \end{aligned}$$

...active only over  $kT/q$  voltage swing.

Under Large - Signal Operation :

$$\begin{aligned}
 \Delta Q_{\text{base}} &= (\tau_b + \tau_c) I_C \\
 &= \frac{(\tau_b + \tau_c) I_{dc}}{\Delta V_{\text{LOGIC}}} \Delta V_{\text{LOGIC}}
 \end{aligned}$$

Large - signal diffusion capacitance reduced by ratio of

$$\left( \frac{\Delta V_{\text{LOGIC}}}{kT/q} \right), \text{ which is } \sim 10 : 1$$

Depletion capacitances present over full voltage swing, no large-signal reduction

## Gate Propagation delay analysis

We now solve for gate delay

Method : replace transistors with their \* large - signal \* models

Circuit has transfer function of

$$\left[ \frac{V_{out}}{V_{in}} \right] = \left[ \frac{V_{out}}{V_{in}} \right]_{mid-band} \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

It is elementary math to show that the \* mean delay \* of the transfer function is  $(a_1 - b_1)$ , hence 1/2 the mean delay (delay to the 50% switching points) is  $T_{gate} = (a_1 - b_1) / 2$

Find  $a_1$  by the method of time constants

$$\text{Find } b_1 = \sum_{\text{emitter followers}} C_{be} / g_m - \sum_{\text{common-emitter stages}} C_{cb} / g_{m, \text{large-signal}}$$

## Gate Propagation delay analysis

Note that although the methods appear to be quite different, MOTC delay analysis on the linearized (large - signal) circuit, is identical to delay analysis by the charge - control method,

$$\text{e.g. } T_{gate} = \frac{1}{2} \sum \frac{\Delta Q}{\Delta I} = \frac{1}{2} \sum \frac{1}{\Delta I} \int_{V_{low}}^{V_{high}} C(v) dV$$


In both cases it is important to note that 2nd - order effects  $a_2$  in the circuit transfer function are neglected. This means, specifically, that emitter - follower ringing is neglected, which is a serious limitation




## One-level CML Propagation delay analysis

Taking  $T_{\text{prop}} = \tau \ln(2)$  is equivalent to assuming  $(1 - \exp(-t / \tau))$  charging behaviour. To the level of accuracy of the assumptions used, we have instead assumed linear node charging with time, which gives  $T_{\text{prop}} = \tau / 2$ , e.g. (1/2) the mean delay

 
# One-level CML Propagation delay analysis: fan-outs



 Here we are analyzing a gate chain with a fan-out of 2:1




## Simplifying treatment of fan-outs

 

$R_L$  is replaced by  $2R_L$  by symmetry arguments.

In order to count each parasitic capacitance ONCE per gate, we must consider only capacitors in the highlighted area

# Gate Delay Calculation

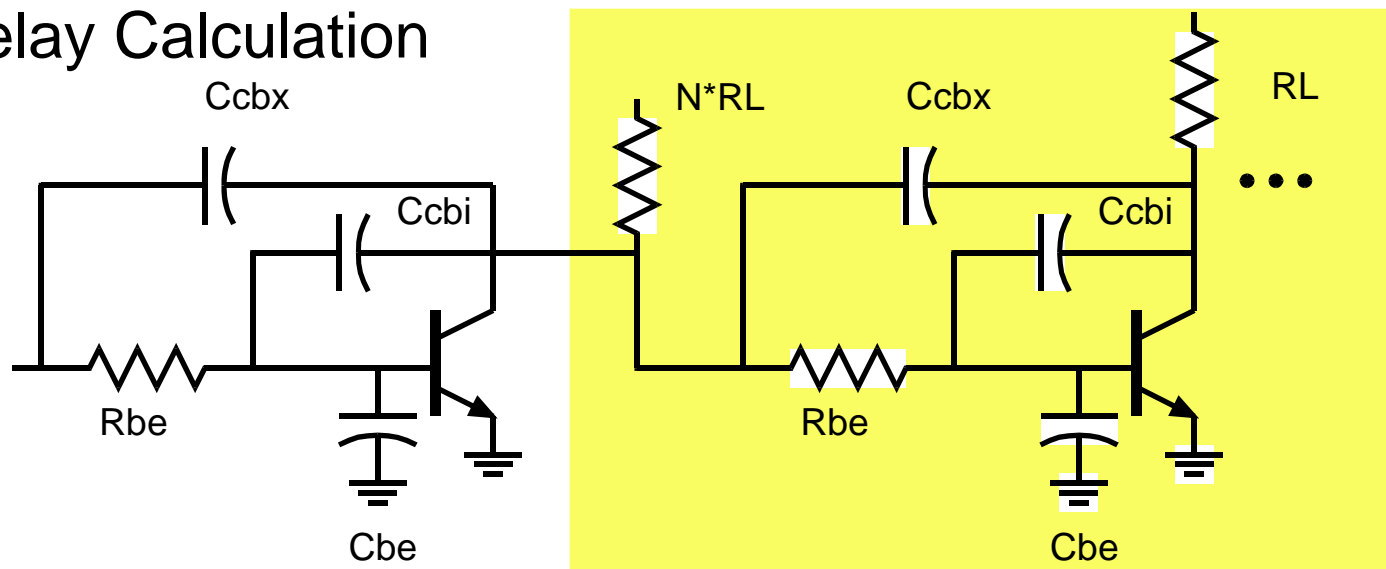

$$a_1 = C_{be}(R_{bb} + NR_L) + C_{cbi}[(NR_L + R_{bb})(1 - A_v) + R_L] + C_{cbx}[NR_L(1 - A_v) + R_L]$$

$$a_1 = \left[ C_{je} + \frac{I_o \tau_f}{\Delta V_{\text{logic}}} \right] \left[ R_{bb} + \frac{N \Delta V_{\text{logic}}}{I_o} \right] + C_{cbi} \left[ \left[ R_{bb} + \frac{N \Delta V_{\text{logic}}}{I_o} \right] (1 + 1) + \frac{\Delta V_{\text{logic}}}{I_o} \right]$$

$$+ C_{cbx} \left[ \left[ \frac{N \Delta V_{\text{logic}}}{I_o} \right] (1 + 1) + \frac{\Delta V_{\text{logic}}}{I_o} \right]$$

$$a_1 = C_{je} R_{bb} + C_{je} \frac{N \Delta V_{\text{logic}}}{I_o} + N \tau_f + R_{bb} \frac{I_o \tau_f}{\Delta V_{\text{logic}}} + (2N + 1) \left[ C_{cbx} + C_{cbi} \right] \left[ \frac{\Delta V_{\text{logic}}}{I_o} \right] + C_{cbi} R_{bb}$$

$$b_1 = -(C_{cbx} + C_{cbi}) / g_m = -(C_{cbx} + C_{cbi})(\Delta V_{\text{logic}} / I_o)$$

## Gate Delay Calculation: Single-level CML gate at N:1 fanout

$$\begin{aligned} 2T_{gate} &= C_{je} R_{bb} + C_{cbi} R_{bb} + N\tau_f \\ &\quad + R_{bb} \frac{I_o \tau_f}{\Delta V_{logic}} \\ &\quad + (2N + 2) \left[ C_{cbx} + C_{cbi} \right] \left[ \frac{\Delta V_{logic}}{I_o} \right] + C_{je} \frac{N\Delta V_{logic}}{I_o} \end{aligned}$$

Note that the  $C_{cb} (\Delta V_{logic}/I_o)$  and  $C_{je} (\Delta V_{logic}/I_o)$  terms usually dominate.

This strongly favors the use of small logic swings and high current density

## Effect of Current Density

$$2T_{gate} = C_{je}R_{bb} + C_{cbi}R_{bb} + N\tau_f$$
$$+ R_{bb} \frac{J_o A_e \tau_f}{\Delta V_{logic}} + (2N + 2) \frac{\epsilon A_c}{T_c} \left[ \frac{\Delta V_{logic}}{A_e J_o} \right] + C_{je} \frac{N \Delta V_{logic}}{A_e J_o}$$

$$2T_{gate} = C_{je}R_{bb} + C_{cbi}R_{bb} + N\tau_f$$
$$+ (R_{bb} A_e) \frac{J_o \tau_f}{\Delta V_{logic}} + (2N + 2) \frac{A_c}{A_e} \left[ \frac{\epsilon \Delta V_{logic}}{T_c J_o} \right] + \frac{C_{je}}{A_e J_o} N \Delta V_{logic}$$

## Effect of Logic Voltage Swing

$$2T_{gate} = C_{je}R_{bb} + C_{cbi}R_{bb} + N\tau_f + R_{bb}\left(I_o\tau_f / \Delta V_{logic}\right) \\ + (2N + 2)\left[C_{cbx} + C_{cbi}\right]\left(\Delta V_{logic} / I_o\right) + NC_{je}\left(\Delta V_{logic} / I_o\right)$$

Note that the linear input voltage range of the gate is

$$\Delta V_{linear} = 2kT / q + 2I_oR_{ex}$$

Recall than we need

$$\Delta V_{logic} \sim > 3 * \Delta V_{linear} = 6kT / q + 6I_oR_{ex} \sim 150 \text{ mV} + 6I_oR_{ex}$$

Logic voltage swing should be as small as possible, consistent with this limit...the  $R_{bb}\left(I_o\tau_f / \Delta V_{logic}\right)$  term usually being nondominant.

## Effect of Logic Voltage Swing

$$2T_{gate} = C_{je}R_{bb} + C_{cbi}R_{bb} + N\tau_f + R_{bb}\left(I_o\tau_f / \Delta V_{logic}\right) \\ + (2N + 2)\left[C_{cbx} + C_{cbi}\right]\left(\Delta V_{logic} / I_o\right) + NC_{je}\left(\Delta V_{logic} / I_o\right)$$

But

$$\Delta V_{logic} \sim 3 * \Delta V_{linear} = 6kT / q + 6I_oR_{ex} \sim 150 \text{ mV} + 6I_oR_{ex}$$

$$\text{Note that } C_{cb}\left(\Delta V_{logic} / I_o\right) = \left(\epsilon / T_c\right)\left(A_c / A_e\right)\left(\Delta V_{logic} / J_e\right)$$


$$\text{Note that } I_oR_{ex} = J_e / \left(R_{ex} / A_e\right)$$

If we push up current density, we do reduce Ccb charging time, but we must reduce the emitter resistance per unit area.

Otherwise, the voltage swing must increase, and no benefit is obtained



 
# Scaling Laws, Collector Current Density, $C_{cb}$ charging time



*Collector Field Collapse (Kirk Effect)*
 
$$V_{cb} + \phi > +(J / v_{sat} - qN_d)(T_c^2 / 2\varepsilon)$$



*Collector Depletion Layer Collapse*

$$V_{cb, \min} + \phi > +(qN_d)(T_c^2 / 2\varepsilon)$$


$$\Rightarrow J_{\max} = 2\varepsilon v_{sat} (V_{cb} + V_{cb, \min} + 2\phi) / T_c^2$$

Note that  $V_{be} \cong \phi$ , hence  $(V_{cb} + \phi) \cong V_{ce}$

$$C_{cb} \Delta V_{LOGIC} / I_C = (\varepsilon A_{\text{collector}} / T_c) (\Delta V_{LOGIC} / I_C) = \frac{\Delta V_{LOGIC}}{(V_{CE} + V_{CE, \min})} \left( \frac{A_{\text{collector}}}{A_{\text{emitter}}} \right) \left( \frac{T_c}{2v_{sat}} \right)$$


Collector capacitance charging time is reduced by **thinning the collector** while increasing current
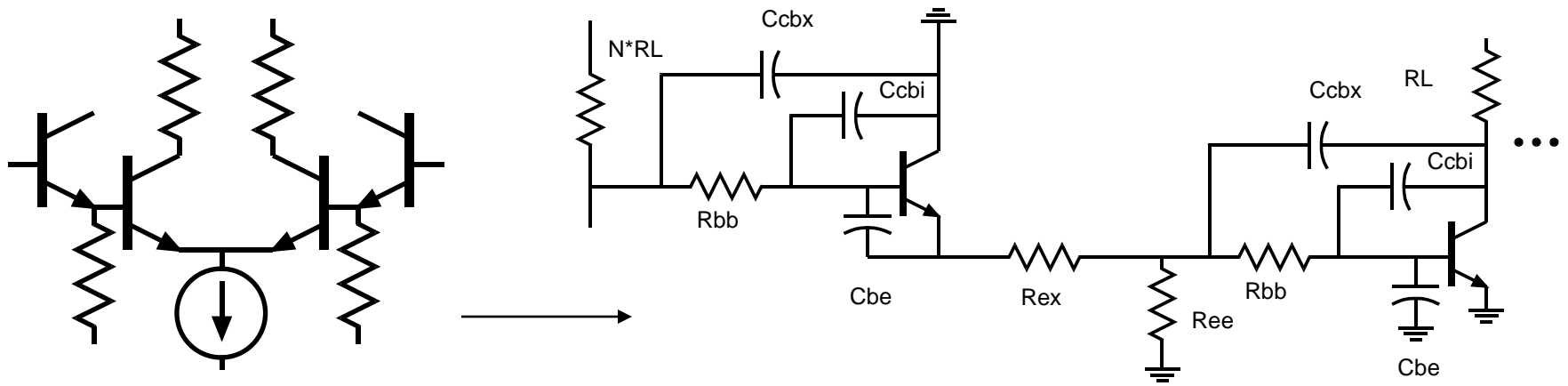
# ECL Propagation delay: upper-level circuit



again assume a fan-out of  $N:1$   
Simplify by assuming  $\beta \gg 1$ ,  $R_{ee} \gg R_e$ .
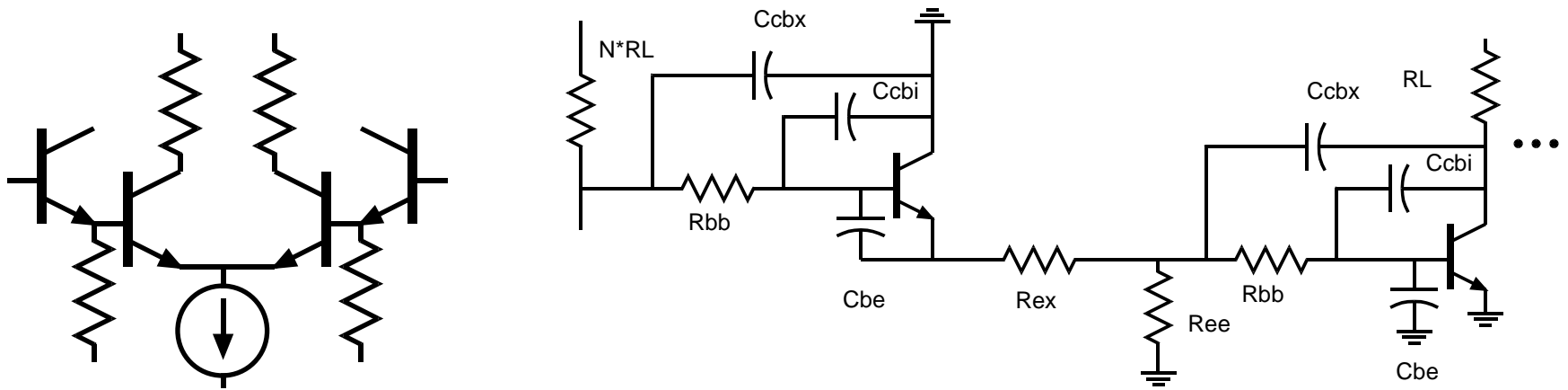
## ECL Propagation delay: upper-level circuit




Next key point:

Depending upon the details of the IC design, the emitter-followers may or may not switch.

For now, let us assume they do not.

 
We consequently use small-signal quantities for the EFs, and large-signal quantities for the CS transistors.



$$\begin{aligned}
 a_1 \approx & C_{cbx1} NR_L + C_{cbi1} (NR_L + R_{bb}) + (C_{je1} + \tau_f qI_{e1} / kT)(kT / qI_{e1}) \\
 & + C_{cbx2} \left[ (R_{ex1} + kT / qI_{e1})(1+1) + \Delta V_{\text{logic}} / I_0 \right] \\
 & + C_{cbi2} \left[ (R_{ex1} + kT / qI_{e1} + R_{bb2})(1+1) + \Delta V_{\text{logic}} / I_0 \right] \\
 & + \left[ C_{je2} + (\tau_f I_o / \Delta V_{\text{logic}}) \right] \left[ R_{ex1} + kT / qI_{e1} + R_{bb2} \right]
 \end{aligned}$$

$$b_1 = (C_{je1} + \tau_f qI_{e1} / kT)(kT / qI_{e1}) - (C_{cbx2} + C_{cbi2})(\Delta V_{\text{logic}} / I_0)$$

$$\begin{aligned}
 2T_{\text{gate}} = a_1 - b_1 = & C_{cbx1} NR_L + C_{cbi1} (NR_L + R_{bb}) + (C_{cbx2} + C_{cbi2})(\Delta V_{\text{logic}} / I_0) \\
 & + C_{cbx2} \left[ 2(R_{ex1} + kT / qI_{e1}) + \Delta V_{\text{logic}} / I_0 \right] \\
 & + C_{cbi2} \left[ 2(R_{ex1} + kT / qI_{e1} + R_{bb2}) + \Delta V_{\text{logic}} / I_0 \right] \\
 & + \left[ C_{je2} + (\tau_f I_o / \Delta V_{\text{logic}}) \right] \left[ R_{ex1} + kT / qI_{e1} + R_{bb2} \right]
 \end{aligned}$$

 


Writing  $C_{cb} = C_{cbx} + C_{cbi}$  :

$$\begin{aligned}
 2T_{gate} &= 2R_{bb2}C_{cbi2} + C_{cbi1}R_{bb1} + C_{je2}R_{bb2} \\
 &+ 2C_{cb2}[R_{ex1} + kT/qI_{e1}] + C_{je2}[R_{ex1} + kT/qI_{e1}] + (\tau_f I_o / \Delta V_{logic})(kT/qI_{e1}) \\
 &+ (\tau_f I_o / \Delta V_{logic})(R_{ex1} + R_{bb2}) \\
 &+ C_{cb1}N(\Delta V_{logic} / I_0) + 2C_{cb2}(\Delta V_{logic} / I_0)
 \end{aligned}$$

Note that the net delay is a little smaller than CML due to

- 1) Reduced number of  $R_L C_{cb}$  charging terms
- 2) \*slight\* improvement due to buffering  $C_{be,diff2} = \tau_f I_o / \Delta V_{logic}$
- 3) Larger  $V_{ce}$  permits increased  $J$ , hence improved  $I_c / C_{cb}$  ratio

# Do the emitter-followers switch ????

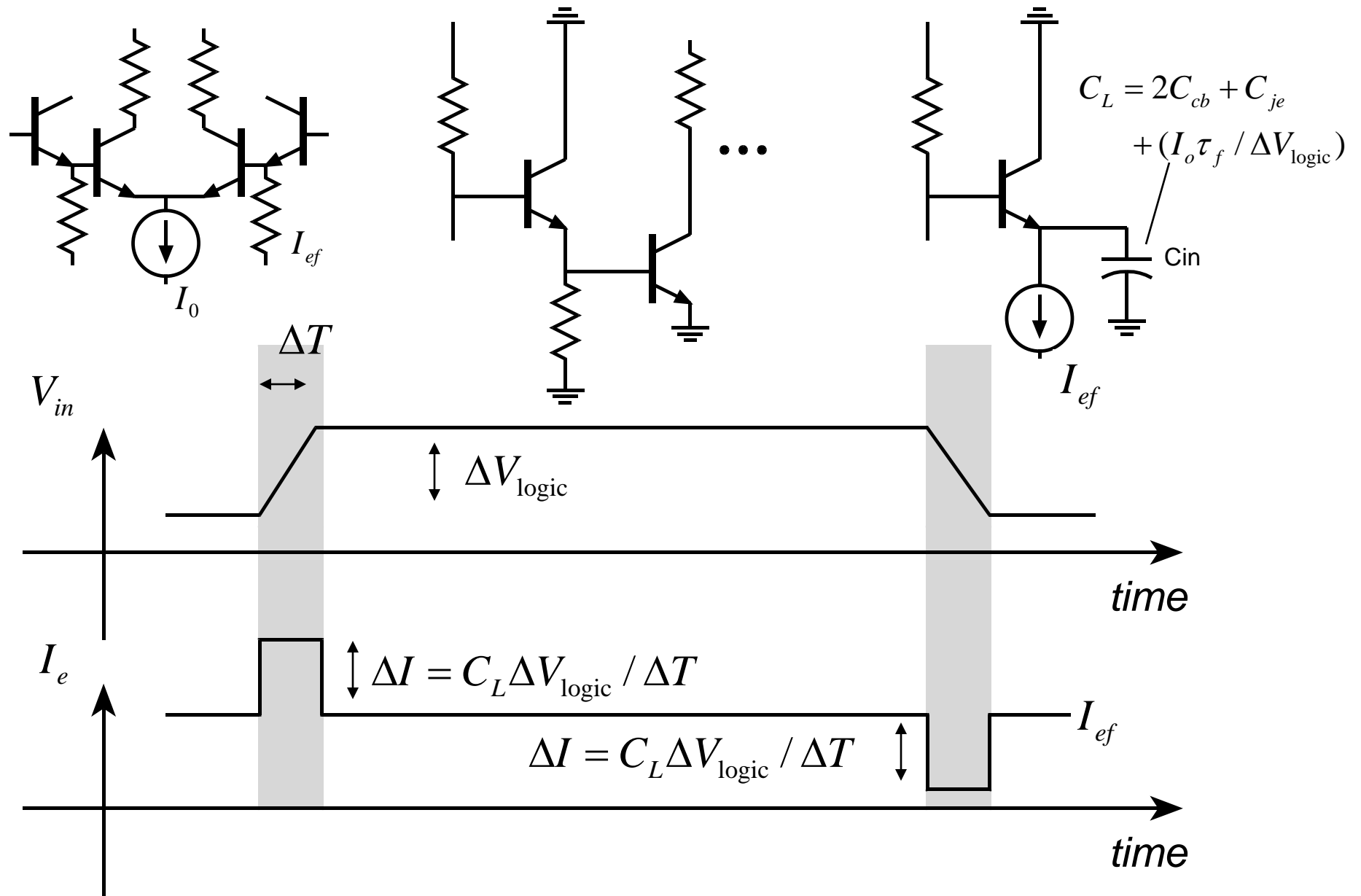

## Do the emitter-followers switch ????

There are 2 dangers. First, on a rising pulse, the peak EF current is

$$I_{ef,peak} = I_{ef} + \Delta I = I_{ef} + C_L \Delta V_{logic} / \Delta T$$

We must ensure that this peak current is below Kirk - effect limits.

Second, on a falling pulse, the minimum EF current is zero :


$$I_{ef,min} = 0 = I_{ef} - \Delta I = I_{ef} - C_L \Delta V_{logic} / \Delta T$$

From which


$$\Delta T_{min} = C_L \Delta V_{logic} / I_{ef}$$

This is slew - rate - limited discharging of  $C_L$ .
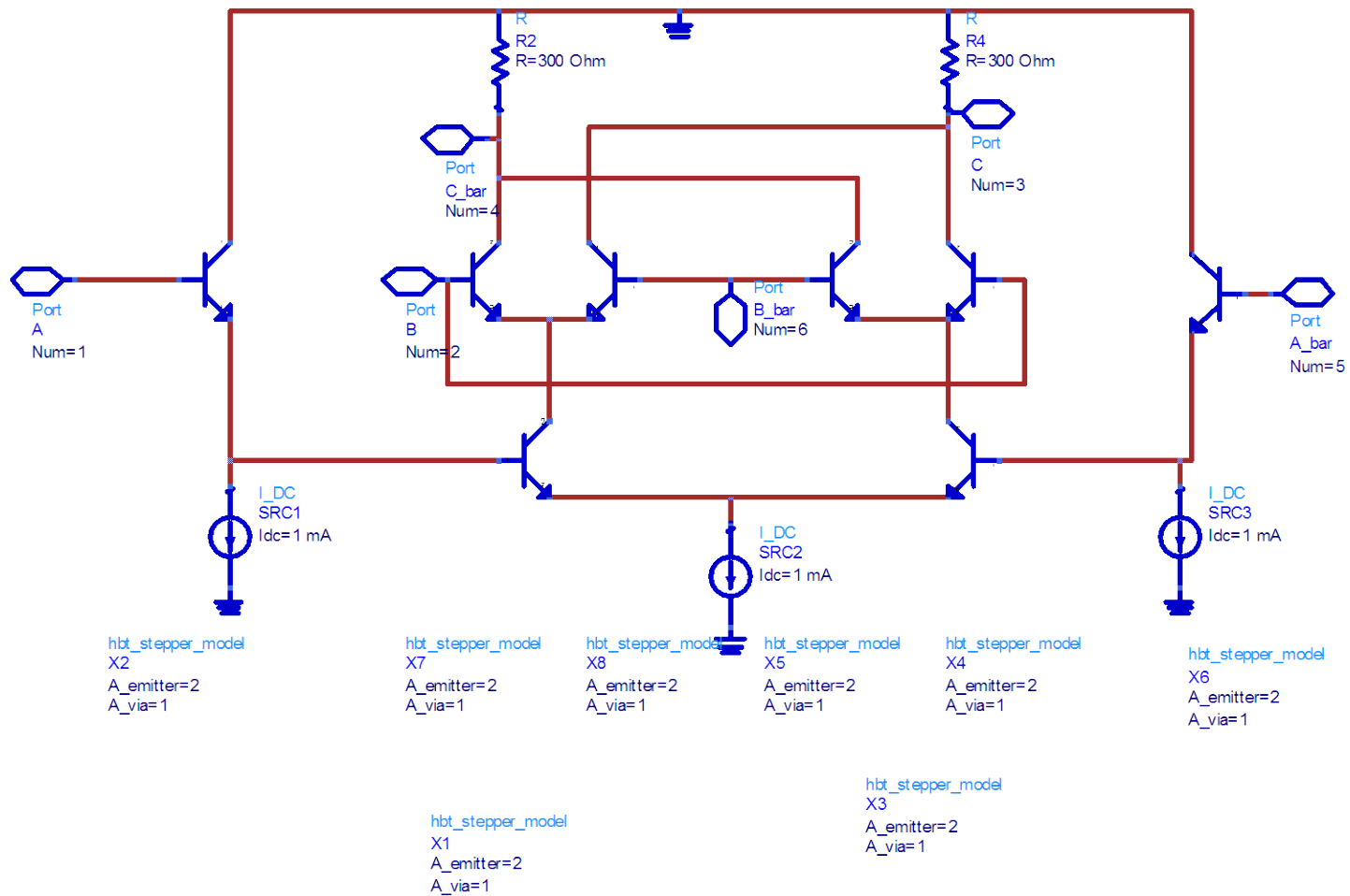
# CML Propagation delay: two-level circuit






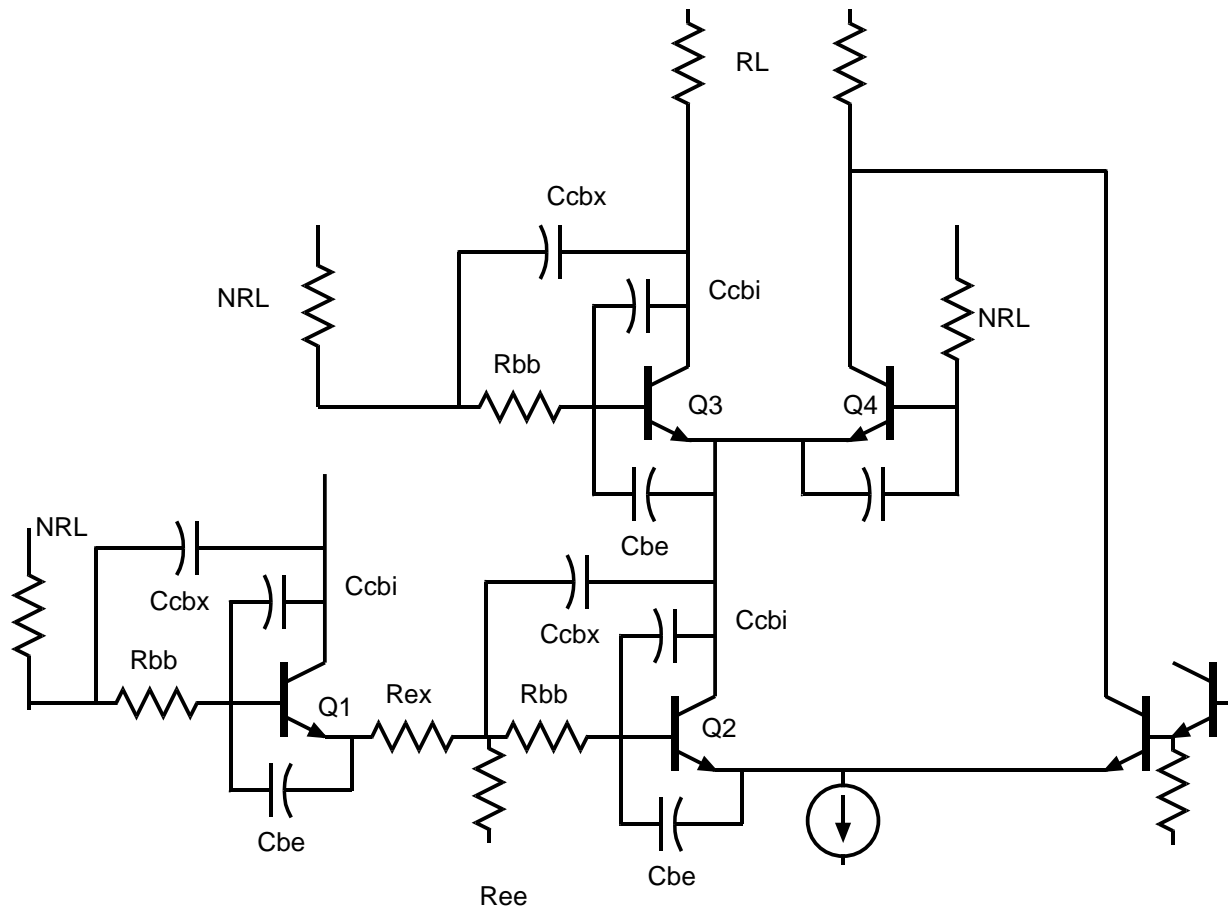


The logic voltage swing on the collector of Q2 is also \*approximately\*  $\Delta V_{\text{logic}}$ . Justification of this is a long and somewhat messy discussion.

 Note that on the B level switching path that Q1 is an EF, Q2 is CE, and Q3 is CB. If the base of Q3 is high and Q4 is low, then Q4 remains off and simply loads the collector of Q3 in  $C_{je4}$




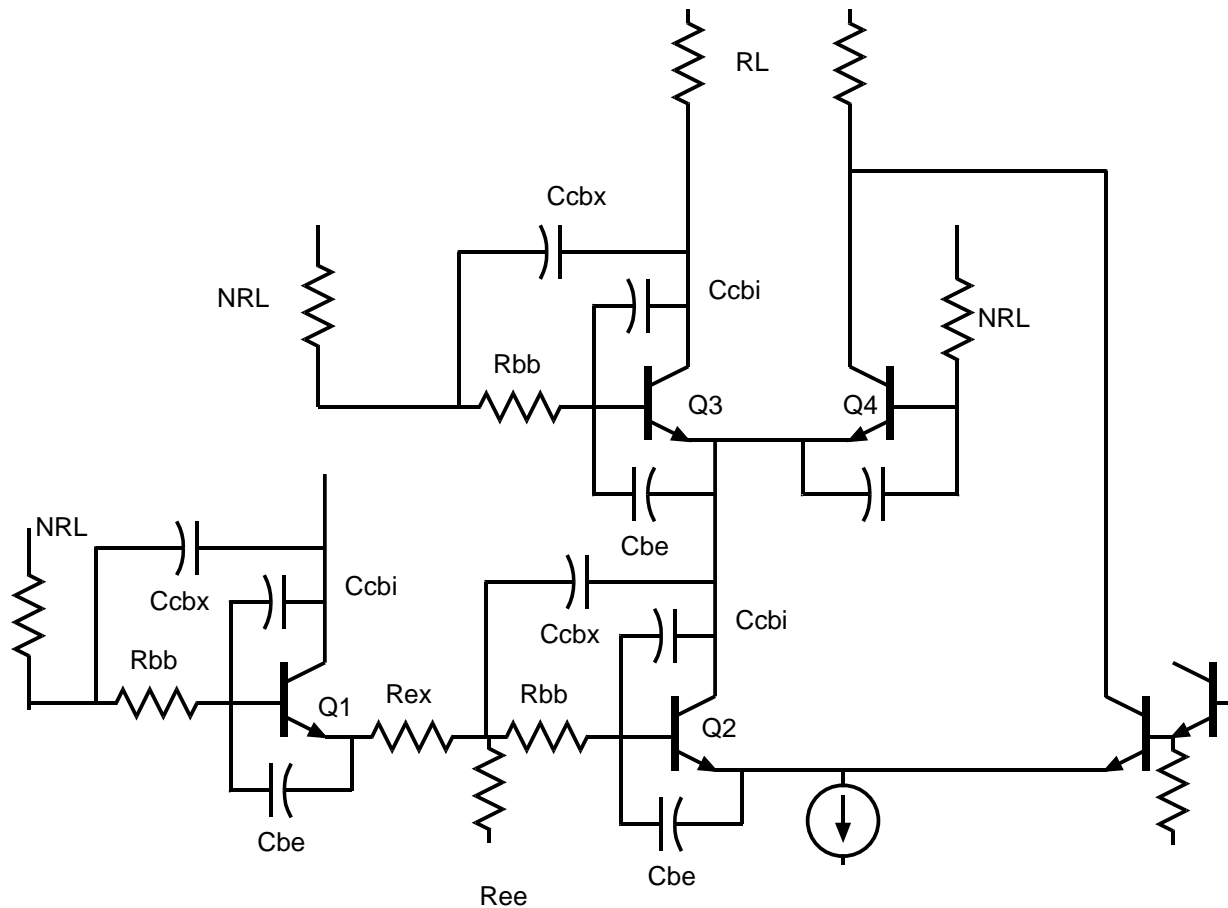Also simplify the answer for clarity by assuming that  $\beta \gg 1$ , & that the EF voltage gain is very close to 1. Note that Q3 operates in CB mode... please refer back to earlier notes to review  $a_1$  terms for CB stages.



$$\begin{aligned}
 2T_{gate} \cong & N(\Delta V_{logic} / I_0)C_{cb1} + R_{bb}C_{cb1} + C_{cb2} \left[ 2(R_{ex1} + 1/g_{m1}) + (\Delta V_{logic} / I_0) \right] \\
 & + C_{cb2} 2R_{bb2} + (C_{je2} + I_0\tau_f / \Delta V_{logic})(R_{bb2} + R_{ex1} + 1/g_{m1}) \\
 & + \left[ C_{je3} + C_{je4} + (I_0\tau_f / \Delta V_{logic}) \right] (\Delta V_{logic} / I_0) \\
 & + (N+1)(\Delta V_{logic} / I_0)C_{cb3} + R_{bb3}C_{cb3}
 \end{aligned}$$
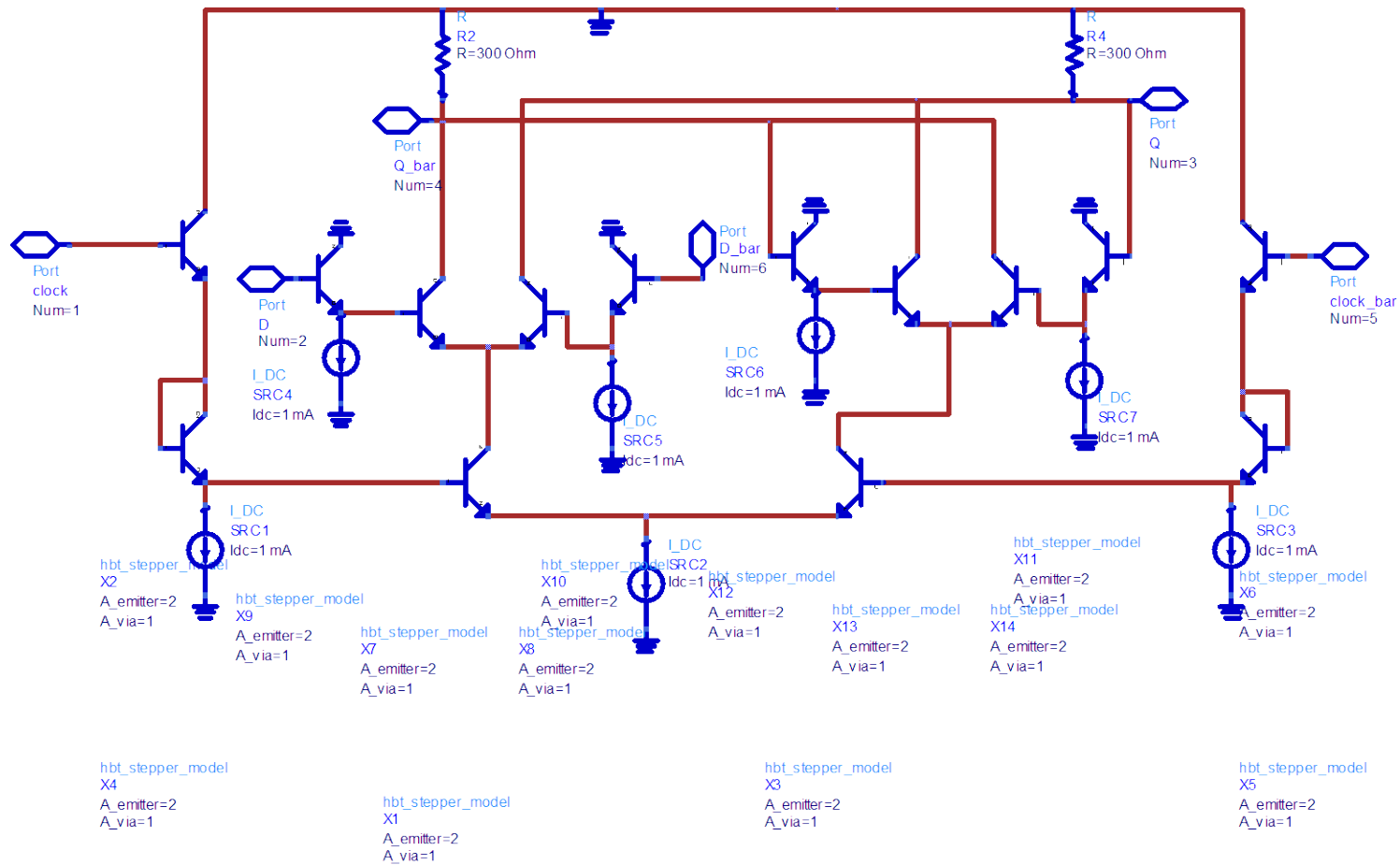
# ECL Propagation delay: two-level circuit



# Logic Speed

..	$C_{je}$	$C_{cbx}$	$C_{cbi}$	$\tau_f J / \Delta V_L$
$\Delta V_L / J$	1	6	6	1
$kT / qJ$	0.5	1	1	0.5
$\rho_e$	-0.25	0.5	0.5	0.5
$r_{bb}$	0.5	0	1	0.5

Approximate delay coefficients  $a_{ij}$  for an ECL master - slave flip - flop, found by hand analysis. Gate delay is of the form  $T_{gate} = 1 / 2 f_{clock, max} = \sum a_{ij} r_i c_j$ , where  $f_{clock}$  is the maximum clock frequency. The minimum logic voltage swing is  $\Delta V_{LOGIC} > 6(kT / q + J\rho_{ex})$

Caveat: ignores interconnect capacitance and delay, which is very significant

Yoram Betser  
Raja Pallela

## ***Logic Speed: definition of terms***

$C_{je}$  : emitter base depletion capacitance per unit emitter area

$C_{cbi}$  : intrinsic collector base capacitance per unit emitter area

$C_{cbx}$  : extrinsic collector base capacitance per unit emitter area

$\tau_f$  : sum of base and collector transit times

$J$  : emitter current per unit emitter area

$\Delta V_{LOGIC}$  : logic voltage swing

$r_{bb}$  : base resistance times emitter area (e.g. "per - area"  $R_{bb}$  )

$\rho_{ex}$  : emitter resistance times emitter area (e.g. "per - area"  $R_{ex}$  )

# What HBT parameters determine logic speed ?

	Cje	Ccbx	Ccbi	( $\tau_b + \tau_c$ ) ( $I/\Delta V$ )	total
$\Delta V / I$	33.5%	6.7%	27.8%		68.4%
$\Delta V / I$				12.3%	12.3%
$(kT/q) I$	1.4%	0.1%	0.4%	0.5%	2.5%
Rex	-1.3%	0.1%	0.3%	0.9%	0.1%
Rbb	10.2%		2.8%	3.7%	16.7%
total	43.8%	6.8%	31.3%	17.5%	100.0%
		38%			

Sorting Delays by capacitances :

44% charging  $C_{je}$ , 38% charging  $C_{cb}$ , only 18% charging  $C_{diff}$  (e.g.  $\tau_b + \tau_c$ )

Sorting Delays by resistances and transit times :

68% from  $\Delta V_{logic} / I_c$ , 12% from  $(\tau_b + \tau_c)$ , 17% from  $R_{bb}$

$R_{ex}$  has very strong indirect effect, as  $\Delta V_{logic} > 6 \bullet (kT / q + I_C R_{ex})$

Caveats:

assumes a specific UCSB InP HBT (0.7 um emitter, 1.2 um collector 2kÅ thick, 400 Å base, 1.5E5 A/cm<sup>2</sup>)  
ignores interconnect capacitance and delay, which is very significant