


mm-Wave IC Design: The Transition from III-V to CMOS Circuit Techniques

Patrick Yue, Mark Rodwell, UCSB

Outline

- Background
 - Emerging mm-wave applications
 - Open design issues for mm-Wave CMOS
- CMOS for mm-wave design
 - Optimizing CMOS device performance – layout & bias
 - On-chip inductors in CMOS
 - Cell-based device modeling and design methodology
 - State of the art CMOS mm-Wave design examples
- mm-Wave design techniques
 - Device characterization issues
 - Unconditionally stable, gain-matched amplifier design procedure
 - Tuned amplifier, power amplifier design examples
 - On-chip transmission line design
- Summary
- References

Emerging mm-Wave Wireless Applications

 


- Unlicensed 60-GHz band for Gbit wireless link:
 - Outdoor, point-to-point wireless link
 - Wireless High-Definition Multimedia Interface (HDMI)
- Licensed point-to-point wireless link in E-band (71-76, 81-86 GHz, and 92-95 GHz)
- Vehicular radar at 76-77 GHz
- 94-GHz band for high-resolution imaging

Questions:

Can we leverage scaled CMOS to produce more cost-effective products and enable new markets?


Recent Evolution for CMOS RF

 

(D. Su, *et al. ISSCC 2002.*)

- ❑ 0.25- μm CMOS
- ❑ 5-GHz RF transceiver

Lower power,
cost and size

 

(S. Mehta, *et al. ISSCC 2005.*)

- 0.18- μm CMOS
- RF + baseband DSP

But difficult to migrate below 0.18 μm even for RF SoC...

State of the Art mm-Wave IC: 330 GHz 16-Finger Power Amp

designs in progress: Michael Jones

device: 5 V, 650 GHz f_{max} InP DHBT

wiring: thin film microstrip with 2 um BCB

Challenges:


line losses are very high

lines $> 60 \Omega$ are not feasible \rightarrow increases Q of output tuning




lines of required impedance are narrow \rightarrow limits on DC current

small unmodeled parasitics will de-tune design

 ....must maintain microstrip environment to device vias with negligible lengths of unmodeled random interconnects



330 GHz 16-Finger Amplifier

   

Open Design Issues

- RF CMOS design are by and large lumped circuits
- mm-Wave design are traditionally distributed circuits
- How will mm-Wave CMOS be designed?
 - Assuming that we will integrate an entire transceiver, should each block be impedance-matched?
 - Do we need new design flow / methodology?
 - Should all interconnect be modeled as T-line and be impedance-controlled?
 - Do we need a well-controlled global ground (plane)?
- How to optimize CMOS device performance?

CMOS Device Parameter Scaling Trend


Process	0.25 μm ('98)	0.18 μm ('00)	0.13 μm ('02)	90 nm ('04)
V_{dd} (V)	2.5 (1x)	1.8 (0.7x)	1.2 (0.5x)	1.0 (0.4x)
I_{dsat} ($\mu\text{A}/\mu\text{m}$)	600 (1x)	600 (1x)	550 (1x)	850 (1.4x)
I_{off} (nA/ μm)	0.01 (1x)	0.02 (2x)	0.32 (32x)	7 (700x)
I_{gate} (nA/ μm)	2.5e-5 (1x)	1.8e-3 (100x)	0.65 (5e4)	6.3 (70000x)
$I_{\text{on}}/I_{\text{off}}$ (10e6)	60 (1x)	30 (0.5x)	1.7 (0.03x)	0.12 (0.002x)
g_{m} (mS/ μm)	0.3 (1x)	0.4 (1.3x)	0.6 (2x)	1.0 (3.3x)
g_{ds} ($\mu\text{S}/\mu\text{m}$)	7.7 (1x)	15 (2x)	42 (5.4x)	100 (13x)
$g_{\text{m}} / g_{\text{ds}}$	39 (1x)	27 (0.7x)	14 (0.36x)	10 (0.26x)
f_{T} (GHz)	30 (1x)	60 (2x)	80 (2.7x)	140 (4.7x)
Delay (ps/gate)	45 (1x)	30 (0.7x)	15 (0.3x)	11 (0.24x)
C_{g} (fF/gate)	0.47 (1x)	0.35 (0.7x)	0.25 (0.5x)	0.16 (0.34x)
C_{j} (fF/gate)	0.83 (1x)	0.80 (1x)	0.88 (1.1x)	0.66 (0.8x)

- **Positive:** f_{T} , f_{max} , F_{min} , I_{dsat} , g_{m} , C_{g} and C_{j}
- **Negative:** V_{dd} and g_{ds}

Challenges for RF/mm-Wave in 0.13- μm CMOS and Beyond

- High mask cost (\$0.5M – \$1M)
 - only makes sense if integration level increases, e.g. RF + large DSP, or mm-wave transceiver
 - Lack of a streamline RF/mm-wave design flow
 - Negative impact of technology scaling
 - Device
 - Process variations
 - Model uncertainty
 - Interconnect parasitic variations
 - Circuit
 - Low voltage headroom due to reduced V_{dd}
- Strongly depend on layout
- Develop a parasitic-aware design methodology
- Explore low-voltage circuit techniques

High Frequency Figures of Merit

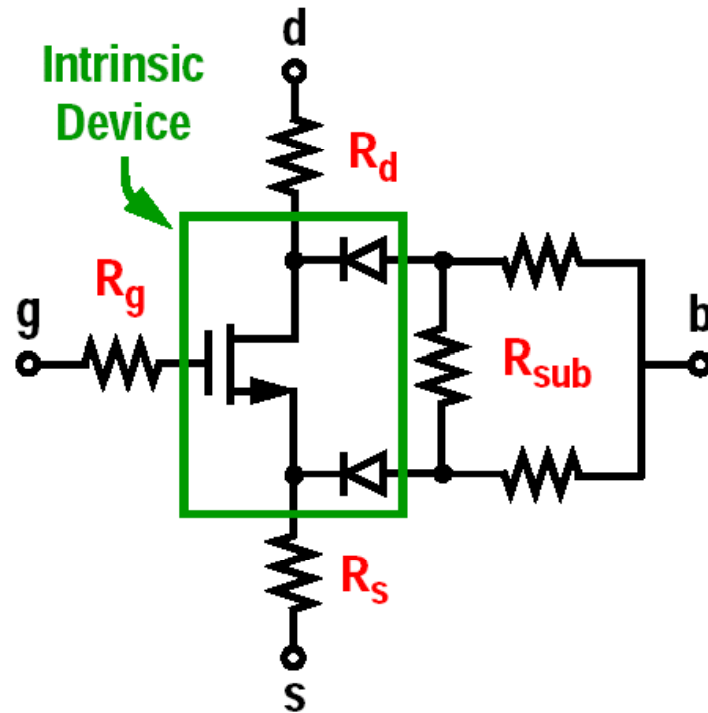

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$


$$f_{max} = \frac{f_T}{2\sqrt{g_{ds}(R_g + R_s)} + 2\pi f_T R_g C_{gd}}$$

$$NF_{min} = 1 + K \cdot \frac{f}{f_T} \cdot \sqrt{1 + g_m(R_g + R_s)}$$


- Minimize R_g , R_s , and R_{sub} for better performance
- Layout and biasing are both critical

Complete Macro Model

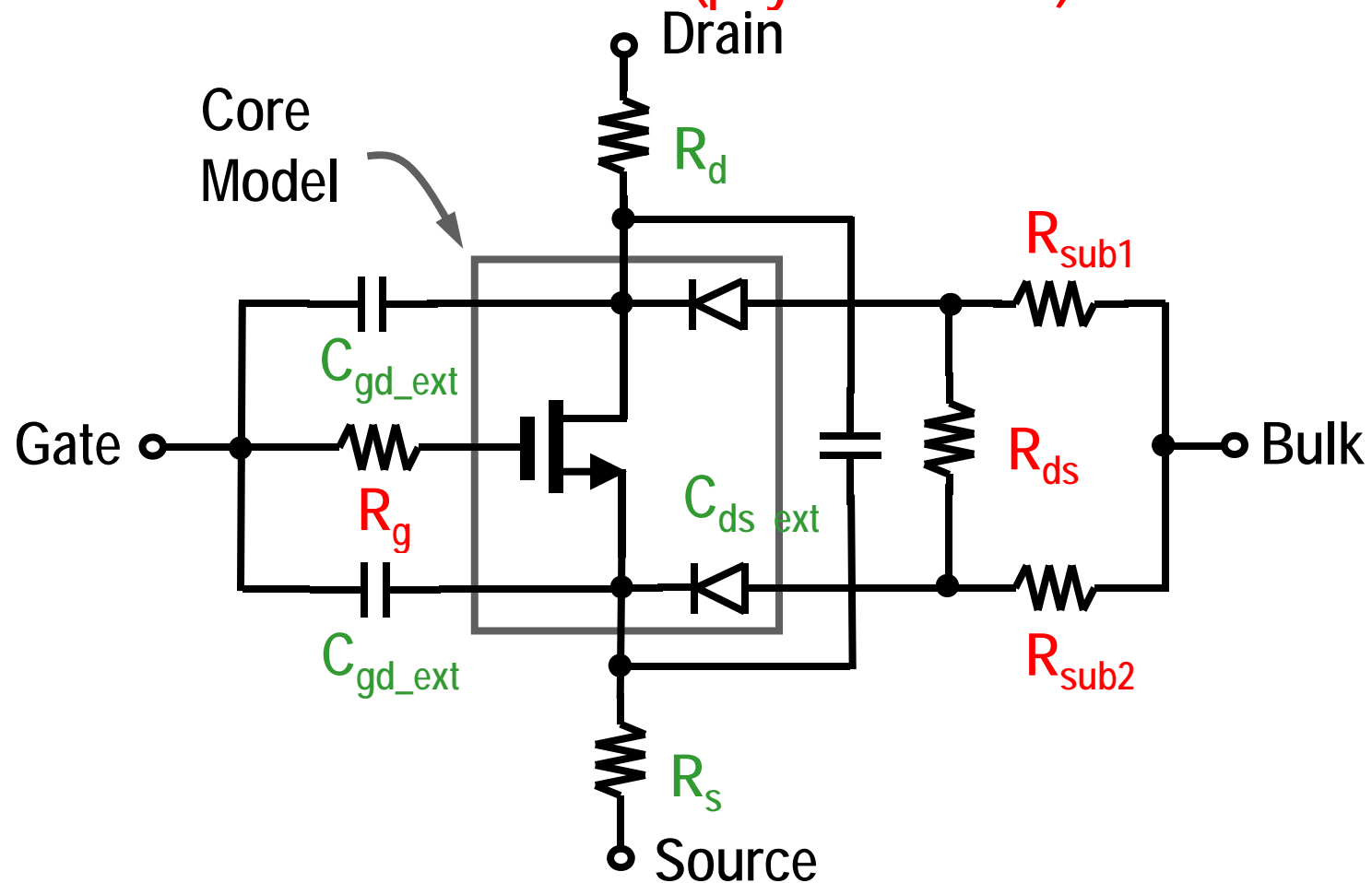- Core model (baseline BSIM model)
- Interconnect RC (3D EM field solver)
- Gate and substrate resistances (physical model)




Gate Resistance Components

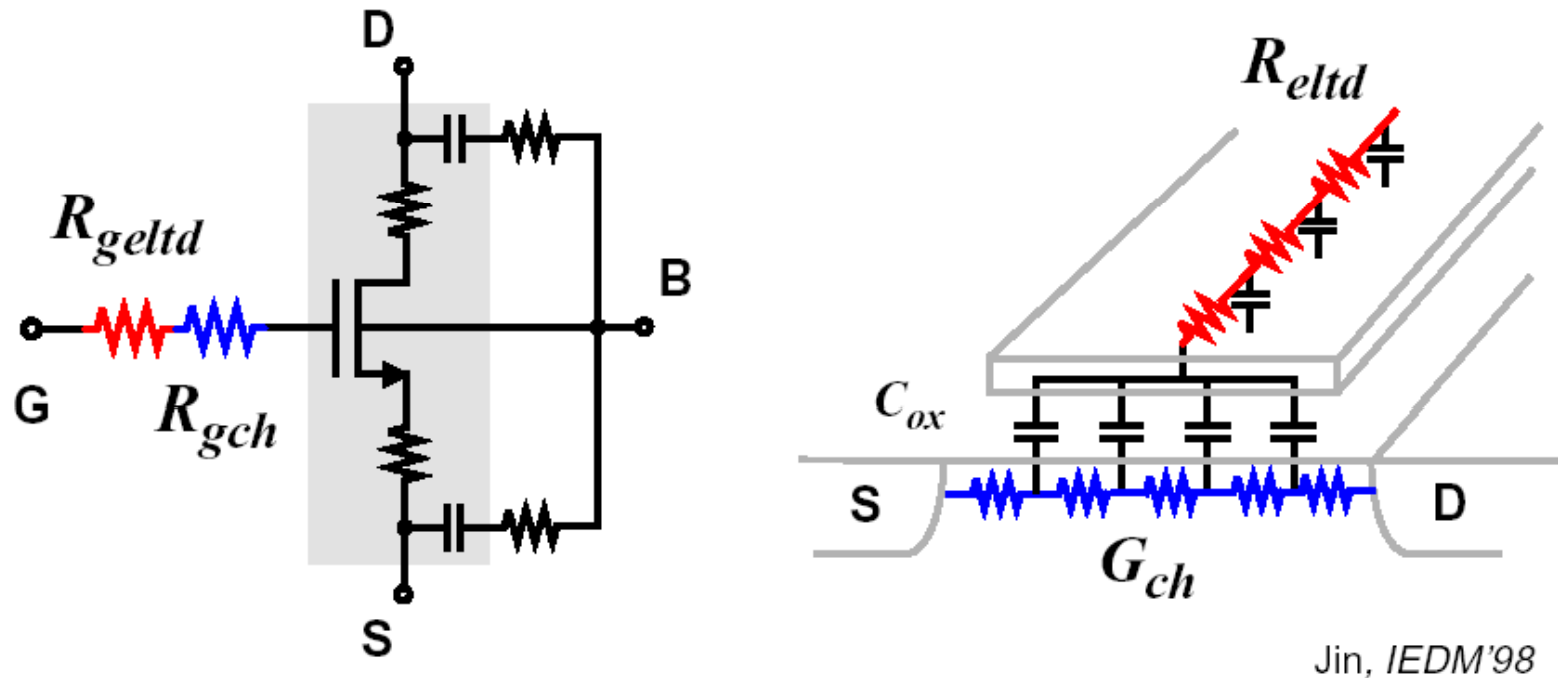

- R_{geltd} : distributed gate electrode resistance
- R_{gch} : channel induced gate resistance

Ref. 16

Gate Electrode Resistance

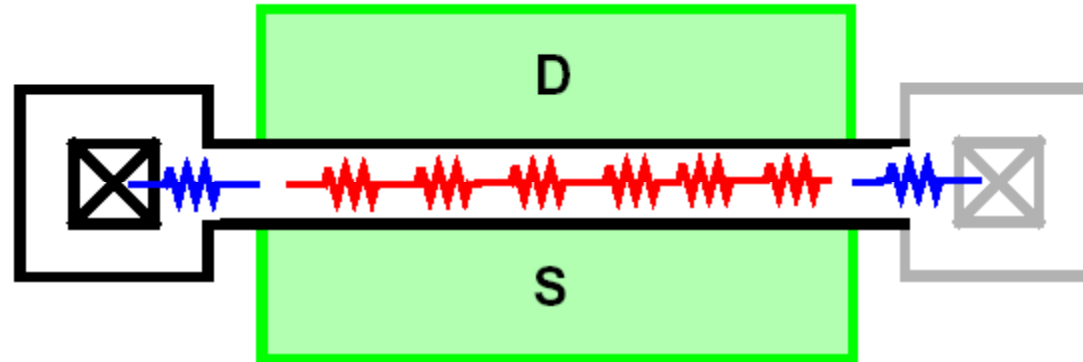


$$R_{geltd} = R_{eltd} \left(\alpha \frac{W}{L} + \beta \right) \quad \alpha = \begin{cases} 1/3 & \text{one side connected} \\ 1/12 & \text{two sides connected} \end{cases}$$

- α models distributed effect of gate electrode
- β models external gate resistance

Ref. 16 & 18

Channel Conductance

 

Two components in G_{ch} : $G_{ch} = G_{st} + G_{ed}$

- **Static** channel conductance $\propto \frac{L}{W}$

$$G_{st} = \frac{1}{\int dR} = \frac{I_d}{\int dV} = \begin{cases} I_d / V_{dsat} & \text{in saturation} \\ I_d / V_{ds} & \text{in triode} \end{cases}$$

- **Excess-diffusion** conductance

$$G_{ed} = \eta \frac{kT}{q} \mu_{eff} C_{ox} \frac{W}{L} \quad \eta \sim 1$$


Ref. 16

(ac effect – channel charge distribution modulated by gate voltage, derived based on diffusion current)

Layout Guideline for Gate Resistance



- Multi-finger layout in RF MOSFET is common to minimize R_{gate} (at the expense of more parasitic capacitance)
- Typical finger width for 0.25 μ m device is about 5 μ m whereas in 0.13 μ m CMOS is 1.5 μ m
- Total gate width ranges from a few 10's of micron for LNA, mixer & VCO to a few millimeters for PA
- R_{eltd} (poly resistance) scales with $1/n^2$
- External portion of R_{geltd} (contact resistance) scale with $1/n$
- R_{ch} is independent of n to the first order

Substrate Resistance Model

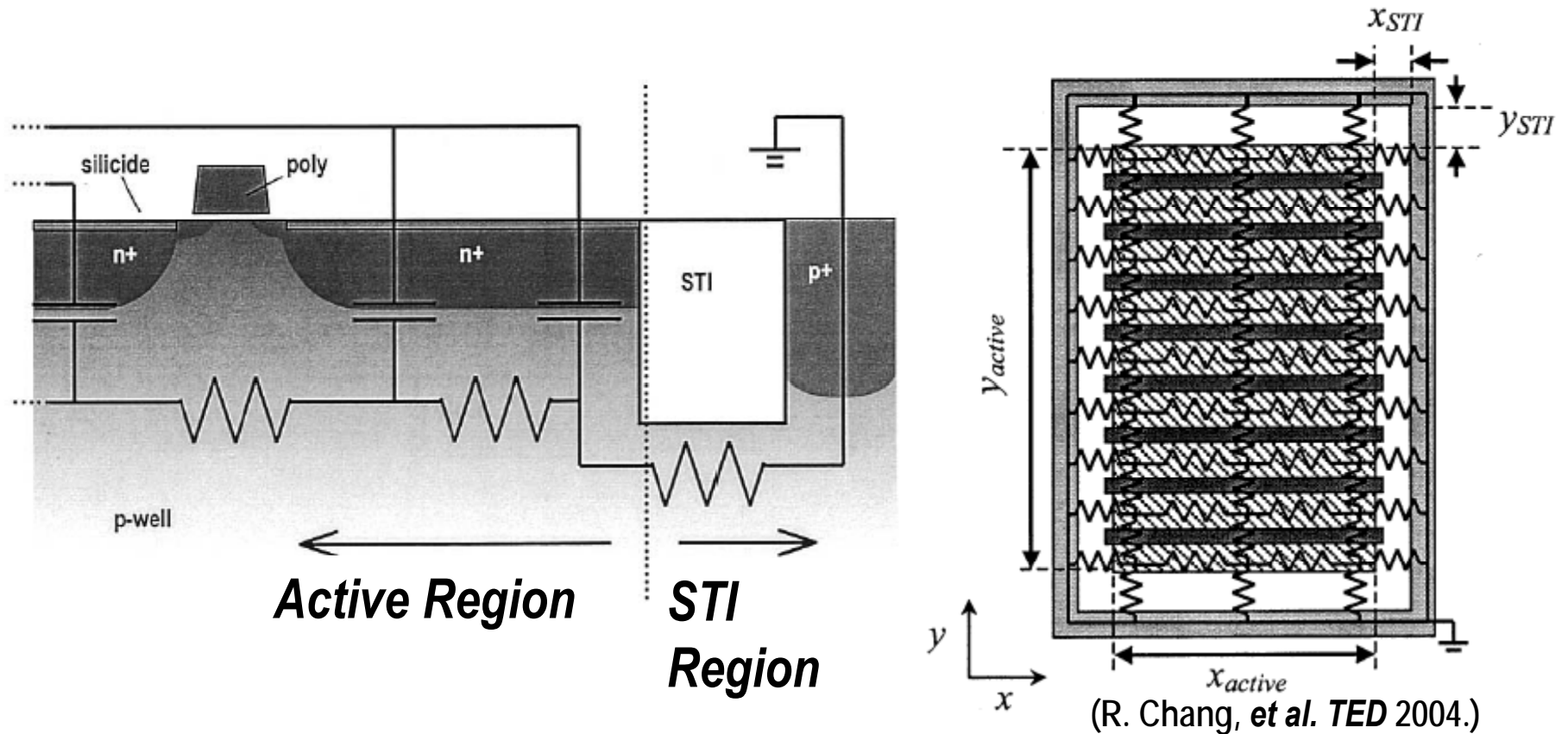

- Active and STI regions have different sheet resistances
- Resistances in x and y directions modeled as parallel resistors

Analytical Model of Substrate Resistance

  


$$R_{STI,x} = \frac{1}{2} R_{sh,STI} \frac{x_{STI}}{y_{act}}$$

$$R_{active,x} = \frac{1}{12} R_{sh,act} \frac{x_{act}}{y_{act}}$$



Ref. 17

Optimization of Substrate Resistance

 

Ref. 17

  
Interconnect RC Modeling Using 3D Field Solver



Width (μm)	nf	$C_{\text{gs_wire}}$ (fF)	$C_{\text{gd_wire}}$ (fF)	$C_{\text{ds_wire}}$ (fF)
2.0	4	2.42	1.61	1.41

- Wire capacitance per finger is extracted

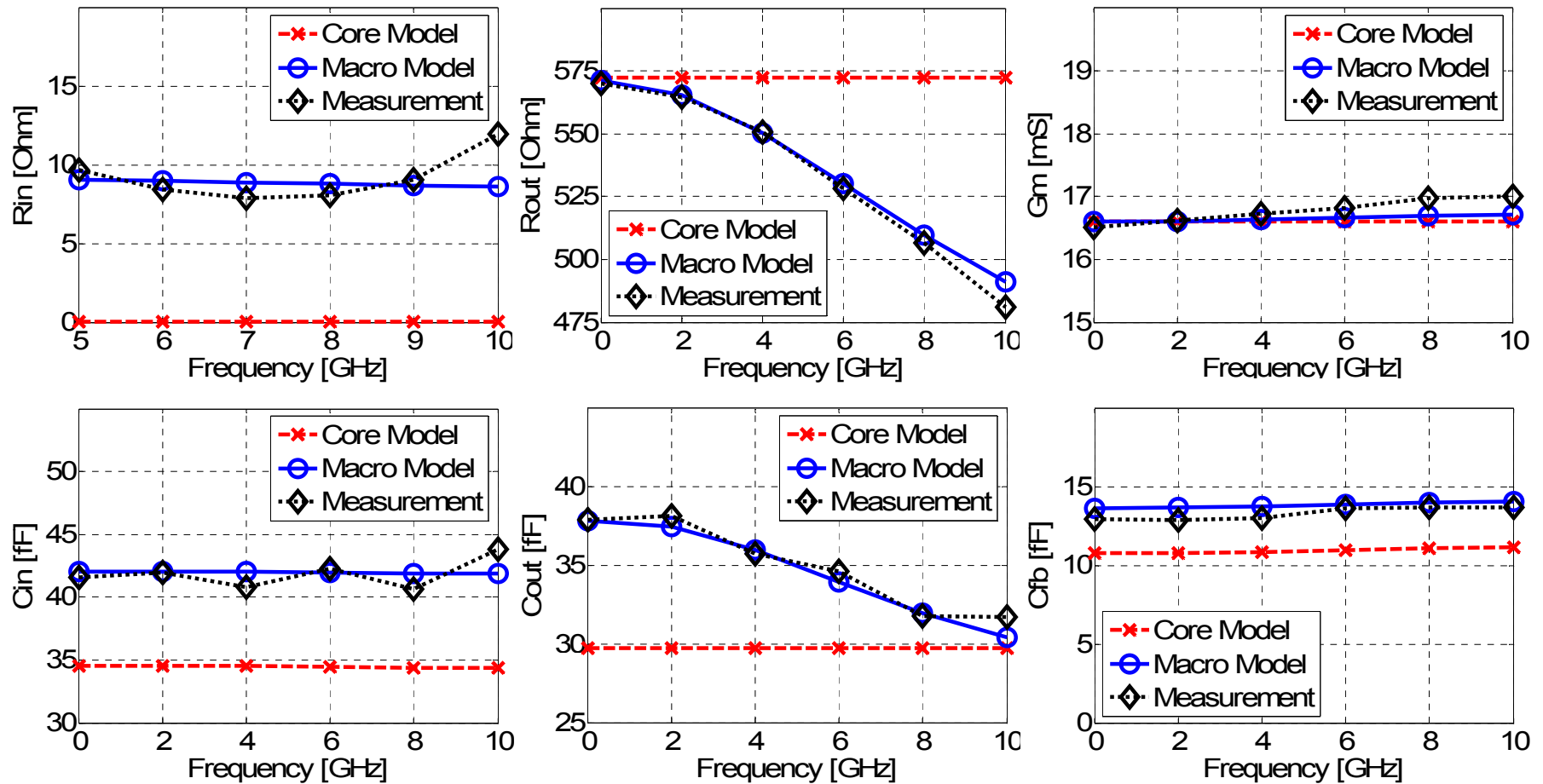
RF Macro Model vs. Measurement (16 x 2 μm / 0.12 μm)





$$R_g = 9.8 \, \Omega, R_{\text{sub}} = 475 \, \Omega, C_{\text{gs_ext}} = 4 \, \text{fF}, C_{\text{gd_ext}} = 2.9 \, \text{fF}, C_{\text{ds_ext}} = 5.2 \, \text{fF}$$

Optimized Layout for f_T , f_{max} and NF

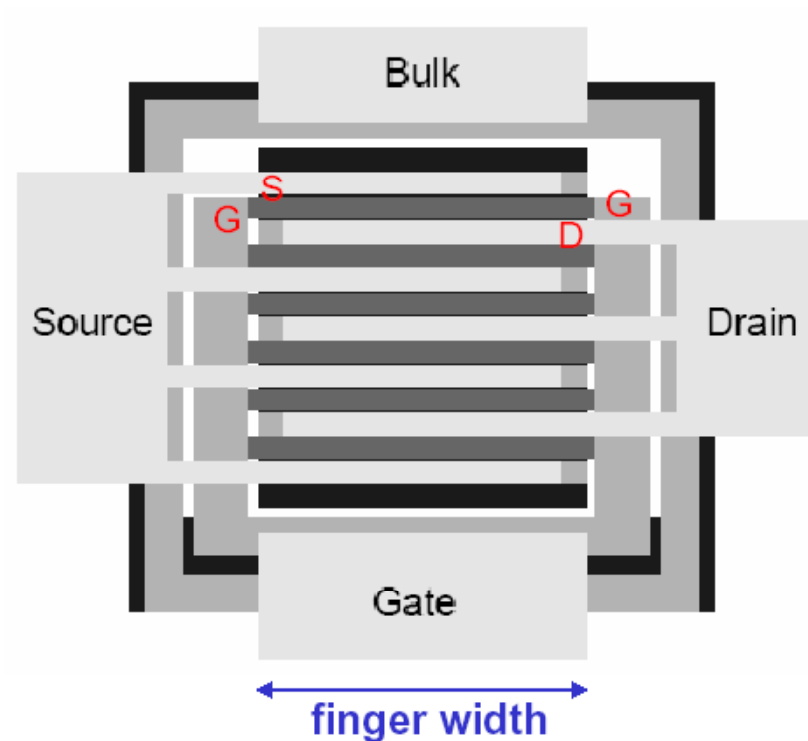- Parallel R_g improves f_{max} and NF_{min}
- Gate connected at both ends
- Source drain metals do not overlap
- Bulk contacts surround device



Optimal Finger Width for f_T

  

- f_T approaches v_{sat} / L deep in velocity saturation



Finger width \downarrow

\Rightarrow No. of fingers \uparrow

\Rightarrow Capacitance \uparrow



$\Rightarrow f_T \downarrow$

Optimal Finger Width for f_{\max}

  

- Reducing R_g vs. increasing C_{gg}
- For 0.13- μm , optimal finger width is $\sim 2\mu\text{m}$
- Optimal finger width decreases with device scaling

Optimal Finger Width for NF


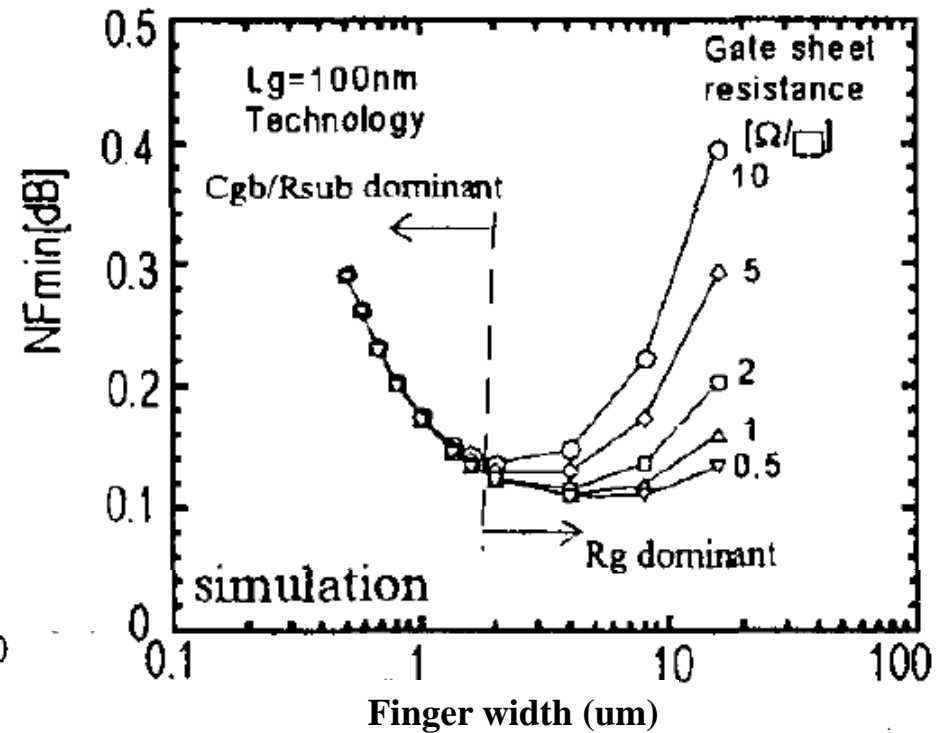
 


- Noise due to Rg and Rsub can be minimized through layout optimization

Ref. 11


Optimal Biasing for f_T , f_{MAX} and NF_{MIN}

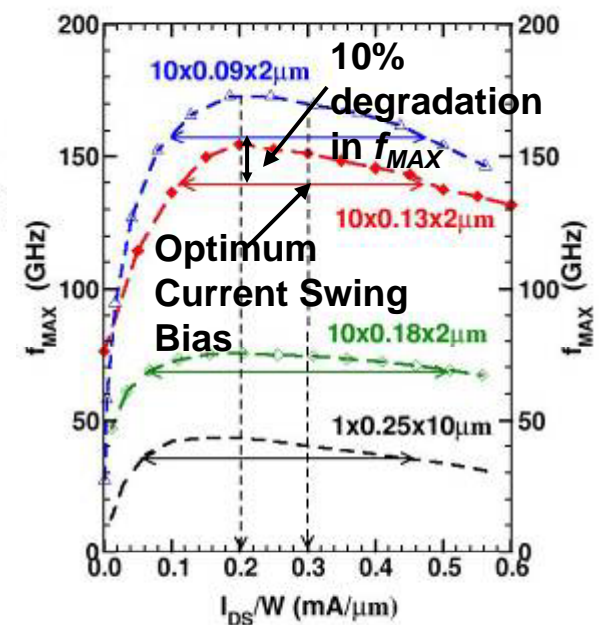 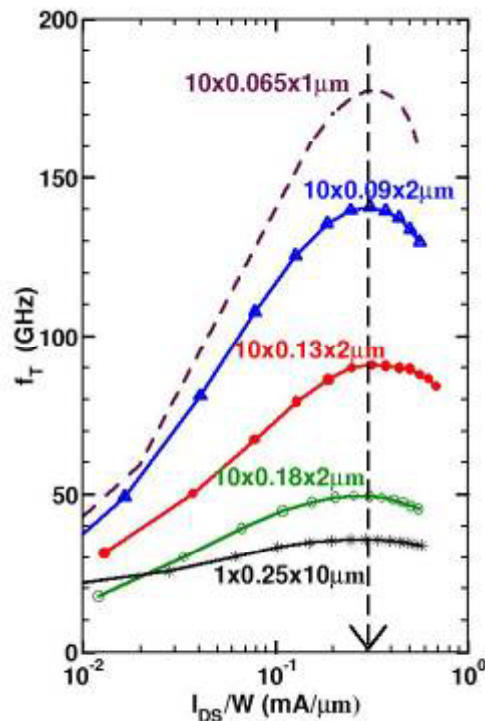- Peak f_T , f_{MAX} and NF_{MIN} characteristic current densities largely unchanged across technology nodes and foundries
- NF_{MIN} (0.15mA/ μ m) and peak f_{MAX} (0.2mA/ μ m) are close \rightarrow LNAs simultaneously optimized for noise and high gain
- In CMOS PAs optimum current swing when biased at 0.3mA/ μ m




Source: Yao, RFIC 2006. - U. of Toronto

Frequency Response of On-Chip Inductor Q

 



First Patterned Ground Shield (PGS)

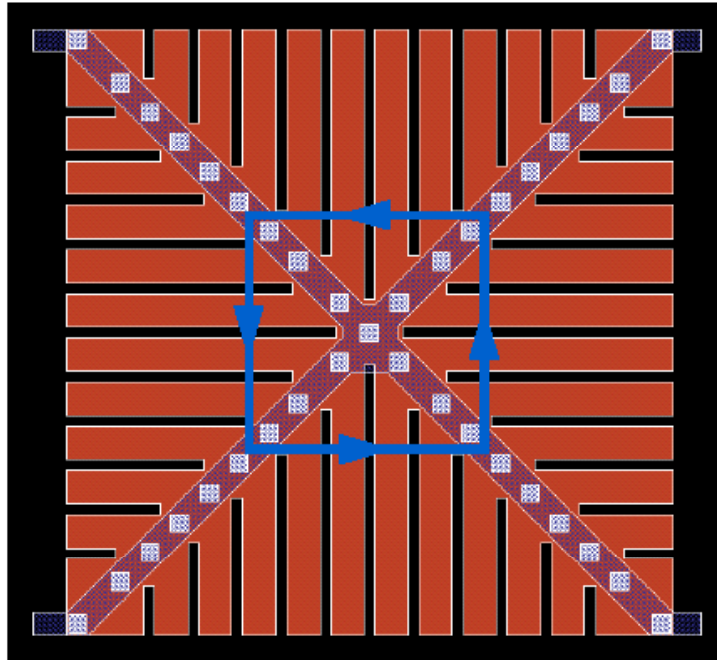

-  Silicided polysilicon
-  Induced eddy current


- Inserted between the inductor and substrate
- PGS fingers connected in a “star” shape
- Terminates the E field
- No effect on the H field
- Improves isolation

  Self-Shielded Stacked Inductors for high SRF




- Self-shielded layout can effectively boost-strap the overlap capacitance *
- 1-nH inductor can be achieved in $25 \times 25 \mu\text{m}^2$ using M5 through M8 in a 0.13- μm CMOS 8-metal process

* C.-C. Tang, *JSSC*, April 2002.

 

Systematic mm-wave Design with P-Cells


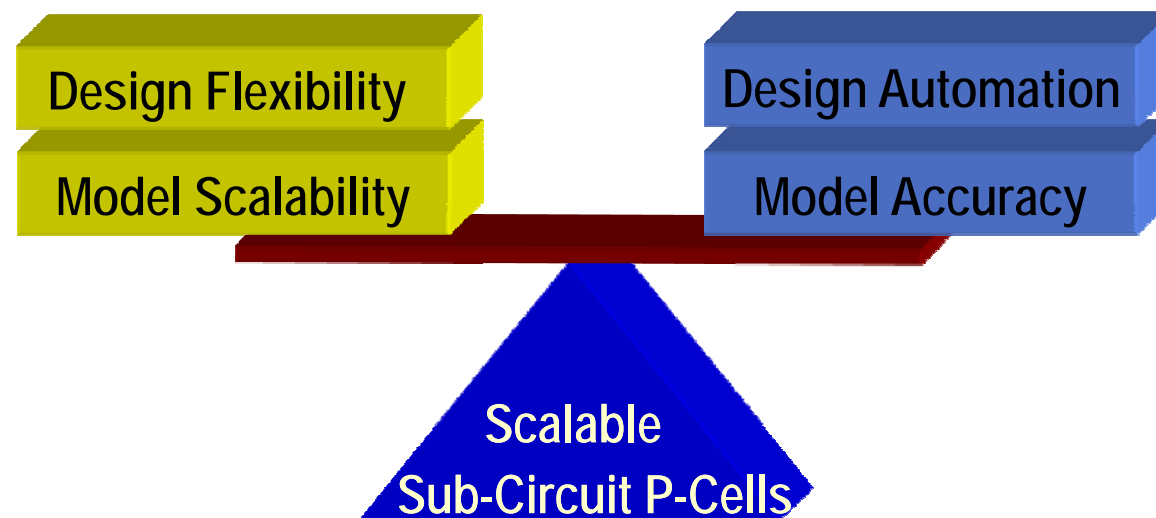
- Stand-alone single device model is insufficient
- Interconnect model accuracy limited by digital RC extraction
- Test structure layout \neq actual circuit layout





- ❑ Leverage the insight to device layout optimization
- ❑ Exploit the modularity at the sub-circuit level

Sample P-Cell Layouts and Circuit Models



Diff Pair

  


Cross-Coupled Pair

  

Cascode

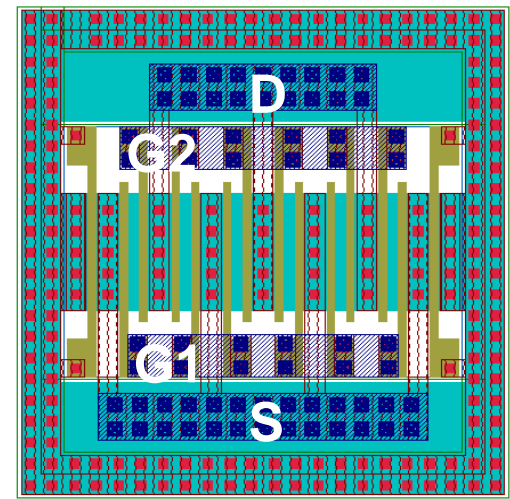 

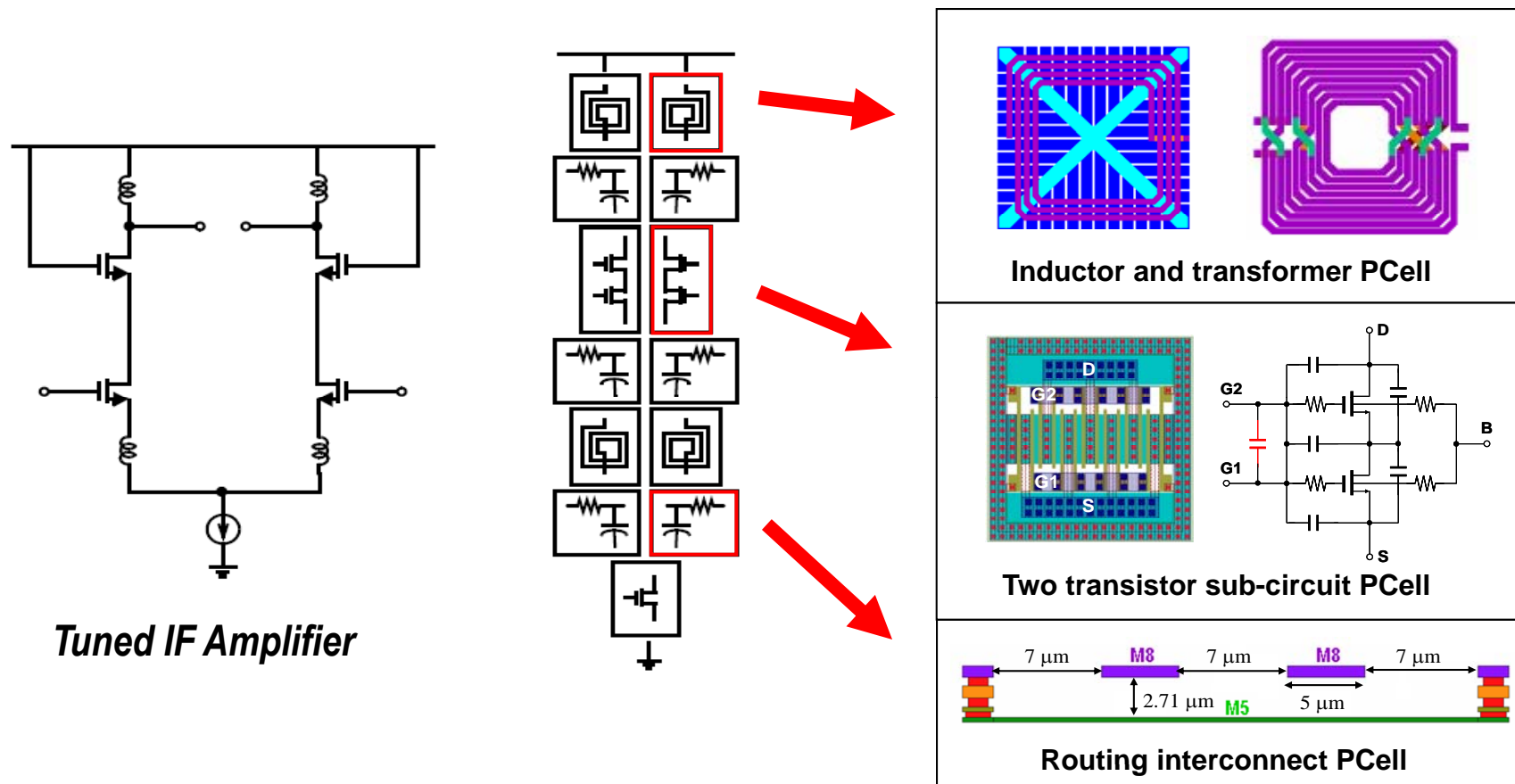
Sub-Circuit Cell Library for mm-wave Design



- ❑ A unified design and modeling framework
- ❑ Each sub-circuit P-Cell has its scalable circuit model

mm-wave P-Cell Characterization Test Structures

 - Measured S-parameters to validate macro models
- UMC 0.13- μm CMOS with 8 copper layers



Outline

- Background
 - Emerging mm-wave applications
 - Open design issues for mm-Wave CMOS
- CMOS for mm-wave design
 - Optimizing CMOS device performance – layout & bias
 - On-chip inductors in CMOS
 - Cell-based device modeling and design methodology
 - State of the art CMOS mm-Wave design examples
- **mm-Wave design techniques**
 - Device characterization issues
 - Unconditionally stable, gain-matched amplifier design procedure
 - Tuned amplifier, power amplifier design examples
 - On-chip transmission line design
- Summary
- References

140-220 & 220-330 GHz On-Wafer Network Analysis

- HP8510C VNA,
Oleson Microwave Lab mm-wave
Extenders
- coplanar wafer probes made by:
GGB Industries, Cascade Microtech
- connection via short length of
waveguide
- Internal bias Tee's in probes for biasing
active devices
- measurements to 100 GHz
can be in coax.



GGB Wafer Probes
330 GHz available with bias Tees



High Frequency Device Gain Measurements : Standard Pads

Measuring wideband transistors is very hard ! Much harder than measuring amplifiers.
Determining f_{max} in particular is extremely difficult on high- f_{max} or small devices

Standard "short pads"

must strip pad capacitance




must strip pad inductance--or f_t will be too high !

cal can be bad due to substrate coupling

make pads small, and shield them from substrate

cal can be bad due to probe coupling

   use small probe pitch, use well-shielded probes









High Frequency Measurements : On-Wafer LRL

Extended Reference planes

transistors placed at center of long on-wafer line
 LRL standards placed on wafer
 large probe separation → probe coupling reduced
 still should use the best-shielded probes available

      Problem: substrate mode coupling

method will FAIL if lines couple to substrate modes
 → method works very poorly with CPW lines
 need on wafer thin-film microstrip lines



Unilateral Power Gain



1) Cancel device feedback with external lossless feedback

$$\rightarrow Y_{12} = S_{12} = 0$$

2) Match input and output

Resulting power gain is Mason's Unilateral Gain

$$U = \frac{|Y_{21} - Y_{12}|^2}{4(G_{11}G_{22} - G_{21}G_{12})}$$

 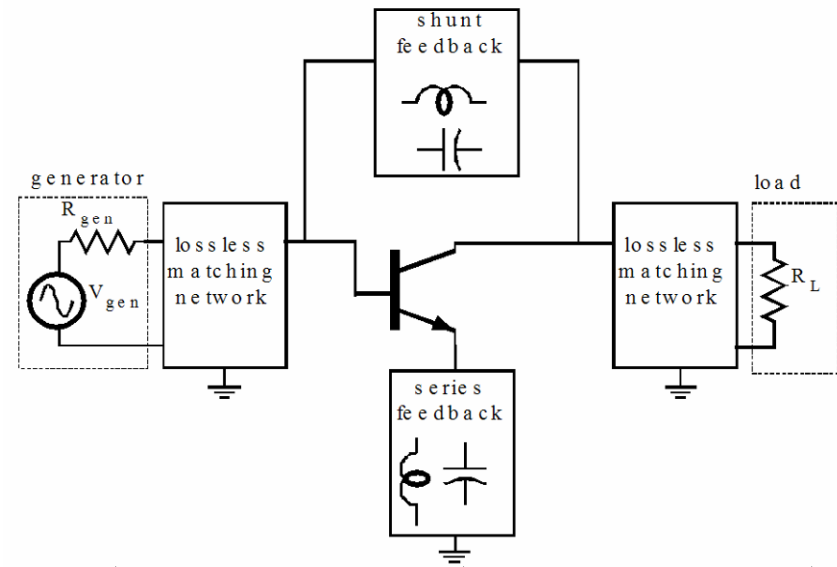

Monolithic amplifiers are not easily made unilateral

→ U mostly of historical relevance to IC design

For simple BJT model, U rolls off at -20 dB/decade

→ U useful for extrapolation to find f_{\max}

In III - V FETs, U shows peak from $C_{ds} - R_s - R_d$ interaction


→ U hard to use for f_{\max} extrapolation

For bulk CMOS, C_{ds} is shielded by substrate

→ U should be OK for f_{\max} extrapolation

Design Tools: Power Gain Definitions

Transducer Gain

 


$$G_T = P_{load} / P_{av,gen}$$

$$= \frac{\text{load power}}{\text{power available from generator}}$$

= general - case gain

Available Gain

 


$$G_A = P_{av,a} / P_{av,gen}$$

$$= \frac{\text{power available from amplifier}}{\text{power available from generator}}$$

= gain with output matched

Insertion Gain

 


$$\|S_{21}\|^2 = P_{av,a} / P_{av,gen}$$

$$= \frac{\text{power delivered to } Z_o \text{ load}}{\text{power available from } Z_o \text{ generator}}$$

= gain in a 50 Ohm environment

Operating Gain

 


$$G_P = P_{load} / P_{gen,delivered}$$

$$= \frac{\text{load power}}{\text{power delivered from generator}}$$

= gain with input matched

Maximum Available Gain

 


$$G_{Max} = P_{av,a} / P_{gen,delivered}$$

$$= \frac{\text{power available from amplifier}}{\text{power delivered from generator}}$$

= gain with both ports matched
 ...MAG may not exist...

After impedance-matching:

 


$$\|S_{21,matched}\|^2 = G_{max,raw}$$

$$S_{11,matched} = S_{22,matched} = 0$$

...but only if unconditionally stable...


Design Tools: Stability Factors, Stability Circles
 
$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{12}S_{21}}{1 - S_{22}\Gamma_L}$$




Load Stability Circle
 
$$\Gamma_{out} = S_{22} + \Gamma_S \frac{S_{12}S_{21}}{1 - S_{11}\Gamma_S}$$




Source Stability Circle

 

L_StabCircle1

Values of Γ_L which make $\|\Gamma_{in}\| = 1 \rightarrow$ beyond lies negative R_{in}

 

S_StabCircle1

Values of Γ_S which make $\|\Gamma_{out}\| = 1 \rightarrow$ beyond lies negative R_{out}


Unconditionally stable
(stable with all (Γ_L, Γ_S) if :

$K =$ Rollet stability factor

$$= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \det^2[S]}{2|S_{21}S_{12}|} > 1$$

and $B =$ stability measure

$$= 1 - |S_{11}|^2 - |S_{22}|^2 - \det^2[S] > 0$$


 


Negative port impedance \rightarrow negative-R oscillator
Tuning for highest gain \rightarrow infinite gain (oscillation)

Design Tools: Maximum Stable Gain


Maximum stable gain = MSG

$$= \frac{|S_{21}|}{|S_{12}|} = \frac{|Y_{21}|}{|Y_{12}|} = \frac{|Z_{21}|}{|Z_{12}|}$$


 
 


Adding series/shunt resistance excludes source or load from unstable regions → stabilizes



circles at 50 GHz

 

stabilization methods

   




results

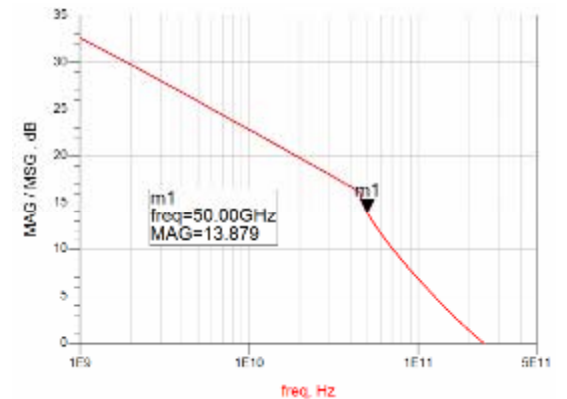 


Design Procedure: Simple Gain-Matched Amplifier

First:
stabilize at the design frequency

 
 
 
---device is potentially unstable
 at 100 GHz design frequency



 source stability circle:
 ~5 Ohm on input will
 overstabilize the device



   After stabilizing
 (slightly over-stabilizing)




Design Procedure: Simple Gain-Matched Amplifier

Second:

Determine required interface impedances

The G_a & G_p circles define the source & load impedances which the transistor must see

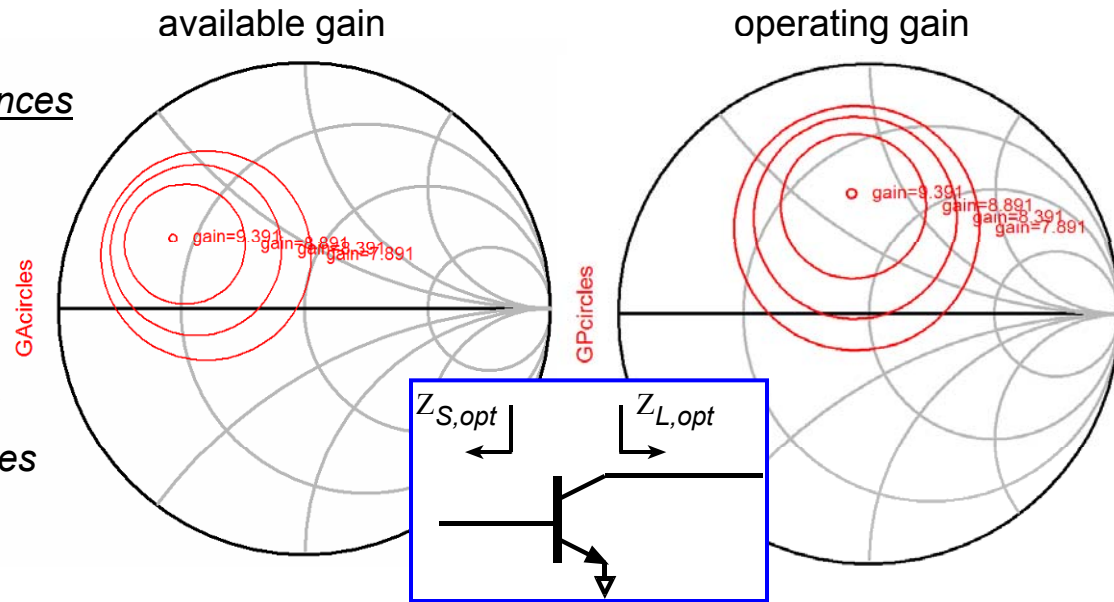...it is necessary to **OVERSTABILIZE** the device to move the G_a & G_p circles towards the Smith chart center





Third:

Design Input & Output Tuning Networks


...to provide these impedances...

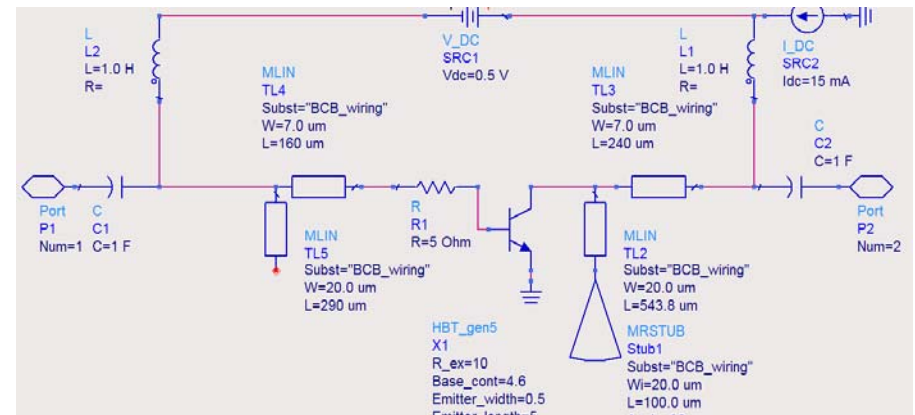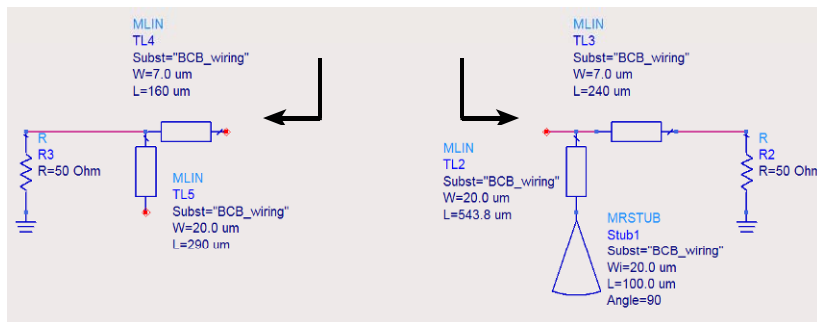...added to device, the amplifier is not yet complete...




Design Procedure: Simple Gain-Matched Amplifier


 
Forth:
Add out-of-band stabilization
 potentially unstable
 below 75 GHz



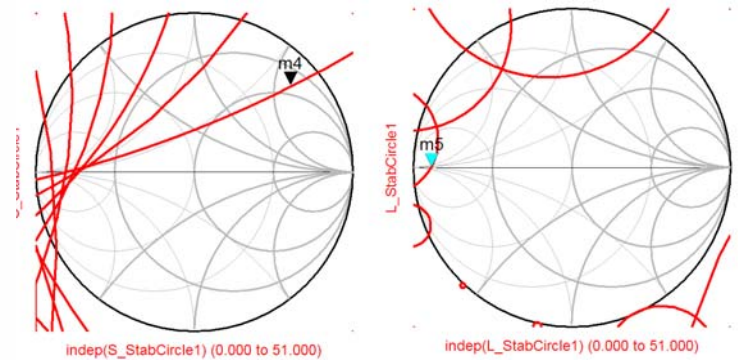
source & load stability circles & 10,20,...,100 GHz



 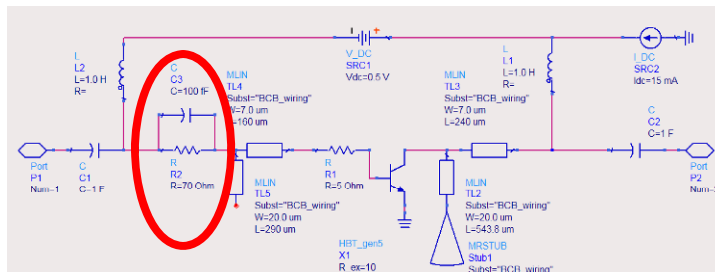with frequency-selective
 series stabilization



 ...caused only slight mistuning
 & slight gain drop @ 100 GHz



...and is unconditionally
 stable above 10 GHz

Design Procedure: Effect of Line Losses




Finally:
adjusting for line losses

high line skin effect losses → reduced gain

but line losses also increase stability factor

loss in gain are partly recovered
by reducing stabilization resistance &
re-tuning the design

 
 
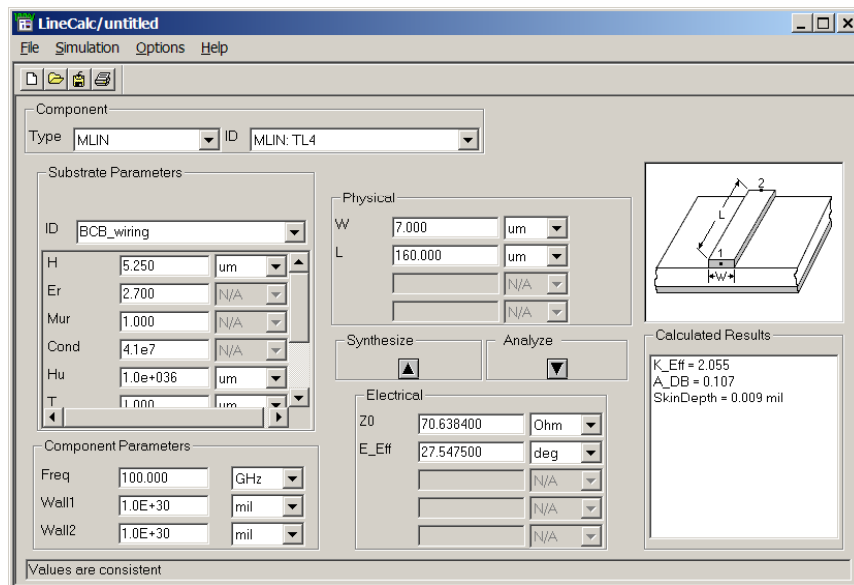
--no analytical procedure; just component tweaking







**line losses have severe impact
...in VLSI wiring environment
...particularly at 50 + GHz
...particularly with high-power amplifiers**

Tuned Amplifier Examples

3-stage cascode in 180 nm CMOS

   

III-V HBT small-signal amplifiers

    

Note: simple gain-tuned amplifiers → limited applications

Transmitters need power amplifiers: need output loadline-match, not gain-match




Receivers need low-noise amplifiers: need input noise-match, not gain-match

Power Amplifier Design (Cripps method)

For maximum saturated output power, & maximum efficiency device intrinsic output must see optimum loadline set by:

$$P_{\max} = (1/8)(V_{\max} - V_{\min})I_{\max}$$

 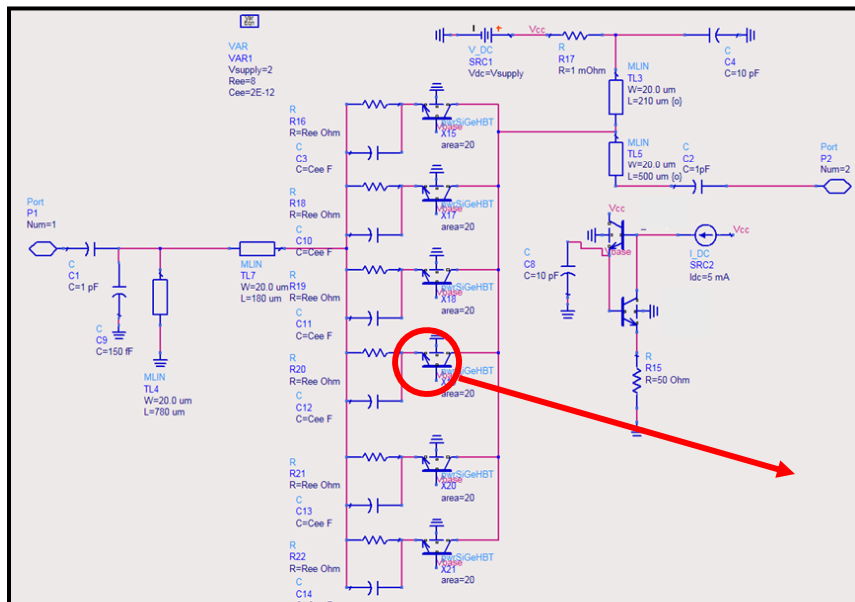 breakdown, maximum current, maximum power density.




ammeter monitors intrinsic junction current without including capacitive currents

...($V_{\text{collector}} - V_{\text{emitter}}$) measures voltage internal to series parasitic resistances...



Power Amplifier Design (Cripps Method)

Design steps are


 
- 1) input stabilization (in-band)
- 2) output tuning for correct load-line
- 3) input tuning (match)
- 4) out-of-band stabilization




Example: 60 GHz, 30 mW PA, 130 nm BiCMOS

 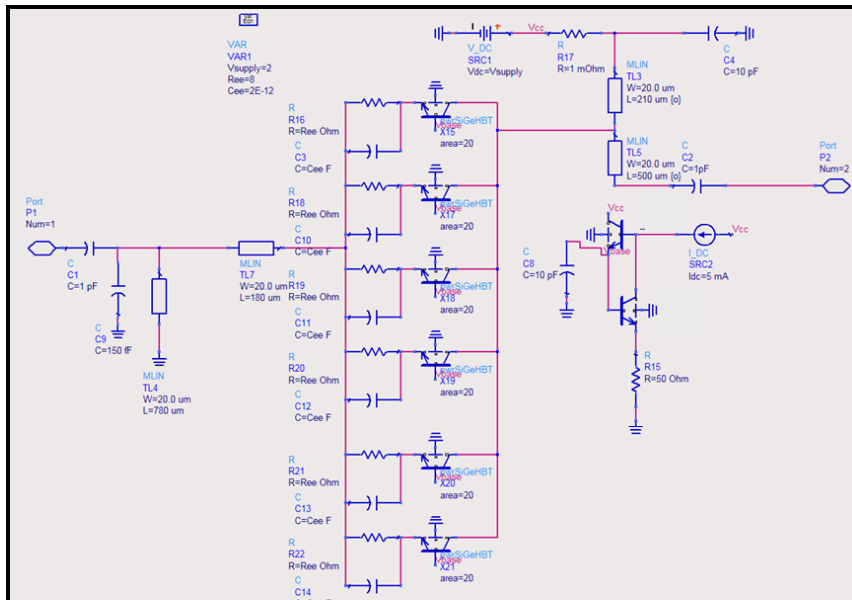

 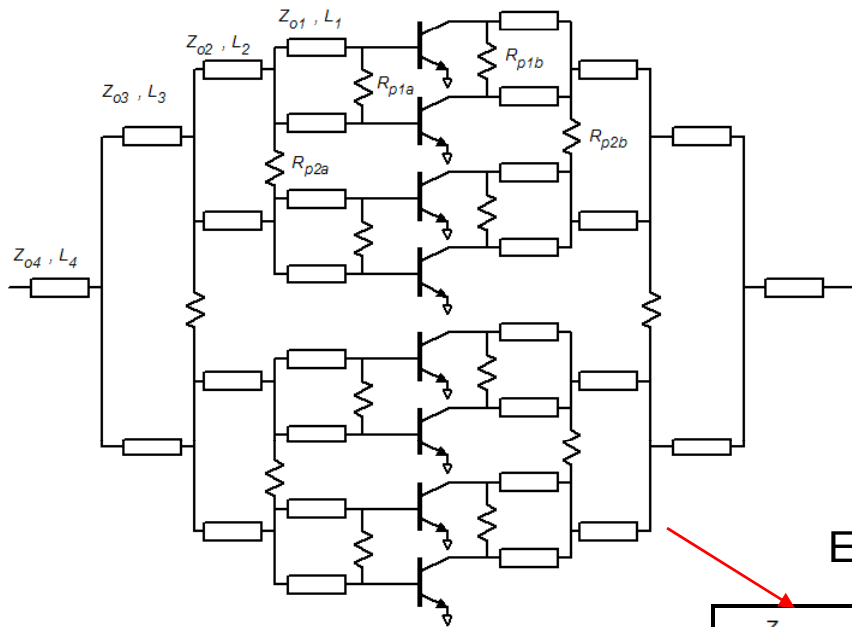Design: Multi-Finger Power Amplifiers: Even-mode method




Even-mode equivalent circuit

 

- Most multi-finger amplifiers do not use Wilkinson combiners: lines are too long
- Even-mode equivalent circuit maps combined design into single-device design
- Final design tuning (E&M simulation) with full circuit model

***This method explicitly models all feed parasitics in a large multi-finger transistor
MUCH more reliable than using single lumped model for multi-finger device***

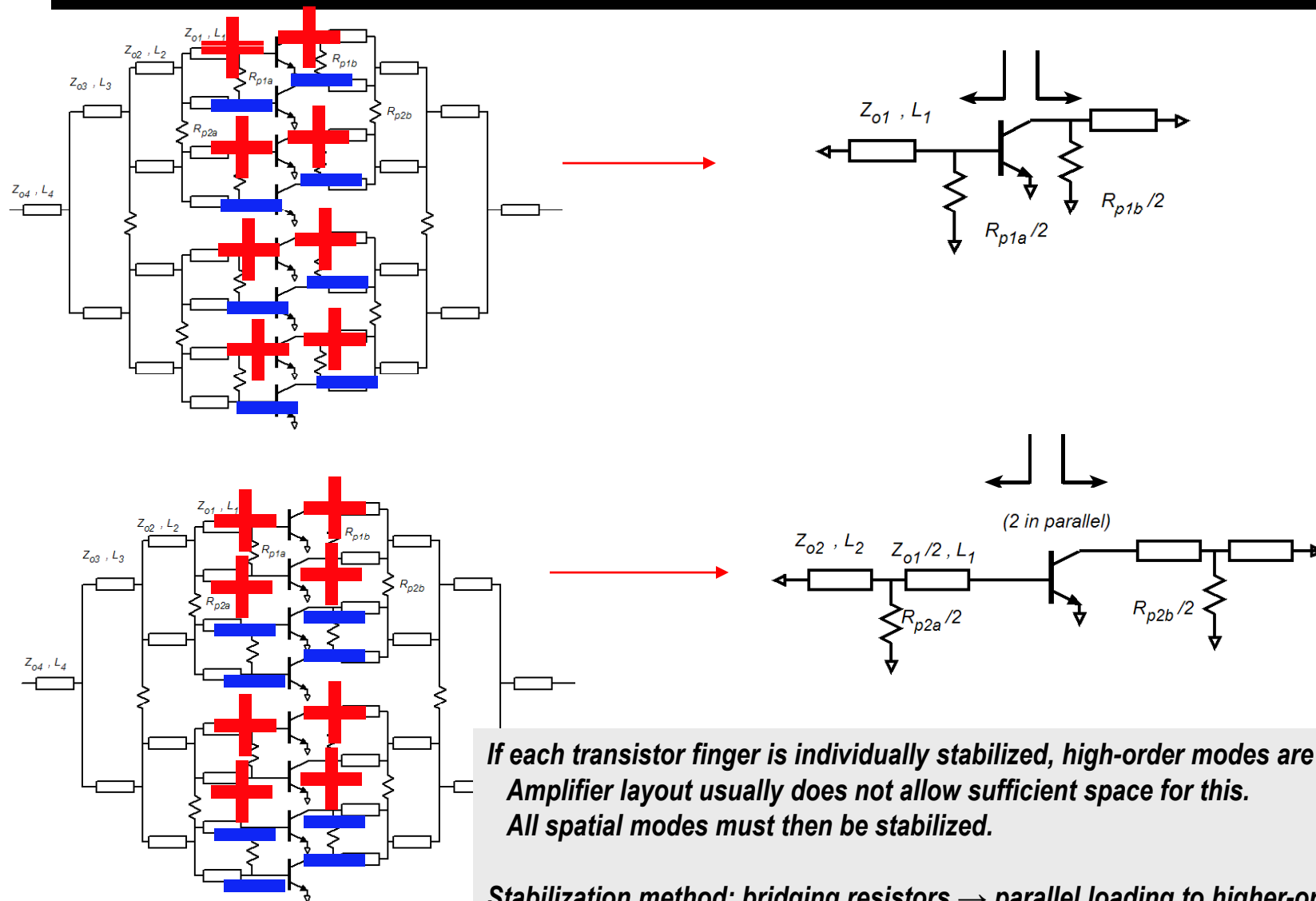Design: Multi-Finger Amplifiers: spatial mode instabilities




If each transistor finger is individually stabilized, high-order modes are stable. Amplifier layout usually does not allow sufficient space for this. All spatial modes must then be stabilized.


*Stabilization method: bridging resistors → parallel loading to higher-order modes
Select so that (Z_S, Z_L) presented to device lie in the stable regions*

etc...

 
Design: Multi-Finger Amplifiers: Layout Examples



 mm-wave InP HBT power amplifier - Rockwell



W-band InP HBT power amplifier - UCSB

 

mm-wave InP HBT power amplifier - Rockwell

Low-Noise Amplifier Design-- device model

Basic model : Van der Ziel

$$S_{VV,R_g} = 4kTR_g \quad (V^2 / Hz)$$

$$S_{VV,R_i} = 4kTR_i \quad (V^2 / Hz)$$

$$S_{VV,R_s} = 4kTR_s \quad (V^2 / Hz)$$

$$S_{II,channel} = 4kT\Gamma g_m \quad (A^2 / Hz)$$

$$\Gamma = \begin{cases} 2/3 : \text{long channel, constant mobility} \\ > 2/3 \text{ under high field} \end{cases}$$

Cross spectral - densities can be neglected
(B. Hughes, IEEE Trans MTT)



Simplified noise model

$$S_{VV,R_{in}} = 4kTR_{in} \quad (V^2 / Hz)$$

$$S_{II,channel} = 4kT\Gamma' g_m$$

$$\Gamma' \rightarrow \Gamma \text{ as } g_m R_s \rightarrow 0$$
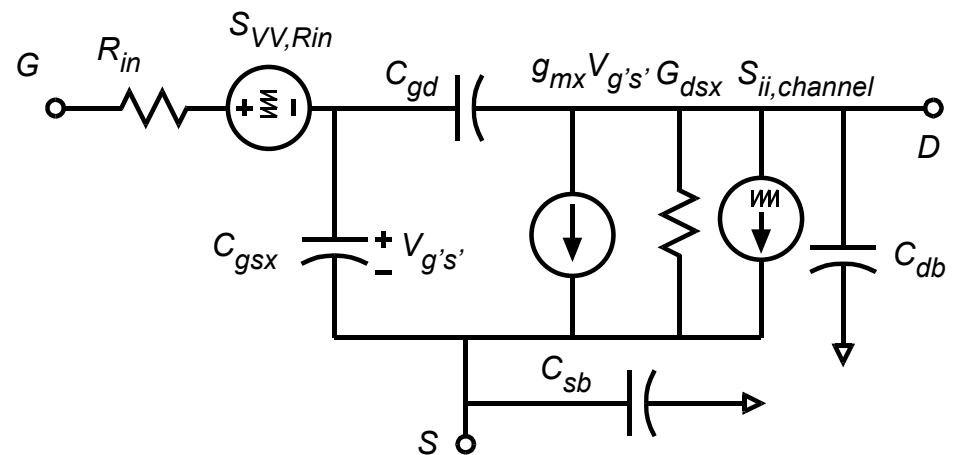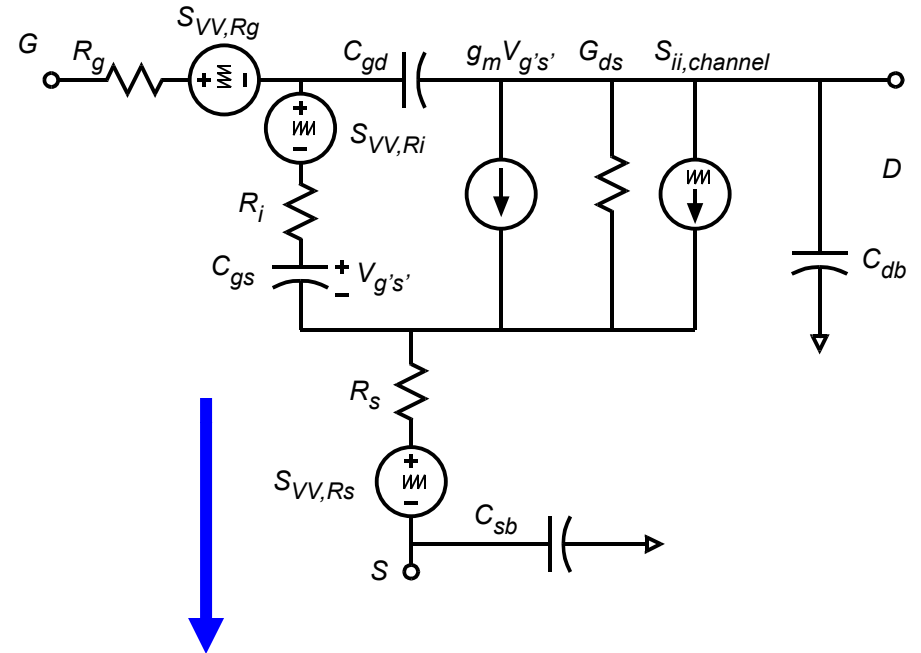
$$\Gamma' \rightarrow 1 \text{ as } g_m R_s \rightarrow \infty$$




Low-Noise Amplifier Design-- sketch of steps in F_{min} calculation

Total input noise voltage & current spectral densities :

$$S_{E_n}(f) = 4kTR_{in} + \frac{4kT\Gamma}{g_m} \left(1 + (2\pi f C_{gs})^2 R_{in}^2 \right) \quad (V^2 / Hz)$$


$$S_{I_n}(f) = \frac{4kT\Gamma}{g_m} (2\pi f C_{gs})^2 \quad (A^2 / Hz)$$
 
$$S_{E_n I_n}(f) = \frac{4kT\Gamma}{g_m} (1 + j2\pi f C_{gs} R_{in}) (j2\pi f C_{gs})^* \quad (V \times A / Hz)$$



Noise figure with a particular source impedance :

$$F = 1 + \frac{S_{E_n} + |Z_s|^2 S_{I_n} + 2 \cdot \text{Re}(Z_s^* S_{E_n I_n})}{4kT \text{Re}(Z_s)}$$

 

Minimum noise figure


$$F_{min} = 1 + \frac{1}{4kT} \left[2\sqrt{S_{E_n} S_{I_n} - (\text{Im}[S_{E_n I_n}])^2} + 2 \text{Re}[S_{E_n I_n}] \right]$$

$$Z_{opt} = R_{opt} + jX_{opt} = \sqrt{\frac{S_{E_n}}{S_{I_n}} - \left(\frac{\text{Im}[S_{E_n I_n}]}{S_{I_n}} \right)^2} - j \frac{\text{Im}[S_{E_n I_n}]}{S_{I_n}}$$

→ Fukui Expression (rough)

$$F_{min} \sim 1 + 2\sqrt{\Gamma(R_s + R_g + R_i)g_m} \cdot \left(\frac{f_{signal}}{f_\tau} \right)$$

 
$$Z_{opt} \sim \sqrt{\frac{R_s + R_g + R_i}{\Gamma g_{mx}}} \cdot \left(\frac{f_\tau}{f_{signal}} \right) + \frac{1}{j2\pi f_{signal} C_{gs}}$$




Low-Noise Amplifier Design

Design steps are

 - 1) output stabilization (in-band)
- 2) input tuning for F_{min}
- 3) output tuning (match)
- 4) out-of-band stabilization





Noise and Available Gain Circles

 


Discrepancy in input noise-match & gain-match can be reduced by adding source inductance (R. Van Tuyt)

Example: 60 GHz, LNA, 130 nm BiCMOS

 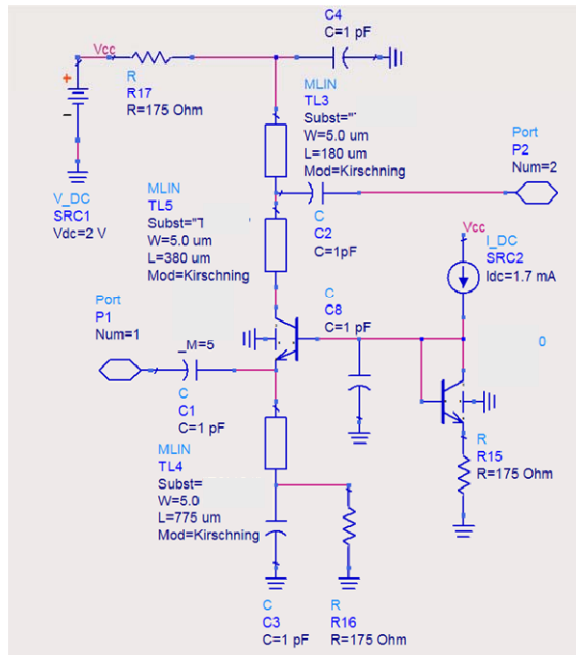

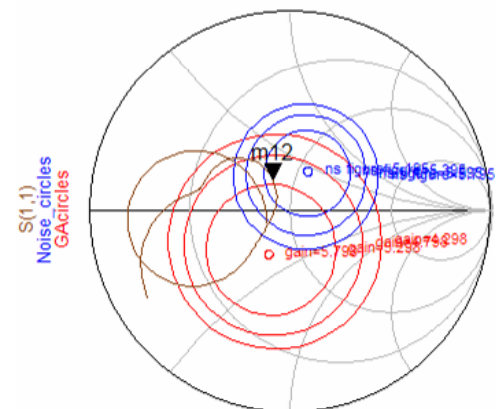gain & noise circles after input matching
note compromise between gain & noise tune




III-V MIMIC Interconnects -- Classic Substrate Microstrip

Thick Substrate
→ low skin loss

$\alpha_{skin} \propto \frac{1}{\epsilon_r^{1/2} H}$

Zero ground inductance in package


No ground plane breaks in IC

 

High via inductance


12 pH for 100 μm substrate -- 7.5 Ω @ 100 GHz

TM substrate mode coupling

 


Strong coupling when substrate approaches ~λ_g/4 thickness

lines must be widely spaced

 

Line spacings must be ~3*(substrate thickness)


ground vias must be widely spaced

 


all factors require very thin substrates for >100 GHz ICs
→ lapping to ~50 μm substrate thickness typical for 100+ GHz

Coplanar Waveguide

 
No ground vias
No need (???) to thin substrate




Hard to ground IC to package

 

Parasitic microstrip mode

 


 ground plane breaks → loss of ground integrity



Parasitic slot mode

 
substrate mode coupling or substrate losses




III-V: semi-insulating substrate → substrate mode coupling

Silicon conducting substrate → substrate conductivity losses

 
Repairing ground plane with ground straps is effective only in simple ICs
In more complex CPW ICs, ground plane rapidly vanishes
→ common-lead inductance → strong circuit-circuit coupling



 40 Gb/s differential TWA modulator driver
note CPW lines, fragmented ground plane



 35 GHz master-slave latch in CPW
note fragmented ground plane



175 GHz tuned amplifier in CPW
note fragmented ground plane

poor ground integrity



loss of impedance control



ground bounce



coupling, EMI, oscillation



III-V MIMIC Interconnects -- Thin-Film Microstrip

narrow line spacing → IC density



no substrate radiation, no substrate losses



fewer breaks in ground plane than CPW



... but ground breaks at device placements





still have problem with package grounding




...need to flip-chip bond

  thin dielectrics → narrow lines
 → high line losses
 → low current capability
 → no high- Z_o lines



InP mm-wave PA (Rockwell)
 
$$Z_o \sim \frac{\eta_o}{\epsilon_r^{1/2}} \left(\frac{H}{W + H} \right)$$



III-V MIMIC Interconnects -- Inverted Thin-Film Microstrip

narrow line spacing → IC density



Some substrate radiation / substrate losses



No breaks in ground plane



... no ground breaks at device placements





still have problem with package grounding





...need to flip-chip bond

  
thin dielectrics → narrow lines
 → high line losses
 → low current capability
 → no high- Z_0 lines





InP 150 GHz master-slave latch

  




InP 8 GHz clock rate delta-sigma ADC

 

  
If It Has Breaks, It Is Not A Ground Plane !



   
coupling / EMI due to poor ground system integrity is common in high-frequency systems whether on PC boards ...or on ICs.



 
No clean ground return ? → interconnects can't be modeled !



 *35 GHz static divider
interconnects have no clear local ground return
interconnect inductance is non-local
interconnect inductance has no compact model*



 *8 GHz clock-rate delta-sigma ADC
thin-film microstrip wiring
every interconnect can be modeled as microstrip
some interconnects are terminated in their Z_0
some interconnects are not terminated
...but ALL are precisely modeled*



InP 8 GHz clock rate delta-sigma ADC

VLSI mm-Wave Interconnects with Ground Integrity

narrow line spacing → IC density



no substrate radiation, no substrate losses



negligible breaks in ground plane



negligible ground breaks @ device placement




still have problem with package grounding



...need to flip-chip bond

 thin dielectrics → narrow lines
→ high line losses
→ low current capability
→ no high- Z_0 lines








Example: 150 GHz Master-Slave Latch

Device Technology:
500 nm InP HBT

Interconnects :
inverted thin-film microstrip

     Design:
All lines modeled as microstrip lines
representative lines simulated in Agilent / Momentum
fit to simple lossy line model (loss, Z_0 , velocity)



Example: 20 GHz DDFS Design (Rockwell)

designs in progress: MJ Choe

design target:
20 GHz clock rate



circuit topology:
ECL

device technology:
350 GHz (500 nm) InP HBT (Rockwell)

Interconnect technology:
inverted thin-film microstrip throughout
→ all lines are controlled-impedance

shorter lines:
unterminated, but modeled

longer lines:
modeled and
terminated

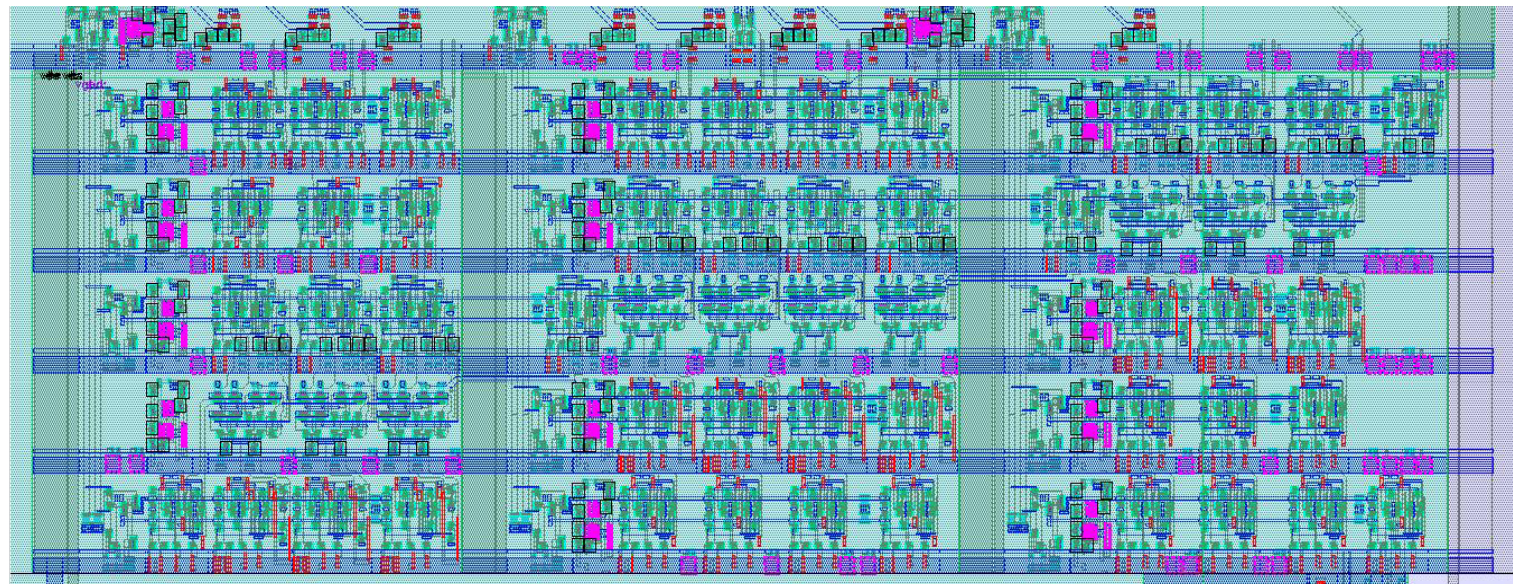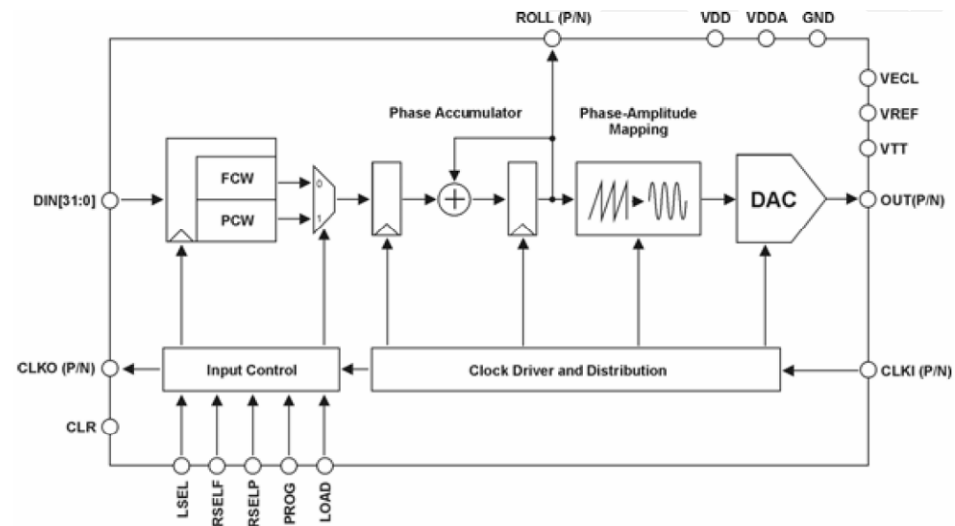

Summary

- At 90-nm or below, CMOS can be a cost-effective choice for highly integrated mm-wave circuits
- Consideration for optimizing device layout and biasing are very similar for mm-wave and RF
- Pre-characterized cell-based mm-wave design flow will be a key enabler

References on other mm-Wave CMOS Efforts

- Prof. B. Brodersen and Prof. A. Niknejad – “Design considerations for 60 GHz CMOS radios,” *IEEE Communications Magazine*, Dec. 2004.
- Prof. A. Hajimiri – “A fully integrated 24-GHz phased-array transmitter in CMOS,” *IEEE JSSC*, Dec. 2005.
- Prof. B. Razavi – “A 60-GHz CMOS receiver front-end” *IEEE JSSC*, Jan. 2006.
- Prof. F. Chang – “A 60GHz CMOS VCO using on-chip resonator with embedded artificial dielectric for size, loss, and noise reduction,” *2006 ISSCC*.
- Prof. J. Laskar – “60-GHz direct-conversion gigabit modulator/demodulator on liquid-crystal polymer,” *IEEE TMTT*, Mar. 2006.

**In case
of questions**