

2025 IMS Workshop WSL "Sub-THz Power Amplifiers in CMOS, SiGe, and III-V"

100-300 GHz power amplifiers: transistor limits, circuit topologies

Mark Rodwell

Doluca Family Chair

University of California, Santa Barbara

rodwell@ece.ucsb.edu

Co-authors: **Amirreza Alizadeh** (Keysight/UCSB), **Ahmed Samir Sayed Ahmed** (Cairo University/ Analog Devices / UCSB), **Yuya Nemoto** (UCSB), **Utku Soylu** (UCSB/IBM), **Miguel Urteaga** (**Teledyne**)



Dr. Miguel Urteaga
Teledyne Scientific
130 nm & 250 nm
InP HBT technology



Dr. Amirreza Alizadeh
Now with Keysight
140 GHz 0.5 W amplifiers
220 GHz high-efficiency PAs
220 GHz LNAs



Prof. Ahmed S. S. Ahmed
Now with Cairo Univ. & ADI
140, 200, 270 GHz
power amplifiers
cascade power-combining
capacitively degenerated CB



Dr. Utku Soylu
Now with IBM Yorktown
LNA design principles
220 GHz LNAs





Yuya Nemoto
UCSB



Also acknowledging:
Dr. Zachary Griffith
Teledyne Scientific
100-300 GHz InP PAs
250 nm InP HBT technology

applications

  

High capacity:

potentially wide available bandwidth
many simultaneous signal beams even with compact arrays

Limited range: (max 500-1000 m)


high λ^2/R^2 Friis (beam diffraction) losses
high worst-case atmospheric attenuation

Need:

arrays with very many elements
low receiver noise figure
efficient medium-power amplifiers

Terminology:

 30-300 GHz $\rightarrow \lambda = 10$ to 1 mm $\rightarrow$ "millimeter-waves"




36×1 transmit array, 6" long
 1×216 receive array, 6" long
 36×216 image; $10^\circ \times 90^\circ$ field of view
 0.3° beamwidth

Sees soccer ball
 @ 200 meters range,
 in heavy fog.

$P_{1dB} = 17 \text{ dBm PAs}$
 $F = 6 \text{ dB LNAs}$

 17 dBm PAs, $F=6 \text{ dB LNAs}$, 2 dB TX packaging losses, 2 dB
 RX packaging losses, 4 dB operating margins, 40 Hz scan,
 10 dB SNR, -10 dB target reflectivity, 22 dB/km fog. soccer
 ball is 22 cm diameter



Video-rate, video-resolution SAR

like infrared: high-resolution, real-time images

better: sees even through fogs/cloud

2012 DARPA VISAR program:

220 GHz, 1km range system


transmitter: 50 W vacuum tube.

Feasible now: InP HBT solid-state-source

2 tiles x (16 x 16 elements) x 100 mW/element

$$P_{1\text{dB}} = 20 \text{ dBm PAs}$$

F = 7 dB LNAs

 

1.6 Tb/s wireless data center links ?

75-165, 195-305 GHz $\rightarrow$ 200 GHz bandwidth

16QAM $\rightarrow$ 4 bits/Hz $\rightarrow$ 800 Gb/s

2 polarizations $\rightarrow$ 1.6 Tb/s

100 m range

pJ/bit = ?

blockage ? crosstalk ?




$P_{1dB} = 12$ dBm PAs

$F = 7$ dB LNAs

~ 10 dBm PAs, $F=7$ dB LNAs, 2 dB TX packaging losses,
2 dB RX packaging losses, 10 dB operating margins,
 1° beamwidths, 10^{-3} uncoded BER.

mechanical alignment

   $P_{1dB} = 12$ dBm if 5 dB backoff from P_{peak}



8-element MIMO array


~ 1m baseline

125 Gb/s/subarray; 1.0 Tb/s total

1.5 km range in 50 mm/hour rain

$P_{1dB} = 25$ dBm PAs

$F = 6$ dB LNAs

 

25 dBm P1dB PAs (5 dB backoff), $F=6$ dB LNAs, 2 dB TX packaging losses, 2 dB RX packaging losses, 10 dB operating margins, $8\lambda \times 8\lambda$ sub-array elements $\rightarrow$ 7 degree beamsteering

Carrier frequency	220 GHz		90 GHz			35 GHz	
Array baseline	0.58 m		0.91 m			1.5 m	
Atmospheric attenuation	23 dB/km		20 dB/km			11.5 dB/km	
subarrays size	78 × 78 mm ²	39 × 39 mm ²	95 mm × 95 mm			250 mm × 250 mm	
# elements	8 × 8	4 × 4	4 × 4			4 × 4	
Modulation	QPSK	QPSK	QPSK	16QAM	64QAM	256QAM	1024QAM
Channel bandwidth	40 GHz	40 GHz	40 GHz	20 GHz	13 GHz	10 GHz	8 GHz
Fractional bandwidth	18%	18%	44%	22%	15%	29%	23%
Total transmit power*	0.17 W	2.8 W	0.33 W	1.5 W	5.5 W	1.1 W	3.7 W


500 m range, 8 dB noise figure, 50 mm/hr. rain, 10⁻³ uncoded error rate, 2dB (each) transmitter and antenna packaging losses, 10 dB total operating margins, 2 polarizations × 4 channels/polarization × 80 Gb/s/channel, 640 Gb/s total

*Summed over all array elements.

High frequencies
competitive
if $\alpha R < \text{about } 5\text{-}10 \text{ dB}$

$$\frac{P_{RX}}{P_{TX}} = \frac{N_{TX} N_{RX}}{\Omega_{scan,TX} \Omega_{scan,RX}} \left(\frac{\lambda^2}{R^2} \right) e^{-\alpha R}$$
 
$$\bar{P}_{RX,min} \approx \text{SNR} \cdot \left(\frac{kTF}{2} \right) \cdot (\text{bits/sec}) \cdot \frac{2}{\pi} \cdot \frac{2^{\text{bits/sec/Hz}}}{\text{bits/sec/Hz}}$$



$$\frac{P_{RX}}{P_{TX}} = \frac{N_{TX} N_{RX}}{\Omega_{scan,TX} \Omega_{scan,RX}} \left(\frac{\lambda^2}{R^2} \right) e^{-\alpha R}$$


50 GHz or 250 GHz ?

Worst-case losses similar at 50 & 250 GHz

Same link budget at 250 GHz if

slightly more elements @ 250 GHz

or less spectrally efficient modulation

and if we can make good PAs and LNAs.

Any terrestrial > 50 GHz system will be short-range.

$$\bar{P}_{RX,min} \simeq \text{SNR} \cdot \left(\frac{kTF}{2} \right) \cdot (\text{bits/sec}) \cdot \frac{2}{\pi} \cdot \frac{2^{\text{bits/sec/Hz}}}{\text{bits/sec/Hz}}$$

Low frequency (6-12 GHz) or high (28-50, 110-270 GHz)?

Low communications density (Gb/s/km²) ?


low deployment costs: widely spaced hubs

long link distances → use lower frequencies.


High communications density (Gb/s/km²) ?

can afford more closely spaced hubs

 short link distances → can use high frequencies



Transistor performance comparison


 


Urteaga, 2011 DRC


Alizadeh, 2024 BCICTS

Alizadeh, 2023 BCICTS


Griffith, 2024 IMS

  

$F \sim 5.75$ dB,
@215 GHz



 


500 mW,
15% PAE,
150 GHz

 

What parameters are important for high PAE at 100-300 GHz ?

transistor\circuit co-design

   



$$I_{\max} \propto W_g \cdot (\# \text{ fingers})$$

$$R_L = \Delta V / I_{\max}$$

$$P_{\text{out}} = \Delta V \cdot I_{\max} / 8 = (\Delta V)^2 / 8R_L$$


more fingers $\rightarrow$ more power

  minimum $R_L \rightarrow$ maximum P_{out}



$$P_{\text{out}} = \Delta V \cdot I_{\max} / 8$$

$$R_L = \Delta V / I_{\max}$$

 

Transmission lines: minimum $Z_{0,\text{line}}$

lateral modes, junction parasitics



High P_{out} with small ΔV ?

R_L smaller than interconnect $Z_{0,\text{line}}$



Substantial impedance shift on interconnect

Desired low R_L cannot be presented to transistor

Large ΔV is necessary for high power

  

  Increased transistor bandwidth:
Thinner collector depletion layers
→ **reduced breakdown voltage**



to double the bandwidth:

to double the bandwidth:	change
emitter & collector junction widths	decrease 4:1
current density ($\text{mA}/\mu\text{m}^2$)	increase 4:1
current density ($\text{mA}/\mu\text{m}$)	constant
collector depletion thickness	decrease 2:1
base thickness	decrease 1.4:1
emitter & base contact resistivities	decrease 4:1

Breakdown voltage: $V_{br} \approx \mathcal{E}_{\max} T_C$

Collector transit time: $\tau_c \approx T_C / 2v_{\text{electron}}$

Current gain cutoff frequency: $f_\tau = 1 / 2\pi(\tau_c + \dots)$

$V_{br} f_\tau \leq v_{\text{electron}} \mathcal{E}_{\max} / \pi \leftarrow$ Johnson figure-of-merit

$P_{\text{out}} \propto V_{br}^2 / R_{L,\min} \rightarrow P_{\text{out}} \propto (v_{\text{electron}} \mathcal{E}_{\max} / f)^2$


Wide bandgap $E_{\text{gap}} \rightarrow$ greater $\mathcal{E}_{\max}$.

InP: moderate $\mathcal{E}_{\max}$, very high v_{electron}

GaN: extremely high $\mathcal{E}_{\max}$, moderate v_{electron}

The Johnson F.O.M. has long guided microwave transistor development.

 
What else matters for 100-300 GHz power amplifiers ?



Breakdown is never less than the bandgap


Impact ionization:
 
$$qV_{CE} \geq E_{\text{gap,collector}}$$



Band-band tunneling:
 
$$qV_{CE} \geq E_{\text{gap,base}} + \text{base doping degeneracy}$$



Impact ionization: electron + hole from energetic carrier

Avalanche: alternating electron and hole ionization

BVCBO: multiplication $m = \infty$; avalanche

BVCEO: multiplication $m = 1 / \beta$; avalanche or just ionization.


Avalanche is slow:

repeated electron transits, hole transits

InP: $v_{hole} \ll v_{electron} \rightarrow$ long hole transit time

Silicon: electrons impact ionize more readily than holes

 $\rightarrow$ **BVCBO significantly larger than BVCEO**



Breakdown varies between


BVCBO and BVCEO

as the impedance

presented to the base

varies from zero to infinity.


BVCBO

 

breakdown: $m \rightarrow \infty$

BVCEO

breakdown: $m = 1 / \beta$

 

$$\Delta T / P = \frac{1}{\pi K_{th} L_E} \sinh^{-1} \left(\frac{L_E}{W_E} \right) + \frac{1}{\pi K_{th} W_E} \sinh^{-1} \left(\frac{W_E}{L_E} \right)$$

$$\approx \frac{1}{\pi K_{th} L_E} \ln \left(\frac{L_E}{W_E} \right) + \frac{1}{\pi K_{th} W_E}$$

Cylindrical heat flow for $W_E/2 < r < L_E/2$,

Spherical heat flow for $L_E/2 < r$



Near the emitter:

$$T(R) = \frac{P}{\pi K_{th} L_E} \ln \left(\frac{L_E}{2R} \right) + \frac{P}{\pi K_{th} L_E} ;$$

Steep temperature gradient

Finger thermal coupling is $\ll 100\%$.

  Bias circuits cannot compensate transistor self-heating



Formula from Carslaw & Jaeger, Conduction of heat in solids, 1959, page 265

Thermally unstable unless



$$K_{th} = \left. \frac{-\partial V_{be}}{\partial T} \right|_{\text{constant } I_C} \times \frac{V_{CE} \theta_{JA}}{R_{ex} + R_{EE} + R_b / \beta + nkT / qI_E} < 1$$

Thermal runaway $\rightarrow$ increasing current $\rightarrow$ destruction

Teledyne 250 nm InP HBT technology:

$$\theta_{JA} \approx 55 \frac{\text{Kelvin}}{\text{mW}} \cdot \frac{1 \mu\text{m}}{L_E} \quad \text{Griffith, 2007 IEEE IPRM}$$
  
$$\text{InP HBT @ } J_E \sim 8 \text{ mA}/\mu\text{m}^2 : \frac{\partial V_{be}}{\partial T} \approx -0.8 \text{ mV/Kelvin}$$



Thermal compensation does not help: weak thermal coupling.



Currents will distribute unequally in a multifinger HBT unless

$$K_{\text{thermal stability}} = \left(\frac{-dV_{be}}{dT} \right) \frac{V_{CE} \theta_{JA}}{R_{ex} + R_{EE} + R_b / \beta + nkT / qI_E} < 1$$



R_{b2} and R_{EE2} do not help.

Unequal currents $\rightarrow$ destruction

  Finger-finger thermal coupling is too weak to suppress runaway.





Yun Wei, PhD. thesis, UCSB, 2003

  

4 finger cell ($4 \times 0.25 \mu\text{m} \times 6 \mu\text{m}$); 250 nm InP HBT



Normal cell:

  parallel RF connection
parallel DC connection
prone to electro-thermal runaway



Segmented cell:

  parallel RF connection
independent DC connection
reduced electro-thermal runaway
no degradation in high-frequency performance.
operates at higher currents at a given V_{ce} .



Amirreza, IEEE Trans MTT 2024

DC and RF breakdown are **not the same**

Thermal time-constants

breakdown depends on temperature

temperature can't track RF cycle

Electrothermal runaway (thermal positive feedback)

contributes to breakdown

temperature can't track RF cycle

Avalanche multiplication



impact ionization is fast (electron transit time)

avalanche is slower (hole + electron times)

BVCEO vs. BVCBO

depends on **RF impedances**,

not on **DC impedances**.

  

What do 100-300 GHz power transistors need ?

RF/microwave emphasis (DC-30 GHz)

- need high V_{br} for high output power

- need high V_{br}/V_{sat} for high drain\collector efficiency

- need high gain for high PAE (hence high f_{max})

These are insufficient at 100-300 GHz.

- need **high current density** for compact transistor layout


 - transistor cell parasitics, circuit layout parasitics

- need **high current density** for adequate large-signal gain

Electrode RC charging time $\propto (\text{finger length})^2$

Maximum finger length $\propto 1/\sqrt{\text{frequency}}$

 
Current per finger $\propto 1/\sqrt{\text{frequency}}$



Maximum cell width $\propto 1/\text{frequency}$

Maximum number fingers $\propto 1/\text{frequency}$

 Maximum current per cell $\propto 1/\text{frequency}^{3/2}$



Maximum cell power $\propto (\text{maximum load resistance}) \cdot (\text{maximum current})^2 \propto 1/(\text{frequency})^3$

Johnson: maximum power $\propto (\text{maximum voltage})^2 / (\text{minimum load resistance}) \propto 1/(\text{frequency})^2$

Current density (mA/ μm) is a key figure of merit



Low mA/ μm $\rightarrow$ many fingers

Transistor layout:

large interconnect parasitics
 uncontrolled, unmatched impedances
 degraded f_{τ} , f_{max} , G, F, P_{sat} , PAE...

IC layout:

 
 
large transistor footprint
 longer interconnects to combiner
 impairs low-Z (high power) design
 reduces feasible P_{out}



$$\text{PAE} = \frac{P_{out} - P_{in}}{P_{DC}} = \frac{1}{2} \frac{V_{max} - V_{min}}{V_{max} + V_{min}} \cdot \left(1 - \frac{1}{G}\right)$$

$$= \eta_{\text{drain/collector}} \cdot \left(1 - \frac{1}{G}\right)$$

  where $\eta_{\text{drain/collector}} = \frac{P_{out}}{P_{DC}} = \frac{1}{2} \frac{V_{max} - V_{min}}{V_{max} + V_{min}}$



$$I_{max} = J_{max} n_g W_g$$

What factors determine PAE ?

Can G approach the maximum small-signal gain ?

PAE and $(P_{\text{out}} - P_{\text{in}})$ are network invariant:
no change given lossless passive embedding.

Given correct Z_L ,
All (lossless) PAs the same PAE and same $(P_{\text{out}} - P_{\text{in}})$.

PAE and $(P_{\text{out}} - P_{\text{in}})$ are that of the transistor itself.

Things that do not change PAE:




CE/CS emitter/source inductance

CB/CG base/gate capacitance

Neutralization

Unconditionally stable positive feedback
(Singhakowinta 1966)

   For highest PAE pick circuit with smallest loss.



Maximum transistor PAE

Classic expression: $PAE = \frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) \left(1 - \frac{1}{G} \right)$ What is G ???????

Can show: $PAE = \frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) \left(1 - \frac{f^2}{f_{\max}^2} \right)$ *IF* transistor $I_{\max}$ is sufficient

...if (BJTs) $I_{\max} \geq I_{\text{peak,opt}} = 2\pi f_{\tau} C_{cbi} (V_{\max} - V_{\min})$;

...if (FETs) $I_{\max} \geq I_{\text{peak,opt}} = 2\pi f_{\tau} C_{gd} (V_{\max} - V_{\min})$;




Can show: $PAE = \frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) \left(1 - \frac{f^2}{f_{\text{power}}^2} \right)$ *IF* $I_{\max}$ is insufficient

where $f_{\text{power}} = \frac{2f_{\max}}{\left(I_{\text{peak}} / I_{\text{peak,opt}} \right)^{1/2} + \left(I_{\text{peak}} / I_{\text{peak,opt}} \right)^{-1/2}} \rightarrow f_{\max}$ if $I_{\text{peak}} = I_{\text{peak,opt}}$

BJT cutoff frequencies: $f_{\tau} = g_m / 2\pi (C_{be} + C_{cbi})$; $f_{\max} = (f_{\tau} / 8\pi R_{bb} C_{cbi})^{1/2}$

FET cutoff frequencies $f_{\tau} = g_m / 2\pi (C_{gs} + C_{gd})$; $f_{\max} = (f_{\tau} / 8\pi R_g C_{gd})^{1/2}$;

   All parameters are large-signal: $g_m \triangleq \Delta I_D / \Delta V_{gs}$ not $\partial I_D / \partial V_{gs}$, etc.



200 nm InP HBT; Rode 2015 IEEE TED

$$f_\tau = 480 \text{ GHz}, f_{\max} = 1.07 \text{ THz}$$

$$V_{\max} = 4 \text{ V}, V_{\min} = 0.7 \text{ V}$$


$$I_{\max} = 3 \text{ mA}/\mu\text{m} \cdot 2.9 \mu\text{m} = 8.7 \text{ mA}$$

$$I_{\text{opt}} = 2\pi f_\tau C_f (V_{\max} - V_{\min})$$

$$= (V_{\max} - V_{\min}) \cdot g_m C_{cbi} / (C_{be} + C_{cb})$$

$$= 8.0 \text{ mA}$$
 
$$I_{\text{opt}} = 8.0 \text{ mA} < I_{\max} = 8.7 \text{ mA}$$



45 nm GaN HEMT; Shinohara 2011 IEEE EDL

$$f_\tau = 257 \text{ GHz}, f_{\max} = 396 \text{ GHz}$$

$$V_{\max} = 13 \text{ V}, V_{\min} = 1.5 \text{ V}$$

$$I_{\max} = 2.3 \text{ mA}/\mu\text{m} \cdot 80 \mu\text{m} = 184 \text{ mA}$$

$$I_{\text{opt}} = 2\pi f_\tau C_f (V_{\max} - V_{\min})$$

$$= (V_{\max} - V_{\min}) \cdot g_m C_{gd} / (C_{gs} + C_{gd})$$

$$= 161 \text{ mA}$$

$$I_{\text{opt}} = 161 \text{ mA} < I_{\max} = 184 \text{ mA}$$



Model parameters

g_m (mS)	84.9
g_d (mS)	9.4
C_{gs} (fF)	39.9
C_{gd} (fF)	7.9
R_i (Ohm)	0.21
R_g (Ohm)	5.5
R_s (Ohm)	2.6
R_d (Ohm)	2.6
$f_{T,\text{model}}$ (GHz)	257
$f_{\max,\text{model}}$ (GHz)	396

$$W_g = 2 \times 40 \mu\text{m}$$

48 nm GaN HEMT;

Asko 2023 IEEE Microwave & Wireless Tech. Lett.

$$f_\tau = 114 \text{ GHz}, f_{\max} = 241 \text{ GHz}$$

$$V_{\max} = 34 \text{ V}, V_{\min} = 6 \text{ V}$$

$$I_{\max} = 2 \text{ mA}/\mu\text{m} \cdot 100 \mu\text{m} = 200 \text{ mA}$$

$$I_{\text{opt}} = 2\pi f_\tau C_f (V_{\max} - V_{\min})$$

$$= (V_{\max} - V_{\min}) \cdot g_m C_{gd} / (C_{gs} + C_{gd})$$

$$= 281 \text{ mA}$$

$$I_{\text{opt}} = 281 \text{ mA} > I_{\max} = 200 \text{ mA} \dots \text{but not far off}$$



SMALL SIGNAL MODEL PARAMETERS OF THE $4 \times 25 \mu\text{m}$ DEVICE

g_m (mS)	C_{GS} (fF)	C_{GD} (fF)	C_{DS} (fF)	r_{DS} (ohm)	r_{GS} (ohm)	r_{GD} (ohm)	τ (fsec)
56.9	65.5	14	27	268	2.65	18	311
r_G (ohm)	r_D (ohm)	r_S (ohm)	L_G (pH)	L_D (pH)	L_S (pH)	outer finger	inner finger
1.2	3.2	1.6	15.5	6.1		≈ 0	3.2

Teledyne 250 nm InP HBT, 220 GHz

$$V_{\max} = 4.2 \text{ V}, V_{\min} \approx 0.8 \text{ V}, f_{\max} = 580 \text{ GHz}$$

$$\frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) = 34\%$$

$$(1 - f^2 / f_{\max}^2) = 86\%$$

$$PAE_{theory} = 29.1\%$$

$$PAE_{CAD} = 30\% \text{ (4-finger, @} P_{sat} \text{)}$$

$$\approx 33\% \text{ (1-finger, @} P_{sat} \text{)}$$

*long finger; reduces $f_{\max}$.

Teledyne 130 nm InP HBT, 220 GHz

$$V_{\max} = 4 \text{ V}, V_{\min} \approx 0.8 \text{ V}, f_{\max} = 1.15 \text{ THz}$$

$$\frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) = 33.3\%$$

$$(1 - f^2 / f_{\max}^2) = 96\%$$

$$PAE_{theory} = 32.1\%$$

$$PAE_{CAD} = 35\% \text{ (4-finger, @} P_{sat} \text{)}$$

$$\approx 38\% \text{ (1-finger, @} P_{sat} \text{)}$$

Teledyne 130 nm InP HBT, 280 GHz

$$V_{\max} = 4 \text{ V}, V_{\min} \approx 0.8 \text{ V}, f_{\max} = 1.15 \text{ THz}$$

$$\frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) = 33.3\%$$

$$(1 - f^2 / f_{\max}^2) = 94\%$$

$$PAE_{theory} = 31.4\%$$

$$PAE_{CAD} = 32.6\% \text{ (4-finger, @} P_{sat} \text{)}$$

$$\approx 35\% \text{ (1-finger, @} P_{sat} \text{)}$$

Theory works reasonably for InP HBT; less well for Ga-polar GaN. Why ?

Should use large-signal, not small-signal $f_{\max}$. (s.s. is optimistic)

CAD and measurements: heavily saturated; enhances PAE

Harmonic tuning, when feasible, further enhances PAE

4-finger HBTs are ~3% less efficient than 1-finger HBTs

150-300 GHz PAs are ~10% less efficient than 4-finger HBTs (InP)

InP HBT PA measurements are reasonably close to simulation.

UCSB N-polar GaN, 132 GHz

$$V_{\max} = 34 \text{ V}, V_{\min} \approx 6 \text{ V}, f_{\max} = 241 \text{ GHz}$$

$$\frac{1}{2} \left(\frac{V_{\max} - V_{\min}}{V_{\min} + V_{\min}} \right) = 35\%$$

$$(1 - f^2 / f_{\max}^2) = 70\%$$

$$PAE_{theory} = 24.5\%$$

$$PAE_{measured} = 25\% \text{ (load-pull)}$$

Model assumes constant values for (g_m, C_{gs}, C_{gd})

Reality: these vary very strongly across loadline

So: use large-signal quantities:

$$g_m = \Delta I_D / \Delta V_{GS}, C_{gs} = \Delta Q_{gate} / \Delta V_{GS}, C_{gd} = \Delta Q_{gate} / \Delta V_{GD}$$

As these vary over the (I_{out}, V_{out}) plane, there will be further optimization beyond the above analysis

Even given this correction, analysis remains very approximate.

The goal of this analysis is to provide 1st understanding of current drive requirements:

Specifically, what load current is required for the optimum loadline impedance


to be the same as the optimum impedance for small-signal gain ?

And, if the transistor cannot deliver this, how much gain is sacrificed ?

For GaN, trapping behavior plays critical role in setting large-signal gain near peak PAE


(thanks to Keisuke Shinohara, Teledyne, for this and other guidance)

power amplifier design

 


100-300 GHz Power combining: what is best ?

Corporate T-line

 


Direct series-connected

 M. Shifrin: 1992 IEEE μ Wave/mmWave Monolithic Circuits Symp. (Raytheon)




Cascade combining

A. Ahmed 2018 EuMIC, 2021 RFIC (UCSB)

 

Distributed Active Transformer

 
I. Aoki, IEEE Trans MTT, Jan. 2002 (CalTech)




Balun series-connected

$\lambda/4$ baluns: Y. Yoshihara, 2008 IEEE Asian Solid-State Circuits Conference (Toshiba)

 sub- $\lambda/4$ baluns: H. Park, et al., IEEE JSSC, Oct. 2014 (UCSB)





 Example: 4:1 Balun Series-Connected @ 81 GHz



81GHz, 17 dB Gain
 470 mW P_{sat} , **23% PAE**
 Teledyne 250 nm InP HBT
 2 stages, 1.0 mm²(incl pads)

  $\lambda/4$ baluns: Y. Yoshihara, 2008 IEEE Asian Solid-State Circuits Conference (Toshiba)
 sub- $\lambda/4$ baluns: H. Park, et al, IEEE JSSC, Oct. 2014 (UCSB)



Interconnects in packages and on PCBs:

$H \propto 1/\text{frequency}$ (to control radiation loss)

$\text{loss (dB/mm)} \propto (\text{frequency})^{3/2}$


$\text{loss (dB/wavelength)} \propto \sqrt{\text{frequency}}$

Interconnects in ICs:

H is independent of frequency

$\text{loss (dB/mm)} \propto \sqrt{\text{frequency}}$

 $\text{loss (dB/wavelength)} \propto 1/\sqrt{\text{frequency}}$



loss (dB/wavelength) $\propto 1/\sqrt{\text{frequency}}$

length $\propto 1/\text{frequency}$


Big problem @ 10-100 GHz

No problem @ 100-300 GHz

Small # transistor fingers per cell

Not an advantage at @ 10-100 GHz

Big advantage at @ 100-300 GHz

 

Compact power-combining networks


Big advantage at @ 10-100 GHz

Limited advantage at @ 100-300 GHz

Large # transistor fingers per cell

No problem at @ 10-100 GHz

 Significant disadvantage at @ 100-300 GHz



Transformer shown: same issues with stacking & baluns:


Many fingers per cell: big transistor footprint

Low impedances at combiner port

Impedance shift between transistor and combiner

Gets worse as combining ratio is increased

 No problem at 10-100 GHz; big problem at 100-300 GHz




Balun:




ports connected in series
shunt loading by shorted stubs.

 1:1 transformer:




ports connected in series
shunt loading by shorted stubs.
series loading by shorted stub






balun

   

transformer

   

   Reduced stage gain
 local negative feedback
 reactive, no loss in PAE
 reduces P_{out}/P_{in}
 does not change $(P_{out} - P_{in})$
 $\rightarrow P_{out}$ increases








Requires higher-power driver stages

Driver power contributes to output power


Cascade combining as stacking plus matching

A. S. H. Ahmed et al.,
2018 EuMIC (UCSB)

     


Also: A. S. H. Ahmed, "8.6-13.6 mW Series-Connected Power Amplifiers Designed at **325 GHz** Using 130 nm InP HBT Technology," 2018 IEEE BCICTS

 Lower gain, same peak PAE, higher PAE at P_{1dB} .



 This is the same as a stack with internal matching





Capacitive degeneration:
no effect on peak PAE



No capacitive degeneration:
more gain compression @ P_{1dB} . ✗
more gain @ P_{1dB} ✓
 input matching losses have less effect on PAE ✓

With capacitive degeneration:
less gain compression @ P_{1dB} . ✓
less gain @ P_{1dB} ✗
 input matching losses have more effect on PAE ✗

  Design for greatest PAE @ P_{1dB}
 balances these two considerations.







examples

  

PAs with corporate & cascade combining

Teledyne 250nm InP HBT technology


 
 
 
 
Ahmed et al., 2020 IMS, 2020 EuMIC, 2021 IMS, 2021 RFIC



140GHz, 20.5dBm, 20.8% PAE 130GHz, 200mW, 17.8% PAE

194GHz, 17.4dBm, 8.5% PAE

266GHz, 16.8dBm, 4.0% PAE

     




Class-B bias: $I_{C,DC} = \frac{I_{RF,peak}}{\pi} \propto \sqrt{P_{out}}$

Constant I_C or I_B bias:
class B only at one RF power level

Constant- V_{be} bias:
electrothermally unstable $\rightarrow$ destruction

Need adaptive bias circuit

   I_C bias increasing in proportion to $\sqrt{P_{out}}$



Q1: RF gain & adaptive bias

Q2: adaptive bias

Q1-4: current mirror; sets I_{c1}

RF drive:


V_{be1}, V_{be2} decrease

I_{c1} increases

Why use Q2 for adaptive bias ?

More RF $\rightarrow$ DC rectification



 
R_1 can be larger for given dI_{c1}/dP_{RF}
 $\rightarrow$ greater electrothermal stability




adaptive class-AB bias

Alizadeh, 2023 IEEE BCICTS


2 mm x 1.5 mm

   


Output power, PAE, and Gain

 

 Peak PAE with associated output power & gain vs. frequency



 Adaptive class-AB bias currents vs. output power









InP HBT Amplifier: 78 mW, 18.4% PAE, 220 GHz

Teledyne 250 nm InP HBT (reduced base post)

Thermally ballasted 4-finger common-base cell:
increases maximum V_{ce} .

Alizadeh, 2023 IEEE MTT Trans

0.78 mm x 0.75 mm

      


Key record result: Z. Griffith, 2024 IMS: 25% PAE, 16.7 dBm @ 220 GHz, 130 nm InP HBT

130 nm InP HBT technology

Design: Amirreza Alizadeh

Transistors, IC technology: Miguel Urteaga


150 GHz

 


estimated
Same passive
element losses ?

37.5 % amplifier PAE ?
(19 dBm design, **estimated**)

225 GHz

 


 simulated
9.9% PAE drop
HBT cell → power amplifier



29.5% amplifier PAE
(19 dBm design, **simulated**)

280 GHz

 




estimated
Same passive
element losses ?

24.5% amplifier PAE ?
(19 dBm design, **estimated**)



$F = 6.3-5.5$ dB over 180-217 GHz; record for bipolar transistor

$F_{\text{cascade,LNA}} = 6.4-5.6$ dB, 7 mW DC power .

~5.5-6 dB LNA noise @ 200 GHz


 
 
 


  4.9-5.2 dB minimum transistor F_{cascade}



$F_{\text{LNA, cascade}} \sim F_{\text{LNA}} + 0.15$ dB = 5.6-6.1 dB
given that $G_{\text{LNA}} = 15$ dB

100-300 GHz Power Amplifiers

    

Power amplifier performance limited by transistor: PAE invariance

Design: pick topologies to minimize passive element loss.

Corporate combining is compact and low-loss

Series techniques at best moderately helpful (may be more compact)

Transistors: more mA/ μm $\rightarrow$ fewer fingers

- less parasitics, better transistor performance.

- smaller footprint, better circuit performance

Transistors need high V_{br} and high mA/ μm

- if not, layout problems

- if not, either can't use full V_{br} or can't benefit from f_{max} .

Better transistors make better power amplifiers

End

R_{ce} , R_{ds} can't be part of power transistor model

Transistor output characteristics look like the upper plot, not like the lower plot.

→ model cannot include R_{DS} or R_{CE}

