

## BIPOLAR JUNCTION TRANSISTOR AMPLIFIER

### OBJECTIVE

To study and learn how to use a common-emitter BJT configuration to amplify an AC signal.


### INTRODUCTION

In previous labs you have studied DC characteristics of BJT circuits. In this lab, you will be using a biased circuit to amplify an AC signal. The common-emitter amplifier that you will be using provides large voltage gain with moderate input and output impedance. You have learned how to calculate voltage gain, input impedance and output impedance, however, techniques for measuring these values may prove to be more difficult and will require more thought.

### PROCEDURE

#### 1. Analyzing the Amplifier

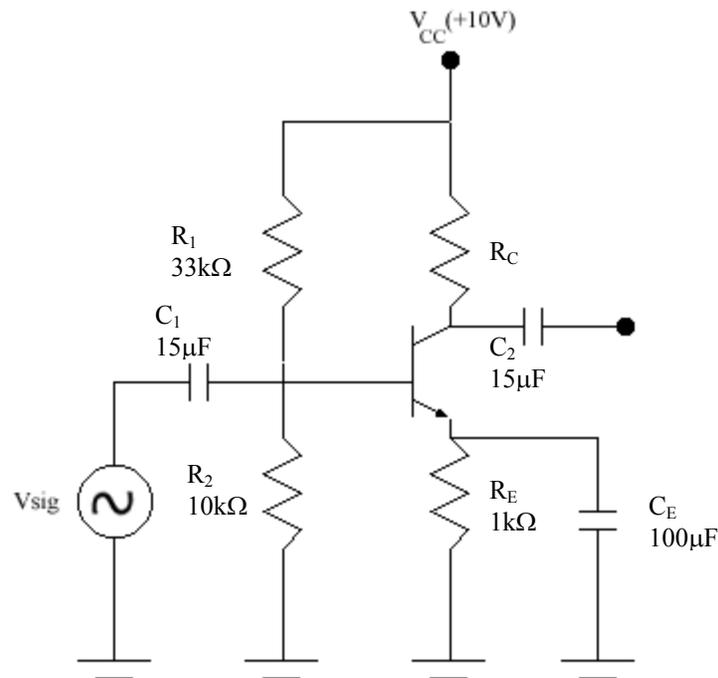(a) The wiring of the BJT will follow the circuit diagram shown below.




- (b) Choose a value for  $R_C$  for your circuit so that  $V_{CE}$  is approximately 5 V. Why is this a good bias point to choose?
- (c) Calculate the value of the DC emitter current,  $I_E$ .
- (d) Draw in your lab notebook the AC model of the circuit above.
- (e) Calculate the input and output impedances  $Z_i$ ,  $Z_o$ , of the circuit. The input impedance of the amplifier is the impedance of the amplifier as 'seen' by the input signal. The output impedance is the impedance as 'seen' looking from the load into the output of the amplifier.
- (f) Calculate the expected voltage gain,  $A_V$ .
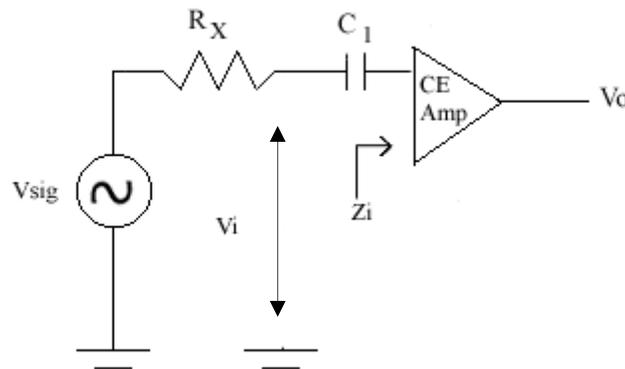
## 2. Making the Measurements

Materials Required: one 1 k $\Omega$  resistor, one 10k $\Omega$  resistor, one 33k $\Omega$  resistor, one resistor of value determined in the previous section, two 15 $\mu$ F capacitors, one 100 $\mu$ F capacitor, one 2N3904 NPN BJT

- Build the circuit shown above. Use the value you choose for  $R_C$ .
- Apply  $V_s$ , an AC signal with an amplitude of approximately 20mV (RMS) and frequency of approximately 2kHz.
- Measure the output waveform on the oscilloscope. Check to see that there is no distortion in the output waveform. If there is distortion, how would you 'fix it'?
- Calculate your circuit voltage gain, using  $V_o/V_s$ . Compare the value you obtain with the value calculated for voltage gain in part 1-(f). Are there differences between your measured values and your calculated values? If so, why? Do the input voltage and the output voltage have the same measured phase? What phase difference did you expect?
- Measure the input impedance,  $Z_i$ . To do this, you can use the circuit diagram shown below. The BJT and its biasing resistors have been modeled as a C-E amplifier, represented symbolically by the triangle. Use the same input AC signal and measure the output voltage just as you did in (d). The difference now, as can be seen in the diagram is that a 'probe resistor',  $R_x$ , with a value of 1k $\Omega$  has been added.



- Measure the value of  $V_i$ . Set up an equation relating  $V_s$  and  $V_i$ . Use that equation to solve for the value of the AC input impedance,  $Z_i$ . Compare the value you measure with the value you calculated previously. How good is the agreement between the two values? How would you explain any discrepancies?
- Measure the output impedance,  $Z_o$ . To do this, remove the  $R_x$  resistor from the circuit. Add a load resistor,  $R_L$ , with a value of 3 k $\Omega$ . (Think carefully if how you would add the load resistor to the circuit!) Measure the value of the output voltage without the load resistor in place and call it  $V_o$ . Measure the value of the output voltage with the load resistor in place and call this value  $V_L$ .
- Set up an equation relating  $V_L$  and  $V_o$  and use that equation to solve for the value of the AC output impedance,  $Z_o$ . Compare the value you measure with the value you calculated previously. How good is the agreement between the two values? How would you explain any discrepancies?