

## Phase Locked Loop Circuits


**Reading:** General PLL Description: T. H. Lee, Chap. 15. Gray and Meyer, 10.4  
Clock generation: B. Razavi, *Design of Analog CMOS Integrated Circuits*, Chap. 15, McGraw-Hill, 2001.

### A. General Description

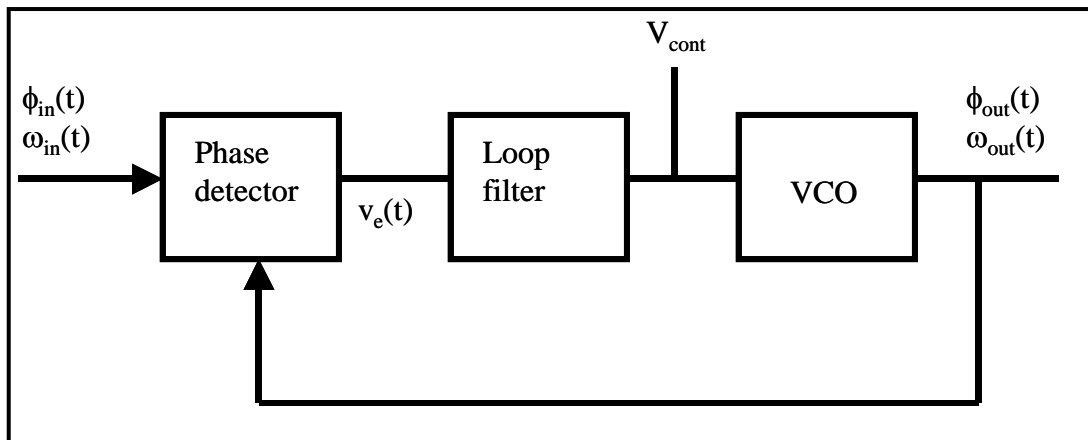1. **Definition.** A PLL is a feedback system that includes a VCO, phase detector, and low pass filter within its loop. Its purpose is to force the VCO to replicate and track the frequency and phase at the input when in lock. The PLL is a control system allowing one oscillator to track with another. It is possible to have a phase offset between input and output, but when locked, the frequencies must exactly track.

$$\begin{aligned}\phi_{out}(t) &= \phi_{in}(t) + const. \\ \omega_{out}(t) &= \omega_{in}(t)\end{aligned}$$

The PLL output can be taken from either  $V_{cont}$ , the filtered (almost DC) VCO control voltage, or from the output of the VCO depending on the application. The former provides a baseband output that tracks the phase variation at the input. The VCO output can be used as a local oscillator or to generate a clock signal for a digital system. Either phase or frequency can be used as the input or output variables.



Of course, phase and frequency are interrelated by:

$$\begin{aligned}\omega(t) &= \frac{d\phi}{dt} \\ \phi(t) &= \phi(0) + \int_0^t \omega(t') dt'\end{aligned}$$

**Applications:** There are many applications for the PLL, but we will study:

- Clock generation
- Frequency synthesizer
- Clock recovery in a serial data link

You should note that there will be different design criteria for each case, but you can still use the same basic loop topology and analysis methods.

**2. Phase detector:** compares the phase at each input and generates an error signal,  $v_e(t)$ , proportional to the phase difference between the two inputs.  $K_D$  is the gain of the phase detector (V/rad).

$$v_e(t) = K_D[\phi_{out}(t) - \phi_{in}(t)]$$

As one familiar circuit example, an analog multiplier or mixer can be used as a phase detector. Recall that the mixer takes the product of two inputs.  $v_e(t) = A(t)B(t)$ . If,


$$A(t) = A \cos(\omega_0 t + \phi_A)$$

$$B(t) = B \cos(\omega_0 t + \phi_B)$$

$$\text{Then, } A(t)B(t) = (AB/2)[\cos(2\omega_0 t + \phi_A + \phi_B) + \cos(\phi_A - \phi_B)]$$

Since the two inputs are at the same frequency when the loop is locked, we have one output at twice the input frequency and an output proportional to the cosine of the phase difference. The doubled frequency component must be removed by the lowpass loop filter. Any phase difference then shows up as the control voltage to the VCO, a DC or slowly varying AC signal after filtering.

 The averaged transfer characteristic of such a phase detector is shown below. Note that in many implementations, the characteristic may be shifted up in voltage (single supply/single ended).



If the phase difference is  $\pi/2$ , then the average or integrated output from the XOR-type phase detector will be zero (or  $V_{DD}/2$  for single supply, digital XOR). The slope of the characteristic in either case is  $K_D$ .


**3. VCO.** In PLL applications, the VCO is treated as a linear, time-invariant system. Excess phase of the VCO is the system output.

$$\phi_{out} = K_O \int_{-\infty}^t V_{cont} dt'$$

The VCO oscillates at an angular frequency,  $\omega_{out}$ . Its frequency is set to a nominal  $\omega_0$  when the control voltage is zero. Frequency is assumed to be linearly proportional to the control voltage with a gain coefficient  $K_O$  or  $K_{VCO}$  (rad/s/v).

$$\omega_{out} = \omega_0 + K_O V_{cont}$$

 Thus, to obtain an arbitrary output frequency (within the VCO tuning range, of course), a finite  $V_{cont}$  is required. Let's define  $\phi_{out} - \phi_{in} = \phi_o$ .



(Figure from B. Razavi, Ch. 15, op. cit.)


In the figure above, the two inputs to the phase detector are depicted as square waves. The XOR function produces an output pulse whenever there is a phase misalignment. Suppose that an output frequency  $\omega_1$  is needed. From the upper right figure, we see that a control voltage  $V_1$  will be necessary to produce this output frequency. The phase detector can produce this  $V_1$  only by maintaining a phase offset  $\phi_0$  at its input. In order to minimize the required phase offset or error, the PLL loop gain,  $K_D K_O$ , should be maximized, since

$$\phi_0 = \frac{V_1}{K_D} = \frac{\omega_1 - \omega_0}{K_D K_O}$$

Thus, a high loop gain is beneficial for reducing phase errors.

 **4. PLL dynamic response:** To see how the PLL works, suppose that we introduce a phase step at the input at  $t = t_1$ .

$$\phi_{in} = \omega_1 t + \phi_0 + \phi_1 u(t - t_1)$$



(Figure from B. Razavi, Ch. 15, op. cit.)

Since we have a step in phase, it is clear that the initial and final frequencies must be identical:  $\omega_1$ . But, a temporary change in frequency is necessary to shift the phase by  $\phi_1$ . The area under  $\omega_{out}$  gives the additional phase because  $V_{cont}$  is proportional to frequency.

$$\phi_1 = \int_{t_1}^{\infty} \omega_{out} dt = \int_{t_1}^{\infty} K_O V_{cont}(t) dt$$


After settling, all parameters are as before since the initial and final frequencies are the same. This shows that  $V_{cont}(t)$  [shown as  $V_{LPF}(t)$  in the figure above] can be used to monitor the dynamic phase response of the PLL.

Now, let's investigate the behavior during a frequency step:

$$\omega_2 = \omega_1 + \Delta\omega$$

The frequency step will cause the phase difference to grow with time since a frequency step is a phase ramp. This in turn causes the control voltage,  $V_{cont}$ , to increase, moving

 the VCO frequency up to catch up with the input reference signal. In this case, we have a permanent change in  $\omega_{out}$  since a higher  $V_{cont}$  is required to sustain a higher  $\omega_{out}$ .




(Figure from B. Razavi, Ch. 15, op. cit.)

If the frequency step is too large, the PLL will lose lock.

**5. Lock Range.** Range of input signal frequencies over which the loop remains locked once it has captured the input signal. This can be limited either by the phase detector or the VCO frequency range.

a. If limited by phase detector:

 

$0 < \phi < \pi$  is the active range where lock can be maintained. For the phase detector type shown (Gilbert multiplier or mixer), the voltage vs. phase slope reverses outside this

range. Thus the frequency would change in the opposite direction to that required to maintain the locked condition.

$$V_{e-\max} = \pm K_D \pi/2$$

When the phase detector output voltage is applied through the loop filter to the VCO,

$$\Delta\omega_{\text{out-max}} = \pm K_V \pi/2 = \omega_L \text{ (lock range)}$$

where  $K_V = K_O K_D$ , the product of the phase detector and VCO gains.

This is the frequency range around the free running frequency that the loop can track.

Doesn't depend on the loop filter

Does depend on DC loop gain

b. The lock range could also be limited by the tuning range of the VCO. Oscillator tuning range is limited by capacitance ratios or current ratios and is finite. In many cases, the VCO can set the maximum lock range.

**6. Capture range:** Range of input frequencies around the VCO center frequency onto which the loop will lock when starting from an unlocked condition. Sometimes a frequency detector is added to the phase detector to assist in initial acquisition of lock.

You will see later that the loop filter bandwidth has an effect on the capture range.

**7. Approach:** We will discuss the details of phase detectors and loop filters as we proceed. But, at this point, we will treat the PLL as a linear feedback system. We assume that it is already "locked" to the reference signal, and examine how the output varies with the loop transfer function and input. A frequency domain approach will be used, specifically describing transfer functions in the s-domain.


$$V_e(s)/\Delta\phi = K_D$$

$$\phi_{\text{out}}(s)/V_{\text{cont}}(s) = K_O/s$$

Note that the VCO performs an integration of the control voltage and thus provides a factor of  $1/s$  in the loop transfer function. Because of this, a PLL is always at least a first order feedback system.

## B. System Level Description

### PLL is a feedback system

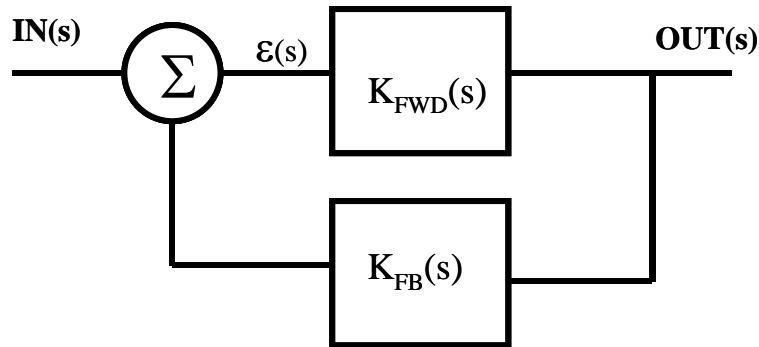

**Loop Gain:**  $T(s) = K_{FWD}(s) K_{FB}(s)$

**Transfer Function:**  $\frac{OUT(s)}{IN(s)} = H(s) = \frac{K_{FWD}(s)}{1 + T(s)}$

The Loop gain can be described as a polynomial:

$$T(s) = \frac{K' (s + a)(s + b) \cdots}{s^n (s + \alpha)(s + \beta) \cdots}$$

**ORDER** = the order of the polynomial in the denominator

**TYPE** = n (the exponent of the s factor in the denominator)

**PHASE ERROR** =  $\varepsilon(s) = \frac{IN(s)}{1 + T(s)}$


**STEADY STATE ERROR** =  $\varepsilon_{SS} = \lim_{s \rightarrow 0} [s\varepsilon(s)] = \lim_{t \rightarrow \infty} \varepsilon(t)$

(this is the Laplace Transform final value theorem)

SS error is a characteristic of feedback control systems. This is the error remaining in the loop at the phase detector output after all transients have died out. Once again, you can see that a large loop gain  $T(s)$  leads to a small phase error.
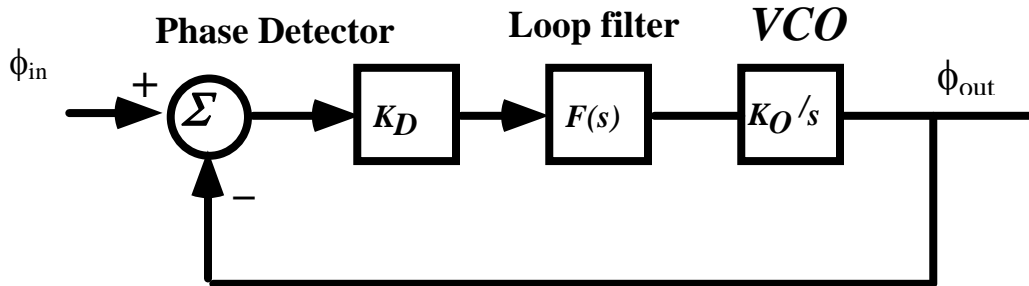
### C. Frequency and phase tracking loop:

First we will consider the PLL with feedback = 1; therefore, input and output frequencies are identical. The input and output phase should track one another, but there may be a fixed offset depending on the phase detector implementation.



**Transfer Function:**  $H(s) = \text{forward path gain} / [1 + T(s)]$ .

With feedback = 1,

$$H(s) = T(s)/[1 + T(s)]$$

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_D K_O F(s) / s}{1 + K_D K_O F(s) / s}$$

**Phase error function:**


$$\varepsilon_s = \phi_{in} - \phi_{out} = \frac{s\phi_{in}}{s + K_D K_O F(s)}$$



We will start from the open loop gain,  $T(s)$ .

$$T(s) = K_D F(s) K_O / s$$

 We know that the phase detector will be producing an output equal to or at twice the carrier frequency, thus some low pass filtering will be needed. Let's start with a simple RC lowpass network.




This network has a cutoff (3 dB) frequency  $\omega_1 = 1/RC$ . Thus, the filter transfer function is a simple lowpass,

$$F(s) = \frac{1}{1 + s/\omega_1} .$$

Then,  $T(s)$  becomes second order, Type 1:

$$T(s) = \frac{K_O}{s} \frac{K_D}{1 + s/\omega_1} = \frac{K_V}{s(1 + s/\omega_1)}$$

 **Bode Plot:** Now look at the Bode plot of  $T(j\omega)$ .




If the loop filter frequency is lower than the crossover frequency, which you might want to do to attenuate the high frequency ripple from the phase detector, then the phase margin can become unacceptably small. And, if we increase the loop gain,  $K_V = K_D K_O$ , to reduce the residual phase error, we get even smaller phase margin. Thus, we have a conflict between stability of the loop and minimizing the phase error. However, the loop can be made to work if  $\omega_1 > \omega_{\text{crossover}}$ . But, then we may have insufficient filtering of the phase detector output.

Before we fix this problem, let's look at the root locus and then the closed loop response of this PLL.

**Root Locus:** Since there are no zeros, the root locus represents the roots of the denominator of the closed loop transfer function. Set  $1 + T(s) = 0$  and solve for  $s$  as a function of  $K_V$ .

$$s = -\frac{\omega_1}{2} \left( 1 \pm \sqrt{1 - \frac{4K_V}{\omega_1}} \right)$$

 We see that as  $K_V$  is increased, the roots approach one another then become complex conjugates.



We can have a very underdamped response when  $\omega_1 \ll K_V$ . Think about the inverse Laplace transform of the complex conjugate pole pair.

$$e^{-\omega_1 t / 2} \sin \left( \frac{\omega_1}{2} \sqrt{1 - \frac{4K_V}{\omega_1}} t \right)$$

There is an exponentially decaying term determined by the real part of the roots that shows how long it takes the system to settle after a phase or frequency step and a ringing

frequency dictated by the imaginary part of the pole pair. Again, when  $\omega_1 \ll K_V$ , we have a high ringing frequency and a long settling time, characteristic of a system that is not very useful.

It is sometimes useful to define a natural frequency,  $\omega_n$ , and a damping factor,  $\zeta$ . This is standard control system terminology for a second order system. The key is to put the denominator of the closed loop transfer function,  $1 + T(s)$ , into a “standard” form: either

$$s^2 + 2\zeta\omega_n s + \omega_n^2$$

or

$$\frac{s^2}{\omega_n^2} + \frac{2\zeta}{\omega_n} s + 1 .$$

Taking the first formula,  $1 + T(s)$  can be written as:

$$s^2 + \omega_1 s + K_V \omega_1$$

so, we can associate  $\omega_n$  and  $\zeta$  with:

$$\omega_n = \sqrt{K_V \omega_1}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_V}}$$

This form allows you to use standard equations and normalized plots to describe the frequency and transient response of the system. As we saw with the other ways of representing the frequency response of the system, a large  $K_V$ , which we like for reducing phase error, leads to a small  $\zeta$ , which is bad for stability and settling time.

For example, the transient response for a Type 1, second order lowpass system such as this is plotted in the next figure taken from Motorola App. Note AN-535. It is clear that damping factors less than 0.5 produce severe overshoot and ringing.

These parameters will have a strong effect on the loop dynamics which control overshoot and settling time. From the system design perspective, overshoot can be quite harmful, since it will cause the frequency to temporarily exceed the steady state value. Thus, the output of the synthesizer might land in an adjacent channel during part of the transient response. Settling time can also be critical since many TDM applications use different receive and transmit frequencies. The settling time determines how long you must wait until transmitting or receiving after a hop in frequency.

 


Figure 8.33 Variation of VCO frequency during synthesizer settling.


 


Figure 8.34 Effect of synthesizer settling on received and transmitted channels.

Ref. B. Razavi, RF Microelectronics, Prentice-Hall, 1998.

Here you see the consequences of PLL settling time if the PLL is being used as a local oscillator for a receiver or transmitter.

 


**Figure 4. Type 1 Second Order Step Response**

In the frequency domain, the closed loop transfer function will also exhibit gain peaking when the system is underdamped. This is the same effect that we see with feedback amplifiers.

So, it is clear that we need a better transfer function that gives us more flexibility in determining the bandwidth of the filter and the stability of the system. You can't obtain a narrow loop bandwidth without reducing the phase margin/damping factor.

Add a zero to the loop filter transfer function to manipulate the root locus and improve stability.

 Adding a resistor to the lowpass loop filter contributes a zero to its transfer function.



$$F(s) = \frac{1 + s/\omega_2}{1 + s/\omega_1}$$


where

$$\omega_1 = \frac{1}{(R_1 + R_2)C}$$

$$\omega_2 = \frac{1}{R_2C}$$

Thus, the zero frequency is always higher than the pole frequency.

 Check out the Bode plot, root locus and transient response again.



Note that the phase margin has increased. Now, small values of  $\omega_1$  can be used for narrower filter bandwidth, or higher  $K_V$  values can be used for lower phase error without sacrificing phase margin. Note how phase margin now improves when the crossover frequency is increased due to higher gain.

**Root Locus:** Calculate the closed loop transfer function for this PLL with the pole-zero loop filter.

$$\frac{\phi_o}{\phi_{in}} = \frac{(1 + s/\omega_2)}{\frac{s^2}{K_V \omega_1} + s \left( \frac{1}{K_V} + \frac{1}{\omega_2} \right) + 1}$$

The denominator is of the form  $1 + T(s)$ . We can also extract  $\omega_n$  and  $\zeta$  from the closed loop transfer function since the denominator is in one of the standard forms.




$$\omega_n = \sqrt{K_V \omega_1}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_V}} + \frac{1}{2} \frac{\omega_n}{\omega_2}$$

Then, solve for s; these are the poles.
 
$$s = -\zeta \omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$



We see that  $\omega_n$  is the same as with the simple RC filter, but the damping factor has an added term. The first term is quite small in most cases, but the second term can be made large by increasing  $K_V$  or reducing  $\omega_2$ . We still have a type 1 system, but we have an added term that we can use to improve stability, the zero frequency. Note that the zero is in the forward path and therefore shows up in the closed loop transfer function. It will affect the frequency and transient response.

## FREQUENCY RESPONSE


According to Gardner<sup>1</sup>, the loop bandwidth for this Type 1, second-order loop with a forward path zero is given by:

$$\omega_h = \omega_n \left[ 1 + 2\zeta^2 + \sqrt{(1 + 2\zeta^2) + 1} \right]^{1/2}$$

According to this, we have a bandwidth of about  $2\omega_n$  for  $\zeta = 0.707$ .

Refer to Fig. 2.3 from Gardner. This is a plot of the closed loop frequency response of a high gain second order PLL:  $20 \log |H(j\omega)|$ . A high gain PLL is defined by  $K_V/\omega_2 \gg 1$ .

*F.M. Gardner, Phaselock Techniques, Wiley 1979.*

 

**Figure 2.3** Frequency response of a high-gain second-order loop.

<sup>1</sup> F. M. Gardner, Phaselock Techniques, Second ed., Wiley, 1979.

From this plot, we can see how the 3 dB frequency and gain flatness varies with  $\zeta$ . Also, we see that the natural frequency must be significantly greater than the maximum frequency of phase variation for the reference ( $\phi_{in}$ ) when  $\zeta < 1$  in order to avoid gain peaking. This is a consequence of the zero added to the transfer function. For applications that require very small gain peaking (such as clock recovery),  $\zeta > 2$  is often employed.

## PHASE ERROR

There is no frequency error when the loop is locked

- Input frequency = output frequency

But, it is possible to have a phase error for some input transient phase conditions. The phase error must remain bounded in order to keep the loop locked. To analyze in the frequency domain, we assume a sinusoidal phase variation at the input.


$$\text{PHASE ERROR} = \varepsilon(s) = \frac{IN(s)}{1 + T(s)}$$

$$\text{STEADY STATE ERROR} = \varepsilon_{SS} = \lim_{s \rightarrow 0} [s\varepsilon(s)] = \lim_{t \rightarrow \infty} \varepsilon(t)$$

Fig. 2.4 from Gardner's book illustrates how the phase error, expressed as

$$\varepsilon(s) = 20 \log (\phi_{out}/\phi_{in}) \text{ dB}$$

increases as the input frequency approaches the natural loop frequency for the case with  $\zeta = 0.707$ . For input phase variations well below the loop bandwidth, the loop tracks very well. This is because  $|T(j\omega)|$  is large at low frequency.

 

**Figure 2.4** Error response of high-gain loop,  $\zeta = 0.707$ .

### TRANSIENT PHASE ERROR

- Inverse Laplace transform of  $\varepsilon(s)$

Now, let's look more closely at how the phase error is affected by the type of transient phase signal at the input of the Type I PLL.

**1. Phase step.** Because  $\phi_{in}(t) = \Delta\theta u(t)$ , in the frequency domain,

$$\phi_{in}(s) = \frac{\Delta\theta}{s}$$

The steady-state phase error can be calculated from  $\varepsilon(s)$  and  $\varepsilon_{ss}$  above.

$$\varepsilon_{ss} = \lim_{s \rightarrow 0} \frac{s \frac{\Delta\theta}{s}}{1 + \frac{K_V}{s} \left( \frac{1 + s/\omega_2}{1 + s/\omega_1} \right)} = 0$$

Thus, there is only a transient phase error for a phase step. This is reasonable, because the control voltage must return to the same value after the phase step is completed. The frequency will be the same before and after the step.

## 2. Frequency step.

$$\epsilon_{ss} = \lim_{s \rightarrow 0} \frac{s \frac{\Delta\omega}{s^2}}{1 + \frac{K_V}{s} \left( \frac{1 + s/\omega_2}{1 + s/\omega_1} \right)} = \lim_{s \rightarrow 0} \frac{\Delta\omega}{s + K_V \left( \frac{1 + s/\omega_2}{1 + s/\omega_1} \right)} = \frac{\Delta\omega}{K_V}$$

There is a static “error”, but it can be made small by increasing  $K_V$ . This is consistent with the idea that a shift in control voltage is needed to give a step in frequency. The phase error needed to generate this control voltage step varies inversely with the loop gain.

**3. Frequency ramp.** We could do the same exercise for a frequency ramp (Doppler shift). This gives an unlimited steady state error. So, a type I loop is not suitable for tracking a moving source.


Summarizing:

Type I; second order:  $F(s) = \frac{1 + s/\omega_2}{1 + s/\omega_1}$

Input	$\phi_{in}(s)$	$\epsilon_{ss}$
Phase step	$\Delta\theta/s$	0
Freq. step	$\Delta\omega/s^2$	$\Delta\omega/K_V$
Freq. ramp	$\Lambda/s^3$	infinite

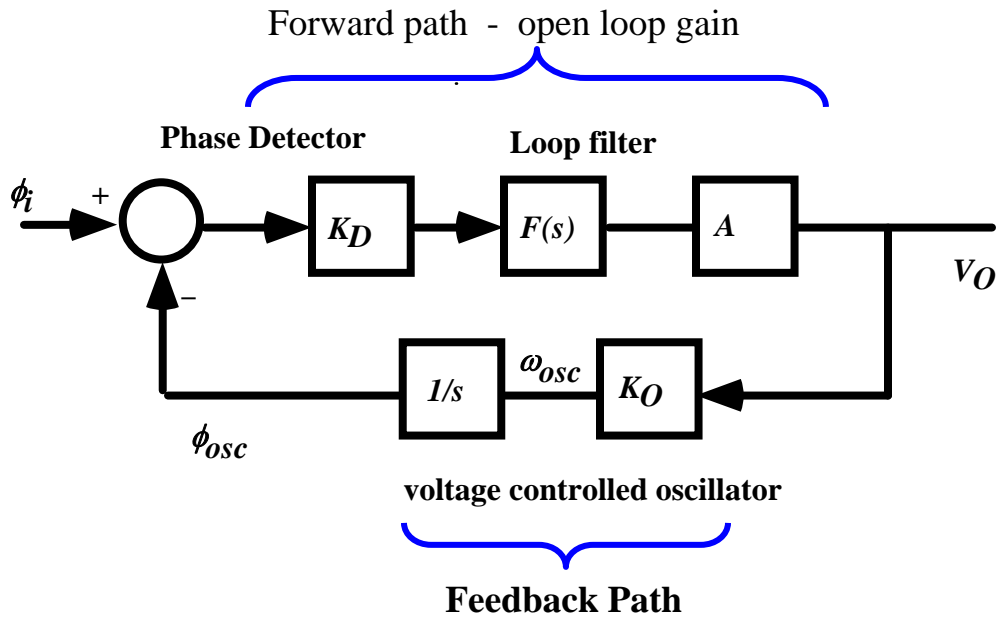**D. FM Demodulator Application. (See Gray and Meyer, Chap. 10, Section 4.)**

Our first application example is the FM Demodulator.



$$\frac{V_O}{\phi_i} = \frac{K_D F(s) A}{1 + K_D F(s) A (K_O / s)}$$

$$\frac{V_O}{\omega_i} = \frac{1}{s} \frac{V_O}{\phi_i} = \frac{K_D F(s) A}{s + K_D F(s) A K_O}$$

For convenience, we define  $K_V = K_D K_O A$

## How does the PLL work as an FM demodulator?

Frequency to voltage conversion: We need to convert the frequency variation of the input signal to a baseband signal whose frequency is equal to  $f_m$ , the modulation frequency, and whose amplitude is proportional to  $\Delta f$ , the frequency deviation. The input carrier frequency will be centered at the IF frequency, but will vary in time around this frequency.

$$\begin{aligned} \text{Input Variable:} \quad & \omega_i = \omega_c + \Delta\omega \sin \omega_m t \\ \text{Output Variable:} \quad & V_o = \Delta\omega / K_o \sin \omega_m t \end{aligned}$$

In the FMD application, the output is the VCO control voltage, not the phase of the VCO. This voltage will track the input FM signal modulation frequency and deviation. The loop filter is lowpass. The block A represents a gain factor, usually 1 with a passive LPF, but it can be higher if the filter is implemented with an active filter.

Assume that the loop is locked at the IF frequency,  $\omega_c$ . Frequency modulation will shift the instantaneous frequency around  $\omega_c$  by  $\Delta\omega$  at rate  $\omega_m$ . As the frequency shifts with time, the phase detector will sense a phase error that increases with time. The filtered error voltage,  $V_{\text{cont}} = V_o$ , will send the VCO closer to  $\omega_c + \Delta\omega$ , tracking the frequency shift. If the bandwidth of the loop is greater than  $\omega_m$ , the loop will track the frequency deviation of the input signal and  $V_o$  will be the demodulated baseband signal,

$$\Delta\omega / K_o \sin(\omega_m t).$$

Now we will consider the frequency and time response of a PLL in the FMD application. The loop filter transfer function  $F(s)$  has a big influence on these responses.

There are two typical applications.<sup>2</sup>

1. Analog baseband demodulation. This would be the case for an FM radio where speech or music is the baseband signal to be recovered.
2. Digital demodulation. The simplest application of this is Binary FSK or Frequency Shift Keying. The frequency is changed in a binary step from  $f_{m1}$  to  $f_{m2}$  and back in order to transmit digital information.

---

<sup>2</sup> Note that there are many other techniques besides PLLs that are used to demodulate PM or FM signals, but this application of the PLL is a good one that helps to illustrate how they function.

In the demodulator application, we can see that the Type 1 second-order PLL will give zero steady state phase error for a PSK input (thus, it isn't useful as a PSK demodulator) and finite phase error for an FSK input if frequency deviation  $\Delta\omega$  is small and  $K_V$  is large, but will have unbounded error for a constantly drifting frequency such as might be caused by the Doppler effect on a moving signal source.

### **Sinusoidal baseband modulation**

Figure 4.1 from Gardner plots the steady state phase error for a frequency modulated source with a single frequency sinusoidal baseband signal. Note that this error is normalized to the ratio of the frequency deviation  $\Delta\omega$  to the loop natural frequency.

Looking at this from a slightly different perspective, suppose that we have a sinusoidal FM source with modulation frequency  $\omega_m$  and deviation  $\Delta\omega$ . We see that the steady state phase error can be small if  $\omega_m/\omega_n$  is small and  $\zeta > 0.7$ .

The steady state phase error can be read from the plot:

$$\varepsilon_{ss} = \theta_e = (\Delta\omega/\omega_n) \times (\text{normalized phase error from the plot})$$

This steady state phase error must remain within the operational range of the phase detector or the loop will lose lock.



 


Figure 4-1 Steady-state peak phase error due to sinusoidal FM.  
 (High-gain, second-order loop.)  
 By permission of L. A. Hoffman.

**Example. FM broadcast application.**

Channel bandwidth	200 kHz
Maximum modulation frequency	$\omega_{m,\max} = 2\pi \times 15 \text{ kHz} = 9.4 \times 10^4 \text{ rad/s}$
Maximum frequency deviation	$\Delta\omega, \max = 2\pi \times 75 \text{ kHz} = 4.7 \times 10^5 \text{ rad/s}$

1. Determine  $K_V$ . Let's use rough numbers just for illustration  
phase detector gain = 1 volt/rad  
VCO gain =  $10^7$  rad/s/volt

So,  $K_V = 10^7 \text{ s}^{-1}$

2. To obtain low phase error and small gain peaking, we need  $\omega_n \gg \omega_{m,\max}$

arbitrarily choose  $\omega_n = 5 \omega_{m,\max}$

then the pole frequency,  $\omega_1 = \omega_n^2 / K_V = 2.2 \times 10^4 \text{ rad/s}$  is determined.

From Fig. 4-1, this gives us a maximum transient phase error of

$$\theta_e = 0.2 \frac{\Delta\omega}{\omega_n} = 0.2 \text{ radians.}$$

3. choose  $\zeta$ . Then,  $\omega_2$  can be calculated:

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_V}} + \frac{\omega_n}{2\omega_2}$$


Typically the second term is much larger than the first.

Let  $\zeta = 0.707$ . Then  $\omega_2 = \omega_n / 2\zeta = 3.4 \times 10^5 \text{ rad/s}$


4. Check the maximum steady state phase error for this case. From the plot, we have a normalized value = 0.2 for  $\omega_n / \omega_m = 0.2$ . Thus,  $\varepsilon_{ss} = 0.2$  radians since  $\Delta\omega / \omega_n = 1$  in this example. This should be well within the operating range of most phase detectors.

Here is a block diagram of the IF and demodulator sections of an FM receiver.

### Receiver for Sinusoidal FM signal

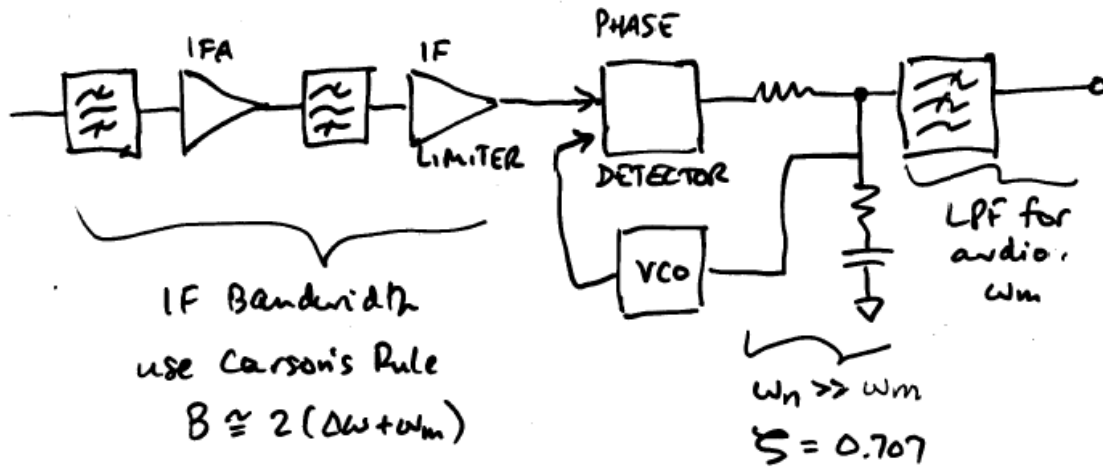

**Frequency shift keying:** In FSK we have a frequency step. We know that the steady state phase error is bounded when  $K_V$  is large, but we should also consider the peak transient phase error. If this exceeds the phase detector operating range, we may lose lock and skip cycles before lock is recovered. Referring to Gardner again, Fig. 4.3 shows the transient phase error for a frequency step.

 

**Figure 4-3** Transient phase error  $\theta_e(t)$  due to a step in frequency  $\Delta\omega$ . (Steady-state velocity error,  $\Delta\omega/K_v$ , neglected.)  
By permission of L. A. Hoffman.

The worst case overshoot is close to  $\omega_n t = 1$ . With  $\zeta = 0.707$ ,  $\theta_e/(\Delta\omega/\omega_n) = 0.45$ .

If  $\Delta\omega =$  frequency step size (deviation) and  $\theta_{e,max} = \pi/2$  radians, we can determine a minimum value of  $\omega_n$  to avoid losing lock.


$$\omega_n \geq 0.45 \frac{\Delta\omega}{\theta_e} = 0.29 \Delta\omega$$

### E. Frequency Synthesizer Application:

How does the design of a frequency synthesizer differ from the FM Demodulator?

For the frequency synthesis application, we want to have ideally perfect phase tracking for phase and frequency steps. An output frequency that is a multiple of the reference frequency is obtained when digital frequency dividers are included in the reference and VCO feedback path. The phase detector will keep the phase and frequency equal at its inputs. The block diagram below is often referred to as an

#### INTEGER-N Frequency Synthesizer.

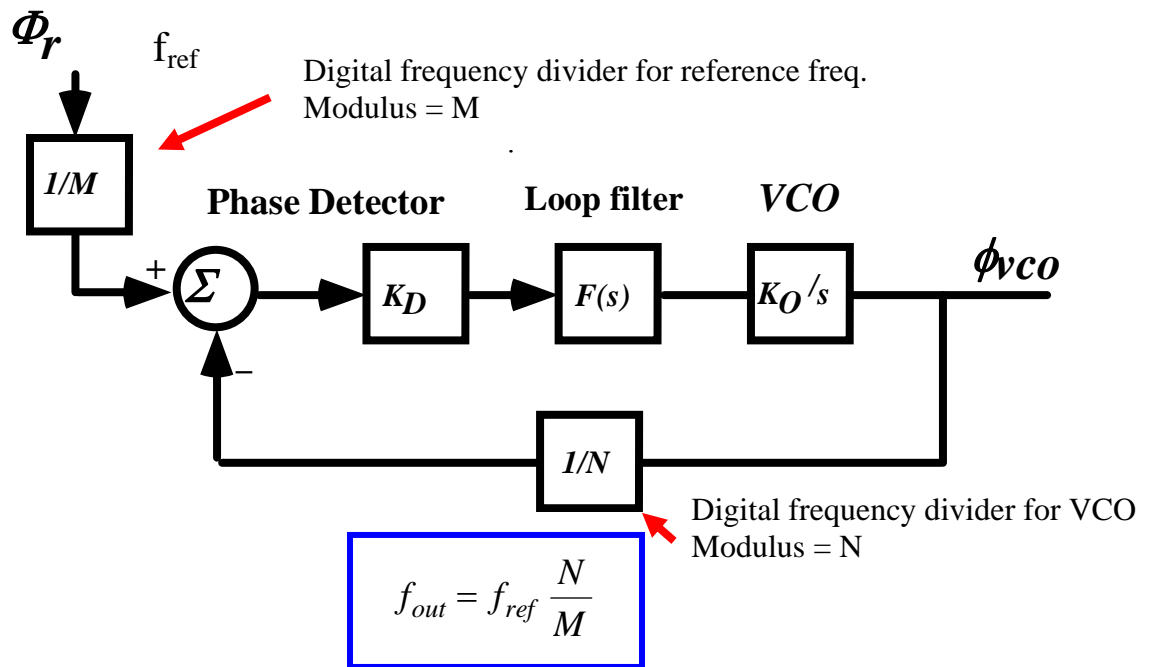

	FMD	FS
Input level	Can have low S/N	You choose the S/N for best performance. Crystal oscillator may have 100 dB S/N
Function	Tracking of frequency	Frequency up/down conversion
We want	Low THD Low noise	Low phase noise
Loop BW	Narrow – similar to IF bandwidth	As wide as possible while preserving low spurious outputs
Transfer function	$V_O(s)/\omega_{in}(s)$	$\phi_{out}(s)/\phi_{in}(s)$

The frequency synthesis application is concerned with:

1. Transient response to a frequency step
2. Steady state phase error for frequency step
3. Stability of feedback loop
4. Phase noise and timing jitter
5. Suppression of spurious output frequencies

In the phase error analysis for the type 1 passive pole-zero lag filter, we found that there was a static phase error for a frequency step. To eliminate this phase error, we need a TYPE = 2 loop gain function. This requires an ideal integrator rather than a passive lead-lag filter.

Type 2; second order:

$$F(s) = \frac{1 + s/\omega_2}{s/\omega_1}$$

Input	$\phi_{\text{ref}}(s)$	$\epsilon_{\text{ss}}$
Phase step	$\Delta\theta/s$	0
Freq. step	$\Delta\omega/s^2$	0
Freq. ramp	$A/s^3$	kA

Placing an opamp RC integrator or charge pump in the loop will give a filter transfer function of the form:

$$F(s) = \frac{1 + s/\omega_2}{s/\omega_1}$$

where providing a pole at  $s = 0$  and a zero at  $\omega_2$ . Then, the loop gain  $T(s)$  will be that of a type 2 control system:

Details regarding the implementation of these filters will be presented later.


 


Figure 6. Type 2 Second Order Step Response

Ref. Motorola AN535

Here we see the phase and frequency step response for a type 2 PLL in terms of the key loop parameters. The settling time can be determined by setting an error tolerance around  $\theta_o(t) = 1$ . For example, if settling to 5% were the criteria and if  $\zeta = 1$ , the response first falls within the boundary of 0.95 or 1.05 for  $\omega_n t = 4.5$ . Then settling time  $t$  can be determined since natural frequency  $\omega_n$  will also be known.

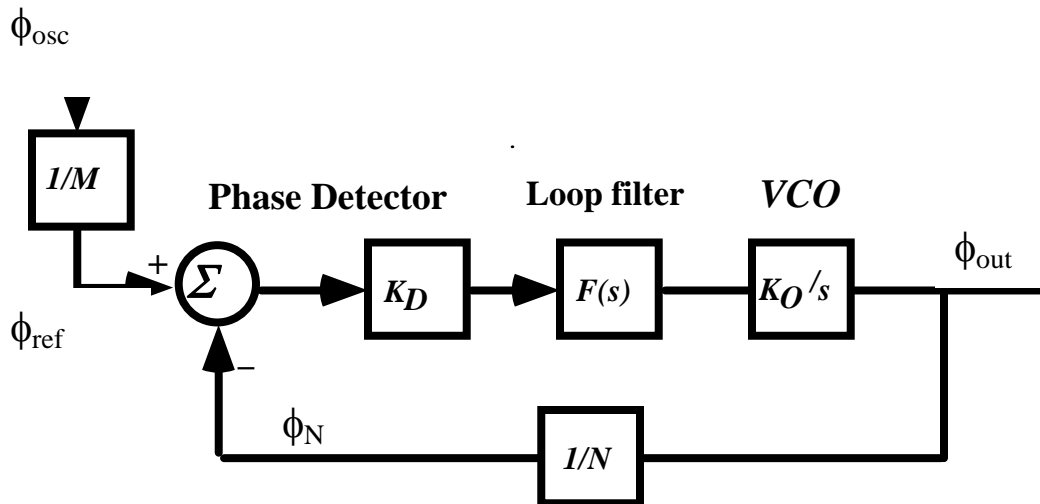

$$\frac{\phi_N}{\phi_{out}} = \frac{1}{N}$$

and also,  $N = \frac{\omega_{out}}{\omega_{ref}}$

We can calculate the loop gain,  $T(s)$ :

$$T(s) = \frac{K_D K_O F(s)}{Ns}$$

- We see that the loop gain is reduced by a factor of  $N$ .
- Also, in most applications,  $N$  is not constant, and
- $K_O$  is not a constant – varies with frequency according to the choice of  $N$

Using the  $F(s)$  determined for the ideal integrator type 2 pole-zero loop filter:

$$F(s) = \frac{1 + s/\omega_2}{s/\omega_1}$$

$$1 + T(s) = 1 + \frac{K_V}{Ns} \left( \frac{1 + s/\omega_2}{s/\omega_1} \right) = 0$$



$$1 + T(s) = \frac{Ns^2}{K_V \omega_1} + \frac{s}{\omega_2} + 1 = 0$$

We can now determine how the natural frequency and damping are affected by N:

$$\omega_n = \sqrt{\frac{K_V \omega_1}{N}}$$
$$\zeta = \frac{\omega_n}{2\omega_2}$$

If  $K_V = K_O K_D$  were constant (it is usually not) then the damping factor  $\zeta$  is decreased as N is increased. But, the frequency dependence of the VCO tuning coefficient  $K_O$  must also be considered when evaluating how damping varies with frequency.


## Root Locus:

Now, find the poles of  $1 + T(s) = \frac{Ns^2}{K_V \omega_1} + \frac{s}{\omega_2} + 1 = 0$

$$s = -\zeta\omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$


where  $\zeta$  and  $\omega_n$  are as defined above.

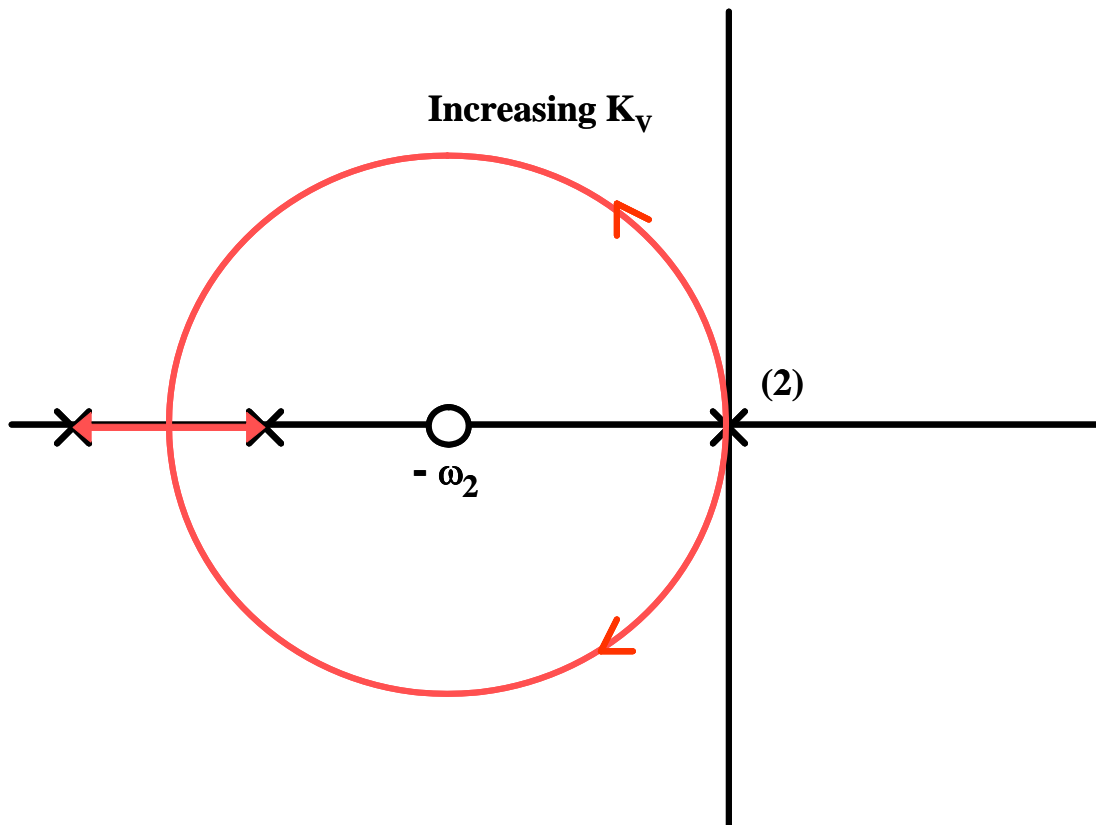Now examine the root locus. As the loop gain  $K_V$  increases, both real and imaginary parts grow. The locus follows a circle centered around the zero. The poles become real again when  $\zeta = 1$ . This happens when  $K_V = 4\omega_2^2/\omega_1$ . We have the same geometric interpretation that was discussed in the FMD notes.



## F. Some hardware implementation considerations
 
### 1. Loop Filter – OpAmp Implementation



An op amp can be used to form a filter that includes a pole at  $s = 0$  and a finite zero. For example, the circuit above can be analyzed using the virtual ground approximation to obtain  $F(s)$ .

$$F(s) = \frac{V_{out}}{V_{in}} = \frac{1 + sR_2C}{sR_1C}$$

These values correspond to the  $\omega_1 = 1/R_1C$  and  $\omega_2 = 1/R_2C$  used in the derivation of  $T(s)$ .

$V_{bias}$  can be used to level shift between the phase detector and the VCO if needed.

For this loop filter, we can evaluate  $\omega_n$  and  $\zeta$  in terms of the 3 components:

$$\omega_n = \sqrt{\frac{K_V}{R_1CN}}$$
$$\zeta = \frac{R_2}{2} \sqrt{\frac{K_VC}{R_1N}}$$

## 2. Let's design a synthesizer

We can start with a transient specification for locking of the synthesizer PLL

- Overshoot < 20%
- Settling time = 1 mS

From Fig. 6 of AN535 we see that a  $\zeta = 0.8$  meets the overshoot spec.

Settling to within 1% happens at  $\omega_n t = 5.5$

$$\text{So, } \omega_n = 5.5/1\text{mS}$$

Note that:

1.  $K_D$  is fixed. Depends on the phase detector
2.  $K_O$  is found from the slope of the VCO tuning curve.  
In general, this is not constant, but varies with tuning voltage.
3.  $N$  is determined by  $\omega_{\text{out}}/\omega_{\text{ref}}$

The change in  $N$  required to tune over the required range and the change in  $K_O$  causes the loop gain  $T$  to vary with frequency.


Since damping also increases with  $K_V$  and decreases with  $\sqrt{\frac{1}{N}}$ , loop dynamics will depend on  $N$ .

4. The phase detector will have a maximum output current.  
 $R_1$  must be consistent with  $V_{DD}/I_{\text{max}}$  Refer to the data sheet.
5. Choose  $C$  to determine  $\omega_n$
6. Use  $\zeta$  to determine  $R_2$ .

An alternate design sequence could have used the loop bandwidth,  $\omega_h = \omega_{3\text{dB}}$  as a starting point. We will show later that this is the phase noise corner frequency. From  $\omega_{3\text{dB}}$  and  $\zeta$ ,  $\omega_n$  could be determined. The settling time is then set by default.

### 3. Phase Frequency Detector


The phase-frequency detector shown below is a widely used architecture in frequency synthesizers. As opposed to the XOR phase detector that we first considered, this one produces two outputs:  $Q_A$  and  $Q_B$ , or as is customary, UP and DOWN respectively.

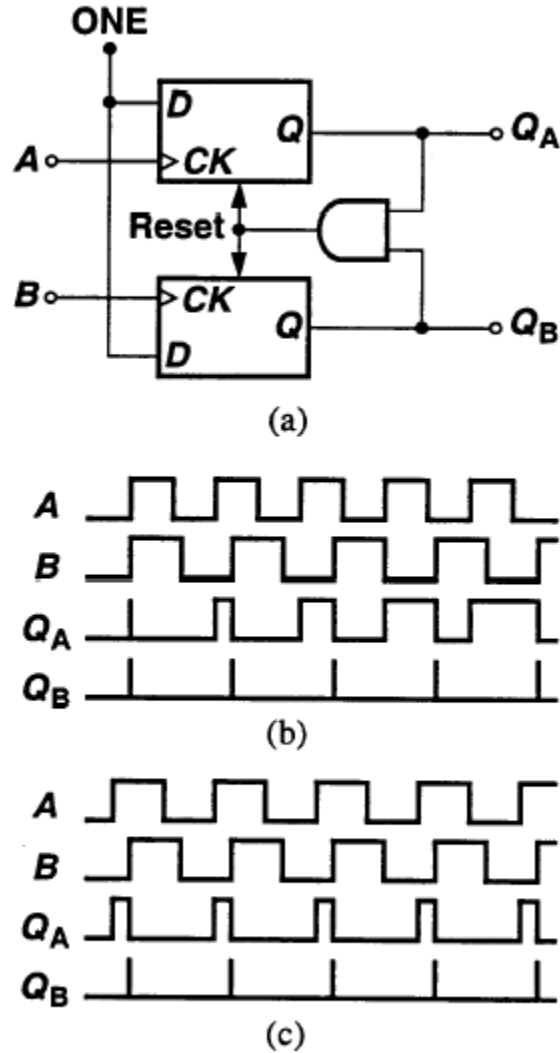

**Figure 3.26.** (a) Phase/frequency detector. Circuit response with (b)  $\omega_A \geq \omega_B$ , ( $A$  leading  $B$ ).

Ref. J. Savoj and B. Razavi, High Speed CMOS for Optical Receivers, Kluwer Academic Publishing, 2001. (and many other books)

 
This phase detector has a much larger phase range ( $4\pi$ ) of operation, and it will produce an output that drives the frequency in the right direction when it is out of lock. It also has zero offset when the phases are aligned and is insensitive to the duty cycle of the inputs since edge-triggered flip-flops are used.



PFD characteristic.

When the phases coincide, both outputs produce minimum width pulses. When there is a phase or frequency error, the width of the UP or DOWN pulses increases. When integrated by the loop filter, this causes the control voltage of the VCO to move toward the locked condition of equal frequency and phase.

 Because both outputs must be combined to obtain the desired output, the loop filter must be modified for differential inputs as shown below.  $F(s)$  is the same as that of the single ended version.




## I. Reference Spurs.

The Integer N PLL has an inherent conflict between the frequency step size (increment) and the settling time/bandwidth. The phase detector produces pulses that are at the reference frequency,  $f_R$ . These pulses are filtered by the loop lowpass filter,  $F(s)$ , but not completely. Any residual reference frequency component on the VCO tuning voltage port produces frequency modulation. FM sidebands, called reference spurs, appear on both sides of the desired output spectral line. The sidebands are spaced at  $f_R$ .

The crossover frequency of the open loop gain,  $T$ , (where  $|T| = 1$ ), must be well below the reference frequency so that the reference frequency component is well attenuated by the loop filter. Once beyond crossover, the loop gain is less than 1, and so attenuates the spurs. The slope beyond crossover (or the closed loop 3 dB bandwidth) is 20 dB/decade for the second order loop with zero. For example, if you need 40 dB of spur attenuation, you must choose a crossover frequency that is a factor of 100 less than the reference frequency.

 Since the settling time and loop bandwidth are directly affected by the crossover frequency, we have conflicting requirements. Compromises must be made.



Spectral display of PLL output with reference spur sidebands

#### 4. Charge Pump Loop Filter

An alternative loop filter implementation called the charge pump is widely used for many applications. It is very convenient to implement in CMOS, so is more frequently used than the opamp version.

- The PFD output produces UP ( $Q_A$ ) and DOWN ( $Q_B$ ) pulses whose width is proportional to the phase error.
- Charge pump current sources  $I_1$  and  $I_2$  must produce exactly equal currents. They charge and discharge the capacitor,  $C_P$ , in discrete steps.
- If there is a static phase error  $\Delta\phi$  at the PFD input, the capacitor,  $C$ , will be charged indefinitely – therefore, the DC gain is infinite: an ideal integrator. So, we expect to have zero static phase error. This is unlike the type I loop which gave  $\Delta\phi = \Delta\omega/K_V$  steady state phase error.
- The CP PLL will detect small phase errors and correct them as long as the frequency of the phase error (jitter frequency) is within the loop 3 dB bandwidth. This phase comparison occurs on every cycle.


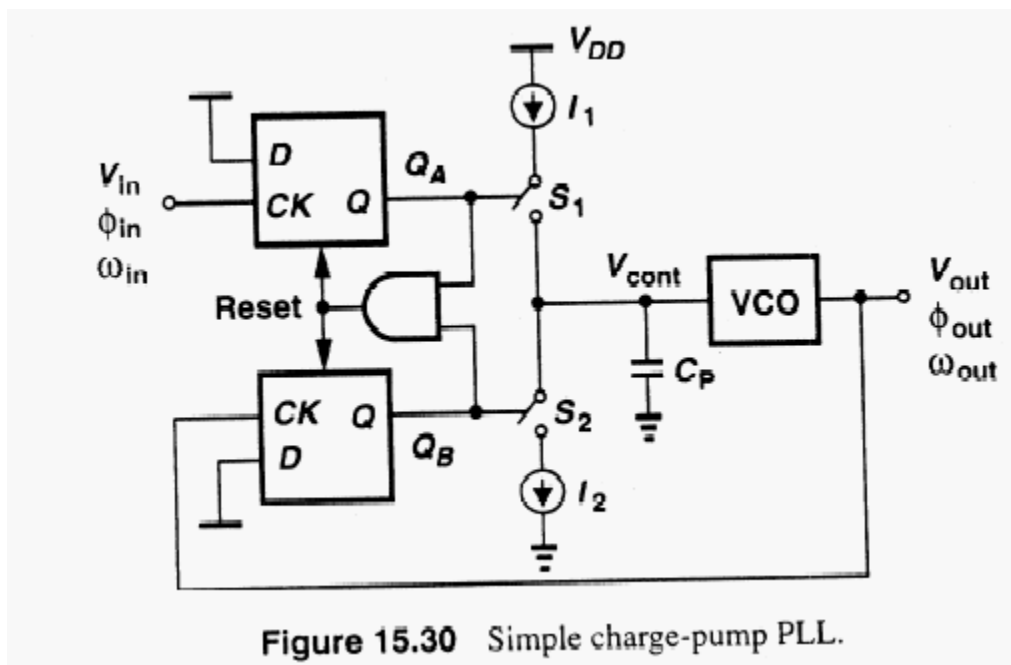


Figure 15.30 Simple charge-pump PLL.

(from B. Razavi, Design of Analog CMOS Integrated Circuits, McGraw-Hill, 2001.)

To illustrate how the charge pump works and how it might be analyzed in a linearized model, refer to Fig. 15.32. Here we assume that  $I_1 = I_2 = I_P$  and that a phase step  $\Delta\phi$  occurs at  $t = 0$ .

 



**Figure 15.32** Step response of PFD/CP/LPF combination.

(from B. Razavi, Design of Analog CMOS Integrated Circuits, McGraw-Hill, 2001.)

First consider the time domain picture above.  $\Delta\phi = \phi_0 u(t)$

$Q_A$  produces pulses that are of width

$$\frac{\Delta\phi}{2\pi} T_{in} = \Delta t .$$

$I_P$  charges  $C_P$  by

$$\Delta V = \frac{I_P}{C_P} \Delta t = \frac{I_P}{C_P} \frac{\phi_0}{2\pi} T_{in}$$

in every period. We can approximate this as a linear ramp with slope

$$slope = \frac{I_P}{2\pi C_P} \phi_0$$

Thus, the output voltage from the charge pump can be described by


$$V_{out}(t) = \frac{I_P \phi_0}{2\pi C_P} t u(t)$$

The derivative of the step response is the impulse response, so we can determine the frequency domain transfer function.

$$h(t) = \frac{dV_{out}}{dt} = \frac{I_P}{2\pi C_P} u(t)$$

Take the Laplace transform to obtain the frequency domain transfer function.

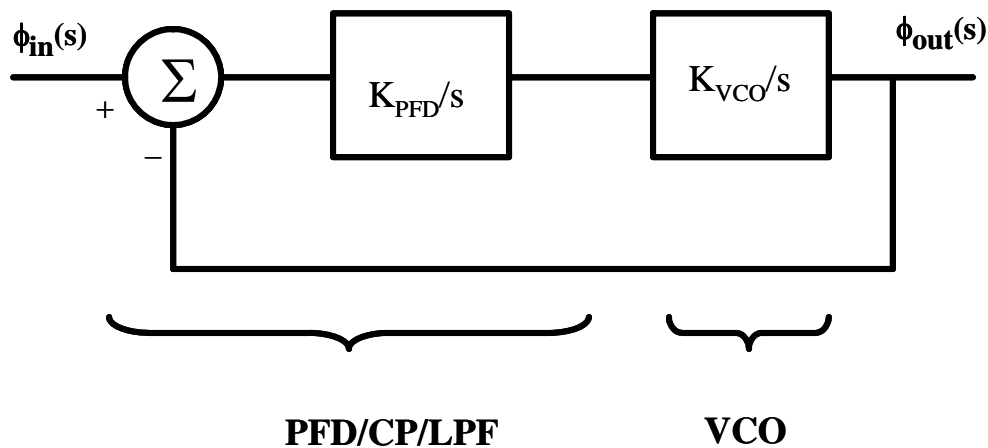
$$H(s) = \frac{V_{out}(s)}{\Delta\phi} = \frac{I_P}{2\pi C_P} \frac{1}{s} = \frac{K_{PFD}}{s}$$




Here is the block diagram of the CP PLL. We see that the loop gain function  $T(s)$  has a factor of  $s^2$  in the denominator. Thus, it is a type II loop.


$$T(s) = \frac{K_{PFD}}{s} \frac{K_{VCO}}{s}$$

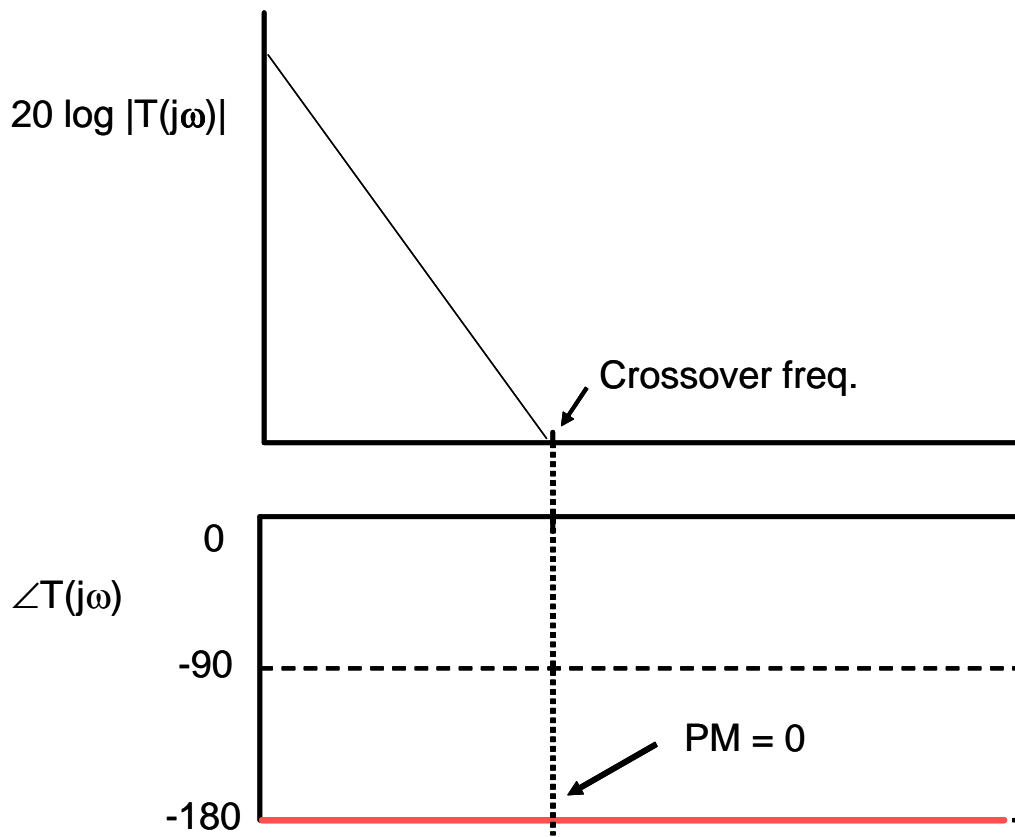But, because of that, we have a big problem. The phase margin is always zero as shown by the Bode plot below.



 Therefore, we must add a zero to the loop filter transfer function to provide some phase lead to stabilize the PLL.




 

Now, we can see that an increase in the loop gain will improve phase margin.

To determine  $T(s)$  for this case, we want to calculate  $V_{out}(s)/\Delta\phi$  again, adding the resistor to the charge pump filter.

New filter:

 

The phase frequency detector (PFD) with single capacitor  $C_P$  has

$$H(s) = \frac{V_{out}(s)}{\Delta\phi} = \frac{I_P}{2\pi C_P} \frac{1}{s} = \frac{K_{PFD}}{s}$$

To find the frequency response of the input current, we note that,

$$I(s) = V_{out}(s)/Z(s) = V_{out}(s)/(1/sC_P)$$

where  $Z(s)$  is the complex impedance. So, the current source can be modeled as:

$$\frac{I(s)}{\Delta\phi} = \frac{I_P}{2\pi}$$

Now, let's use this to modify  $H(s)$  for the series RC loop filter. To do this, just replace the impedance  $1/sC_P$  with  $Z(s) = R_P + 1/sC_P$ .

$$\frac{V_{out}(s)}{\Delta\phi} = \frac{I_P}{2\pi} \left( R_P + \frac{1}{sC_P} \right)$$

The loop gain  $T(s)$  is therefore


$$\begin{aligned} T(s) &= \frac{\phi_{out}(s)}{\phi_{in}} = \frac{I_P}{2\pi} \left( R_P + \frac{1}{sC_P} \right) \frac{K_{VCO}}{s} \\ &= \frac{I_P K_{VCO}}{2\pi C_P} \frac{(R_P C_P s + 1)}{s^2} \end{aligned}$$

We see that a zero at  $\omega = 1/R_P C_P$  has been added to the transfer function. This provides the necessary phase lead to achieve stability.

Of course a frequency divider can be placed in the feedback path if the output frequency is to be multiplied by the PLL. Divide by  $N$  gives

$$\begin{aligned} \phi_{out} &= N\phi_{in} \\ \omega_{out} &= N\omega_{in} \end{aligned}$$

 This added divider would be needed in a frequency synthesizer application or clock multiplier application.



$T(s)$  is then modified by a factor of  $1/N$ .

$$T(s) = \frac{I_P K_{VCO}}{2\pi N C_P} \frac{(R_P C_P s + 1)}{s^2}$$

Now, let's derive the closed loop transfer function. Define  $K_V = I_P K_{VCO} / 2\pi C_P$  and zero frequency  $\omega_z = 1/R_P C_P$ .


$$\begin{aligned} H(s) &= \frac{\phi_{out}(s)}{\phi_{in}} = \frac{K_V (s/\omega_z + 1) / s^2}{1 + K_V (s/\omega_z + 1) / N s^2} \\ &= \frac{N(s/\omega_z + 1)}{\frac{N}{K_V} s^2 + \frac{s}{\omega_z} + 1} \end{aligned}$$

Having put this in one of the standard forms, we can extract  $\omega_n$  and  $\zeta$  from the denominator.

$$\begin{aligned} \omega_n &= \sqrt{\frac{K_V}{N}} = \sqrt{\frac{I_P K_{VCO}}{2\pi C_P N}} \\ \zeta &= \frac{\omega_n}{2\omega_z} = \frac{R_P}{2} \sqrt{\frac{I_P K_{VCO} C_P}{2\pi N}} \end{aligned}$$

We can see now with  $R_P = 0$ ,  $\zeta = 0$ , therefore there is no phase margin and the system is unstable as expected. With added  $R_P$ , the damping factor can be increased. Also note that stability will decrease with increasing  $N$ . Loop gain must be increased to compensate for this.

 The root locus of the modified charge pump PLL is shown below. It is the same as was obtained for the opamp loop filter.



As loop gain is increased by increasing  $I_p K_{VCO}$ , the dual poles at  $s = 0$  split and form a circular locus, rejoining the real axis at  $-1/2R_p C_p$ .

The pole locations are found at

$$s = -\zeta\omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$


## G. Closed Loop Frequency Response

The closed loop frequency response can be evaluated from  $H(j\omega)$ . Recall that

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_V F(s)/s}{1 + T(s)}$$

In Fig. 2-3, Gardner has plotted the magnitude as a function of  $\omega/\omega_n$ .

*F.M. Gardner, Phase Lock Techniques, Wiley 1979.*

 

**Figure 2.3** Frequency response of a high-gain second-order loop.

We see that the frequency response is a low pass to  $\phi_{in}$ . Thus, the phase noise of the reference source passes through the PLL, is increased in magnitude by  $20 \log N$ , and is filtered as shown in Fig. 2-3. Below the crossover frequency (0 dB in the figure above), we have little attenuation of input noise. Above, noise is reduced by 20 dB/decade.

Also note that for  $\zeta < 2$ , there is gain peaking. Actually there is always some gain peaking for the Type II CP PLL or the opamp filter PLL because the zero frequency is always less than the pole frequency in the strongly damped case. For some applications, this is inconsequential. However, for clock and data recovery (CDR) use, the SONET specification is very strict: less than 0.1 dB of gain peaking is allowed. This is because




in an optical fiber link, the signal may pass through several repeaters that include CDR units. Cascaded transfer functions with gain peaking leads to amplification of jitter (phase noise) close to the 3 dB frequency.
 
## H. PLL Phase Noise

We have considered how the loop crossover frequency and phase margin affect things like settling time and capture range. But it also plays a role in the PLL noise behavior.

Phase noise consists of noise sidebands offset on either side of the oscillator output frequency. These typically drop off at 20 dB/decade in magnitude with offset  $\Delta f$  from carrier. This type of noise is really bad for communication applications because it spreads out the oscillator signal. Rather than looking like an impulse in the frequency domain, the local oscillator now occupies a finite region of the spectrum. If this noise overlaps with adjacent frequency channels, a phenomenon called *Reciprocal Mixing* occurs. On receive, strong signals outside of the desired channel mix with the oscillator phase noise sidebands into the desired channel. If filtering cannot remove this. On transmit, the LO noise shows up in someone else's channel, also bad.



In the spectrum above, the LO frequency has noise sidebands due to phase noise. This can cause mixing of signals from adjacent channels as shown by the interfering signal,  $f_{INT}$  being mixed down to the same IF frequency as  $f_{RF}$ . Thus, the LO phase noise degrades the SNR of the RF signal.

For frequency synthesis, we are interested in low phase noise. There are at least 2 main sources:


1. Reference and PFD-CP noise – Reference noise is usually small since we frequently use a crystal oscillator with very low phase noise. However, if the ratio of  $f_{out}/f_{ref} = N$  is very large, the PLL will multiply the phase noise of the reference by  $N$ . Thus, the noise power at the output is increased by

$$20 \log N.$$

2. VCO noise – often high. We hope that the PLL will suppress most of the noise within the loop bandwidth, at least close to the carrier.

The effect caused by each of these noise sources can be seen from the closed loop transfer functions.

### 1. Reference Noise:

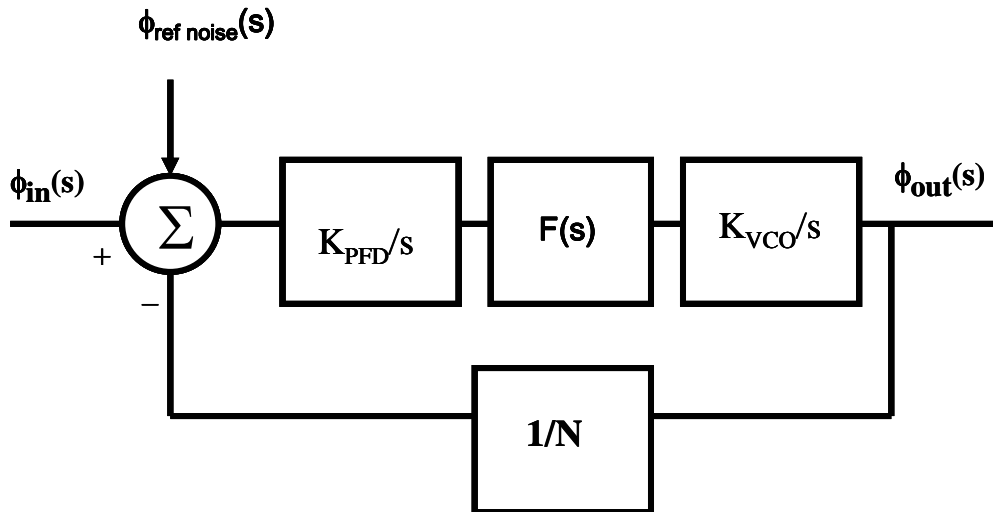

Adding the phase noise of the reference source,  $\phi_{ref\ noise}$ , at the input,


$$\begin{aligned} \frac{\phi_{out}}{\phi_{ref}} &= \frac{\text{Forward Path}}{1 + T(s)} = \frac{K_V F(s) / s}{1 + K_V F(s) / Ns} \\ &= \frac{N(1 + s / \omega_2)}{Ns^2 / K_V + s / \omega_2 + 1} \end{aligned}$$

This is a low pass transfer function. Its magnitude approaches  $N$  as  $s$  becomes small. Thus, reference phase noise is low pass filtered by the loop. Reference phase noise can be quite low when a crystal oscillator is used to generate the reference frequency. However, the phase noise fluctuation gets multiplied by a factor of  $N$  for the integer  $N$  PLL.

$$\frac{\phi_{out}}{\phi_{ref}} = N$$

Because noise power is proportional to the square of the phase, reference phase noise power at the PLL output is increased by a factor of  $N^2$  or **20 log N** for offset frequencies within the loop bandwidth. This is a serious limitation for large  $N$  values. There are better architectures to be used when small step size and low phase noise are both required.

## 2. VCO Noise:

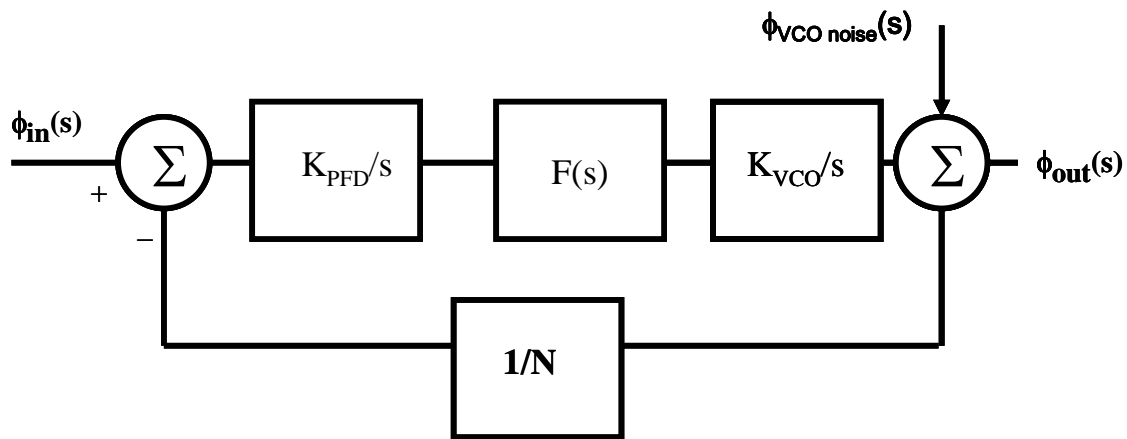

$$\begin{aligned} \frac{\phi_{out}}{\phi_{vco}} &= \frac{\text{Forward Path}}{1 + T(s)} = \frac{1}{1 + K_V F(s) / Ns} \\ &= \frac{Ns^2 / K_V}{Ns^2 / K_V + s / \omega_2 + 1} \end{aligned}$$

This is a high pass closed loop transfer function. It approaches a magnitude of 1 as  $s$  becomes large.

While LC VCOs can have low phase noise, they generally have smaller tuning range. RC or ring oscillator VCOs can be built with very wide tuning range but poor phase noise. The PLL can be used to clean up the VCO phase noise within the loop bandwidth. VCO phase noise is unattenuated at offset frequencies beyond the loop bandwidth.

### Conclusions:

1. Reference input noise (reference source noise, data jitter, phase noise on FM input signal, etc.) sees a low-pass transfer function. It is passed through and multiplied by  $N$ . All we can do is try to avoid making it worse with our loop. A narrow bandwidth loop filter will help to suppress high frequency noise coming into the PLL from the reference port.
2. VCO jitter is suppressed by the PLL within the loop bandwidth. It has a high-pass transfer function. Thus, to suppress VCO noise, we want a large loop bandwidth.

## Lock and Capture Behavior

Up until now, we have assumed that the loop is always locked:

$$\phi_{out} = \phi_{in} \quad \omega_{out} = \omega_{in}$$

But, we have seen that some finite phase error is necessary to drive the VCO. If  $K_V$  is large and/or we use a Type II loop filter, the steady state error is very small or zero.

1. **Static Tracking.** When the input or reference frequency is changed slowly or the divide modulus change is small, the loop remains locked. The VCO control voltage coming from the loop filter varies slowly to track the change in frequency. As long as the VCO frequency is capable of providing what is required, and the phase detector range is not exceeded, the PLL continues to follow. Locking range is either

$$\Delta\omega_L = \pm K_D K_O (\text{PFD range})$$

OR

$$\Delta\omega_L = \pm \text{VCO freq range}$$

2. **Dynamic Tracking.** If the input frequency or  $N$  is changed by a large step, the loop responds with an exponential envelope.

$$e^{-\omega_n \zeta t}$$

It is possible for the PLL to lose lock temporarily until the control voltage catches up. This referred to as cycle slipping. The PLL must then *capture* lock again.

Consider a mixer or XOR type of phase detector. If the two input frequencies,  $\omega_{in}$  and  $\omega_{VCO} = \omega_{in} + \Delta\omega$  are different, then,

$$V_e = \cos(\omega_{in} t) \cos[(\omega_{in} + \Delta\omega)t]$$

The output contains frequency components at  $\Delta\omega$  and  $2\omega_{in} + \Delta\omega$ . The higher frequency component is removed by the loop filter, but the output of the loop filter contains the  $\Delta\omega$  frequency. If the loop were open, as seen in the figure below, part (a), the VCO is frequency modulated and produces sidebands separated by the beat frequency.<sup>1</sup>

---

<sup>1</sup> B. Razavi, in *Monolithic Phase Locked Loops and Clock Recovery Circuits: Theory and Design*, Wiley-IEEE Press, 1996.

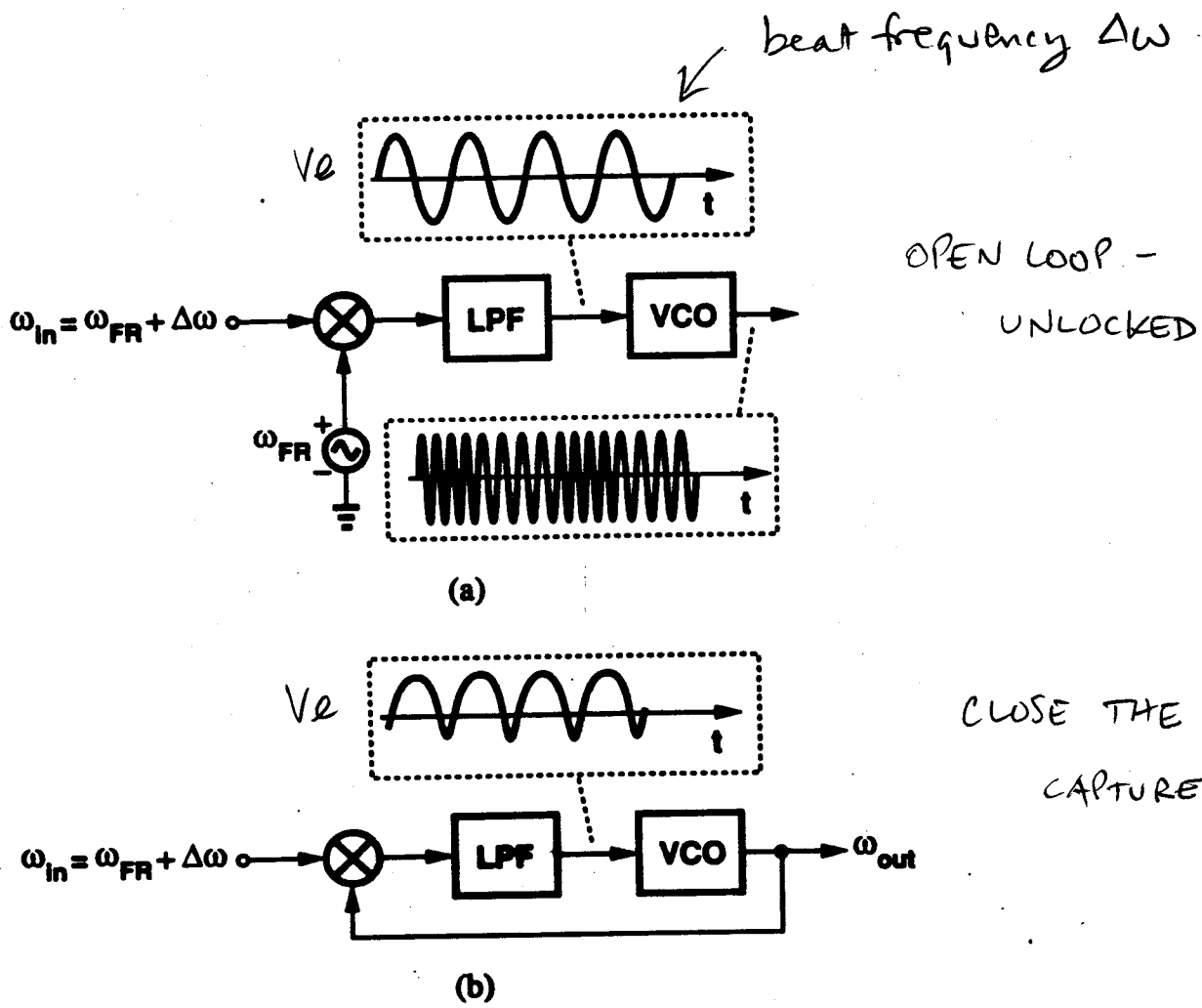


Fig. 22 Acquisition behavior in time domain.

When the loop is closed, part (b) above shows how there is a net DC component in the control voltage that will drive the VCO toward lock. Once the PLL loses lock, the VCO frequency may drift back to its free running frequency. Then, capturing lock requires moving that frequency close to the reference frequency.

### **Why is the capture range always less than the lock range?**

When the loop is unlocked, there is an output of the phase detector at the difference frequency,  $\Delta\omega$ .

When this is filtered by the loop filter, the amplitude reaching the VCO will be reduced by

$$V_{cont} = V_e |F(j\Delta\omega)|$$


Hence, if the loop filter has a narrow bandwidth, only small deviations from  $\omega_{in}$  can be tolerated without losing lock. Once the PLL loses lock, the frequency difference must be brought within  $\Delta\omega$  in order to restore lock.

The figure on the next page illustrates how the lock range is greater than the capture range in a hypothetical example<sup>2</sup>. Note how the error voltage tracks the input frequency change once lock is established.


$$\Delta f_{capture} < \Delta f_{lock}$$

---
 
<sup>2</sup> A. Grebene, Bipolar and Analog Integrated Circuit Design, p.633, Wiley Interscience, 1984.



(a)

 

(b)

FIGURE 12.3. Typical PLL frequency-to-voltage transfer characteristics: (a) Slowly increasing input frequency; (b) decreasing input frequency.