


# Recursive Synthesis of Digital Circuits

Behrooz Parhami

*Department of Electrical and Computer Engineering  
University of California, Santa Barbara, USA*





[parhami@ece.ucsb.edu](mailto:parhami@ece.ucsb.edu)

 **Presentation on Behalf of IEEE Computer Society's  
Distinguished Visitors Program**


 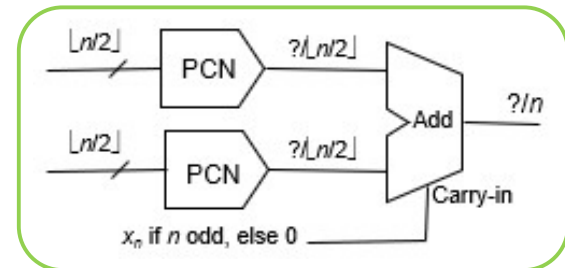  
## Outline

- Intro: HW Design and Recursion
- Iterative Refinement (SW & HW)
- Algor/SW/HW Recursion Example
- Example 1: Fast Fourier Transform
- Example 2: Recursive Multipliers
- Example 3: Counting Networks
  - Parallel Counters
  - Weight-Checkers
  - Threshold Counters
  - Variations in Counting
- Conclusion and Future Work



# Introduction: Hardware Design


- Time- and work-intensive; expensive; error-prone
- Choice of algorithm, technology, design methodology
- Quick proof-of-concept, followed by fine-tuning
- Fine-tuning adds complexity and thus errors
- In some cases, correctness / reliability more important
- Modularity, packageability, reusability are key attributes
- Ditto for testability, serviceability, availability
- We may opt for simpler designs, older technologies
- $O(\sqrt{n})$  &  $O(\lg n)$  complexities about the same for small  $n$

# The Concept of Recursion

To iterate is human, to recurse divine!
 
## Textbook definition:

Recursion is a method where the solution to a problem depends on solutions to smaller instances of the same problem.



Problem {  
Base case  
Subproblem(s)


$$n! = \begin{cases} \text{if } n \leq 1 \text{ then } 1 \\ \text{else } n \times (n - 1)! \end{cases}$$

$$fib(n) = \begin{cases} \text{if } n \leq 2 \text{ then } 1 \\ \text{else } fib(n - 1) + fib(n - 2) \end{cases}$$

Recursive  
Dolls



# Recursive Pizzas

 

# Iterative Refinement

- Compute  $f(z)$  by iteratively refining an approximation
- Example  $x = \sqrt{z}$ :  $x^{(i+1)} = 0.5(x^{(i)} + z/x^{(i)})$


$$\sqrt{z} \approx x^{(0)} = 1.5$$

$$\sqrt{z} \approx 1 + z/4$$

$$\sqrt{z} \approx 7/8 + z/4$$

$$\sqrt{z} \approx 17/24 + z/3$$


Best linear approx.

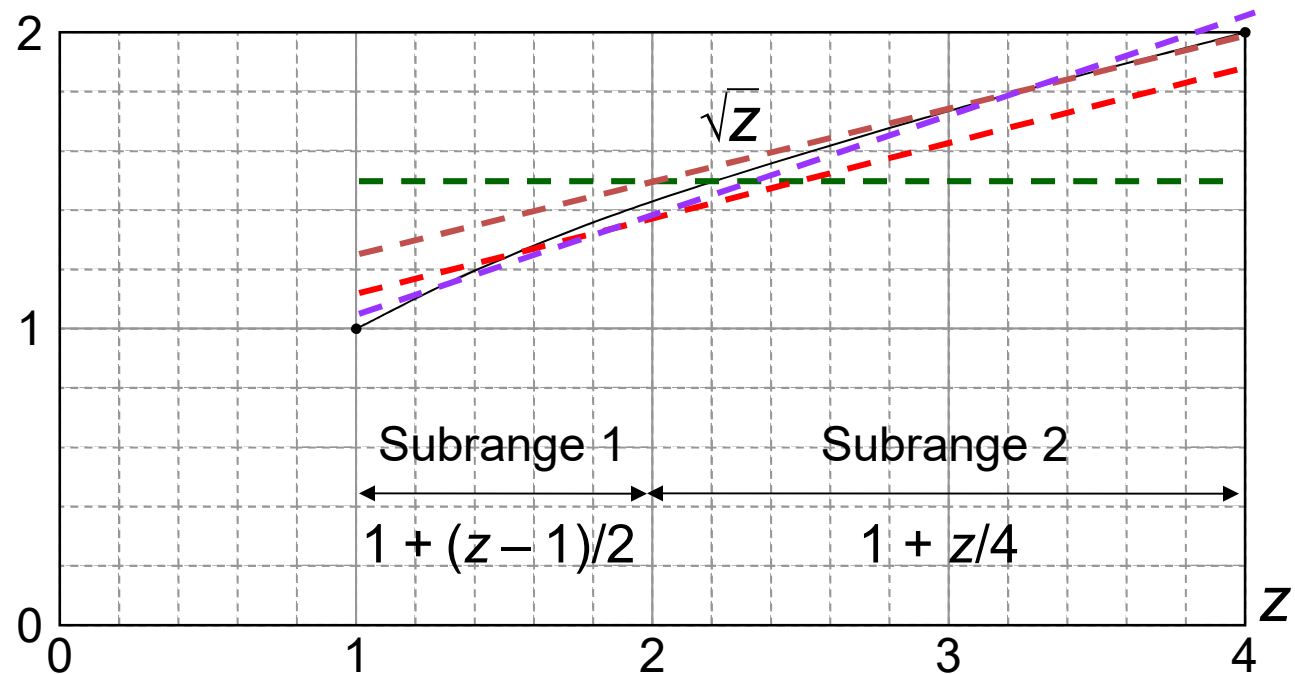

## Unrolling and Pipelining

- Compute  $f(z)$  by iteratively refining an approximation

 
- Example  $x = \sqrt{z}$ :  $x^{(i+1)} = 0.5(x^{(i)} + z/x^{(i)})$



- Pipelining: Five different square-rootings in progress
- No unrolling: One orange box, used four times
- Partial unrolling: Two orange boxes, used twice




 
# Algorithm/SW/HW Example: Selection Sort



```

 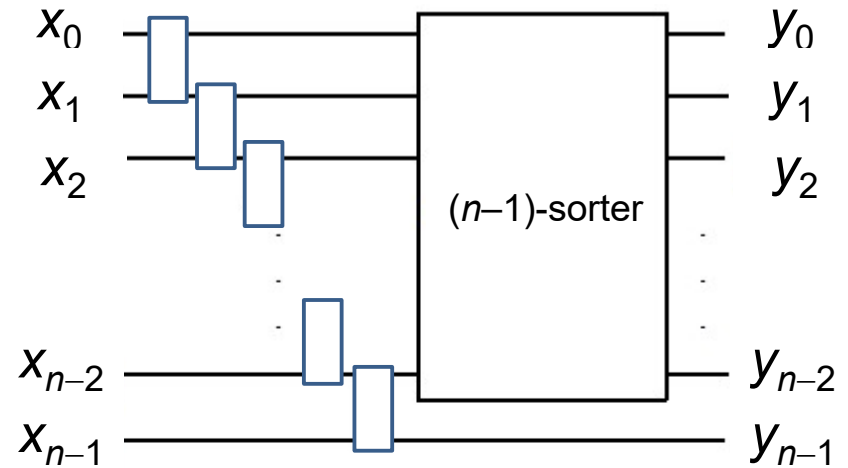selectionsort( $x_0, x_1, \dots, x_{n-1}$ )
if  $n = 1$  then exit
find  $x_j = \max(x_0, x_1, \dots, x_{n-1})$ 
swap  $x_j$  and  $x_{n-1}$ 
selectionsort( $x_0, x_1, \dots, x_{n-2}$ )
    
```



# Recursion Drawbacks and Benefits

- Many procedure calls, with associated overheads
  - Overhead not as bad on modern hardware
  - Tail-recursion: Recursive call is in last statement
  - Unroll the recursion into a loop (smart compiler?)
  - Partial unrolling:  $n! = n \times (n - 1) \times (n - 2) \times (n - 3)!$
- 
- May be preferred, even if not the most efficient
  - In the case of hardware, the design is recursive
  - The circuit-level realization is often fully unrolled
  - Recursive design provides analyzability & reliability



# Discrete Fourier Transform: FFT Network

$$\text{DFT: } y_i = \sum_{j=0}^{n-1} \omega_n^{ij} x_j$$

Naïve algorithm:  $T(n) = O(n^2)$

$$\text{FFT: } \begin{aligned} y_i &= u_i + \omega_n^i v_i \quad (0 \leq i < n/2) \\ y_{i+n/2} &= u_i - \omega_n^i v_i \end{aligned}$$


Seq:  $T(n) = 2T(n/2) + n = O(n \log n)$

Par:  $T(n) = T(n/2) + 1 = O(\log n)$


Inverse DFT is almost exactly the same computation:

$$\text{IDFT: } x_i = (1/n) \sum_{j=0}^{n-1} \omega_n^{-ij} y_j$$

 $u$ : DFT of even-indexed inputs  
 $v$ : DFT of odd-indexed inputs



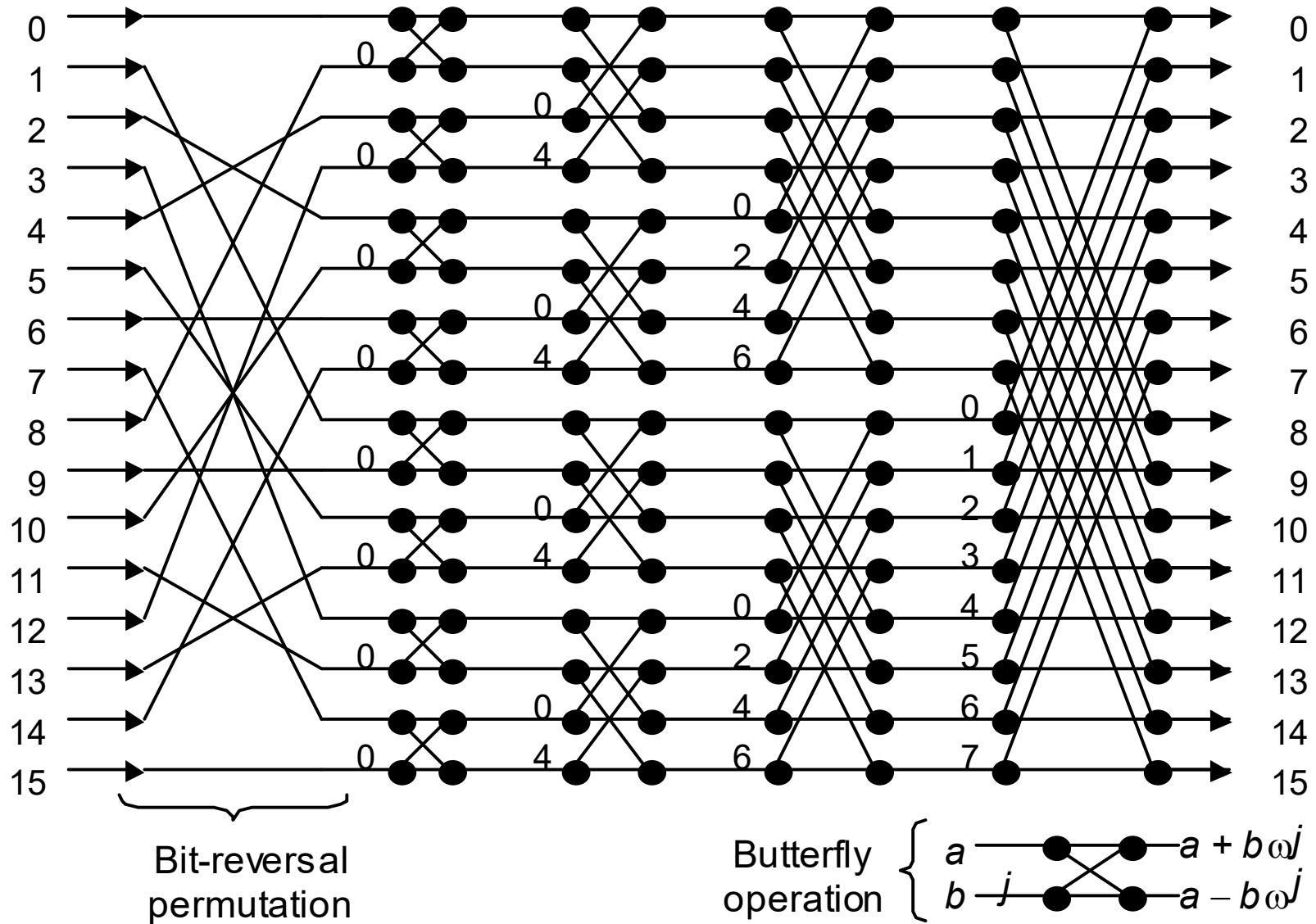
# Recursive Synthesis of Digital Circuits








# Regularized Butterfly: Shuffle-Exchange

Rearranged nodes,  
same connectivity

Removal / sharing  
of some links

 


More  
Economical  
FFT  
Hardware

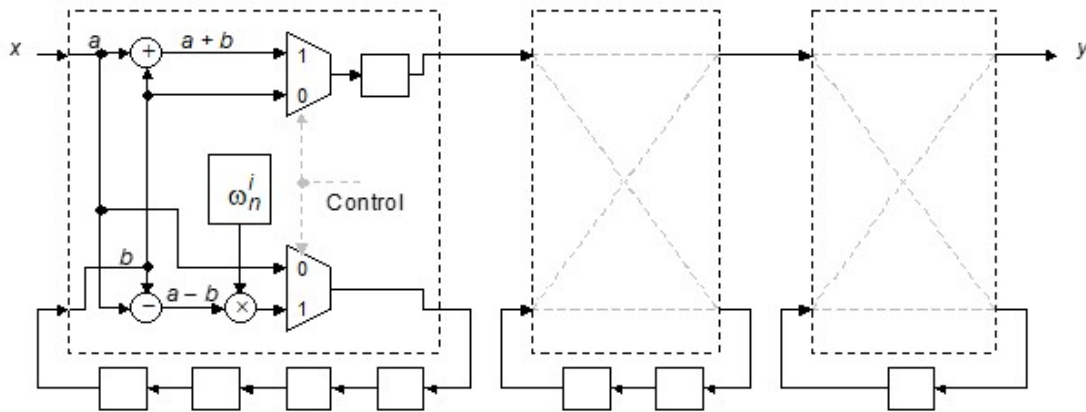    

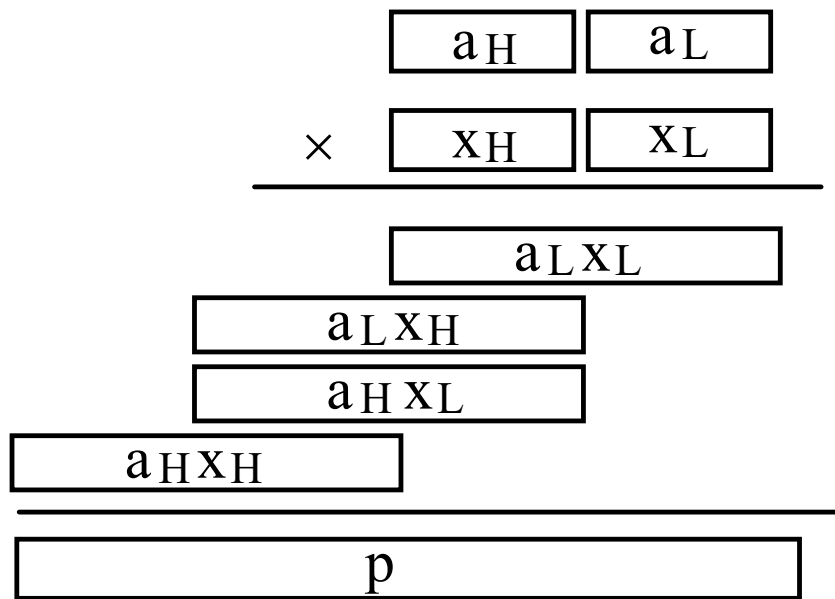
# Recursive Multipliers: Concept

Building wide multiplier from narrower ones



Form the 4 half-products  
 Add the resulting 4 (3) numbers  
 Add much faster than multiply

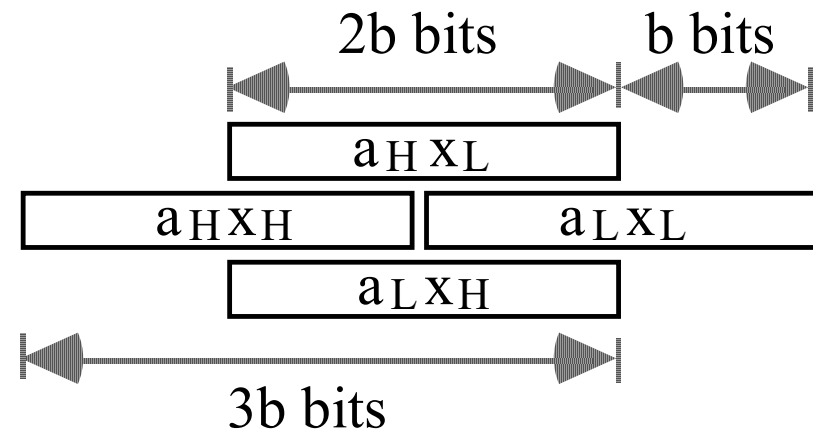Rearranged partial products in 2b-by-2b multiplication




$$D(n) = D(n/2) + O(\log n) = O(\log^2 n)$$

$$C(n) = 4C(n/2) + O(n) = O(n^2)$$
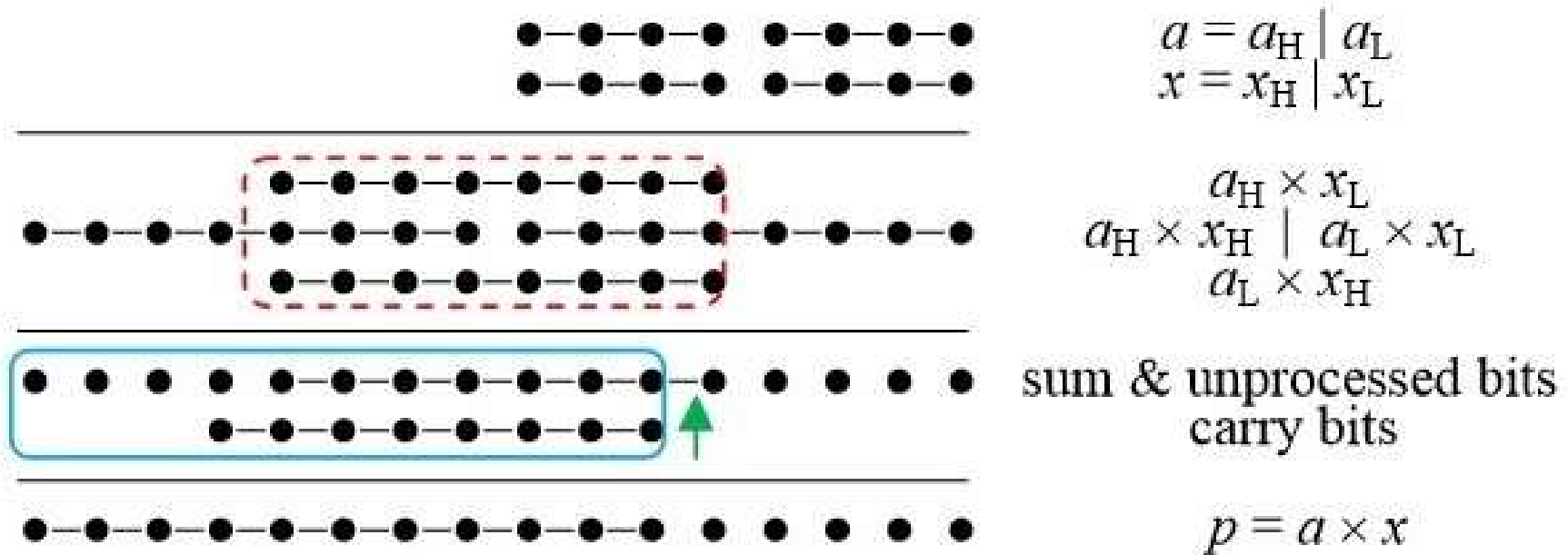
# Recursive Multipliers: Example

Multipliers can be built recursively from square or non-square component multipliers



An  $8 \times 8$  multiplier built from  $4 \times 4$  component multipliers





# Recursive Multipliers: Circuit

A 32-bit array multiplier built of four 16-bit array multipliers

The same design is valid for non-array multipliers of the additive type (square or rectangular)

2 x 4 additive multiplier

 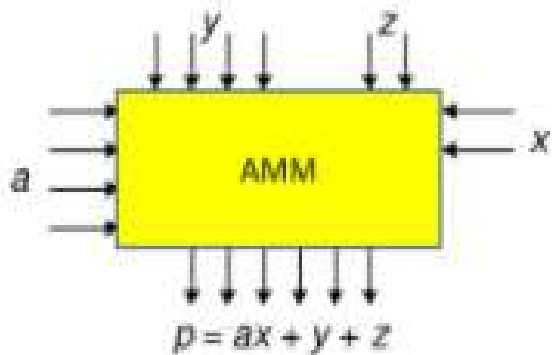

# Karatsuba Multiplication

$2b \times 2b$  multiplication requires four  $b \times b$  multiplications:


$$(2^b a_H + a_L) \times (2^b x_H + x_L) = 2^{2b} a_H x_H + 2^b (a_H x_L + a_L x_H) + a_L x_L$$

Karatsuba noted that one of the four multiplications can be removed at the expense of a few extra additions:

$$(2^b a_H + a_L) \times (2^b x_H + x_L) =$$

$$2^{2b} a_H x_H + 2^b [(a_H + a_L) \times (x_H + x_L)] - a_H x_H - a_L x_L + a_L x_L$$

**Mult 1**
**Mult 3**
**Mult 2**

 


Form the 3 half-products; do additions:  $C(n) = 3C(n/2) + O(n) = O(n^{1.58})$

Benefit is quite significant for extremely wide operands

$$(4/3)^5 = 4.2 \quad (4/3)^{10} = 17.8 \quad (4/3)^{15} = 74.8 \quad (4/3)^{20} = 315.3$$
 
# Special Case of Squaring

Non-square building blocks not beneficial for squarers because we won't be able to use squarers



An  $8 \times 8$  squarer built from  $4 \times 4$  component multipliers/squarers

## Counting Networks

- **Circuits that compute (symmetric) logic functions based on the number of 1s among the inputs**
- $?/n$  How many 1s are there? (Parallel counters)
- $=k/n$  Are there exactly  $k$  1s?
- $\geq l/n$  Are there at least  $l$  1s?
- $< m/n$  Are there fewer than  $m$  1s? (or  $\leq (m-1)/n$ )
- $\in [l, m)/n$  Are there at least  $l$  and fewer than  $m$  1s?
- $\in [l, m-1]/n$  Are there at least  $l$  and at most  $m-1$  1s?
- $\{j_1, j_2, \dots, j_k\}/n$  Is the number of 1s in the set  $\{j_1, j_2, \dots, j_k\}$ ?
- Also, Hamming-weight-comparators, not discussed here




# Recursive Design of Parallel Counters

$$D(\text{LSB } ?/n) = 1 + D(\text{LSB } ?/\lfloor n/2 \rfloor) = \lfloor \log_2 n \rfloor$$

$$D(?/n) = D(\text{LSB } ?/n) + \lfloor \log_2 n \rfloor - 1$$

$$= 2 \lfloor \log_2 n \rfloor - 1$$

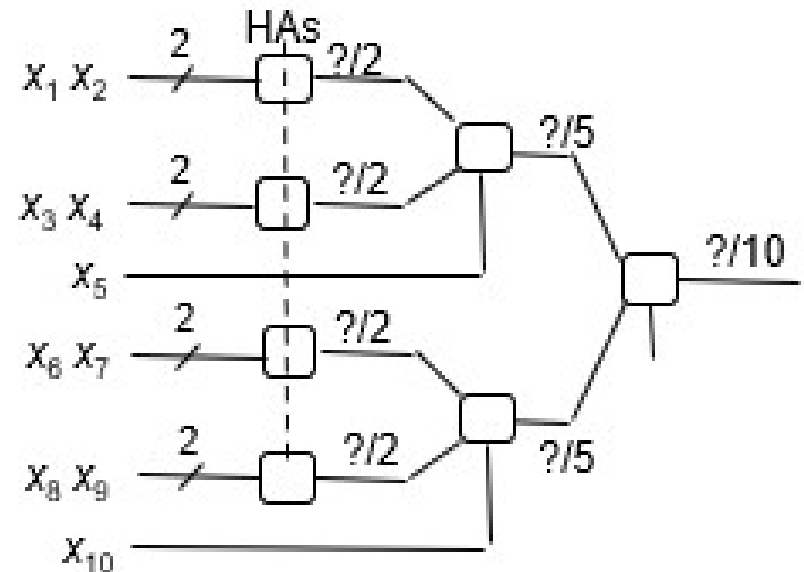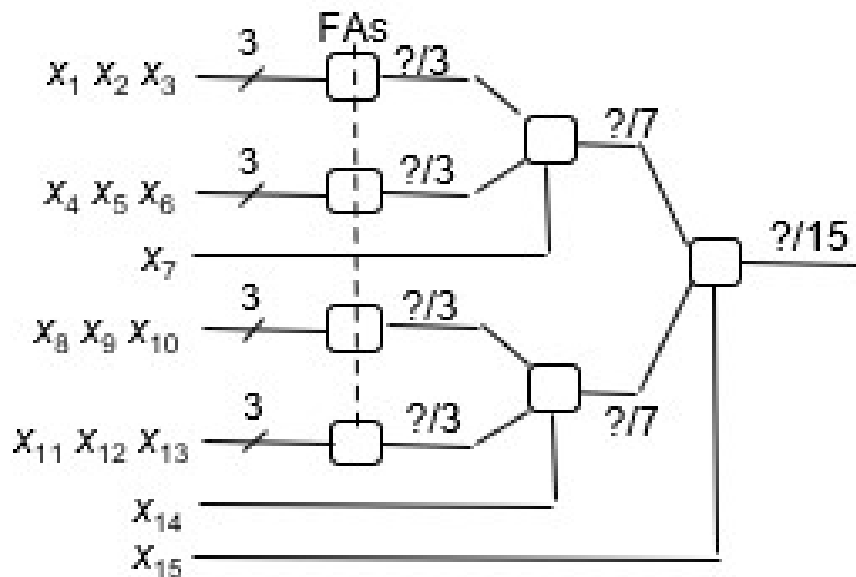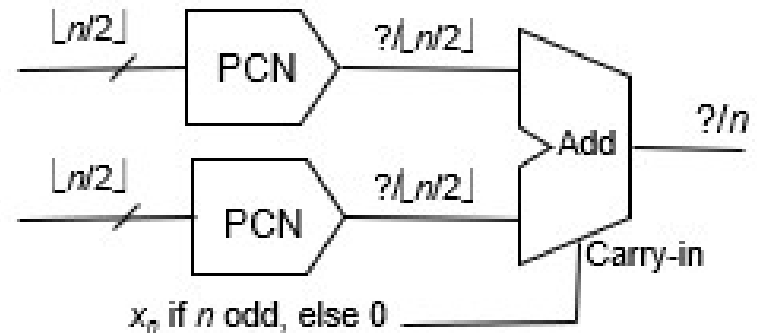
$$C(?/n) = 2C(?/\lfloor n/2 \rfloor) + \lfloor \log_2 n \rfloor \cong 2n$$


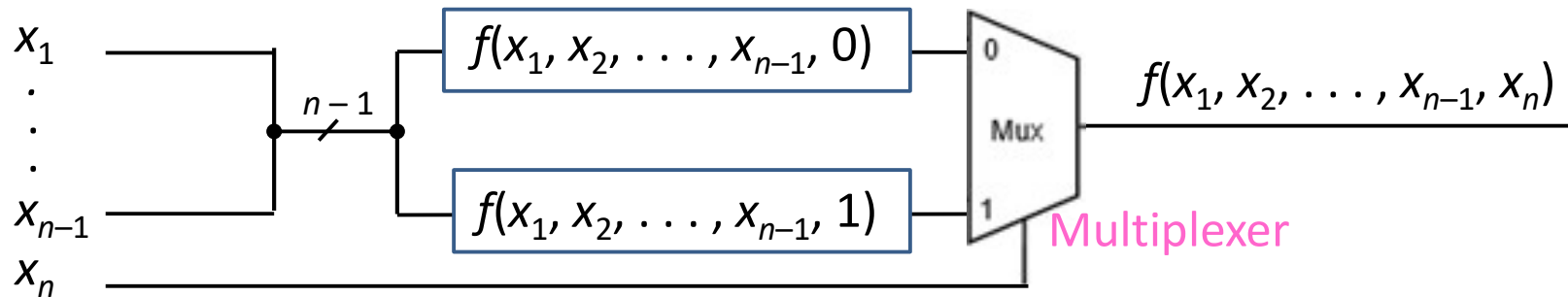
# Mux-Based Hardware Realizations


Shannon expansion or decomposition

$$f(x_1, x_2, \dots, x_{n-1}, x_n) = x_n' f(x_1, x_2, \dots, x_{n-1}, 0) \vee x_n f(x_1, x_2, \dots, x_{n-1}, 1)$$



 Example: Majority voter

$$\begin{aligned} f(x_1, x_2, x_3) &= x_1x_2 \vee x_2x_3 \vee x_3x_1 \\ &= x_3'(x_1x_2) \vee x_3(x_1 \vee x_2) \end{aligned}$$



# Recursive Design of Weight-Checkers

$$B(=k/n) = 1 + B(=k/(n-1)) + B(=(k-1)/(n-1))$$


$$B(=k/n) = 1 + B(=k/(n-1)) + B(=(k-1)/(n-1)) - B(=(k-1)/(n-2))$$

Shared parts

$$= k(n-k) - 1$$

$$C(=k/n) = B(=k/n) + \text{peripheral gates}$$

 
$$D(=k/n) = n - 2 + \max(D_{\text{AND}}(2), D_{\text{NOR}}(2), D_{\text{XOR}})$$



$$B(=3/6) = 1 + B(=3/5) + B(=2/5) - B(=2/4)$$


$$= 1 + 5 + 5 - 3 = 8$$

(AND gates)

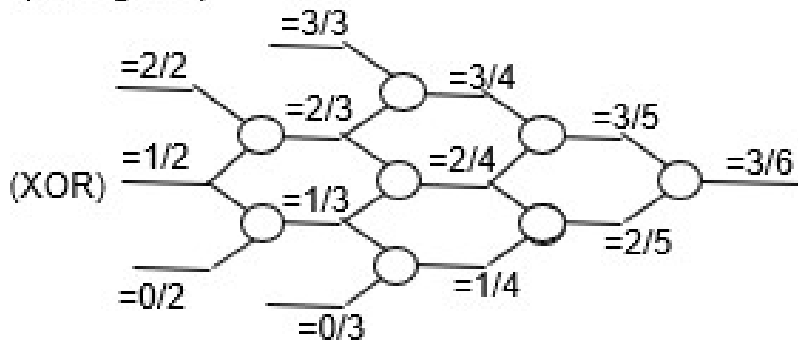

(NOR gates)

(NAND gates)

 





(OR gates)

# Recursive Design of Threshold Counters

$$B(\geq l/n) = 1 + B(\geq l/(n-1)) + B(\geq (l-1)/(n-1)) - B(\geq (k-1)/(n-1)) = (n-l)(l-1) - 1$$

$$C(\geq k/n) = B(\geq k/n) + \text{peripheral gates}$$
    
$$D(\geq l/n) = 1 + \max[D(\geq l/(n-1)), D(\geq (l-1)/(n-1))] = n - 3 + \text{small constant}$$






## Example (Inverse) Threshold Counters


$$B(\geq l/n) = 1 + B(\geq l/(n-1)) + B(\geq (l-1)/(n-1)) - B(\geq (k-1)/(n-1)) = (n-l)(l-1) - 1$$

$$C(\geq k/n) = B(\geq k/n) + \text{peripheral gates}$$

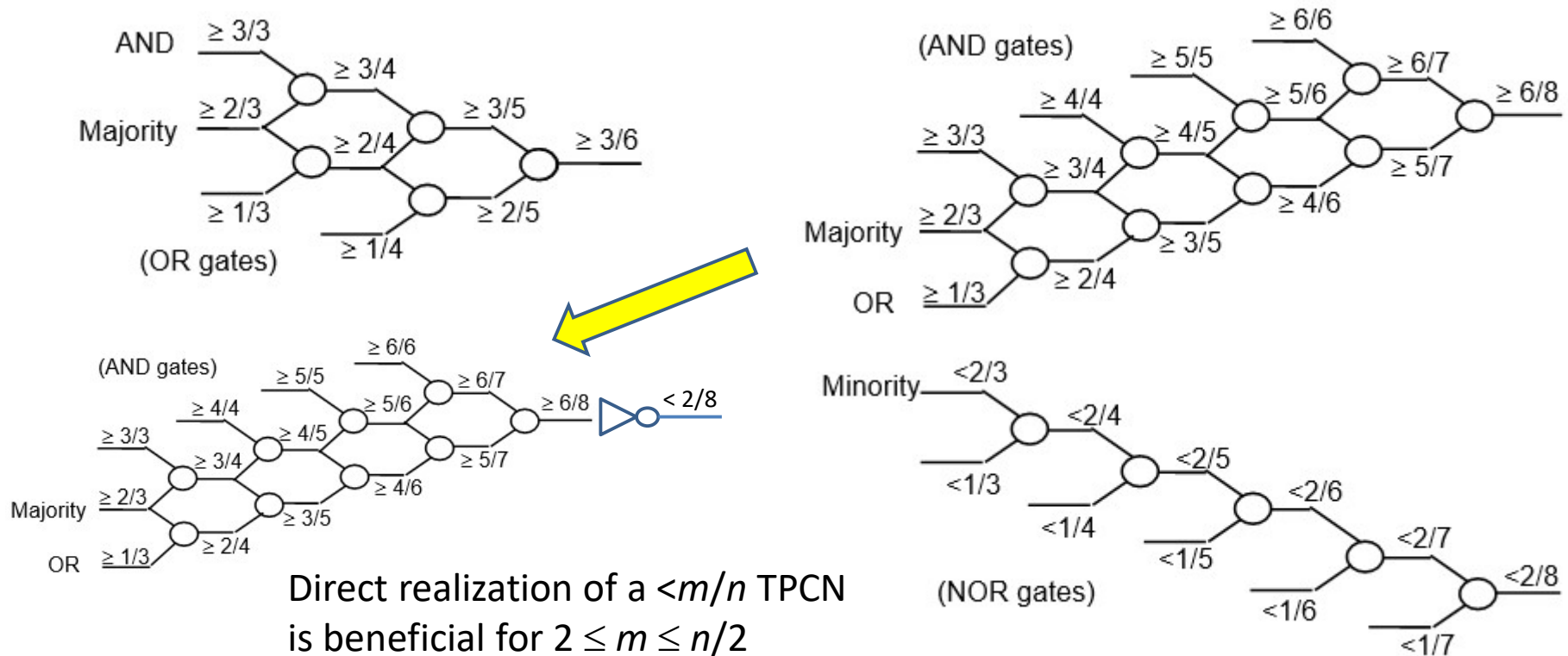
$$D(\geq l/n) = 1 + \max[D(\geq l/(n-1)), D(\geq (l-1)/(n-1))] = n - 3 + \text{small constant}$$




# Example CMOS Implementation

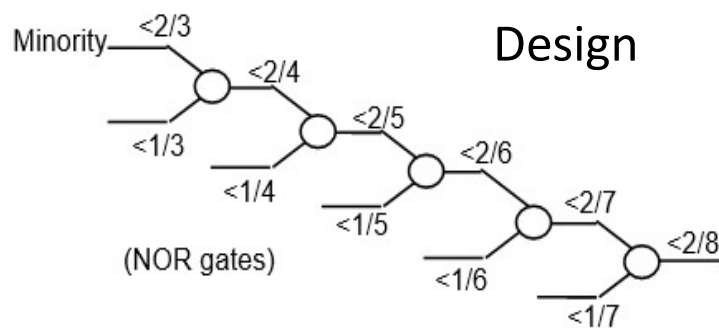

Design

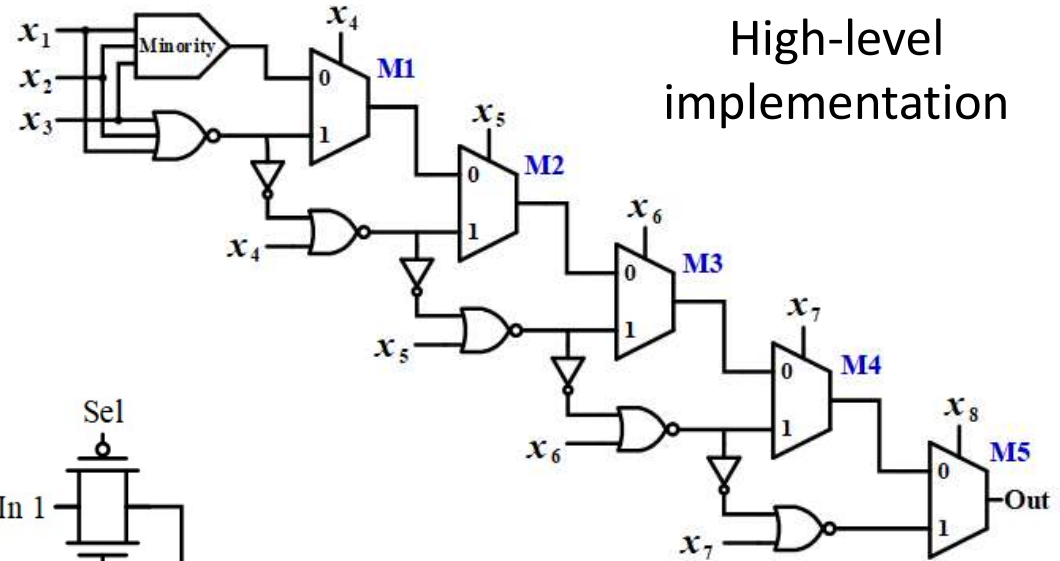

High-level implementation

 

Three possible mux designs:

Ordinary CMOS; bypass transistor; transmission gate

Average improvements:  
 ~10% delay  
 ~65% power  
 ~55% transistor count  
 More results forthcoming

# Between-Limits Threshold Counters

$C(\in[l, m]/n) =$  **Open problem**




$D(\in[l, m]/n) = n - 2 +$  a small constant

Example application:



Codewords of length 9 bits and weights 4 or 5


$$C(4, 9) + C(5, 9) = 126 + 126 = 252$$

 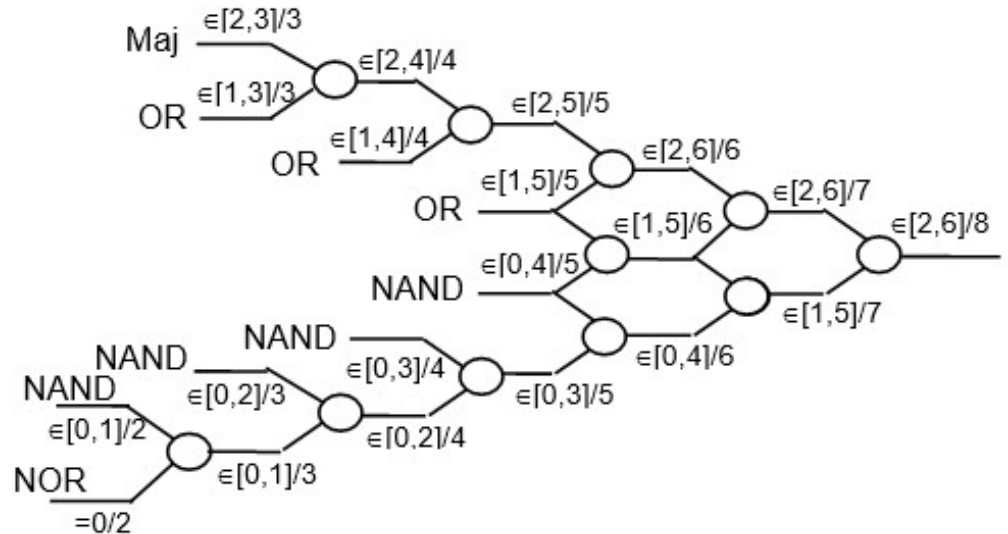 
 
# Membership Checkers

$\{3,4,6\}/8$  membership checker



Negative terms and terms larger than  $n$  are dropped


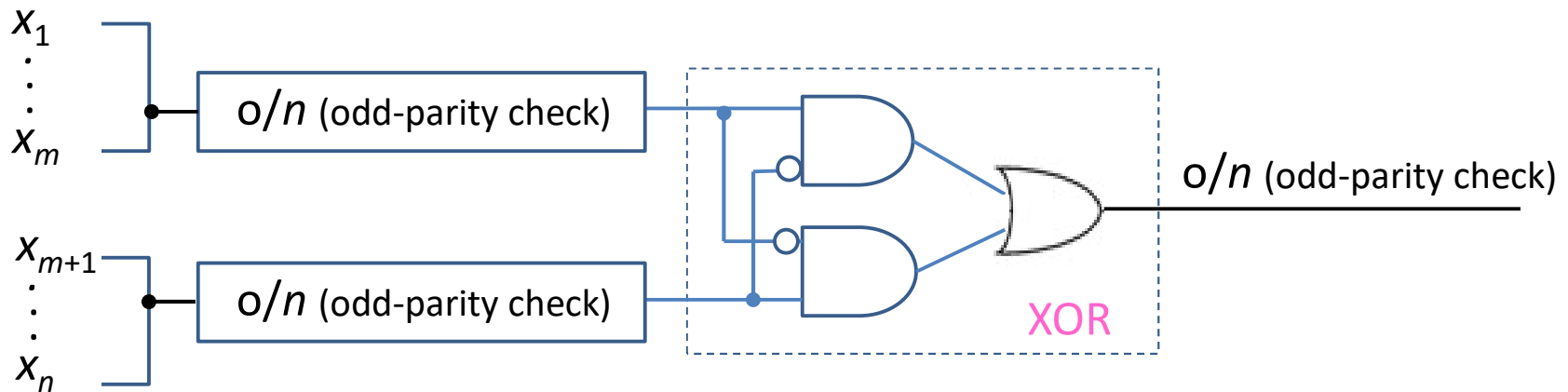 
# Even- or Odd-Parity Checker

Parity checking: XOR-tree networks  
 First attempt at recursive formulation

$$\begin{aligned} \text{odd-parity}(x_1, x_2, \dots, x_{n-1}, x_n) \\ &= \text{odd-parity}(x_1, \dots, x_m) \\ &\oplus \text{odd-parity}(x_{m+1}, \dots, x_n) \end{aligned}$$





## Advantages and Drawbacks

- Recursion not applicable to all of our needs
- May not lead to theoretically-optimal design
- But ... Optimal designs tend to be complex
  - Long design times and many design errors
- Recursive designs: Analyzable and verifiable
- Stop recursion upon hitting a known design
- Commonly-used parts can be fully optimized
- Good for prototyping, if not for final circuit
  
# Speed vs. Regularity

- Tree: Fast, but irregular
- Array: Slow, but regular



## Conclusion and Future Work

- Recursive hardware design is feasible and beneficial
- I covered three examples: FFT; Multiplier; Counter
- Counting-network designs are new
- There are other examples: e.g., sorting networks
- Benefits: Ease of analysis and correctness proof
- May be preferred, even if not the most efficient
- All designs can be pipelined for higher throughput
- Latency, cost, power for implemented networks



# Questions?



[parhami@ece.ucsb.edu](mailto:parhami@ece.ucsb.edu)

PDF files of B. Parhami's publications are available at:  
[www.ece.ucsb.edu/~parhami/publications.htm](http://www.ece.ucsb.edu/~parhami/publications.htm)

# Back-up Slides

[parhami@ece.ucsb.edu](mailto:parhami@ece.ucsb.edu)  
[www.ece.ucsb.edu/~parhami](http://www.ece.ucsb.edu/~parhami)

# Insertion Sort and Selection Sort

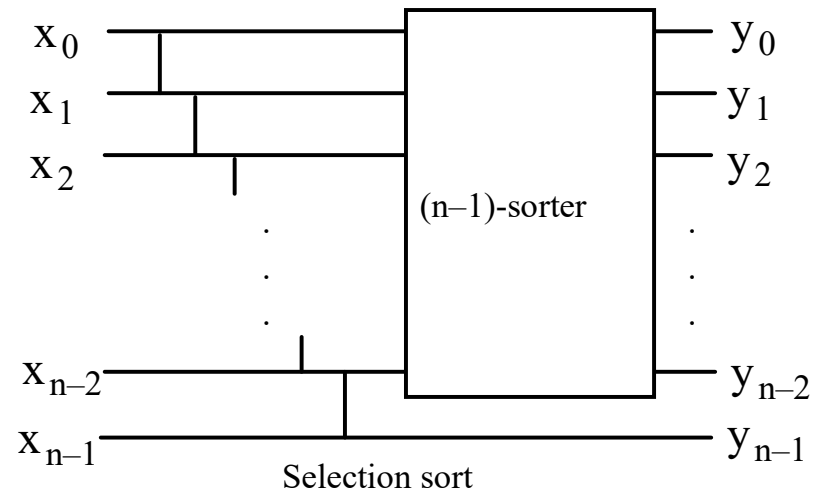 


Parallel insertion sort = Parallel selection sort = Parallel bubble sort!


$$C(n) = n(n - 1)/2$$

$$D(n) = 2n - 3$$
 
$$\text{Cost} \times \text{Delay} = \Theta(n^3)$$



# Batcher's Even-Odd Merge Sorting

 

The recursive structure of Batcher's even-odd merge sorting network.

Batcher's  $(m, m)$  even-odd merger, for  $m$  a power of 2:

$$\begin{aligned} C(m) &= 2C(m/2) + m - 1 \\ &= (m-1) + 2(m/2-1) + 4(m/4-1) + \dots \\ &= m \log_2 m + 1 \end{aligned}$$

$$D(m) = D(m/2) + 1 = \log_2 m + 1$$

$$\text{Cost} \times \text{Delay} = \Theta(m \log^2 m)$$


Batcher sorting networks based on the even-odd merge technique:

$$\begin{aligned} C(n) &= 2C(n/2) + (n/2)(\log_2(n/2)) + 1 \\ &\cong n(\log_2 n)^2 / 2 \end{aligned}$$

$$\begin{aligned} D(n) &= D(n/2) + \log_2(n/2) + 1 \\ &= D(n/2) + \log_2 n \\ &= \log_2 n (\log_2 n + 1) / 2 \end{aligned}$$


$$\text{Cost} \times \text{Delay} = \Theta(n \log^4 n)$$

# Example Batcher's Even-Odd 8-Sorter

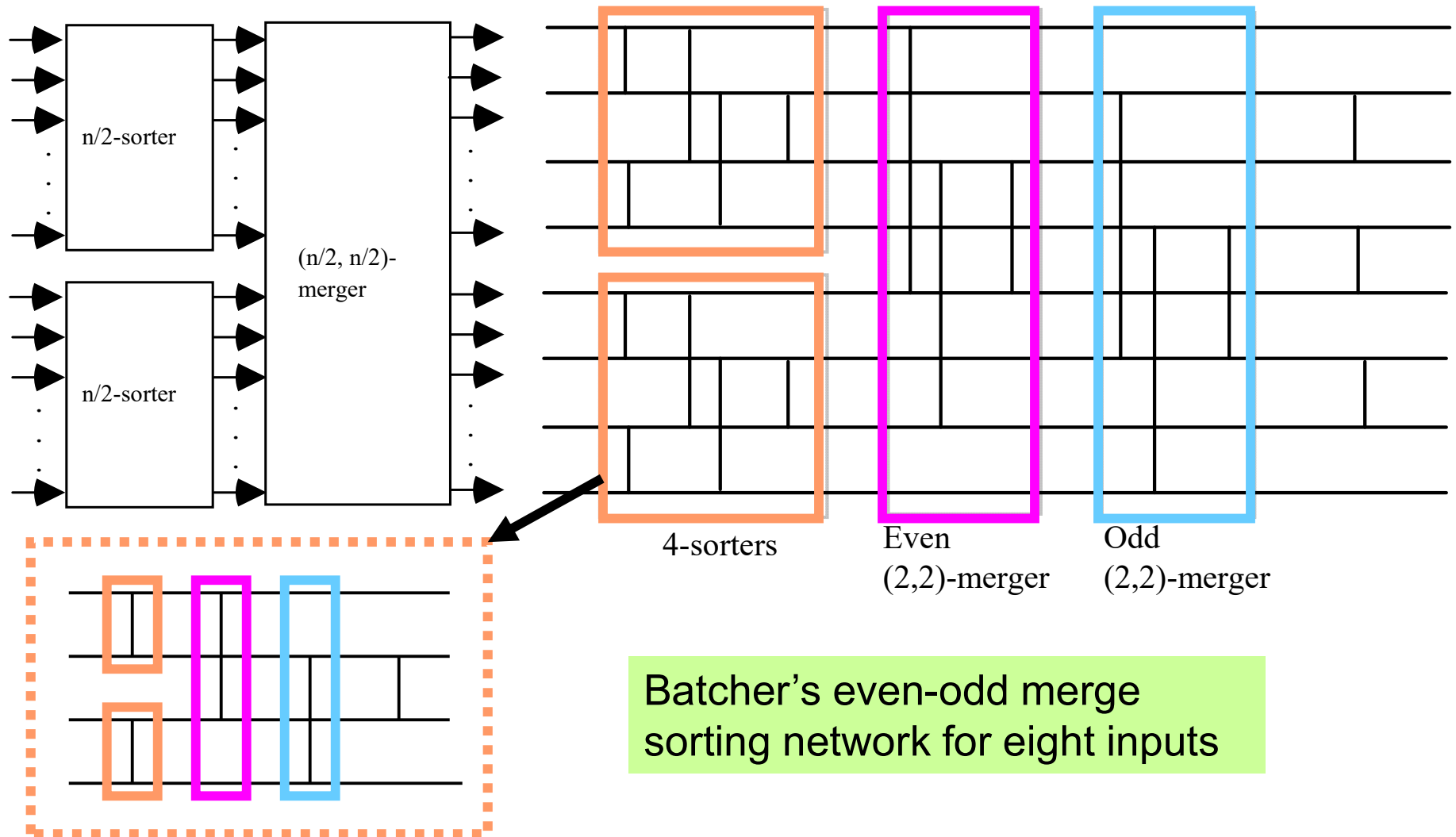

Batcher's even-odd merge sorting network for eight inputs


# (Non-)Square Recursive Multipliers

 

Square components


Non-square components may lead to matrix height reduction

Non-square components

 

# Example with No Height Reduction

12 × 8 multiplication  
3 × 4 components

 

# Examples of Matrix Height Reduction

14 × 4 multiplication  
2 × 2 components

12 × 6 multiplication  
2 × 3 components

